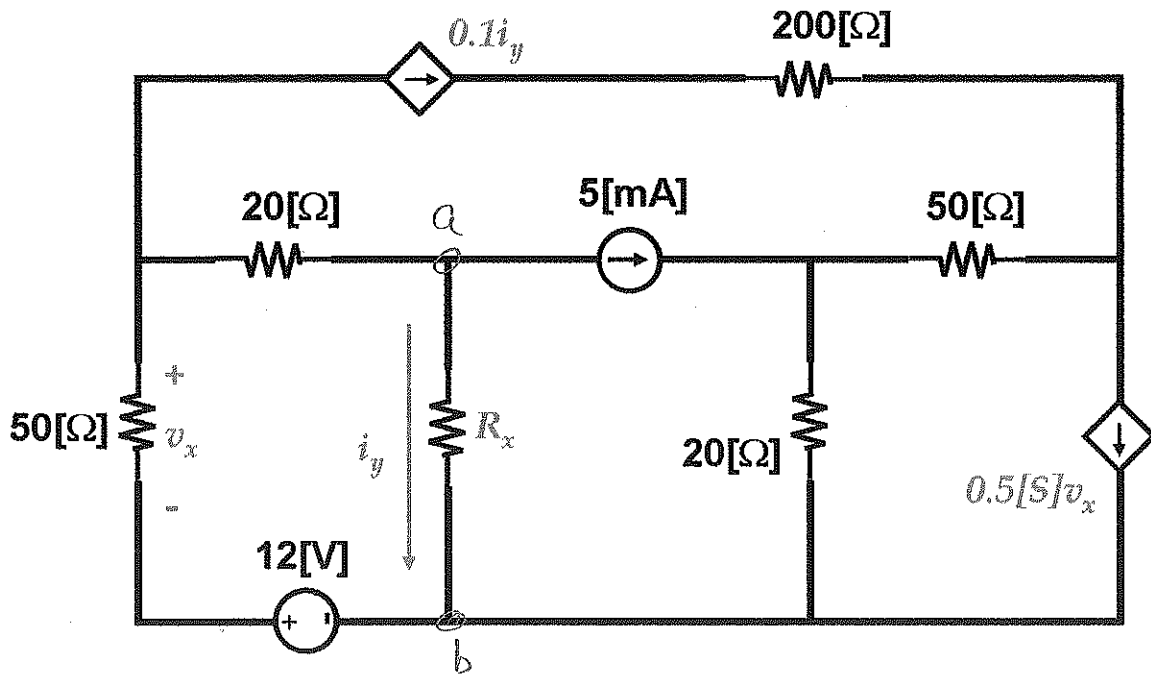


Problem 2 (30 points):

For the circuit shown in Figure 2, do the following.


- Find the Norton equivalent as seen by R_x
- Draw the Norton equivalent and label it, showing how it is connected to R_x .
- If the power absorbed by R_x is 2[mW], find the value of R_x .

**Figure 2**

To properly indicate how the equivalent circuit is connected to R_x , we need to indicate a polarity. In this case we have done this by labelling terminals a, b. This is required for full credit in part b).

we need to choose two of : (i) open circuit voltage, (ii) short circuit current and (iii) test source to get R_N . we will do all three here, but only two were required,

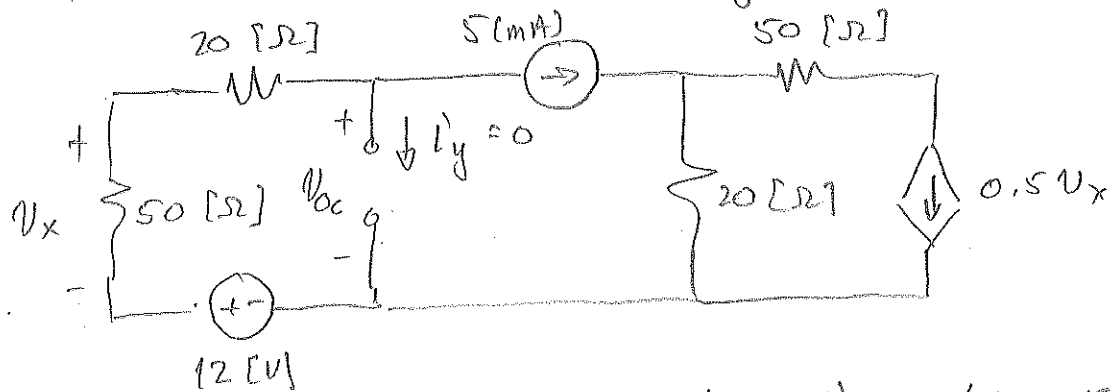
(i) open-circuit voltage $\Rightarrow i_y = 0$, so...



$$V_{oc} - 12 + 50(0.005) + 20(0.005) = 0$$

$$V_{oc} = 11.65 \text{ [V]}$$

(ii) short circuit current

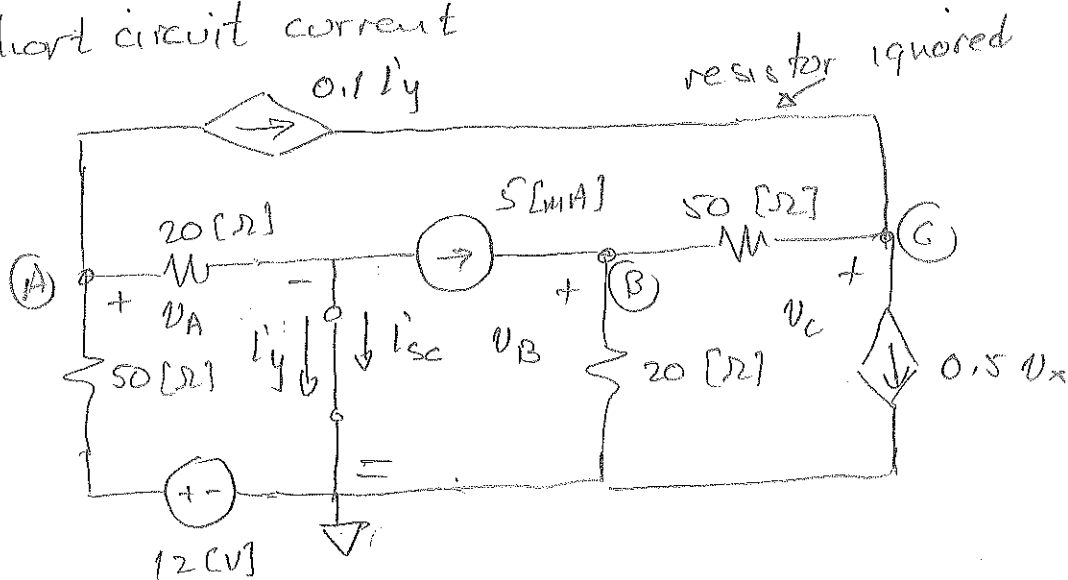

$$\textcircled{A} \quad \frac{V_A - 12}{50} + \frac{V_A}{20} + 0.1 i_y = 0$$


$$\textcircled{B} \quad \frac{V_B}{20} - 0.005 + \frac{V_B - V_C}{50} = 0 \quad \textcircled{C} \quad -0.1 i_y + 0.5 V_x + \frac{V_C - V_B}{50} = 0$$

$$V_x = V_A - 12 \quad i_y = \frac{V_A}{20} - 0.005$$

We have 5 eqns but all we need is $i_{sc} = i_y$, so we only have to solve \textcircled{A} : $V_A = 3.207 \text{ [V]}$

$$i_{sc}' = \frac{V_A}{20} - 0.005 = 155.3 \text{ [mA]}$$

(iii) test source

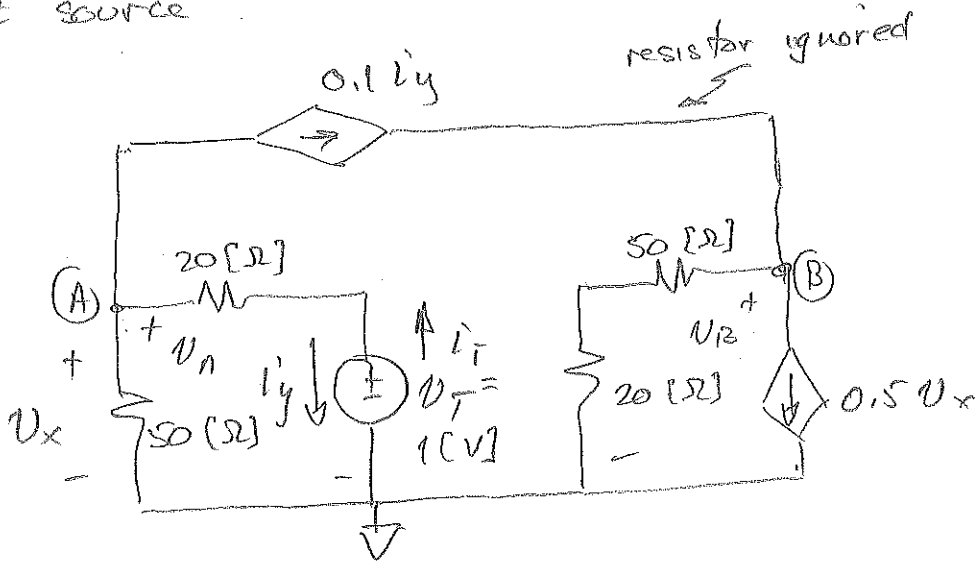

(A) $\frac{V_A}{50} + \frac{V_A - 1}{20} + 0.1 i_y = 0 \quad i_y = -i_T$


(B) $\frac{V_B}{20} + 0.5 V_x - 0.1 i_y = 0 \quad i_T = \frac{1 - V_A}{20}$

$V_A = 0.733 \text{ [V]} \quad i_T = 13.33 \text{ [mA]}$

$\Rightarrow R_N = \frac{1}{i_T} = 75.02 \text{ [}\Omega\text{]} \quad \text{or} \quad R_N = \frac{V_{oc}}{i_{sc}} = \frac{11.65}{0.1553} = 75.02 \text{ [}\Omega\text{]}$

a) So $R_N = 75.02 \text{ [}\Omega\text{]}, \quad i_N = 155.3 \text{ [mA]}$

b)

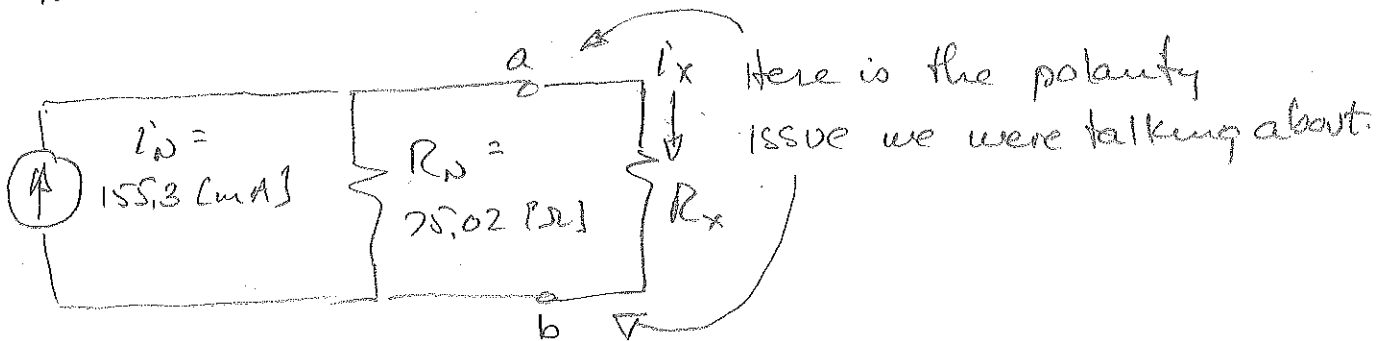

c)



looking at part b, we have

$$i_x = (0.155) \left(\frac{75}{75 + R_x} \right)$$

$$2_i^2 R_x = 0.002$$

$$\Rightarrow \boxed{R_x = 83.07 \text{ m}\Omega \text{ or } R_x = 67.74 \text{ k}\Omega}$$