

Name: SOLUTIONS (please print)

Signature: \_\_\_\_\_

ECE 2300 – Quiz #2  
September 20, 2012


VERSION 1

**Keep this quiz closed and  
face up until you are told to  
begin.**

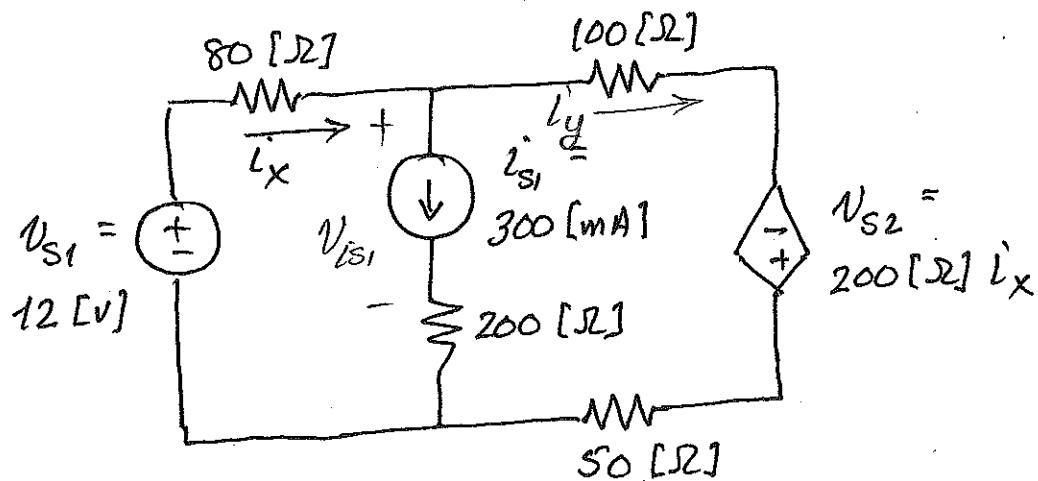1. This quiz is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit.
3. Show all units in solutions, intermediate results, and figures. Units in the quiz will be included between square brackets.
4. Do not use red ink. Do not use red pencil.
5. You will have 30 minutes to work on this quiz.

\_\_\_\_\_/20

In the circuit below, find the power delivered by the independent current source.



we will need  $v_{is1}$  which we get from a KVL:

$$+6 \quad v_{is1} + 0.3(200) - 12 + 80 i_x = 0$$

we need an equation for  $i_x$  ...

$$+4 \quad i_x = 0.3 + i_y$$

... and another since we introduced  $i_y$ :

$$+5 \quad 100 i_y - 200 i_x + 50 i_y - 12 + 80 i_x = 0$$

So we have 3 eqns, 3 unknowns...

$$+2 \quad v_{is1} = -200 \text{ [V]} \quad i_x = 1.9 \text{ [A]} \quad i_y = 1.6 \text{ [A]}$$

$$+3 \quad \therefore P_{del, is1} = -i_s \cdot v_{is1} = (-0.3)(-200) = 60 \text{ [W]}$$

Name: SOLUTIONS (please print)

Signature: \_\_\_\_\_

ECE 2300 – Quiz #2  
September 20, 2012


Version 2

**Keep this quiz closed and  
face up until you are told to  
begin.**

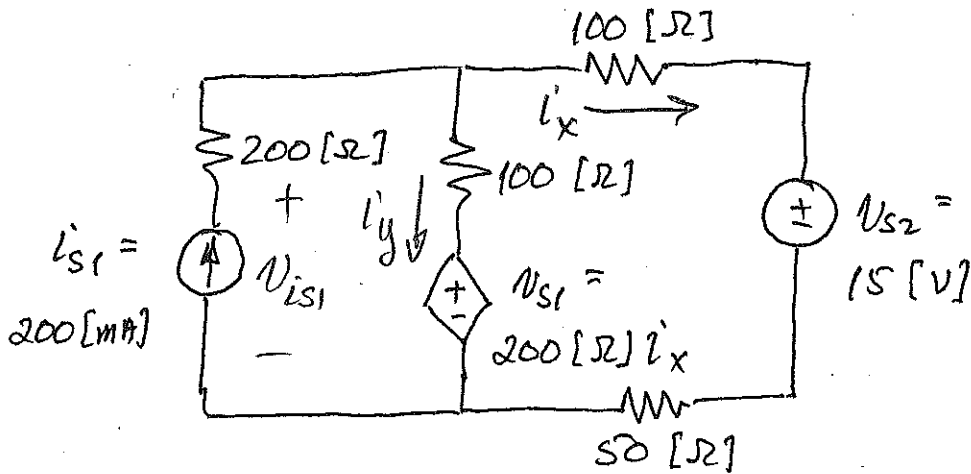1. This quiz is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit.
3. Show all units in solutions, intermediate results, and figures. Units in the quiz will be included between square brackets.
4. Do not use red ink. Do not use red pencil.
5. You will have 30 minutes to work on this quiz.

\_\_\_\_\_ /20

In the circuit below, find the power delivered by the independent current source.



We are going to need  $V_{s1}$ , which we get with a KVL:

$$x6 \quad -V_{s1} + 0.2(200) + 100i_x + 15 + 50i_x = 0$$

we need an equation for  $i_x$ ...

$$x4 \quad -0.2 + i_y + i_x = 0$$

... and another since we have introduced  $i_y$ :

$$x5 \quad 100i_y + 200i_x - 50i_x - 15 - 100i_x = 0$$

So we have 3 eqns, 3 unknowns...

$$x2 \quad V_{s1} = 70 \text{ [V]} \quad i_x = 0.1 \text{ [A]} \quad i_y = 0.1 \text{ [A]}$$

$$x3 \quad \therefore P_{del, i_{s1}} = V_{s1} \cdot i_{s1} = 14 \text{ [W]}$$