

Problem #3. (20 points)

For the circuit shown in Figure 3 find:

- The Thevenin equivalent at terminals a and b. Draw the Thevenin equivalent and clearly indicate terminals a and b.
- If a resistor with a value of $R = 2.228 \text{ [k}\Omega\text{]}$ is placed across terminals a and b, what is the new R_{th} at terminals a and b?


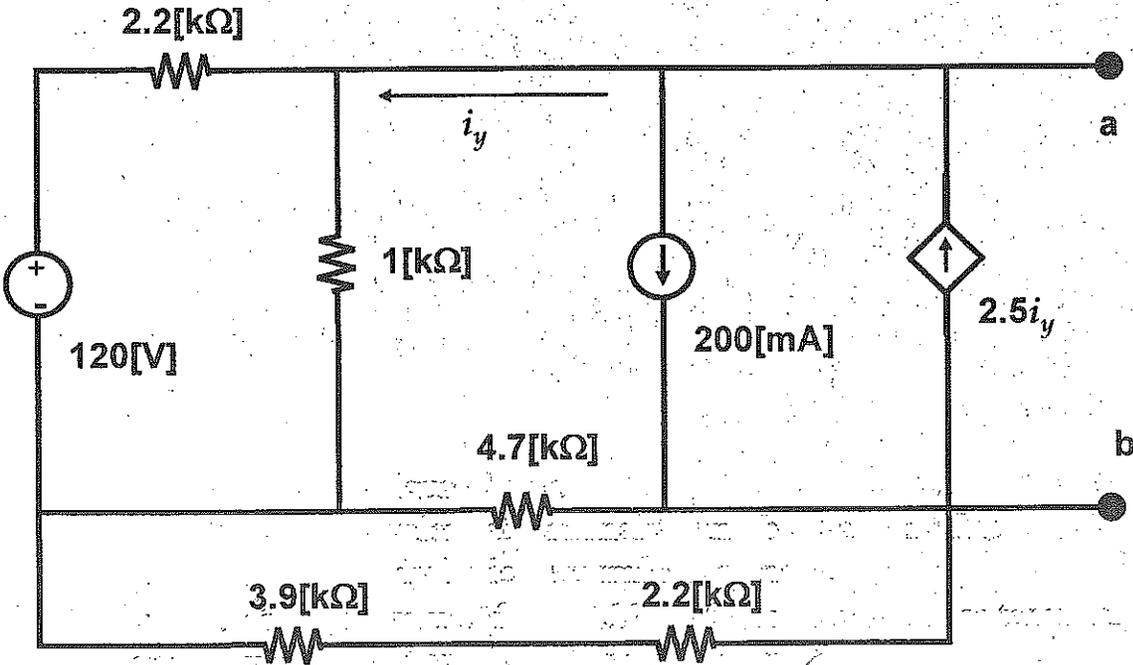


Figure 3

a) We begin with R_{TH} = place a test source at a, b, combine $(3.9 \text{ [k}\Omega\text{]} + 2.2 \text{ [k}\Omega\text{]}) // 4.7 \text{ [k}\Omega\text{]}$, and deactivate the 120 [V] and 200 [mA] sources. we get

Room for extra work

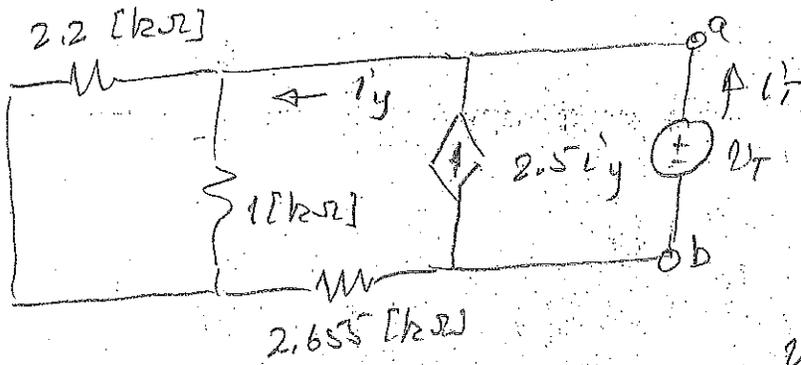


$(R_{eq} = 3343 \text{ } [\Omega])$


Now $i_T = i_y - 2.5 i_y$ $i_y = \frac{V_T \times 10^{-3}}{2.655 + (2.2 \parallel 1)}$

$i_T = -1.5 i_y = -1.5 V_T (2.992 \times 10^{-4}) = -0.4488 \text{ [mA]} \quad \text{if } V_T = 10V$

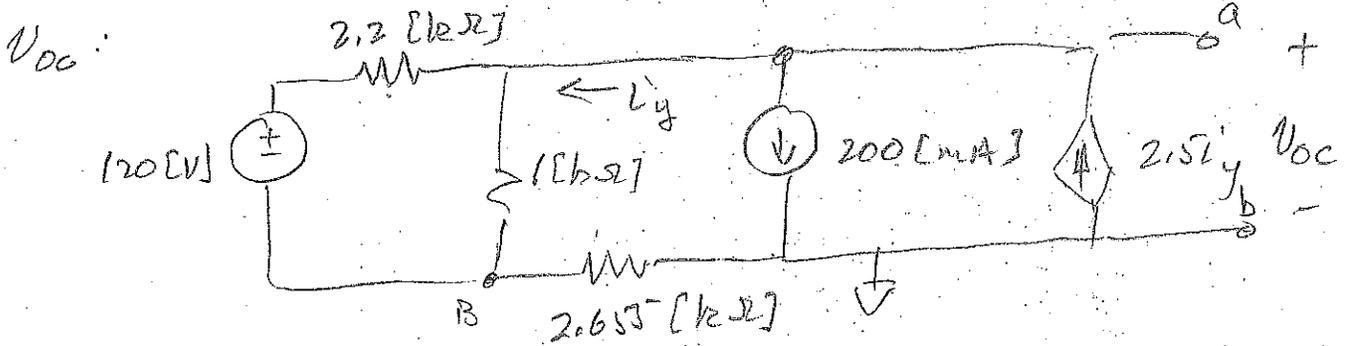$\therefore \frac{V_T}{i_T} = \frac{-1}{1.5(2.992 \times 10^{-4})} = -2228 \text{ } [\Omega]$



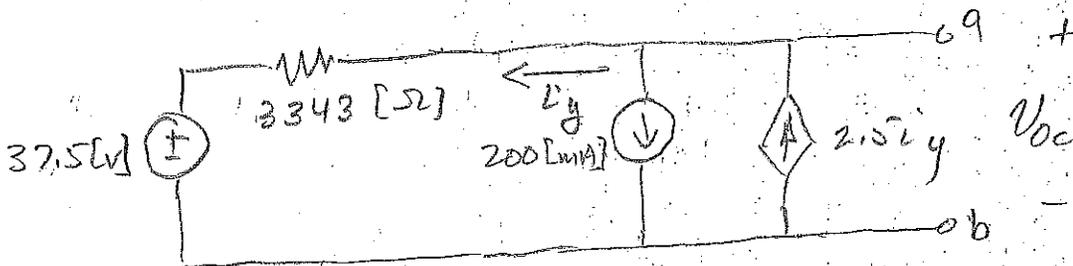
Two source transformations simplifies this to:



$V_{TH} = +8$

$R_{TH} = 8$

$R'_{TH} = 2$

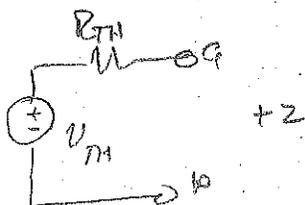


to page 9

KCL $-2.5i_y + 0.2 + i_y = 0 \Rightarrow i_y = 0.1333 \text{ [A]}$

KVL $-37.5 - i_y(3343) + V_{oc} = 0 \Rightarrow V_{oc} = 483.1 \text{ [V]}$

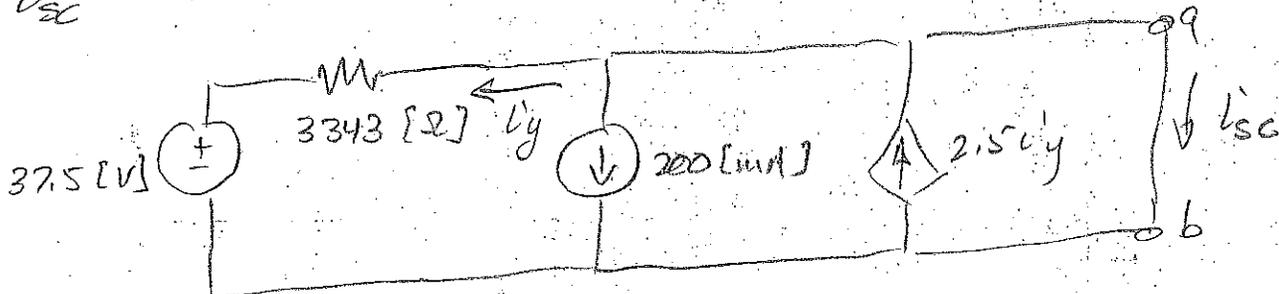i_{sc} (not needed but we do it to check...)




$$i_y = \frac{-37.5}{3343} = -11.22 \text{ [mA]}$$

$$i_{sc} - 2.5i_y + 0.2 + i_y = 0 \Rightarrow i_{sc} = -0.2168 \text{ [A]}$$

$$\therefore R_{TH} = V_{oc}/i_{sc} = \frac{483.1}{-0.2168} = -2228 \text{ [}\Omega\text{]} \quad \checkmark$$

So our Thevenin Equivalent is...

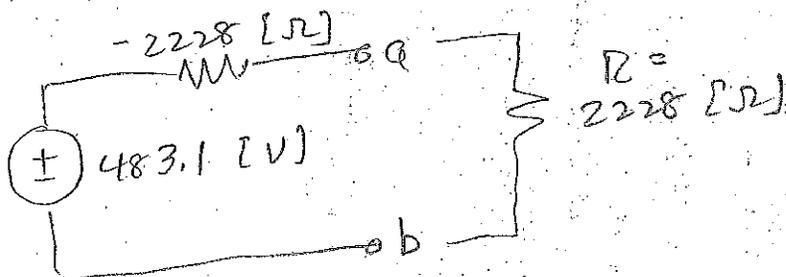

b) with $R = 2228 \text{ [}\Omega\text{]}$ at a, b, the new R_{TH} is

$$R'_{TH} = 2228 \parallel -2228 = \infty$$

The switch was in position 'a' for a long time, and moved to b at $t=0$.
Problem 4 (25 points) For the circuit shown in Figure 4, at $t < 0$, it is known that $i_1 = i_2$. Find $i_2(t)$ for $t > 0$.


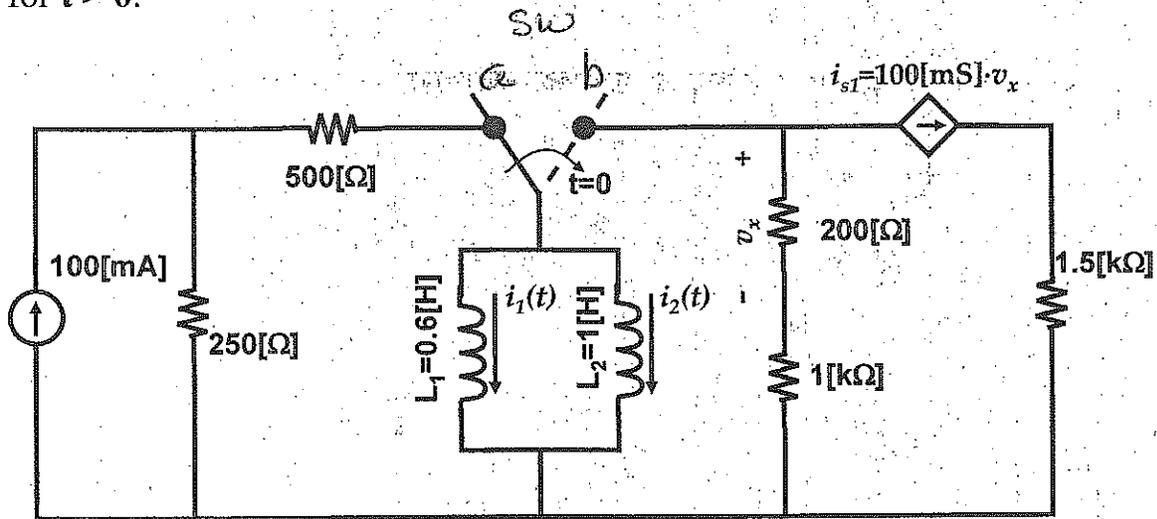


Figure 4

① Initial conditions:

$L_1 \rightarrow$ short
 $L_2 \rightarrow$ short

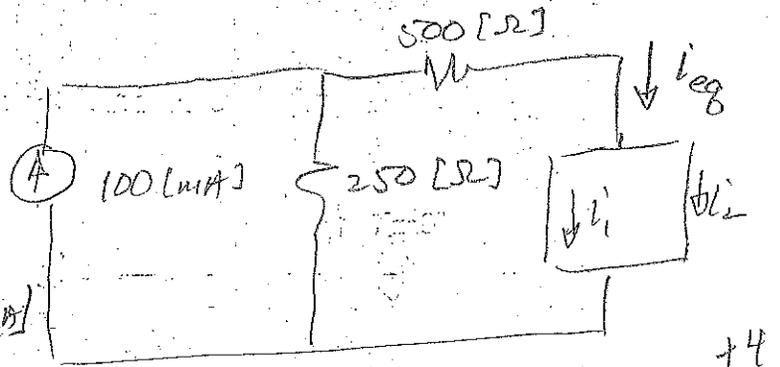
$$i_{eq} = 0.1 \times \frac{250}{250 + 500} = 33.33 \text{ [mA]}$$



$$\therefore i_1 = i_2 = 16.67 \text{ [mA]} = i_1(0^-) = i_1(0^+) = i_2(0^-) = i_2(0^+)$$

Re-draw for $t > 0$. Use $L_{eq} = \frac{L_1 L_2}{L_1 + L_2} = 0.375 \text{ [H]}$

$$i_{eq}(0^+) = 33.33 \text{ [mA]}$$

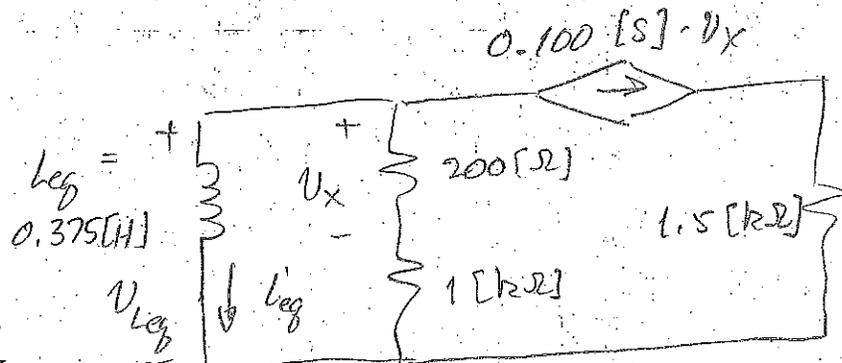


Room for extra work

Con't

Room for extra work

② Find τ : we need R_{TH} seen by Leg

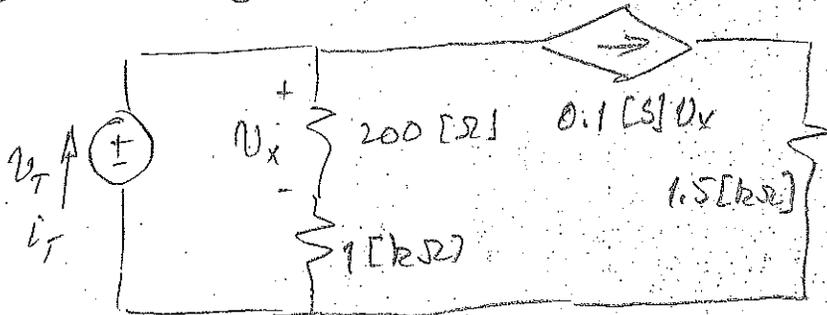

$$V_x = V_T \frac{200}{200 + 1000} = \frac{1}{6} V_T$$

$$i_T = \frac{V_T}{1200} + 0.1 V_x = \frac{V_T}{1200} + 0.1 \frac{V_T}{6} = 12.5 \times 10^{-3} V_T$$

+5, +2

$$R_{TH} = \frac{V_T}{i_T} = 57.14 [\Omega] \Rightarrow \tau = \frac{L}{R} = 6.563 [\text{ms}]$$

③ Final condition: no independent sources

+2

$$\Rightarrow i_{Leg}(\infty) = 0$$

+4

$$i_{leg}(t) = i_{leg}(\infty) + (i_{leg}(0) - i_{leg}(\infty)) e^{-t/\tau_L} = 0 + (33.33 - 0) e^{-t/6.563 [\text{ms}]} [\text{mA}] \quad t \geq 0 [\text{ms}]$$

+2

$$v_{leg}(t) = L_{leg} \frac{di_{leg}}{dt} = 0.375 (0.03333) \left(\frac{-1}{6.563 \times 10^{-3}} \right) e^{-t/6.563 [\text{ms}]} = -1.904 e^{-t/6.563 [\text{ms}]} [\text{V}] \quad t > 0 [\text{ms}]$$

+6

We now integrate to get $i_2(t)$:

$$i_2(t) = \frac{1}{L_2} \int_0^t v_{leg}(t) dt + i_2(0^+) = \frac{1}{1 [\text{H}]} \int_0^t (-1.904) e^{-t/6.563 [\text{ms}]} dt + 0.0167$$

$$i_2(t) = [12.5 (e^{-t/6.563 [\text{ms}]} - 1) + 16.67] [\text{mA}] \quad t \geq 0 [\text{ms}]$$

Problem #6 (20 points)

For the circuit shown in Figure 6, the loads L_1 , L_2 , and L_3 are described as follows:

L_1 is a resistance R in series with a reactance of $+j39.2 \text{ } [\Omega]$, ~~$+j50 \text{ } [\Omega]$~~

L_2 is absorbing $2921.4 \text{ } [W]$ at a pf of 0.832 lagging,

L_3 is absorbing $2482.7 \text{ } [VA]$ at a pf of 0.196 leading.

Find:

- The value of R .
- The total reactive power delivered by the source.

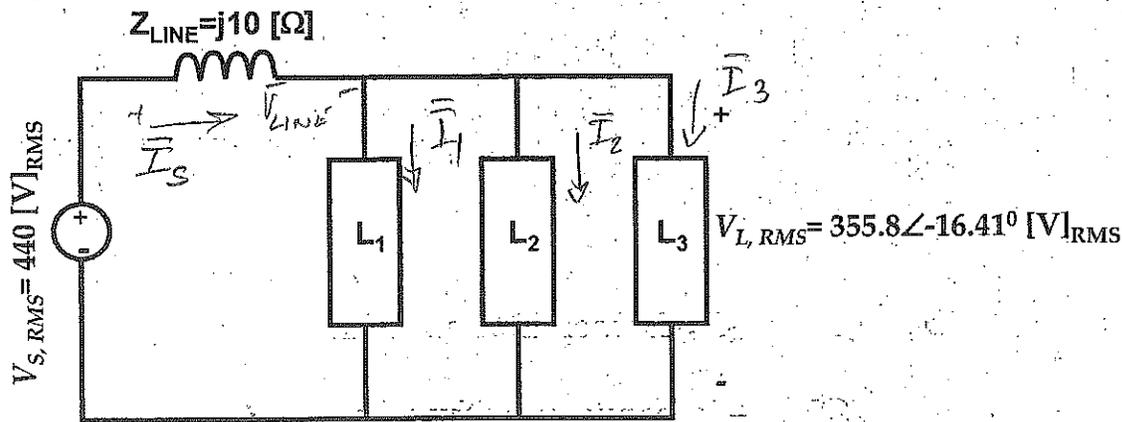


Figure 6.

$$\vec{I}_s = \frac{440 - 355.8 \angle -16.41^\circ}{j10} = \begin{cases} 14.12 \angle -44.46^\circ \\ 10.03 - j9.946 \end{cases} \text{ [A] rms}$$

$$S_{\text{del by } V_s} = \vec{V}_s \cdot \vec{I}_s^* = 6194.5 \angle 44.46^\circ \text{ [VA]} \\ = 4421 + j4339$$

The real power delivered by \vec{V}_s is $4421 \text{ } [W]$. This must be equal to the real power absorbed by the three loads together.

$$\vec{V}_{\text{LINE}} = j10 \vec{I}_s = \begin{cases} 99.42 + j100.3 \\ 141.2 \angle 45.2^\circ \end{cases} \text{ [V] rms}$$

→
pg. 13

Room for extra work

$$\text{LOAD 2} : |S_{L2}| = \frac{2921.4}{0.832} = 3511.3 \text{ [VA]}$$

$$\theta = 33.7^\circ$$

$$\text{pf} = 0.832 \Rightarrow \text{pf} = \sqrt{1 - (0.832)^2} = 0.5548$$

$$\Rightarrow S_{L2} = 2921.4 + j \overset{\text{lag}}{\downarrow} 3511.3(0.5548) = \left. \begin{array}{l} 2921.4 + j 1948.1 \\ 3511.3 \angle 33.7^\circ \end{array} \right\} \text{ [VA]}$$

LOAD 3

$$\text{pf} = 0.196 \Rightarrow \text{pf} = \sqrt{1 - (0.196)^2} = 0.9806$$

$$\theta = 78.7^\circ$$

$$\Rightarrow S_{L3} = 2482.7(0.196) - j \overset{\text{load}}{\downarrow} 2482.7(0.9806) = \left. \begin{array}{l} 487.5 - j 2434.5 \\ 2482.7 \angle -78.68^\circ \end{array} \right\} \text{ [VA]}$$

$$\text{Now } \bar{I}_2^* = \frac{S_{L2}}{\bar{V}_L} = \left. \begin{array}{l} 9.869 \angle 50.11^\circ \\ 6.329 + j 7.572 \end{array} \right\} \text{ [A]}_{\text{rms}}$$

$$\bar{I}_3^* = \frac{S_{L3}}{\bar{V}_L} = \left. \begin{array}{l} 6.978 \angle -62.22^\circ \\ 3.247 - j 6.176 \end{array} \right\} \text{ [A]}_{\text{rms}}$$

$$\bar{I}_1 = \bar{I}_0 - \bar{I}_2 - \bar{I}_3 = \left. \begin{array}{l} 8.559 \angle -86.98^\circ \\ 0.4500 - j 8.547 \end{array} \right\} \text{ [A]}_{\text{rms}}$$

$$\text{a) } Z_1 = \frac{\bar{V}_L}{\bar{I}_1} = \left. \begin{array}{l} 41.57 \angle 70.57^\circ \\ 13.83 + j 39.20 \end{array} \right\} [\Omega] \Rightarrow \underline{R = 13.8 [\Omega]}$$

$$\text{b) } Q_{del,s} = 4339 \text{ [VAR]} \text{ from previous page}$$