

Name: _____ Solution _____ (please print)

Signature: _____

ECE 2201 – Quiz #3
October 3, 2019


**Keep this quiz closed and
face up until you are told
to begin.**

1. This quiz is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution which is not given in a reasonable order will lose credit.
3. It is assumed that your work will begin on the same page as the problem statement. If you choose to begin your work on another page, you must indicate this on the page with the problem statement, with a clear indication of where the work can be found. **If your work continues on to another page, indicate clearly where your work can be found. Failure to indicate this clearly will result in a loss of credit.**
4. Show all units in solutions, intermediate results, and figures. Units in the quiz will be included between square brackets.
5. Do not use red ink. Do not use red pencil.
6. You will have 30 minutes to work on this quiz.

_____/25

Use the circuit shown in the figure below to find the indicated quantities.

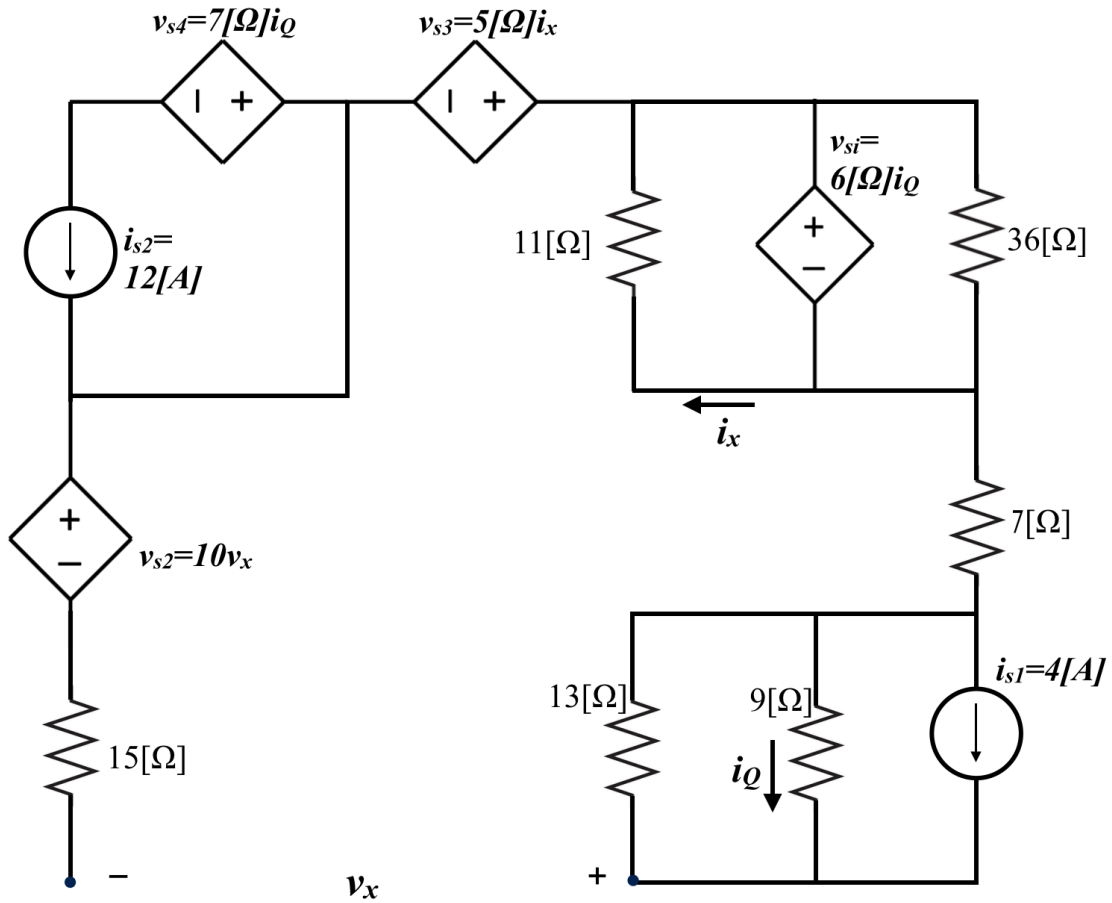- Find v_x .
- Find the power delivered by the v_{s4} voltage source.




ECE 2201, Quiz 3, October 3, 2019

Room for extra work

Use the circuit shown in the figure below to find the indicated quantities.

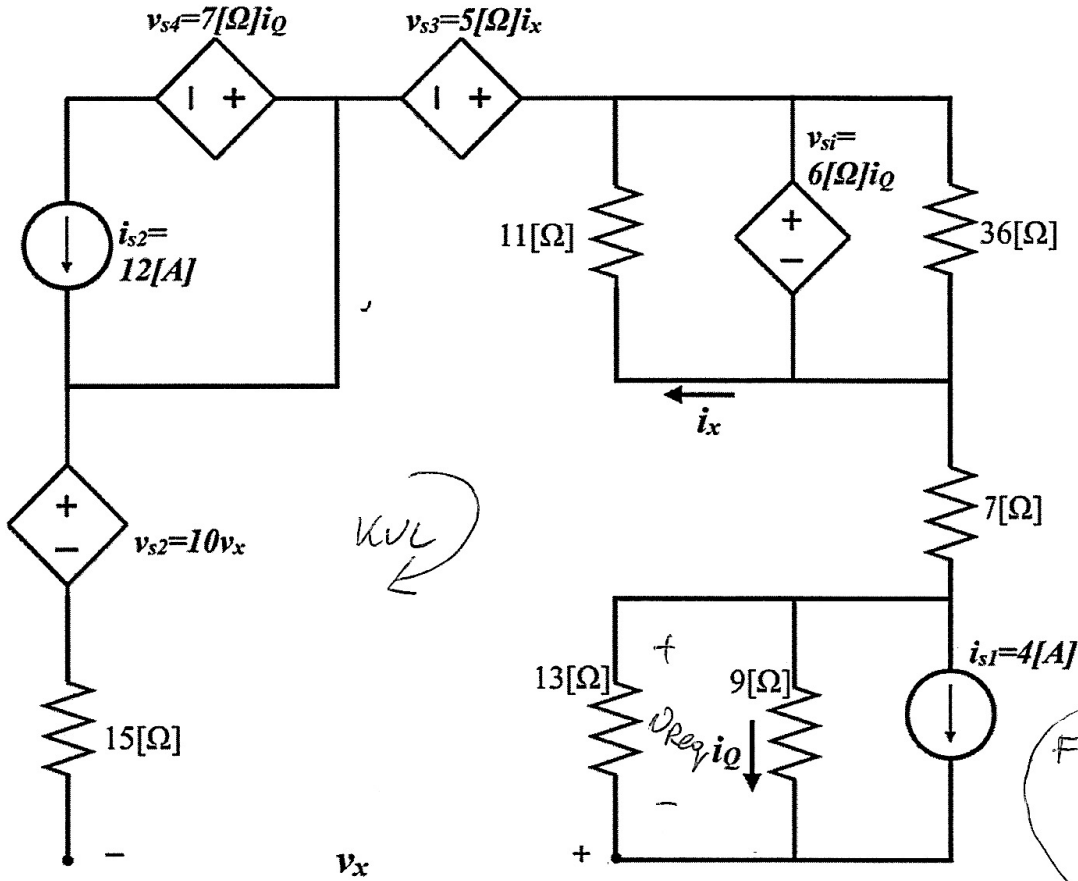- Find v_x .
- Find the power delivered by the v_{s4} voltage source.



a)

KVL

$$+v_x - 10v_x - 5[\Omega] \cdot i_x + 6[\Omega]i_Q + v_{req} = 0$$

$$i_Q = -4[A] \cdot \frac{13[\Omega] \cdot 9[\Omega]}{13[\Omega] + 9[\Omega]} \cdot \frac{1}{9[\Omega]} = -2.364[A]$$

$v_{req} = -21.27[V]$

$$i_x = -\frac{6[\Omega] \cdot i_Q}{11[\Omega]} = +\frac{14.18[V]}{11[\Omega]} = 1.289[A]$$

$$9v_x = -5[\Omega] \cdot 1.289[A] + 6[\Omega] \cdot (-2.364[A]) + (-21.28[V]) \Rightarrow v_x = -4.657[V]$$

$$\begin{aligned} 10) \quad P_{del, v_{s4}} &= -v_{s4} \cdot 12[A] = -7[V] \cdot (-2.364[A]) \cdot 12[A] \\ &= 198.6 [W] \end{aligned}$$

ECE 2201, Quiz 3, October 3, 2019

Room for extra work