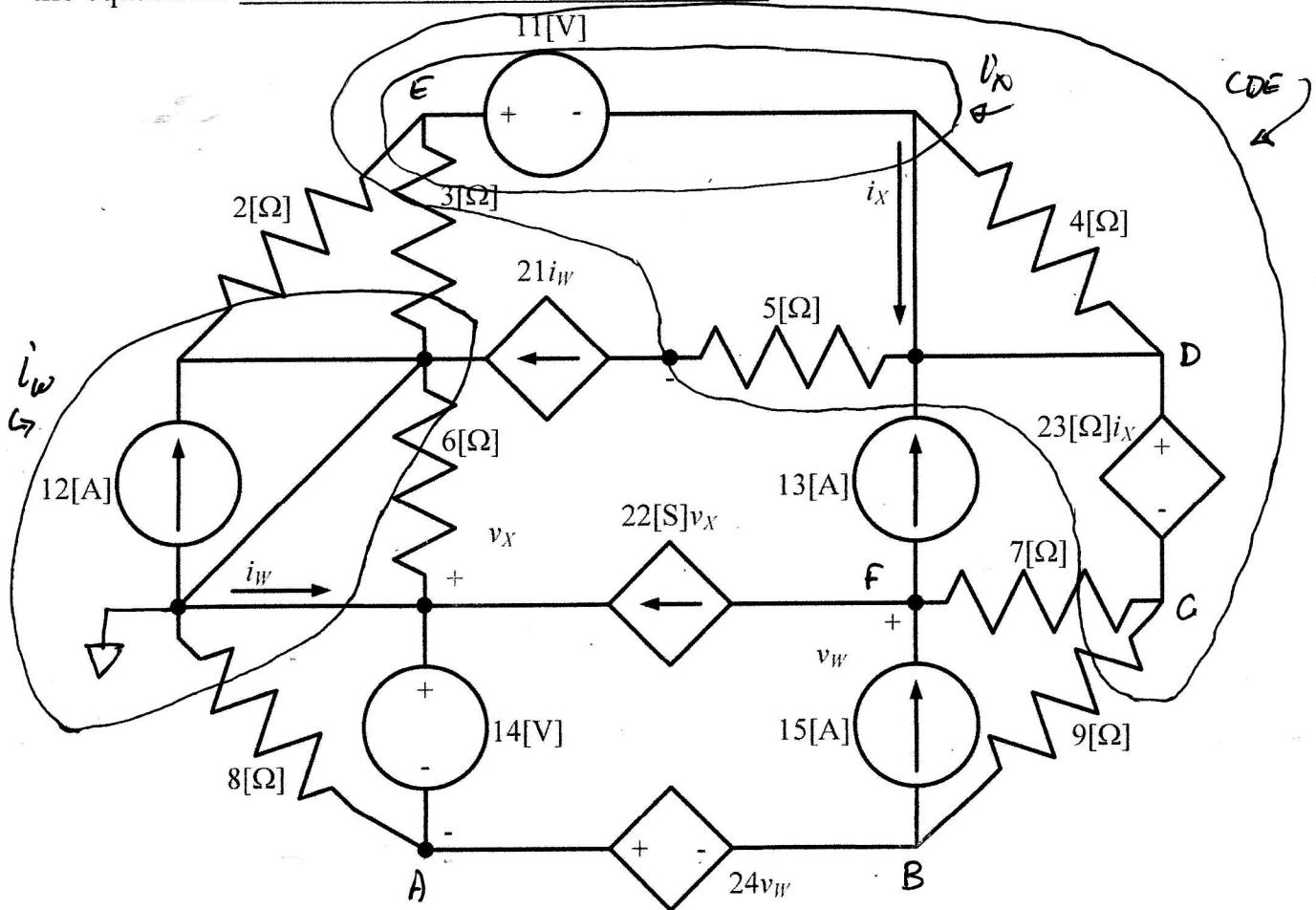


Use the node voltage method to write a complete set of equations that could be used to solve the circuit below. Do not simplify the circuit. Do not attempt to solve the equations. You must define all circuit variables.



$$A: V_A = -14[V]$$

$$C, D, E:$$

$$B: V_B = -24 \cdot V_w - 14$$

$$\frac{V_c - V_B}{9} + \frac{V_c - V_F}{7} - 13[A] + 21i_w + \frac{V_E}{3} + \frac{V_E}{2} = 0$$

$$V_c - V_D = -23[\Omega] i_x \quad V_D - V_E = -11[V]$$

$$F: \frac{V_F - V_c}{7} + 13[A] - 15[A] + 22[S] V_x = 0$$

$$i_x: i_x + \frac{V_E}{3} + \frac{V_E}{2} = 0$$

$$V_x: V_x - 5(21i_w) + V_D = 0$$

$$i_w: i_w - 21i_w - \frac{V_E}{3} - \frac{V_E}{2} - \frac{V_A}{8} = 0$$

$$V_w: -V_w + V_F + 14[V]$$