

Name: _____ (please print)

Signature: _____

ECE 2201 -- Exam #1
February 11, 2017

**Keep this exam closed until you
are told to begin.**

1. This exam is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution that is not given in a reasonable order will lose credit. Clearly indicate your answer (for example by enclosing it in a box).
3. It is assumed that your work will begin on the same page as the problem statement. If you choose to begin your work on another page, you must indicate this on the page with the problem statement, with a clear indication of where the work can be found. **If your work continues on to another page, indicate clearly where your work can be found. Failure to indicate this clearly will result in a loss of credit.**
4. Show all units in solutions, intermediate results, and figures. Units in the exam will be included between square brackets.
5. Do not use red ink. Do not use red pencil.
6. You will have 90 minutes to work on this exam.

1. _____/35

2. _____/30

3. _____/35

Total = 100

Room for extra work

1. {35 Points} Four devices are connected as shown in Figure 1. The power delivered by Device 1 is given by the expression

$$p_{DEL.BY.DEV1}(t) = 36 \left[\frac{\mu W}{s^2} \right] t^2 - 72 \left[\frac{\mu W}{s} \right] t \quad \text{for } 2[s] < t < 5[s].$$

The voltages $v_X(t)$ and $v_Z(t)$ are shown in Figures 2 and 3, respectively.

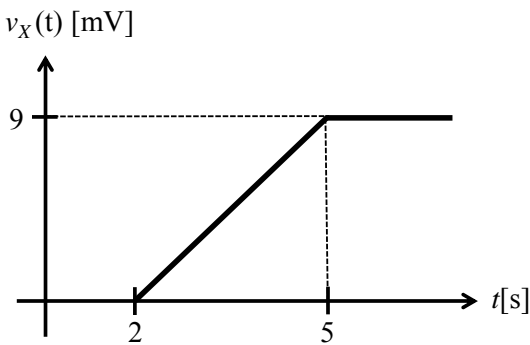
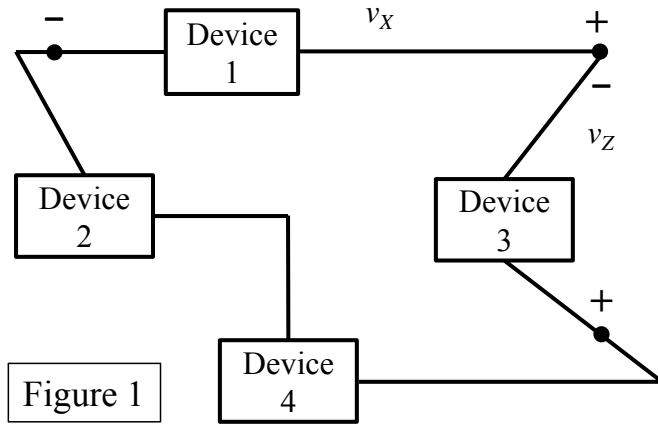


Figure 2

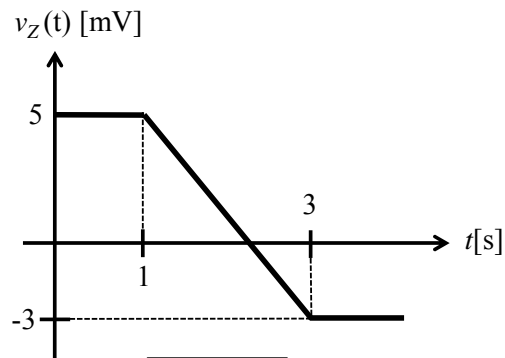


Figure 3

- What is the energy absorbed by Device 1 during the time period $2[s] < t < 4[s]$?
- Which way are the electrons moving through Device 1 at $t=3.5[s]$? Your answer should be either left to right, or right to left. Explain how you got your answer.
- Find the expression for the power delivered to Device 3 for the time interval $2[s] < t < 3[s]$.

Rom for extra work

2. {30 Points} Six components, labeled A, B, C, D, E, and F, are connected as shown in Figure 1.

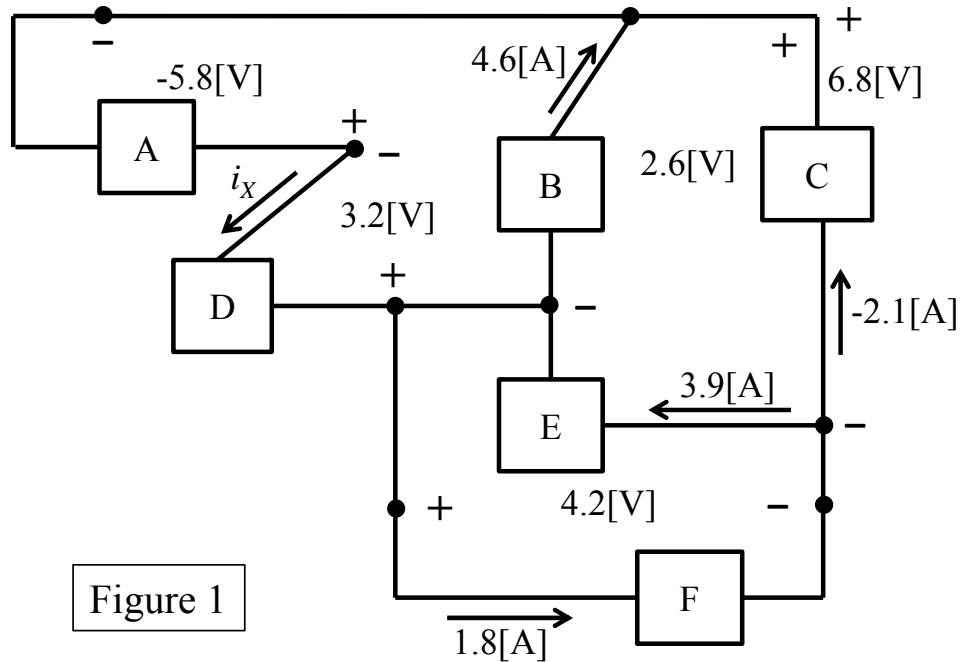


Figure 1

- Find the value of i_x based on the fact that energy is conserved in this circuit. Do NOT use Kirchhoff's Laws in your solution.
- Using the value of i_x that you found in part a), show that the total power absorbed is equal to the total power delivered.
- Are the electrons gaining or losing energy when they move through component F? Explain your answer.

Room for extra work

3. {35 Points} 4 components are connected together as shown in Figure 1. Assume that the charge carriers are electrons.

- Find the expressions for the power delivered by the charger for the time interval $0 < t < 12$ [min] and plot it as a function of time.
- Determine whether the electrons flowing through the charger at $t = 5$ [min] are gaining or losing energy. Explain how you got your answer.
- Find the expression for the power absorbed by the battery for $0 < t < 12$ [min]. Calculate the numerical values of power absorbed by the battery for $t = 5$ [min] and $t = 12$ [min] and decide if power is absorbed or delivered by the battery.
- Within the time interval $0 < t < 12$ [min], calculate the amount of charge that flows through the battery, when battery is absorbing energy.
- Within the time interval $0 < t < 12$ [min], calculate the amount of charge that flows through the battery, when battery is delivering energy.

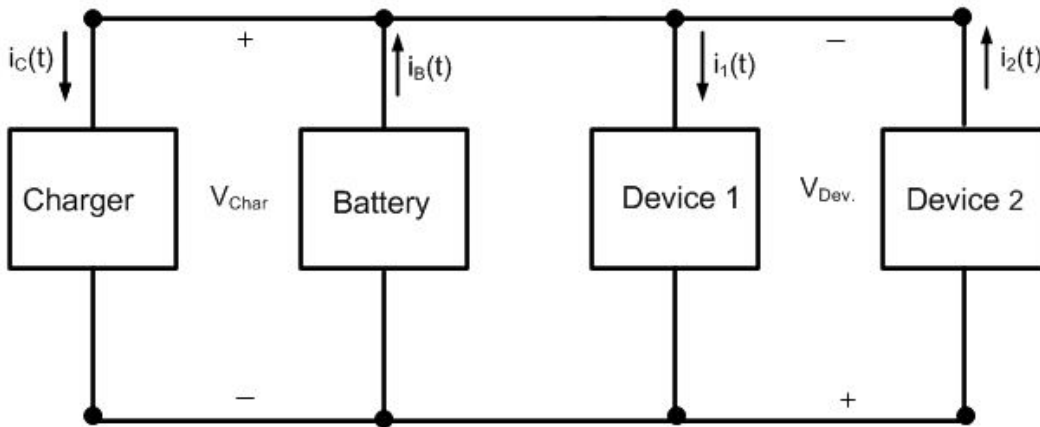


Figure 1

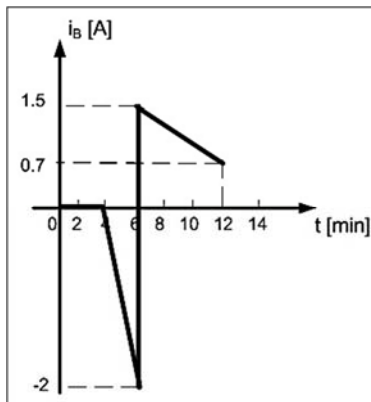


Figure 2

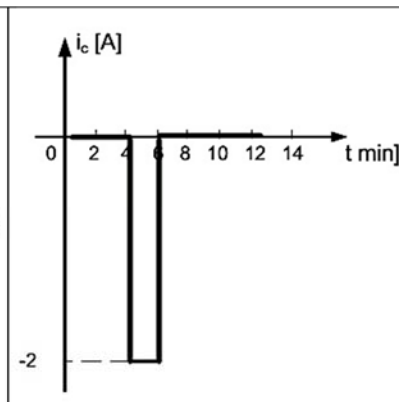


Figure 3

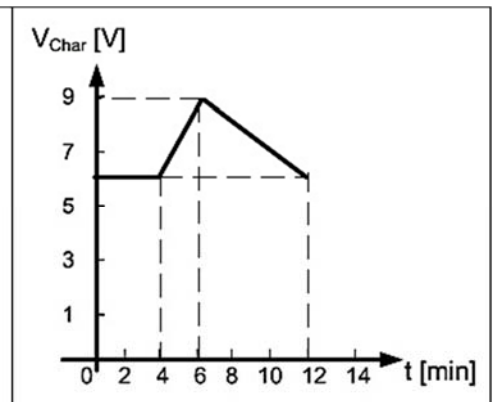


Figure 4

Room for extra work

Name: Solutions (please print)

Signature: _____

ECE 2201 -- Exam #1
February 11, 2017

Keep this exam closed until you
are told to begin.

1. This exam is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution that is not given in a reasonable order will lose credit. Clearly indicate your answer (for example by enclosing it in a box).
3. It is assumed that your work will begin on the same page as the problem statement. If you choose to begin your work on another page, you must indicate this on the page with the problem statement, with a clear indication of where the work can be found. **If your work continues on to another page, indicate clearly where your work can be found. Failure to indicate this clearly will result in a loss of credit.**
4. Show all units in solutions, intermediate results, and figures. Units in the exam will be included between square brackets.
5. Do not use red ink. Do not use red pencil.
6. You will have 90 minutes to work on this exam.

1. _____/35

2. _____/30




3. _____/35

Total = 100

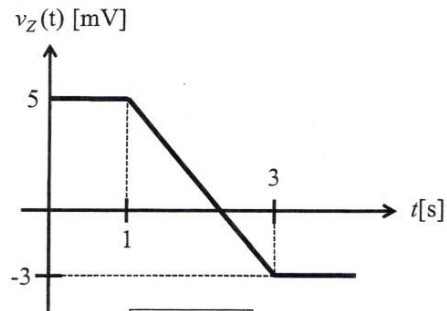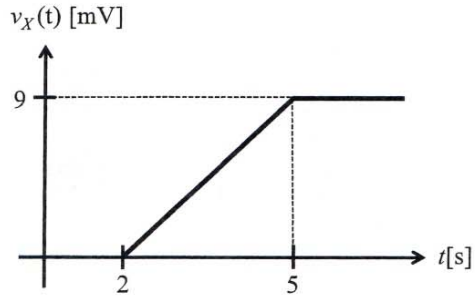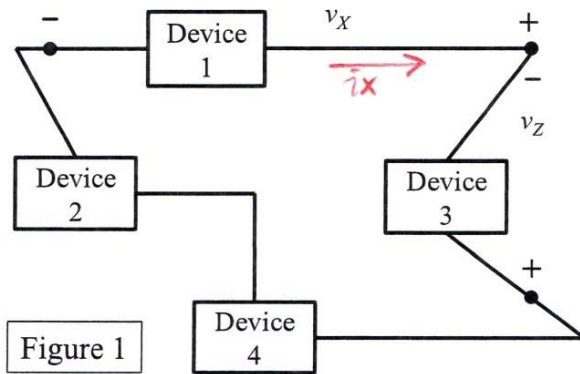1. {35 Points} Four devices are connected as shown in Figure 1. The power delivered by Device 1 is given by the expression

$$p_{DEL.BY.DEV1}(t) = 36 \left[\frac{\mu W}{s^2} \right] t^2 - 72 \left[\frac{\mu W}{s} \right] t \quad \text{for } 2[s] < t < 5[s].$$

The voltages $v_X(t)$ and $v_Z(t)$ are shown in Figures 2 and 3, respectively.



- What is the energy absorbed by Device 1 during the time period $2[s] < t < 4[s]$?
- Which way are the electrons moving through Device 1 at $t=3.5[s]$? Your answer should be either left to right, or right to left. Explain how you got your answer.
- Find the expression for the power delivered to Device 3 for the time interval $2[s] < t < 3[s]$.

$$a) \quad W_{ABS, DEV1} = \int_{2[s]}^{4[s]} \left(-36 \left[\frac{\mu W}{s^2} \right] t^2 + 72 \left[\frac{\mu W}{s} \right] t \right) dt$$

$$= -240 [MJ]$$

b) We need to find the current through Device 1. First we need to define it on the circuit. . .

Room for extra work

We are given an expression for $p_{\text{DEL,DEV1}}$ and also a plot for the voltage across Device 1.

$$v_x(t) = 3 [\text{mV/s}] t - 6 [\text{mV}] \quad 2[\text{s}] < t < 5[\text{s}]$$

$$p_{\text{DEL,DEV1}}(t) = v_x(t) i_x(t)$$

$$i_x(t) = \frac{36 [\text{mW/s}^2] t^2 - 72 [\text{mW/s}] t}{3 [\text{mV/s}] t - 6 [\text{mV}]} = 12 [\text{mA/s}] t$$

for $2[\text{s}] < t < 5[\text{s}]$

For $t = 3.5[\text{s}]$, $i_x(t) > 0$. So electrons are moving from right to left.

$$\cdot \text{c) } p_{\text{DEL TO DEV3}} = p_{\text{ABS, DEV3}} = -v_z \cdot i_x$$

$$v_z(t) = -4 [\text{mV/s}] t + 9 [\text{mV}] \quad (\text{from the graph})$$

$$p_{\text{ABS, DEV3}}(t) = +48 [\text{mW/s}^2] t^2 - 108 [\text{mW/s}] t,$$

for $2[\text{s}] < t < 3[\text{s}]$

Alternative solution for part b)

$$p_{\text{DEL, DEV1}}(3.5[\text{s}]) = 189 [\mu\text{W}] > 0$$

$$v_x(3.5[\text{s}]) > 0 \quad (\text{from graph}) \Rightarrow i_x(3.5[\text{s}]) > 0$$

Electrons flow from right to left. \vdots

2. {30 Points} Six components, labeled A, B, C, D, E, and F, are connected as shown in Figure 1.

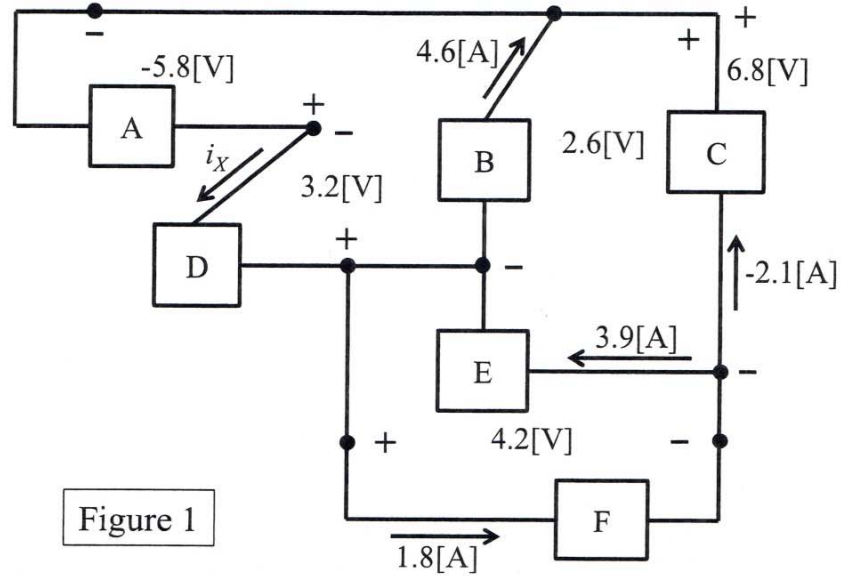


Figure 1

- Find the value of i_x based on the fact that energy is conserved in this circuit. Do NOT use Kirchhoff's Laws in your solution.
- Using the value of i_x that you found in part a), show that the total power absorbed is equal to the total power delivered.
- Are the electrons gaining or losing energy when they move through component F? Explain your answer.

a) Since energy is conserved, $P_{abs,A} + P_{abs,B} + P_{abs,C} + P_{abs,D} + P_{abs,E} + P_{abs,F} = 0$

$$P_{abs,A} + P_{abs,B} + P_{abs,C} + P_{abs,D} + P_{abs,E} + P_{abs,F} = 0$$

$$P_{abs,A} = -(-5.8[V]) i_x \quad P_{abs,B} = -2.6[V] 4.6[A]$$

$$P_{abs,C} = -(-2.1[V]) 6.8[V] \quad P_{abs,D} = -3.2[V] i_x$$

$$P_{abs,E} = -4.2[V] 3.9[A] \quad P_{abs,F} = 1.8[A] 4.2[V]$$

$$0 = 5.8[V] i_x - 11.96[W] + 14.28[W] - 3.2[V] i_x - 16.38[W] + 7.56[W]$$

Room for extra work

$$i_x = 2.5 \text{ [A]}$$

$$\begin{aligned} \text{b) } p_{\text{ABS},A} &= 5.8 \text{ [V]} i_x = 14.5 \text{ [W]} && \text{'A' absorbs } 14.5 \text{ [W]} \\ p_{\text{ABS},B} &= -11.96 \text{ [W]} && \text{'B' delivers } 11.96 \text{ [W]} \\ p_{\text{ABS},C} &= 14.28 \text{ [W]} && \text{'C' absorbs } 14.28 \text{ [W]} \\ p_{\text{ABS},D} &= -3.2 \text{ [V]} i_x = -8 \text{ [W]} && \text{'D' delivers } 8 \text{ [W]} \\ p_{\text{ABS},E} &= -16.38 \text{ [W]} && \text{'E' delivers } 16.38 \text{ [W]} \\ p_{\text{ABS},F} &= 7.56 \text{ [W]} && \text{'F' absorbs } 7.56 \text{ [W]} \end{aligned}$$

$$\begin{aligned} \text{Total power absorbed} &= (14.5 + 14.28 + 7.56) \text{ [W]} = 36.34 \text{ [W]} \\ \text{Total power delivered} &= (11.96 + 8 + 16.38) \text{ [W]} = 36.34 \text{ [W]} \end{aligned}$$

Total power del. = Total power abs.

c) Component 'F' absorbs power. This energy comes from the electrons passing through 'F'. So, electrons lose energy when they move through component 'F'.

3. {35 Points} 4 components are connected together as shown in Figure 1. Assume that the charge carriers are electrons.

- Find the expressions for the power delivered by the charger for the time interval $0 < t < 12$ [min] and plot it as a function of time.
- Determine whether the electrons flowing through the charger at $t = 5$ [min] are gaining or losing energy. Explain how you got your answer.
- Find the expression for the power absorbed by the battery for $0 < t < 12$ [min]. Calculate the numerical values of power absorbed by the battery for $t = 5$ [min] and $t = 12$ [min] and decide if power is absorbed or delivered by the battery.
- Within the time interval $0 < t < 12$ [min], calculate the amount of charge that flows through the battery, when battery is absorbing energy.
- Within the time interval $0 < t < 12$ [min], calculate the amount of charge that flows through the battery, when battery is delivering energy.

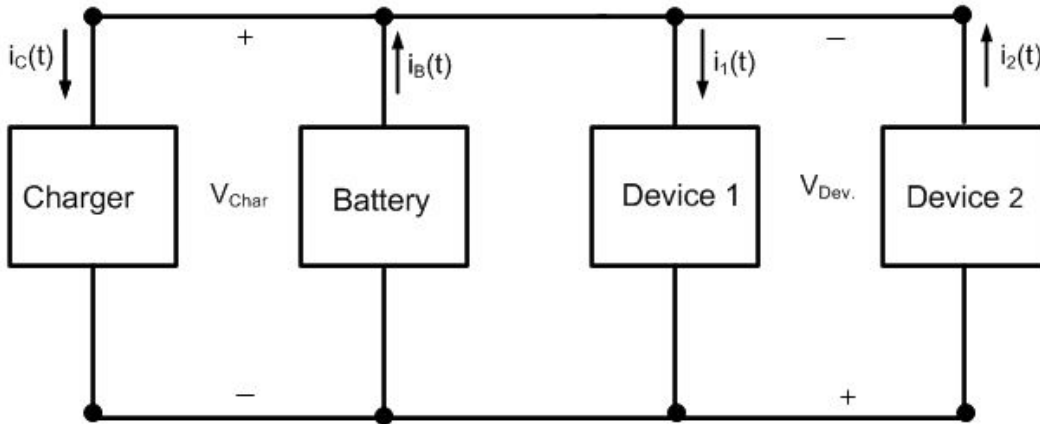


Figure 1

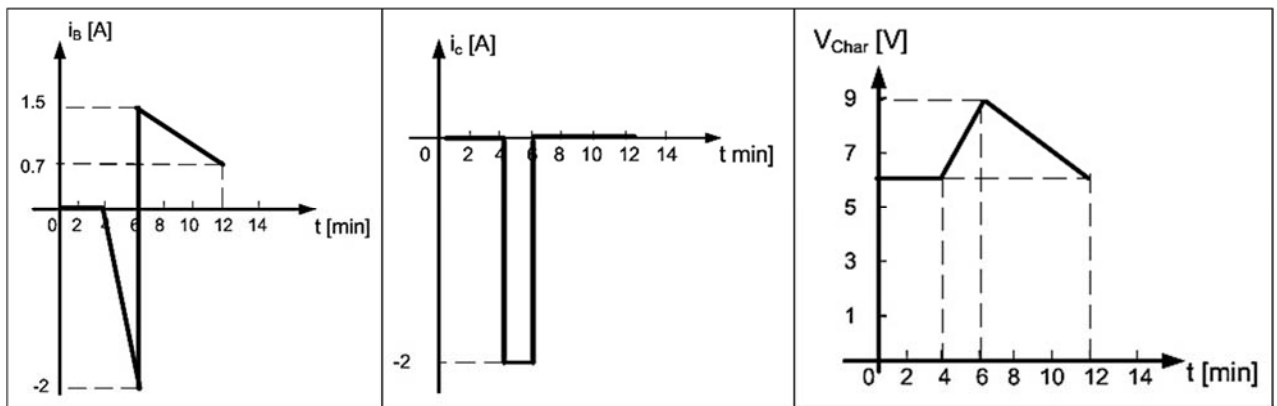


Figure 2

Figure 3

Figure 4

We used passive sign convention for the charger so


$$a) P_{del, char} = -i_c(t) \cdot v_{char}(t)$$

For $4 < t < 6$ min

$$v_{char}(t) = \frac{9-6}{2} \cdot t = \frac{3}{2} \left[\frac{V}{min} \right] \cdot t [min] = \frac{3}{2} t [V]$$

$i_c(t) = -2[A]$ i.e. current flows in opposite direction than marked by the arrow.
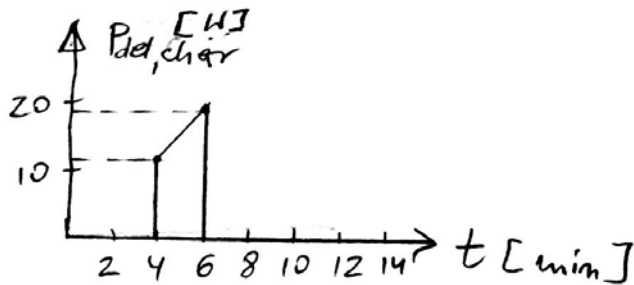
$$P_{del, char} = -(-2) \cdot \frac{3}{2} t = 3t [W]$$



b) Electrons flow from \oplus to \ominus so their potential energy increases therefore they are gaining energy. If we assume that \oplus charges flow (\oplus charge convention), then they would also gain energy. So in both cases the charges are moving in opposite directions then they would normally move \equiv they gain energy.

$$c) P_{abs, Batt} = -i_b(t) \cdot v_{char}(t) \quad (\text{here active sign convention is used})$$

For $t > 6 [min]$ & $0 < t < 4 [min]$

$$P_{abs, Batt} = 0$$

Intervals:

$$4 < t < 6 \text{ [min]} \quad P_{\text{abs, Batt}} = - \left(\underbrace{-\frac{2 \text{ [A]}}{2 \text{ [min]}} \cdot t \text{ [min]} + 4}_{i_B} \right) \cdot \underbrace{\frac{3}{2} t}_{v_{\text{char}}} \\ = +\frac{3}{2} t^2 - 6t \text{ [W]}$$

$$6 < t < 12 \text{ [min]}$$

$$i_B(t) = \frac{0.7 - 1.5}{6} t + 2.3 = -0.133t + 2.3 \text{ [A]}$$

$$v_{\text{char}}(t) = \frac{6 - 9}{6} \cdot t + 12 = -0.5t + 12 \text{ [V]}$$

$$P_{\text{abs, Batt}} = -(-0.133t + 2.3)(-0.5t + 12) = \\ = -(6.65 \cdot 10^{-2} t^2 - 1.15t - 1.6t + 27.6) = \\ = -(6.65 \cdot 10^{-2} t^2 - 2.75t + 27.6) \text{ [W]}$$

$$\text{@ } t = 5 \text{ [min]}$$

$$P_{\text{abs, Batt}} = +7.5 \text{ [W]} \quad \text{the battery absorbs power.}$$

$$\text{@ } t = 12 \text{ [min]}$$

$$P_{\text{abs, Batt}} = -4.18 \text{ [W]} \quad \text{so the battery delivers positive power.}$$

d) Charge - when the battery is being charged

$$Q_1 = \int_4^6 i_B(t) dt = \frac{1}{2} \cdot 2 \text{ [A]} \cdot 2 \cdot 60 \text{ [s]} = 120 \text{ [C]}$$

e) Charge - when the battery delivers power

$$Q_2 = \int_6^{12} i_B(t) dt = [0.7 \cdot (12 - 6) + \frac{1}{2} (1.5 - 0.7)(12 - 6)] \times 60 \\ = 396 \text{ [C]}$$