

Name: Solutions (please print)

Signature: _____

ECE 2201 -- Exam # 3
April 8, 2017

Keep this exam closed until you
are told to begin.

1. This exam is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution that is not given in a reasonable order will lose credit. Clearly indicate your answer (for example by enclosing it in a box).
3. It is assumed that your work will begin on the same page as the problem statement. If you choose to begin your work on another page, you must indicate this on the page with the problem statement, with a clear indication of where the work can be found. **If your work continues on to another page, indicate clearly where your work can be found. Failure to indicate this clearly will result in a loss of credit.**
4. Show all units in solutions, intermediate results, and figures. Units in the exam will be included between square brackets.
5. Do not use red ink. Do not use red pencil.
6. You will have 90 minutes to work on this exam.

1. _____/35


2. _____/30

3. _____/35

Total = 100

Room for extra work

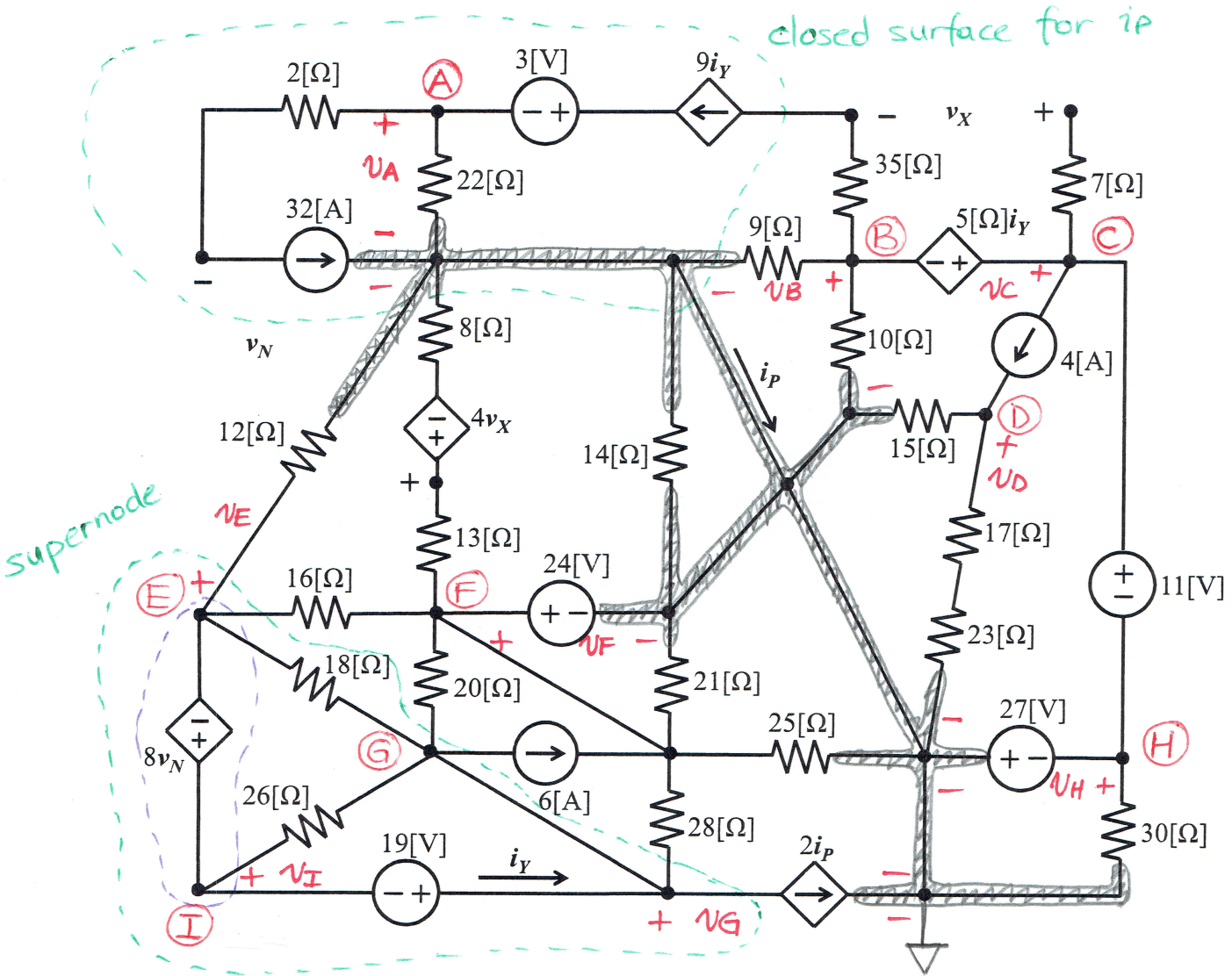1. {35 Points} Use the node-voltage method to write a complete set of equations that could be used to solve this circuit. Do not simplify the circuit. Do not attempt to simplify or solve your equations. **Define all variables clearly.**



10 essential nodes, 4 dep. source variables $\Rightarrow 9+4 = 13$ eq.s.

(A) : $32[A] - 9i_y + \frac{v_A}{22[\Omega]} = 0$

(B+C) : $v_C - v_B = 5[\Omega]i_y$

(C+H) : $v_C - v_H = 11[V]$

(H) : $v_H = -27[V]$

Room for extra work

$$\textcircled{D}: -4[A] + \frac{v_D}{17[\Omega] + 23[\Omega]} + \frac{v_D}{15[\Omega]} = 0$$

$$\textcircled{E+G+I}: \frac{v_E}{12[\Omega]} + \frac{v_E - v_F}{16[\Omega]} + \frac{v_G - v_F}{20[\Omega]} + 6[A] + \frac{v_G - v_F}{28[\Omega]} + 2i_P = 0$$

$$\textcircled{E+I}: v_I - v_E = 8V_N$$

$$\textcircled{I+G}: v_G - v_I = 19[V]$$

$$\textcircled{F}: v_F = 24[V]$$

Auxiliary equations:



$$\textcircled{v_N}: -32[A] \cdot 2[\Omega] + v_A - v_F + \frac{v_F - 4v_X}{21[\Omega]} \cdot 13[\Omega] + v_N = 0$$

$$\textcircled{v_X}: -v_X + v_C - v_B + 9i_Y \cdot 35[\Omega] = 0$$

$$\textcircled{i_P}: i_P = \frac{v_B}{9[\Omega]} = 9i_Y = \frac{v_E}{12[\Omega]} = \frac{v_F - 4[\Omega]i_X}{21[\Omega]} + \frac{0}{14[\Omega]} = 0$$

$$\textcircled{i_Y}: \frac{v_E}{12[\Omega]} + \frac{v_E - v_F}{16[\Omega]} + \frac{v_E - v_G}{18[\Omega]} + \frac{v_I - v_G}{26[\Omega]} + i_Y = 0$$

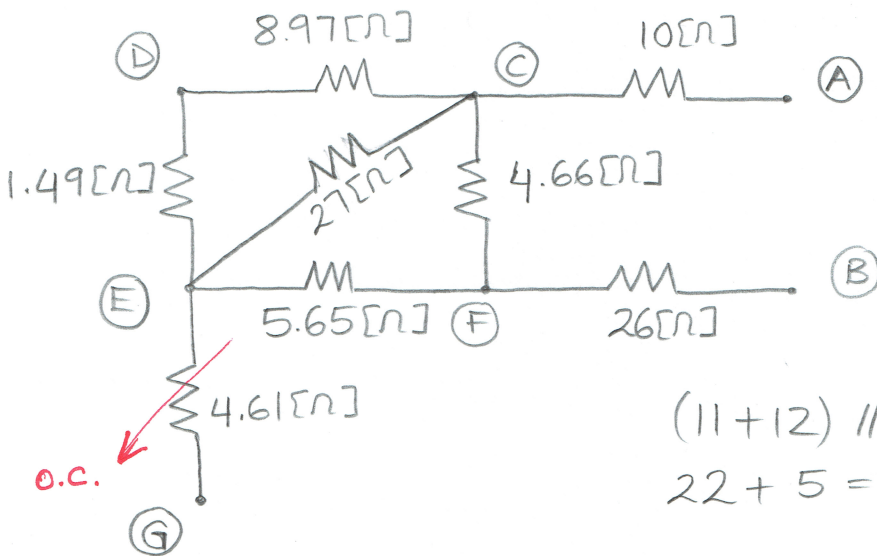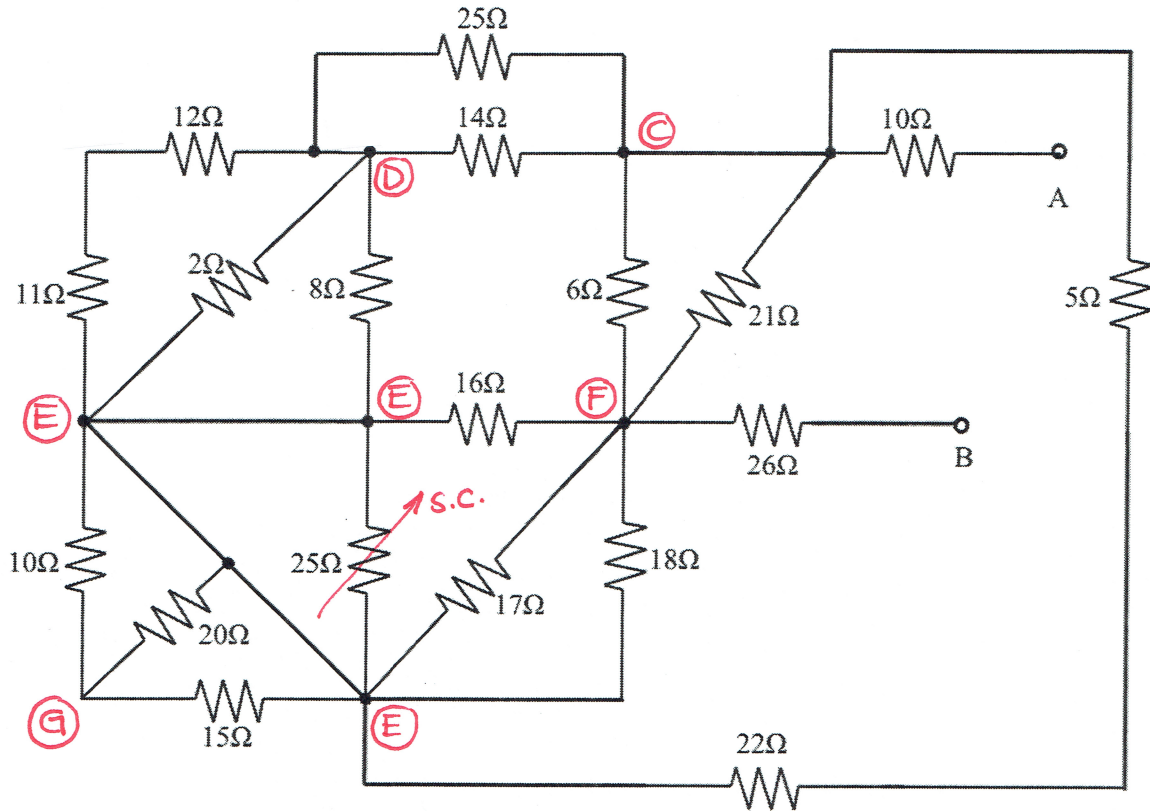2. {30 Points} In the circuit shown below please find the value of the equivalent resistance seen from terminals A and B.



$$25 \parallel 14 = 8.97 [\Omega]$$


$$6 \parallel 21 = 4.66 [\Omega]$$

$$16 \parallel 17 \parallel 18 = 5.65 [\Omega]$$

$$10 \parallel 20 \parallel 15 = 4.61 [\Omega]$$


$$(11 + 12) \parallel 2 \parallel 8 = 1.49 [\Omega]$$

$$22 + 5 = 27 [\Omega]$$

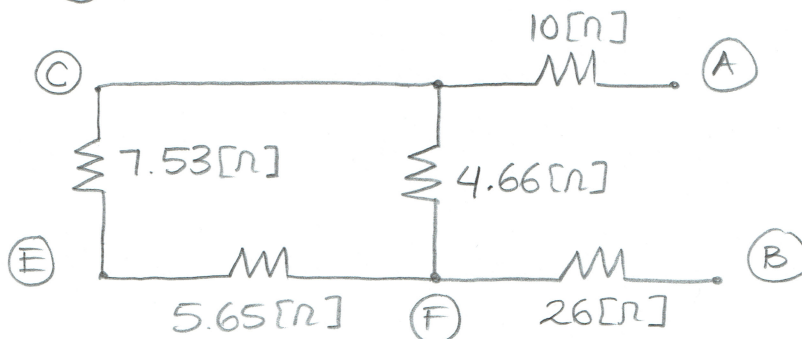


$$(8.97 + 1.49) \parallel 27 = 7.53 [\Omega]$$

Room for extra work

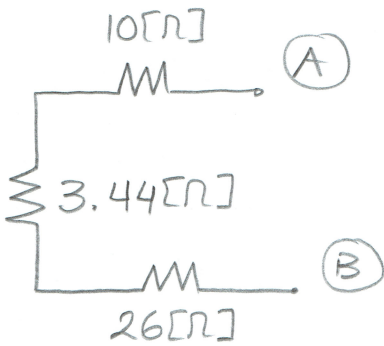
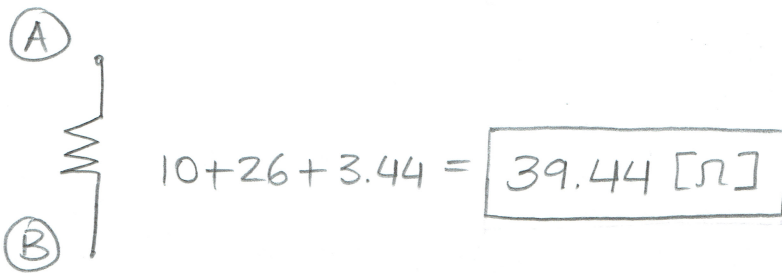
$$(7.53 + 5.65) \parallel 4.66 = 3.44 [\Omega]$$





3. {35 Points} A device (device1), shown in Figure 1, can be modeled as a current source in parallel with a resistance. The relationship between the voltage across device 1, v_D and current through device 1, i_D is shown in Figure 2.

Another device (device2), shown in Figure 3, can be modeled as a voltage source in series with a resistance. The relationship between the voltage across device 2, v_S and current through device 2, i_S is shown in Figure 4.


a) Find a model for Device 2 that would be valid for $9[mA] < i_S < 12[mA]$ and draw it showing terminals C and D.

Device 2 and two identical versions of Device 1 are connected as shown in Figure 5. Pay attention to the way the terminals of the devices are connected. Refer to Figure 5, for the following questions:



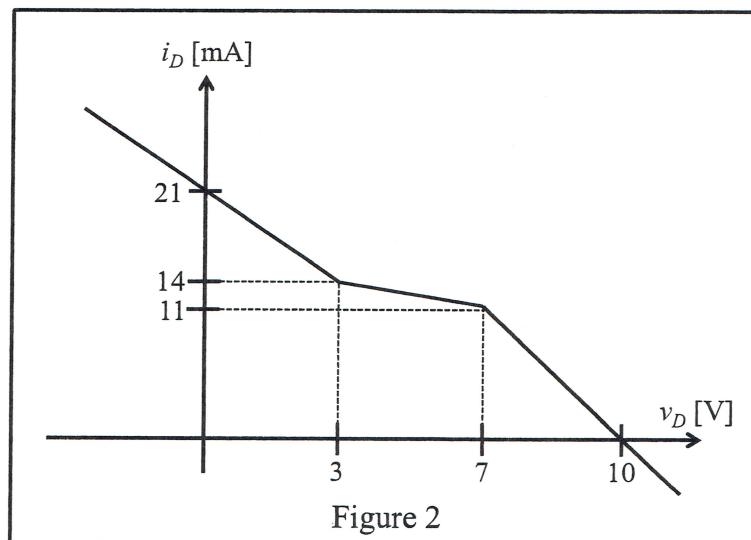
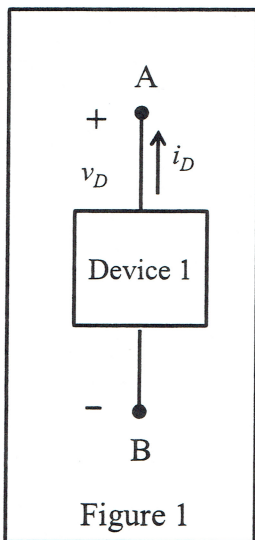
- b) Find v_X .
- c) Find the power absorbed by Device 2.
- d) Find the power delivered by v_P .



a) For $9[mA] < i_S < 12[mA]$

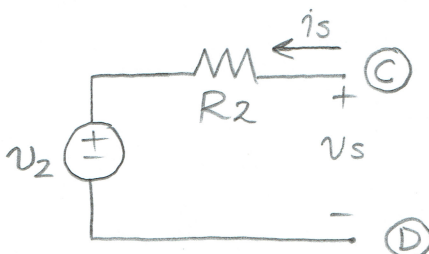
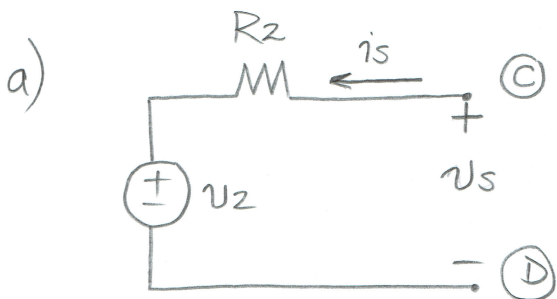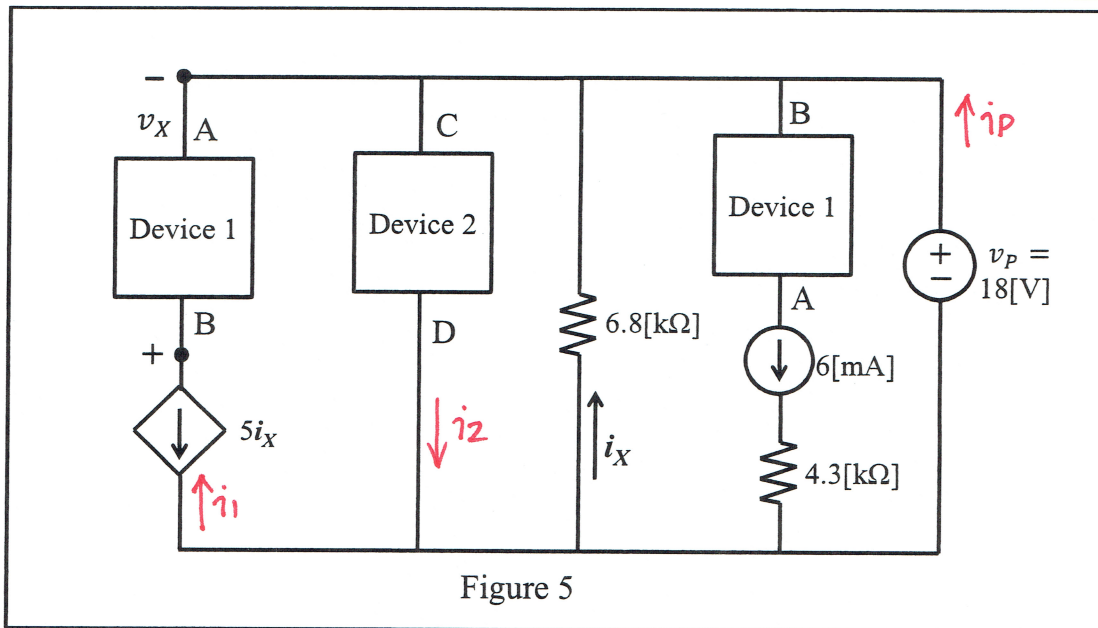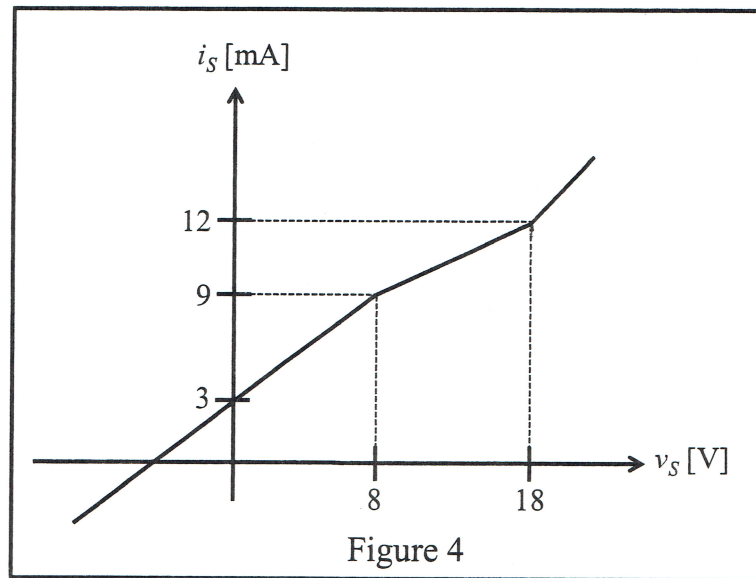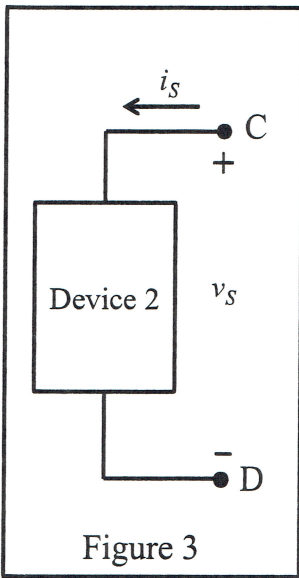
$$\begin{aligned}
 -v_2 - R_2 \cdot i_S + v_S &= 0 \\
 -v_2 - R_2 \cdot 9[mA] + 8[V] &= 0 \\
 -v_2 - R_2 \cdot 12[mA] + 18[V] &= 0
 \end{aligned}$$




$$-v_2 - R_2 \cdot i_s + v_s = 0$$

$$-v_2 - R_2 \cdot 9 \text{ [mA]} + 8 \text{ [V]} = 0$$

$$-v_2 - R_2 \cdot 12 \text{ [mA]} + 18 \text{ [V]} = 0$$

Solving above we get :
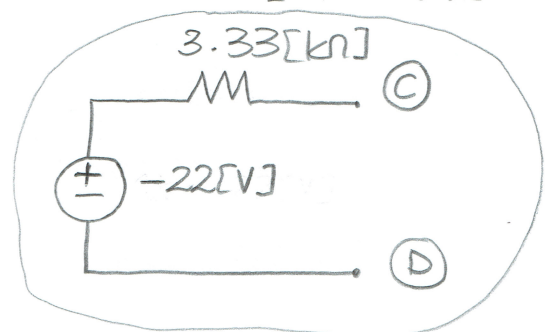
$$v_2 = -22 \text{ [V]} \quad R_2 = 3.33 \text{ [k}\Omega\text{]}$$



Room for extra work

$$b) \quad i_x = \frac{-18[V]}{6.8[k\Omega]} = -2.64 [mA] \quad 5i_x = -13.23 [mA]$$

$$i_1 = 13.23 [mA]$$

We can find v_x , using Figure 2, noting that i_D in Figure 1 is $13.23 [mA]$.

What is v_D , for $i_D = 13.23 [mA]$? We need to find the equation of i_D for the interval $11 [mA] < i_D < 14 [mA]$.

$$i_D = -\frac{3}{4} [mA/V] \cdot v_D + 16.25 [mA]$$

$$\text{For } i_D = 13.23 [mA] \Rightarrow v_D = 4.02 [V]$$

$$v_x = -v_D = \boxed{-4.02 [V]}$$

$$c) \quad p_{ABS, DEV2} = 18 [V] \cdot i_2$$

We can find i_2 , using Figure 4, noting that v_s in Figure 3 (voltage across Device 2) is equal to $18 [V]$.

$$\text{For } v_s = 18 [V] \Rightarrow i_s = 12 [mA] \Rightarrow i_2 = 12 [mA]$$

$$\boxed{p_{ABS, DEV2} = 216 [mW]}$$

$$d) \quad p_{DEL, NP} = v_p \cdot i_p \quad \text{KCL: } -i_p + 6 [mA] - i_x + i_2 + 5i_x = 0$$

$$\Rightarrow i_p = 7.41 [mA]$$

$$p_{DEL, NP} = 18 [V] \times 7.41 [mA] = \boxed{133.38 [mW]}$$

Room for extra work