

Name: Solutions (please print)

Signature: \_\_\_\_\_

ECE 2201 – Final Exam  
May 3, 2018

Keep this exam closed until you  
are told to begin.


1. This exam is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution that is not given in a reasonable order will lose credit. Clearly indicate your answer (for example by enclosing it in a box).
3. It is assumed that your work will begin on the same page as the problem statement. If you choose to begin your work on another page, you must indicate this on the page with the problem statement, with a clear indication of where the work can be found. **If your work continues on to another page, indicate clearly where your work can be found. Failure to indicate this clearly will result in a loss of credit.**
4. Show all units in solutions, intermediate results, and figures. Units in the exam will be included between square brackets.
5. Do not use red ink. Do not use red pencil.
6. You will have 170 minutes to work on this exam.

1. \_\_\_\_\_/30
2. \_\_\_\_\_/30
3. \_\_\_\_\_/35
4. \_\_\_\_\_/35
5. \_\_\_\_\_/35
6. \_\_\_\_\_/35

Total = 200

Room for extra work

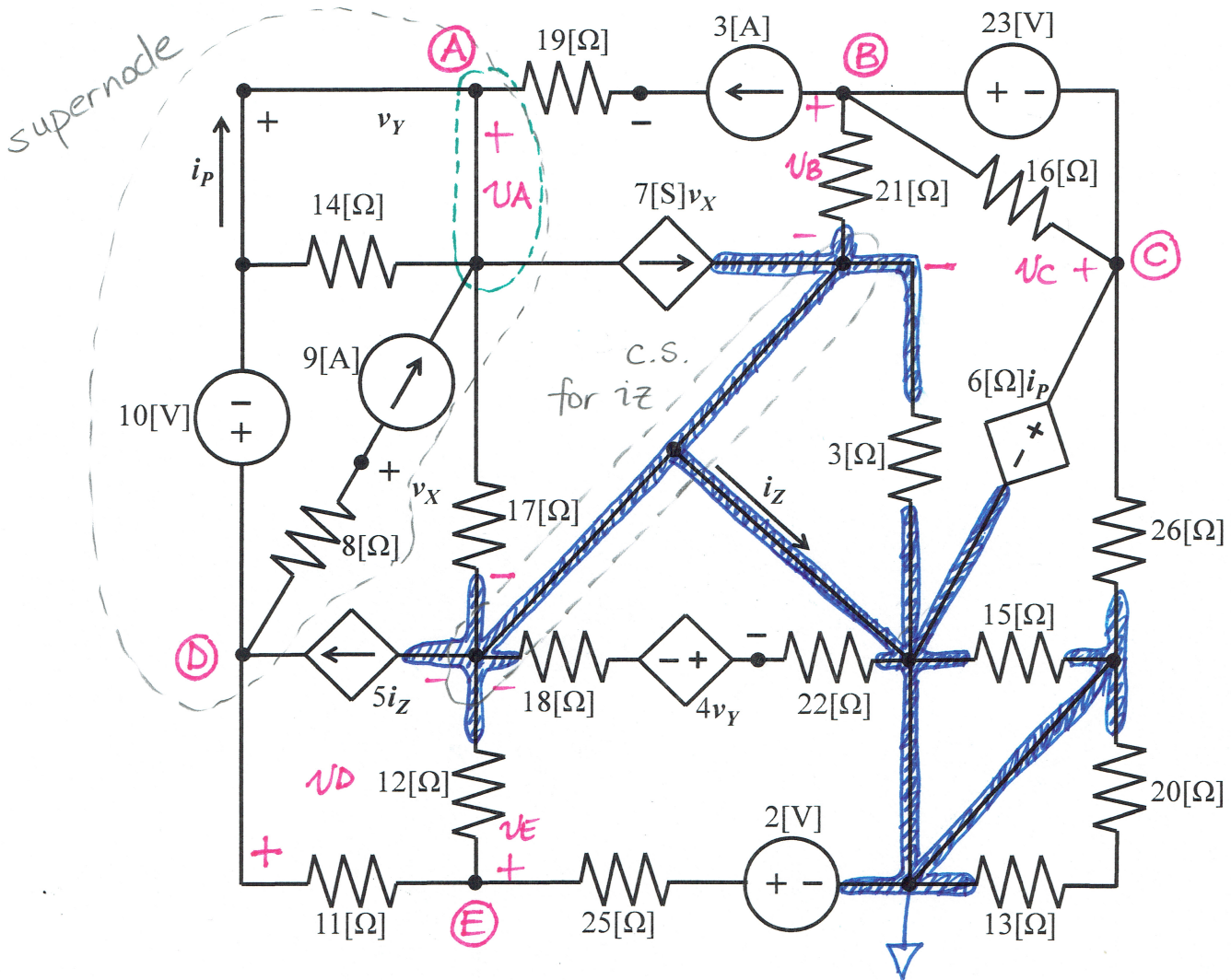1. {30 Points} Use the **node-voltage method** to write a complete set of equations that could be used to solve this circuit. Do not simplify the circuit. Do not attempt to simplify or solve your equations. **Define all variables clearly.**



6-1 eq. + 4 auxiliary eq = 9 equations

$$(A + D) \quad -3[A] + 7[S]v_x + \frac{v_A}{17[\Omega]} - 5i_z + \frac{v_D - v_E}{11[\Omega]} = 0$$

$$(A + D) \quad v_D - v_A = 10[V]$$

$$(B + C) \quad v_B - v_C = 23[V] \quad (C) \quad v_C = 6[\Omega]i_p$$

Room for extra work

$$\textcircled{E} \quad \frac{v_E - v_D}{11[\Omega]} + \frac{v_E}{12[\Omega]} + \frac{v_E - 2[V]}{25[\Omega]} = 0$$

$$\textcircled{v_x} \quad v_x + \frac{4v_y}{40[\Omega]} \cdot 22[\Omega] - v_D + 9[A] \cdot 8[\Omega] = 0$$

$$\textcircled{v_y} \quad v_y + 3[A] \cdot 19[\Omega] = 0$$

$$\textcircled{i_z} \quad -7[S]v_x - \frac{v_B}{21[\Omega]} + \frac{0}{3[\Omega]} + i_z + \frac{4v_y}{40[\Omega]} - \frac{v_E}{12[\Omega]} + \dots$$

$$\dots + 5i_z - \frac{v_A}{17[\Omega]} = 0$$

$$\textcircled{i_p} \quad -i_p - 3[A] + 7[S]v_x + \frac{v_A}{17[\Omega]} - 9[A] + \frac{0}{14[\Omega]} = 0$$




2. {30 Points} In the circuit shown below, positive charges move out from the independent voltage source  $v_s$  through terminal 1. Their number is given by

$$q_s(t) = 10e^{-20\left(\frac{1}{ms}\right)t} [\mu C]$$

The voltage on device D is constant  $v_D=100$  [V].

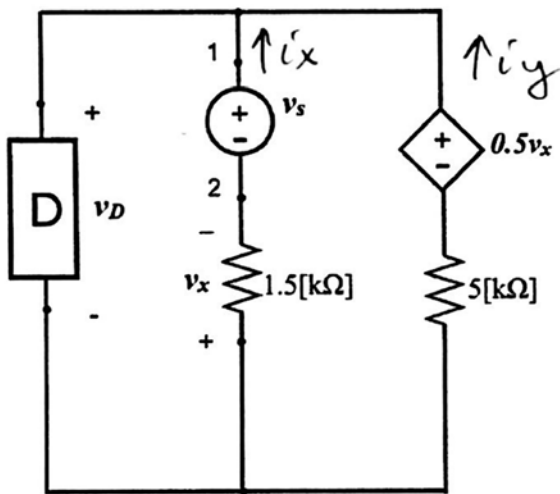- Find an expression for power delivered by the voltage source  $v_s$ .
- Find an expression for power delivered by the dependent voltage source  $0.5v_x$ .
- Find the energy delivered by device D between 0 and 10 [s].



$i_x$  direction is determined by the flow of  $\oplus$  charges.

$$\begin{aligned} i_x(t) &= \left| \frac{dq_s(t)}{dt} \right| \\ &= 20 \cdot 10 \left[ \frac{\mu C}{ms} \right] e^{-20 \left[ \frac{1}{ms} \right] t} \\ &= 200 e^{-20000 \left[ \frac{1}{s} \right] t} [\mu A] \\ &= 0.2 e^{-20000 t} [A] \end{aligned}$$

units:

$$\frac{\mu C}{ms} = \frac{10^{-6} C}{\mu s} \cdot \frac{10^3 ms}{s} \cdot \frac{\mu C}{ms} = 10^{-3} \frac{C}{s} = mA$$

Find  $v_s$

$$a) \quad v_D = v_s - 1.5 [k\Omega] \cdot i_x(t) = 100 [V]$$

$$v_s = 100 + 300 e^{-20,000 t} [V]$$

$$\begin{aligned} P_{del, v_s} &= v_s \cdot i_x(t) \\ &= 20 e^{-20,000 t} + 60 e^{-40,000 t} [W] \end{aligned}$$

Room for extra work

b) Calculate  $v_x \rightarrow i_y \rightarrow \text{power}$ 

$$v_x = -100 + v_s = 300 e^{-20,000t} \text{ [V]}$$

$$i_y = \frac{-100 + 0.5 v_x}{5 \text{ [k}\Omega]} = -20 + 30 e^{-20,000t} \text{ [mA]} \\ = -0.02 + 0.03 e^{-20,000t} \text{ [A]}$$




$$P_{\text{del}, 0.5 v_x} = 0.5 v_x \cdot i_y \\ = 150 e^{-20,000t} \text{ [V]} \cdot (-0.02 + 0.03 e^{-20,000t}) \\ = -3 e^{-20,000t} + 4.5 e^{-40,000t} \text{ [W]}$$

$$\text{c) } P_{\text{del}, D} = -v_D (i_x + i_y) \\ = -100 \cdot (0.2 e^{-20,000t} - 0.02 + 0.03 e^{-20,000t}) \\ = -23 e^{-20,000t} + 2 \text{ [W]}$$


$$W_{\text{del}, D} = -\int_0^{10 \text{ [s]}} 23 e^{-20,000t} dt + \int_0^{10 \text{ [s]}} 2 dt \\ = -\frac{23 \text{ [W]}}{-20,000 \text{ [}\frac{1}{\text{s}}\text{]}} e^{-20,000 \text{ [}\frac{1}{\text{s}}\text{]}t} \Big|_0^{10 \text{ [s]}} + 2t \Big|_0^{10 \text{ [s]}} \\ = -1.15 \text{ [mJ]} + 20 \text{ [J]} \approx 20 \text{ [J]}$$

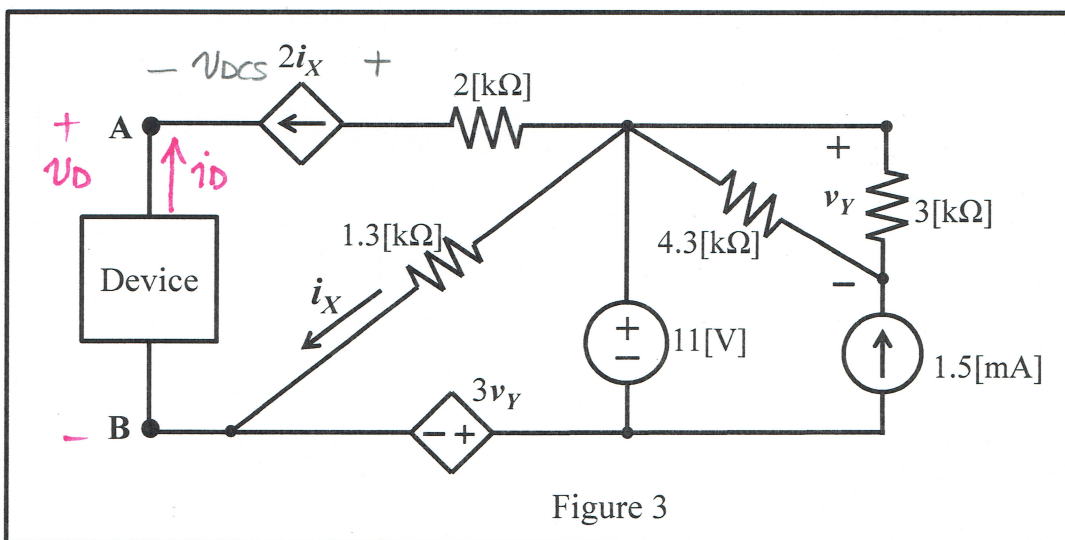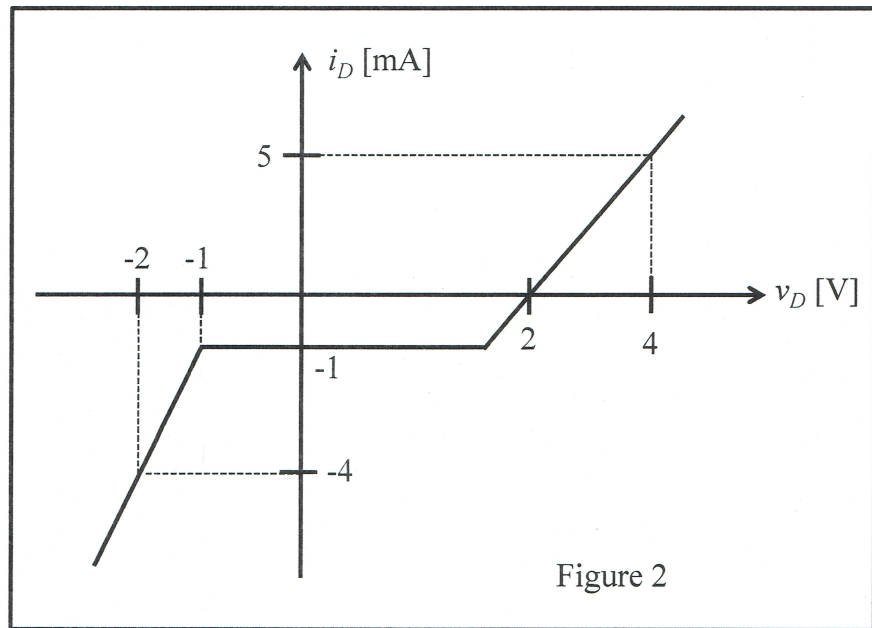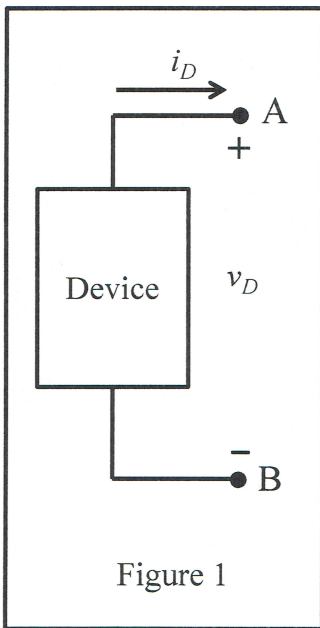3. {35 Points} A device can be modeled as a voltage source in series with a resistance. This device is shown in Figure 1. The relationship between the voltage across the device and the current through the device is shown in Figure 2. This device is connected to the circuit as shown in Figure 3.

- Find a device model that would be valid for the current range,  $i_D \geq -1$  [mA] and draw it, showing terminals **A** and **B**.
- Find the power absorbed by the **dependent current source**.
- Are the electrons moving through the dependent current source losing or gaining energy? Briefly explain your answer.



Room for extra work

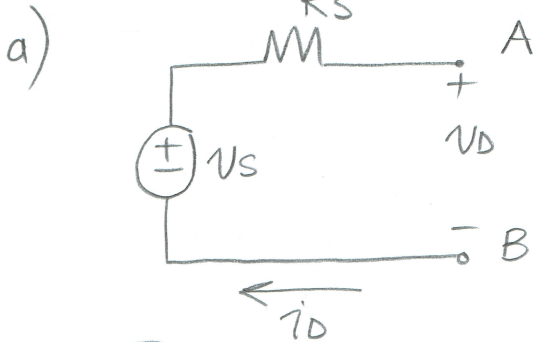


$$-v_s + i_D R_s + v_D = 0$$

$$\text{For } i_D \geq -1 \text{ [mA]}$$

$$-v_s + 2 \text{ [V]} = 0 \Rightarrow v_s = 2 \text{ [V]}$$

$$-v_s + 5 \text{ [mA]} R_s + 4 \text{ [V]} = 0$$
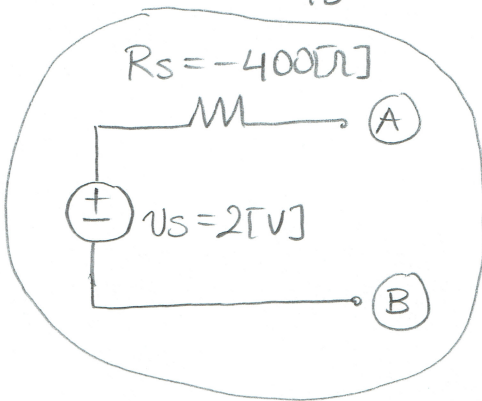
$$\Rightarrow R_s = -400 \text{ [\Omega]}$$



b)

$$v_y = -1.5 \text{ [mA]} \cdot (3 \text{ [k}\Omega] \parallel 4.3 \text{ [k}\Omega])$$

$$v_y = -2.65 \text{ [V]}$$

$$-i_x \cdot 1.3 \text{ [k}\Omega] + 11 \text{ [V]} + 3v_y = 0 \Rightarrow i_x = 2.35 \text{ [mA]}$$

$i_D = -2i_x = -4.7 \text{ [mA]} \rightarrow$  Since  $i_D < -1 \text{ [mA]}$ , the device model found in part (a) is NOT valid.

$$i_D = 3 \left[ \frac{\text{mA}}{\text{V}} \right] \cdot v_D + 2 \text{ [mA]} \quad \text{for } i_D \leq -1 \text{ [mA]}$$

For  $i_D = -4.7 \text{ [mA]}$ ,  $v_D = -2.23 \text{ [V]}$

$$-v_{DCS} - 2i_x \cdot 2 \text{ [k}\Omega] + i_x \cdot 1.3 \text{ [k}\Omega] - v_D = 0$$

$$\Rightarrow v_{DCS} = -4.115 \text{ [V]}$$

$$P_{ABS, DCS} = 2i_x \cdot v_{DCS} = \boxed{-19.34 \text{ [mA]}}$$



c) Since  $P_{ABS, DCS} < 0$ , dependent current source delivers power  $\rightarrow$   $e^-$ s moving through it gain energy.

4. {35 Points} **DO NOT** use the Node-Voltage Method or Mesh-Current Method to solve this problem.

a) Find the Norton equivalent seen at terminals A and B in Figure 1, by applying **ONLY 3** source transformations and combining parallel and series components together.

b) Find the Norton equivalent seen at terminals C and D in Figure 2, by using equivalent resistances.

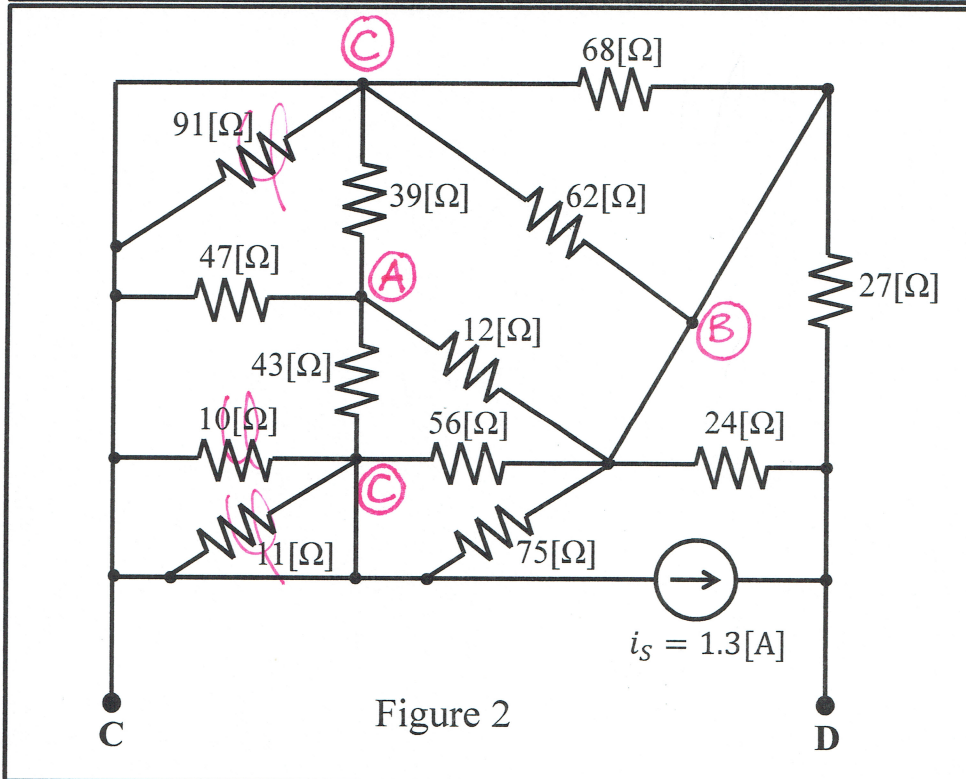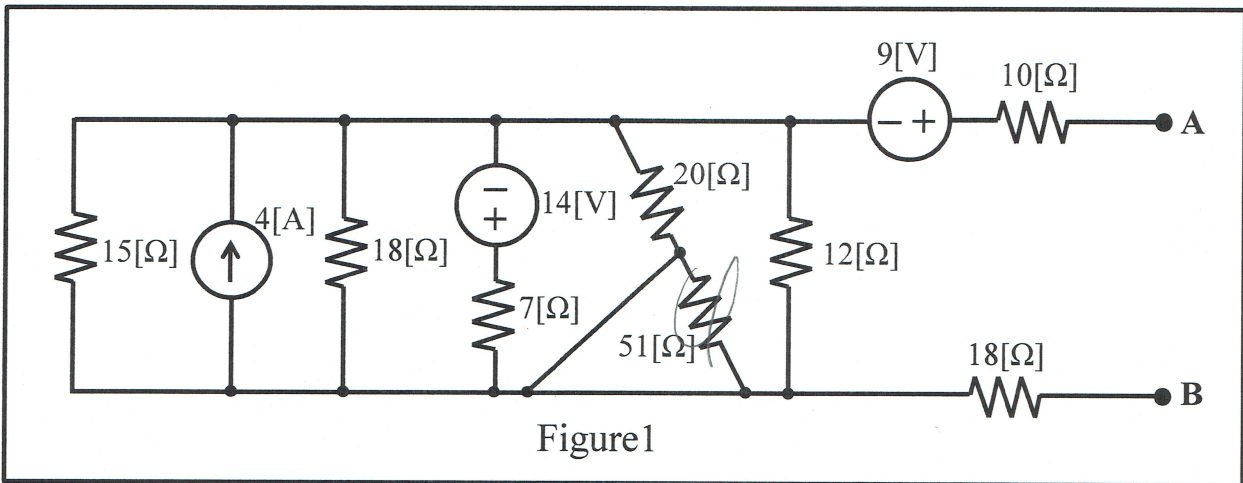
c) Attach the circuit in Figure 2 to the circuit in Figure 1 by connecting terminal C to terminal B and terminal D to terminal A. Find the power delivered by  $i_s$ .






Room for extra work

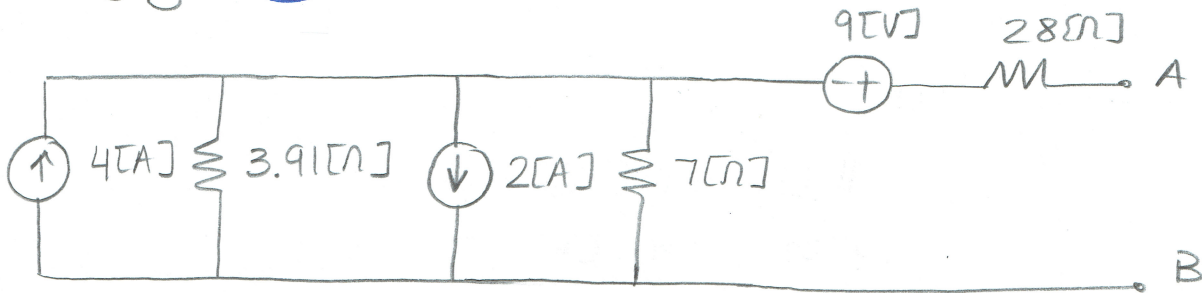
- a)  $5[\Omega]$  is shorted.  $15[\Omega] \parallel 18[\Omega] \parallel 20[\Omega] \parallel 12[\Omega] = 3.91[\Omega]$   
 Applying **(S.T.)<sup>1</sup>** to  $14[V]$  in series w/  $7[\Omega]$  and redrawing:



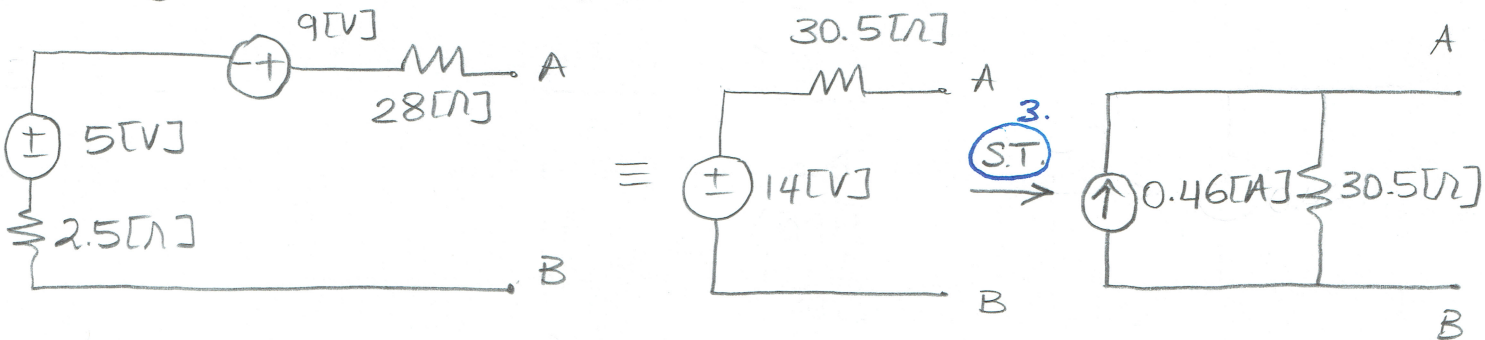
Combining parallel current sources and resistors, and then applying **(S.T.)<sup>2</sup>** we get:  $(3.91[\Omega] \parallel 7[\Omega]) = 2.5[\Omega]$



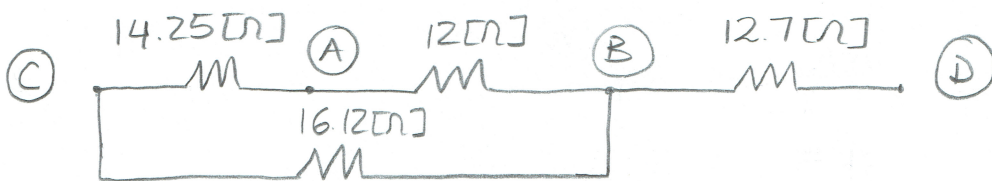
- b)  $39[\Omega] \parallel 47[\Omega] \parallel 43[\Omega] = 14.25[\Omega]$   
 $68[\Omega] \parallel 62[\Omega] \parallel 56[\Omega] \parallel 75[\Omega] = 16.12[\Omega]$   
 $27[\Omega] \parallel 24[\Omega] = 12.7[\Omega]$



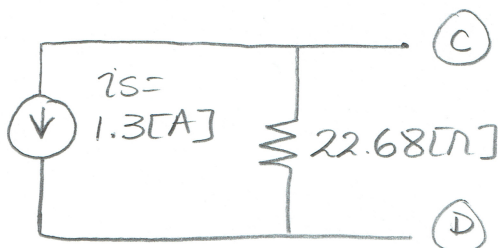
$$R_{CD} = [(14.25[\Omega] + 12[\Omega]) \parallel 16.12[\Omega]] + 12.7[\Omega] = 22.68[\Omega]$$



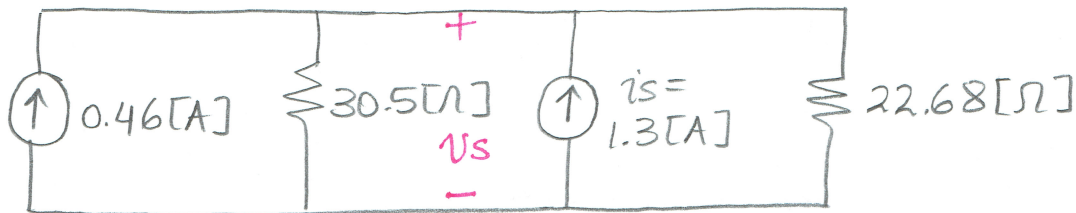c) Attaching the circuits from a) and b) together, we get:


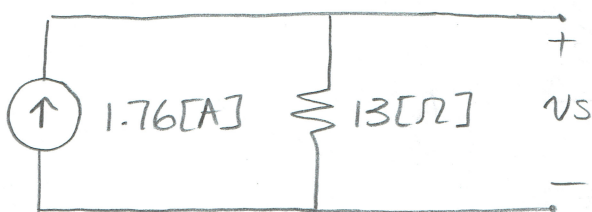
$$22.68 \text{ [\Omega]} \parallel 30.5 \text{ [\Omega]} = 13 \text{ [\Omega]}$$




$$v_s = 22.88 \text{ [V]}$$


$$P_{\text{DEL}, i_s} = v_s i_s = 22.88 \text{ [V]} \cdot 1.3 \text{ [A]} = \boxed{29.744 \text{ [W]}}$$

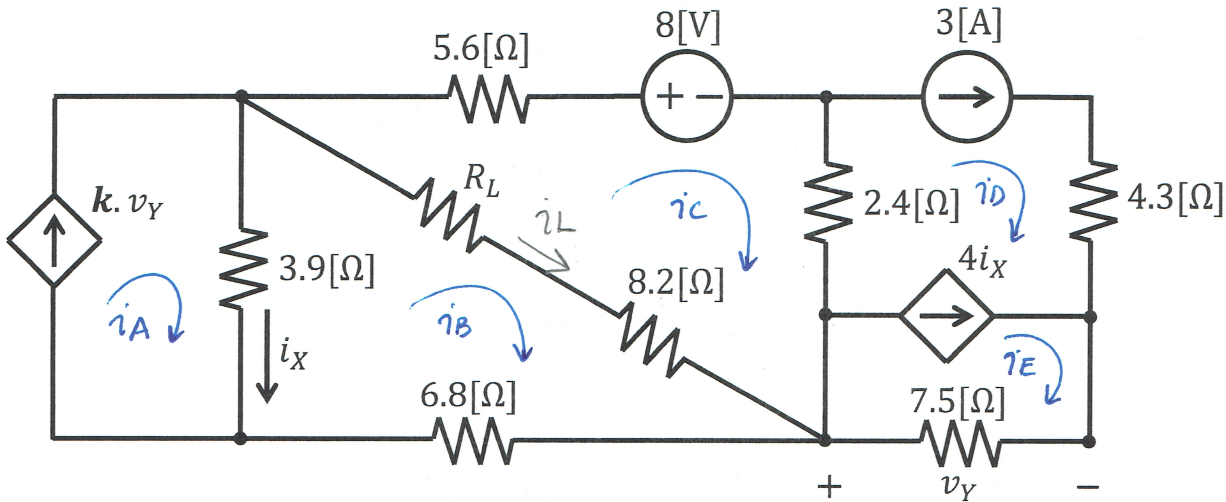5. {35 Points} In the following circuit, the value of  $R_L$  must be chosen to be  $13.2[\Omega]$  in order to deliver maximum power to  $R_L$ .

- Find  $k$ .
- Find the power delivered to  $R_L$ .



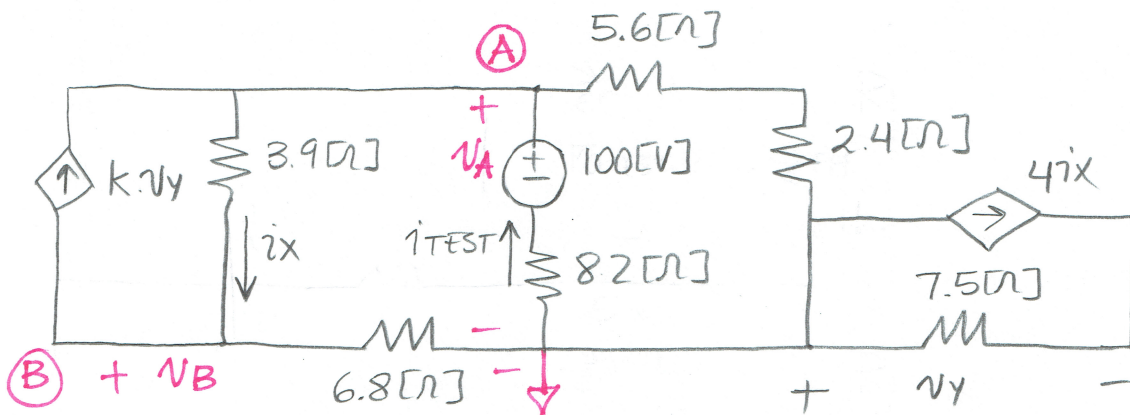a) To deliver max. power to  $R_L$ ,  $R_L$  must be set equal to  $R_{TH}$  seen by  $R_L$ . To find  $R_{TH}$  seen by  $R_L$ , kill ind. sources and apply test source method.



$$R_{TH} = 13.2[\Omega] = \frac{100[V]}{i_{TEST}} \Rightarrow i_{TEST} = 7.57[A]$$

Applying NVM:

$$\textcircled{A} \quad -k v_Y + \frac{v_A - v_B}{3.9[\Omega]} + \frac{v_A - 100[V]}{8.2[\Omega]} + \frac{v_A}{8[\Omega]} = 0$$

Room for extra work

$$\textcircled{B} \quad k.v_Y + \frac{v_B - v_A}{3.9[\Omega]} + \frac{v_B}{6.8[\Omega]} = 0 \quad \textcircled{i_X} \quad \frac{v_A - v_B}{3.9[\Omega]} = i_X$$

$$\textcircled{v_Y} \quad v_Y = -4i_X \cdot 7.5[\Omega] = -30i_X$$

$$\textcircled{i_{TEST}} \quad \frac{v_A - 100[V]}{8.2[\Omega]} = -i_{TEST} = -7.57[A]$$

Solving, we get  $k = -13.65[\text{mS}]$

b)  $P_{ABS,RL} = R_L \cdot i_L^2$  To find  $i_L$ , MCM is applied. Mesh currents are defined on the circuit.

$$\textcircled{i_A} \quad i_A = k \cdot v_Y$$

$$\textcircled{i_B} \quad 3.9[\Omega](i_B - i_A) + (R_L + 8.2[\Omega])(i_B - i_C) + 6.8[\Omega]i_B = 0$$

$$\textcircled{i_C} \quad 5.6[\Omega]i_C + 8[V] + 2.4[\Omega](i_C - i_D) + (R_L + 8.2[\Omega])(i_C - i_B) = 0$$


$$\textcircled{i_D} \quad i_D = 3[A] \quad \textcircled{i_D + i_E} \quad i_E - i_D = 4i_X$$

$$\textcircled{v_Y} \quad v_Y = -7.5[\Omega]i_E \quad \textcircled{i_X} \quad i_X = i_A - i_B \quad \textcircled{i_L} \quad i_L = i_B - i_C$$


Using  $k = -13.65[\text{mS}]$  and  $R_L = 13.2[\Omega]$  and solving,

we get:  $i_L = 47.67[\text{mA}]$   $P_{ABS,RL} = 30[\text{mW}]$

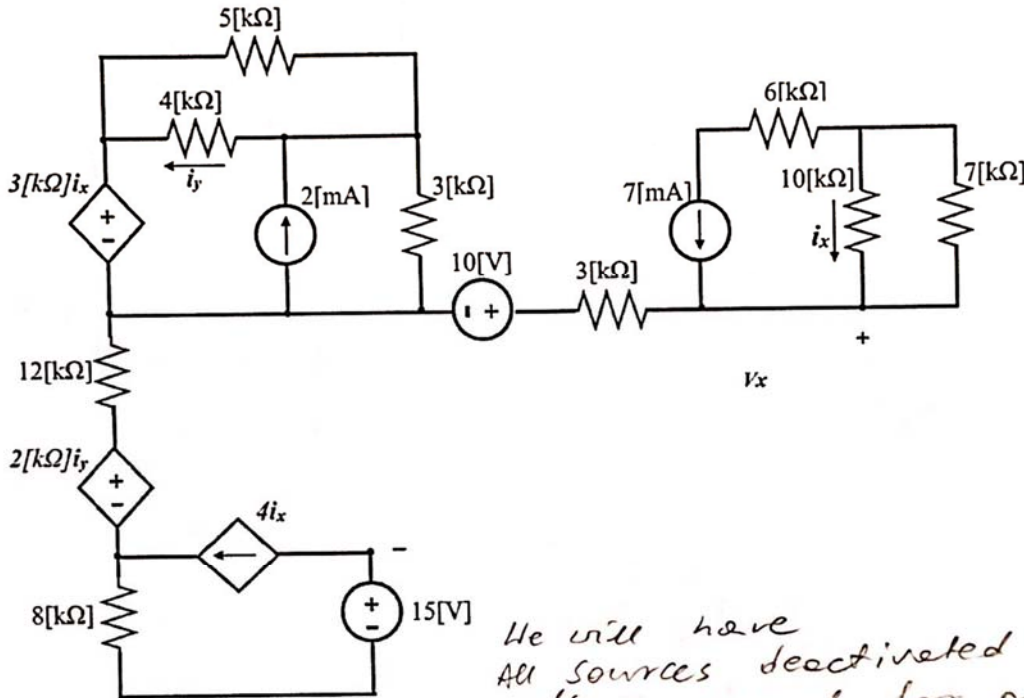6. {35 Points} Use the circuit shown below to solve this problem.  
 a) Use superposition to find the voltage  $v_x$ .  
 b) Find the power delivered by the dependent voltage source  $3[k\Omega]i_x$ .



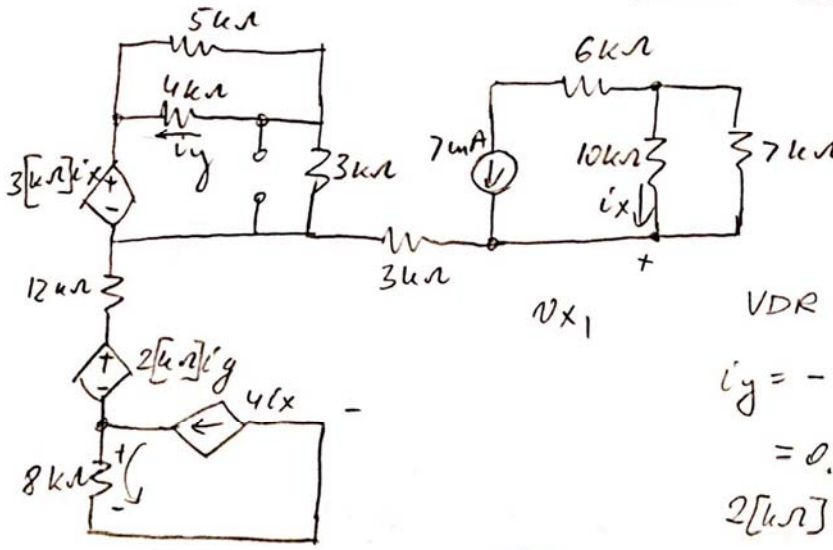We will have all sources deactivated @ a time except for one:



$7 \mu A$

$$i_x = -7 \mu A \cdot \frac{10117}{10} = -2.88 \mu A$$

VDR for  $i_y$




$$i_y = -\frac{3[k\Omega] \cdot (-2.88 \mu A)}{3 + 4115} \cdot 4115 \cdot \frac{1}{4[k\Omega]} = 0.92 \mu A$$

$$2[k\Omega] \cdot i_y = 1.84 [V]$$


First  $v_{x1} = 4 \cdot (-2.88 \mu A) \cdot 8[k\Omega] + 2[k\Omega] \cdot i_y = -90.32 [V]$



Room for extra work

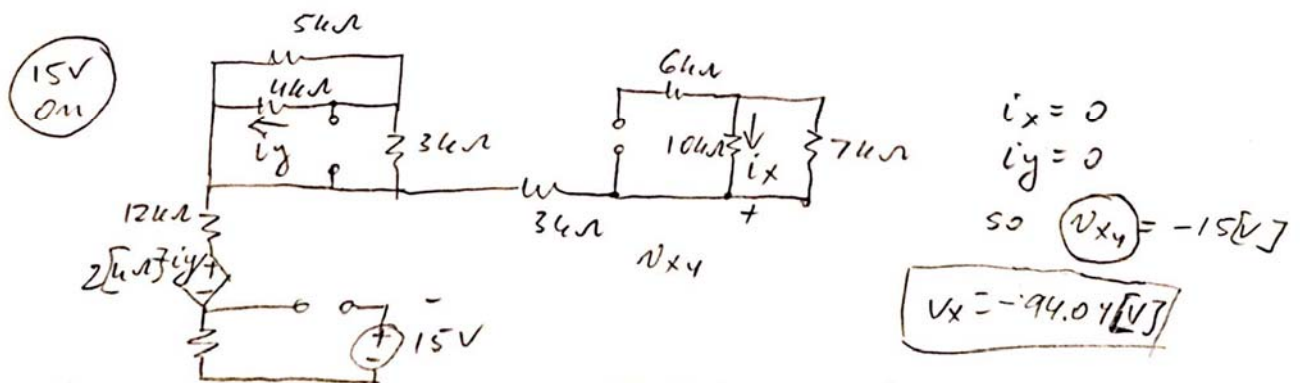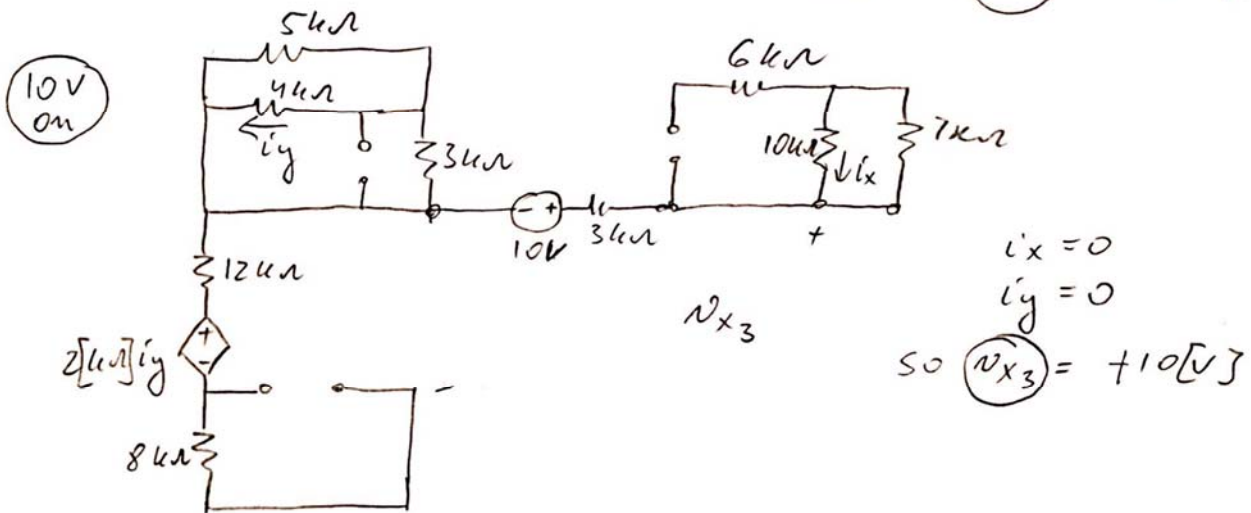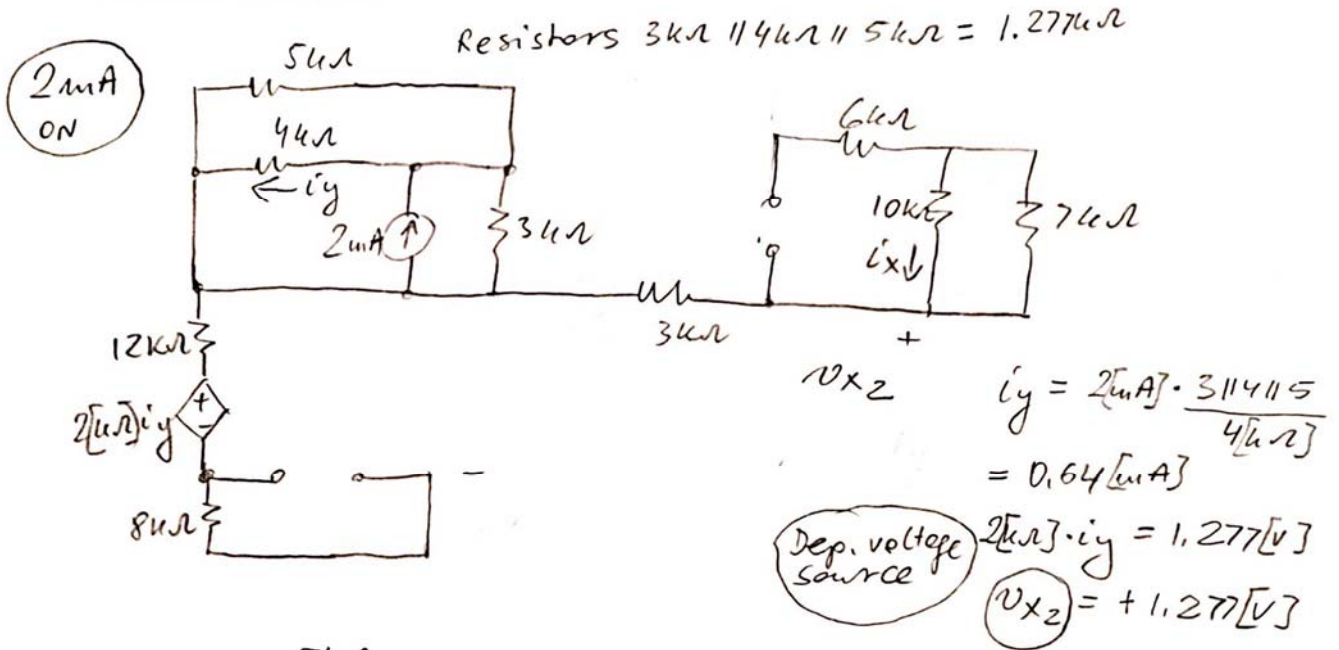

Room for extra work

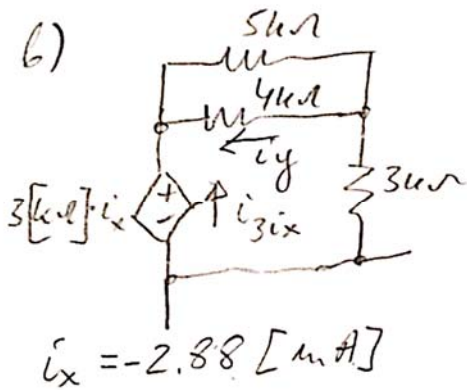

From a) with 7mA current source active we need current  $i_{3ix}$

$$R_{eq} = 5k\Omega \parallel 4k\Omega + 3k\Omega = 5.22k\Omega$$

$$i_{3ix} = \frac{+3[kA] \cdot i_x}{R_{eq}} = \frac{-8.64 [V]}{5.22 [k\Omega]} = -1.66 [mA]$$

$$P_{del, 3ix} = 3[k\Omega] \cdot i_x \cdot i_{3ix} = 14.3 [W]$$