

Name: SOLUTION (please print)

Signature: \_\_\_\_\_

ECE 2201 – Quiz #2  
February 20, 2019


**Keep this quiz closed and  
face up until you are told  
to begin.**

1. This quiz is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution which is not given in a reasonable order will lose credit.
3. It is assumed that your work will begin on the same page as the problem statement. If you choose to begin your work on another page, you must indicate this on the page with the problem statement, with a clear indication of where the work can be found. **If your work continues on to another page, indicate clearly where your work can be found. Failure to indicate this clearly will result in a loss of credit.**
4. Show all units in solutions, intermediate results, and figures. Units in the quiz will be included between square brackets.
5. Do not use red ink. Do not use red pencil.
6. You will have 30 minutes to work on this quiz.

\_\_\_\_\_ /20

For the circuit shown below find the power delivered by the dependent voltage source  $5v_x$  and the dependent current source  $10i_y$ .

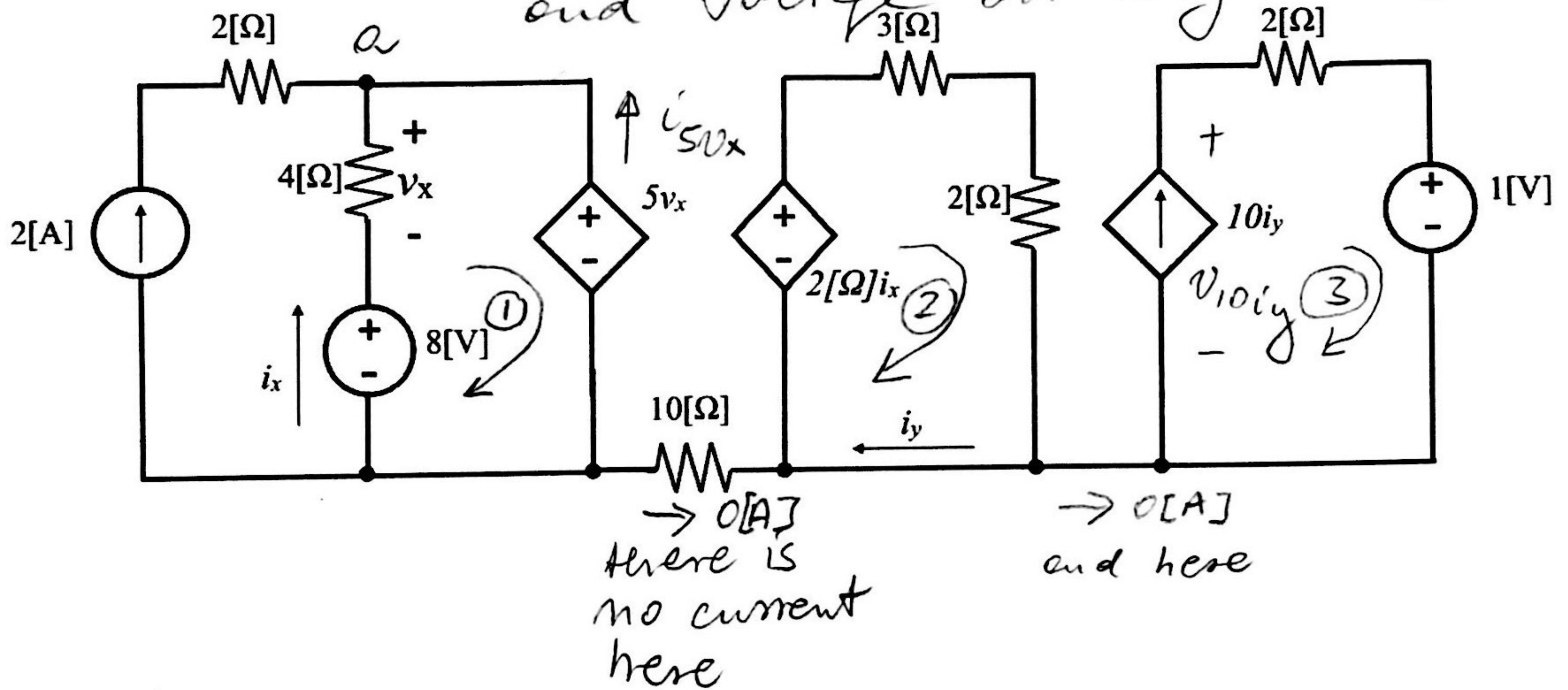We need to find the current in  $5v_x$  source and voltage on  $10i_y$  source.



Find  $v_x$  from Loop 1

KVL ①  $5v_x - 8 - v_x = 0 \rightarrow v_x = 2[V]$

Find  $i_x$  from Ohm's Law

O.L.  $i_x = -\frac{v_x}{4} = -0.5[A]$

Find the current in  $5v_x$  - mark it first

KCL ②  $-2 - i_x - i_{5v_x} = 0 \rightarrow i_{5v_x} = -1.5[A]$

Find  $i_y$  from Loop 2

KVL ②  $-2i_x + i_y \cdot 3 + i_y \cdot 2 = 0 \rightarrow i_y = \frac{-1[V]}{5[\Omega]} = -0.2[A]$

Find  $v_{10i_y}$  from Loop 3

KVL ③  $-v_{10i_y} + 10i_y \cdot 2 + 1 = 0 \rightarrow v_{10i_y} = -3[V]$



Room for extra work

Now calculate power

→  $P_{DEL, 5V_x} = -1.5[A] \cdot 10[V] = -15[W]$   
so this source absorbs the power

→  $P_{DEL, 10V_y} = 10[V] \cdot 0.6[A] = +6[W]$   
this source delivers the power