

Name: \_\_\_\_\_ (please print)

Signature: \_\_\_\_\_

# ECE 2201 – Exam 1

## March 4, 2023

**Keep this exam closed and face up  
until you are told to begin.**

1. This exam is closed book, closed notes. You may use any calculator. You may **not** use a cell phone, tablet computer, nor laptop computer. You may have a crib sheet in the form of one 8 ½" x 11" piece of paper, with material written on both sides.
2. Print your name, and provide your signature above.
3. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution which is not given in a reasonable order will lose credit. You may separate the pages as you work.
4. Show all units in solutions, intermediate results, and figures. Units in the exam will be included between square brackets.
5. If the grader has difficulty following your work because it is messy or disorganized, you will lose credit.
6. Do not use red ink. Do not use red pencil.
7. You will have 90 minutes to work on this exam.

1. \_\_\_\_\_ /30

2. \_\_\_\_\_ /40

3. \_\_\_\_\_ /30

Total = 100

Room for extra work

1. (30 points) The revolutionary new Trombattuck device is shown in the diagram in Figure 1 below and labeled TB. The plots of terminal voltage  $v_T$  and terminal current  $i_T$  for this device are shown in the graphs in Figures 2 and 3. Find the energy delivered by the TB device over the time period 1 to 4[ms].

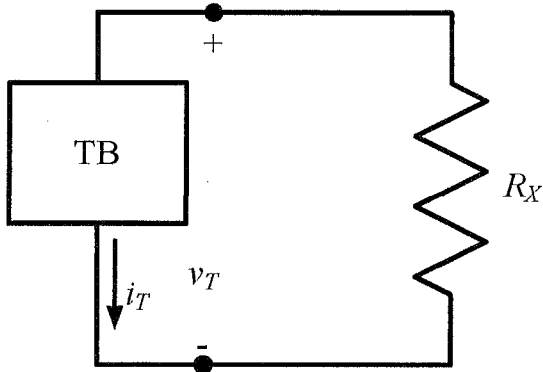


Figure 1

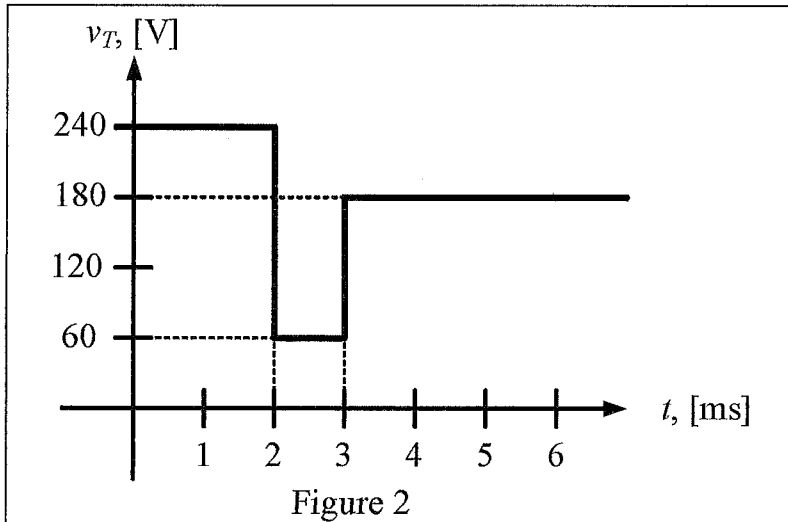


Figure 2


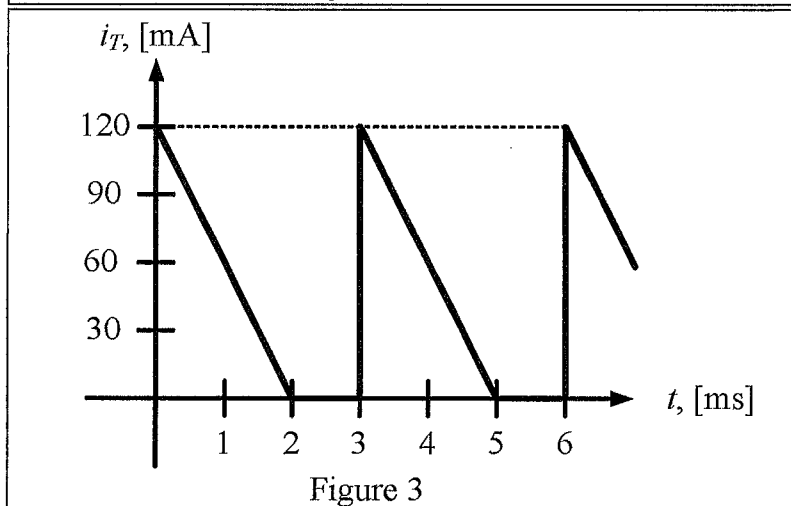


Figure 3

Room for extra work

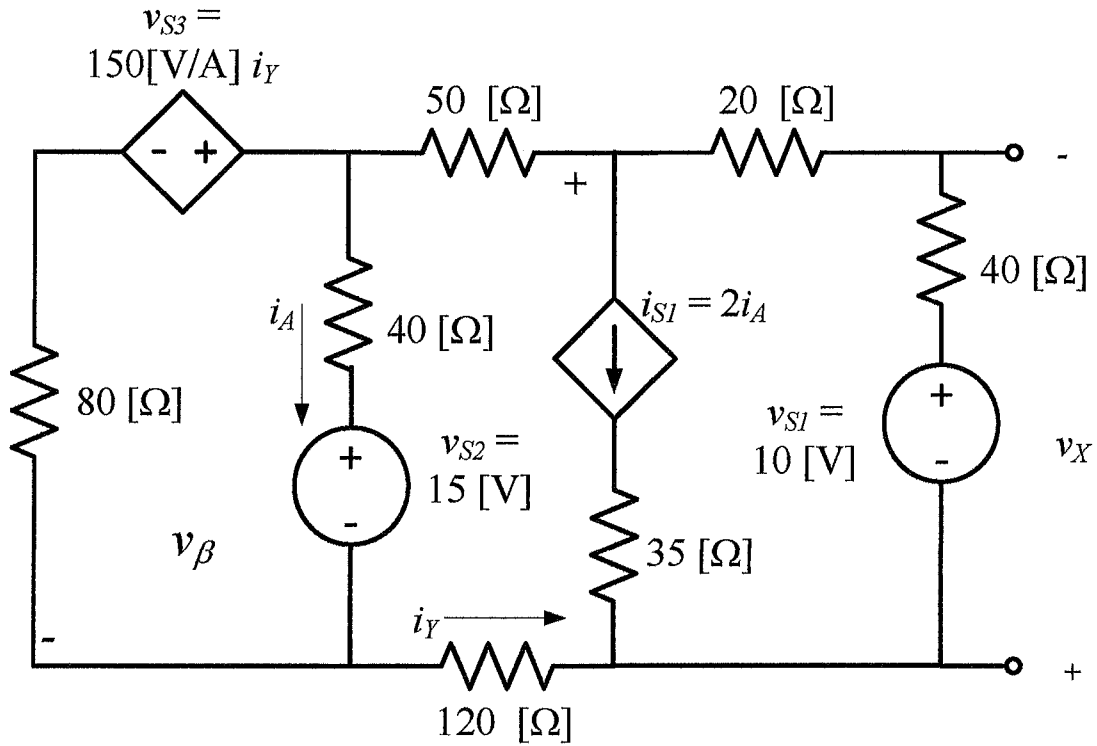2. (40 points) In the circuit below,  $v_x$  is known to be  $-14.60$  [V].


- Find the power delivered by the dependent current source.
- Find  $v_\beta$ .



Room for extra work

3. (30 points) Use the circuit shown below to solve. In your work, show your work clearly enough so that a well-prepared ECE 2201 student would be able to follow your steps. Redraw the circuit diagram as needed.

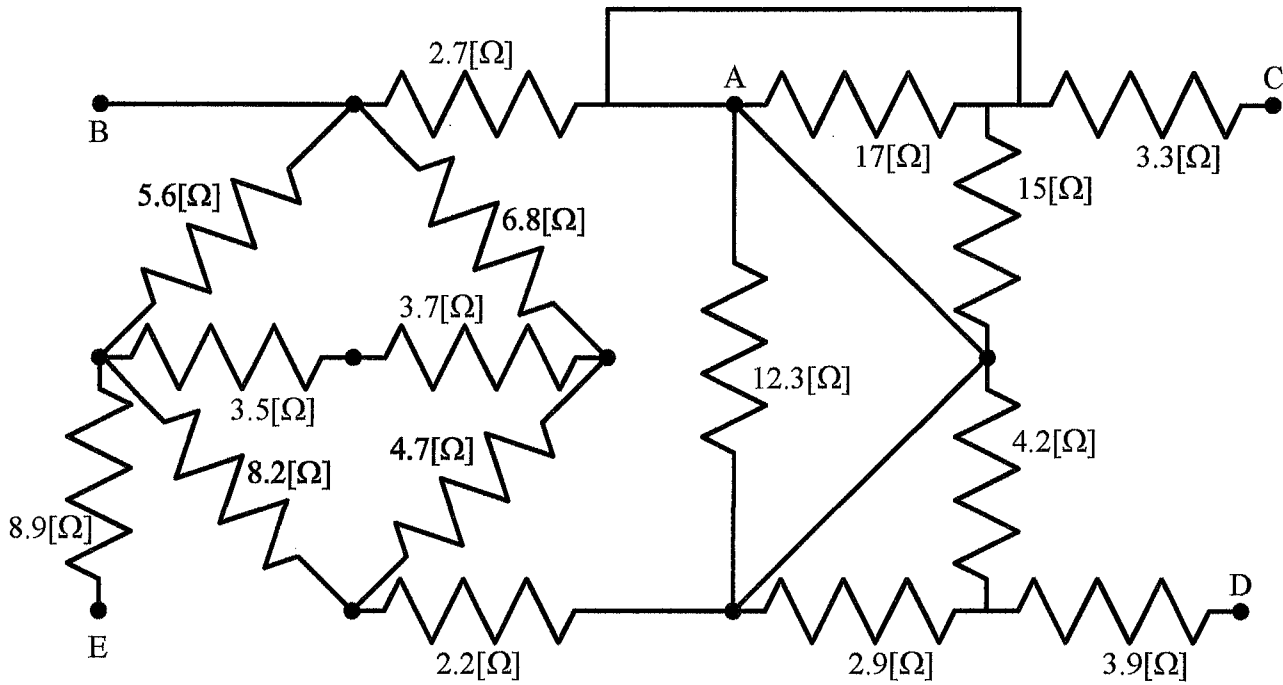- a) Find the equivalent resistance as seen from terminals D and C.
- b) Find the equivalent resistance with respect to terminals B and E.



Room for extra work



Room for extra work

1. (30 points) The revolutionary new Trombattuck device is shown in the diagram in Figure 1 below and labeled TB. The plots of terminal voltage  $v_T$  and terminal current  $i_T$  for this device are shown in the graphs in Figures 2 and 3. Find the energy delivered by the TB device over the time period 1 to 4[ms].

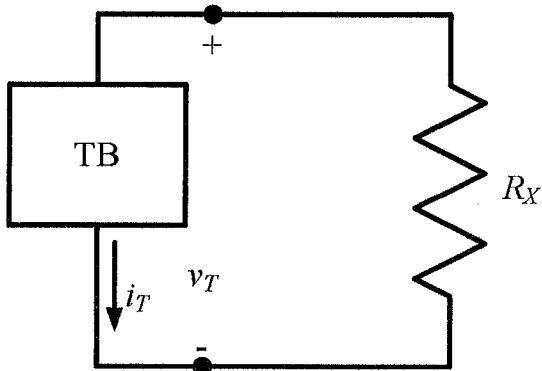


Figure 1

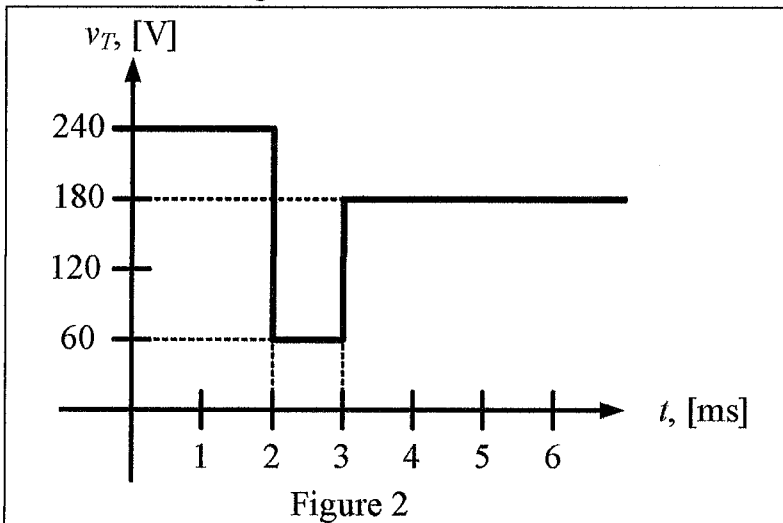


Figure 2

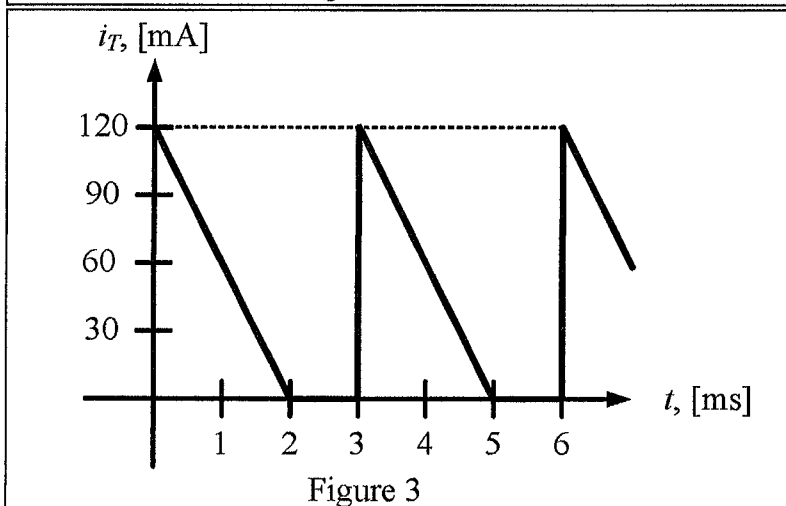


Figure 3

Solution

Room for extra work      Converting to [V], [A], [s], we have...

$$0 < t < 0.002 \text{ [s]} \quad i_T = 0.120 \text{ [A]} - 60 \left[ \frac{\text{A}}{\text{s}} \right] t \quad v_T = 240 \text{ [V]} \quad +2$$

$$0.002 \text{ [s]} < t < 0.003 \text{ [s]} \quad i_T = 0 \quad v_T = 60 \text{ [V]} \quad +2$$

$$0.003 \text{ [s]} < t < 0.005 \text{ [s]} \quad i_T = 0.120 \text{ [A]} - 60 \left[ \frac{\text{A}}{\text{s}} \right] (t - 0.003 \text{ [s]}) \quad v_T = 180 \text{ [V]} \quad +2$$

$$P_{\text{del by TB}} = -v_T i_T \quad \Rightarrow \quad W_{\text{del by TB}} = \int_{0.001 \text{ [s]}}^{0.004 \text{ [s]}} -v_T i_T dt \quad +3$$

$$W_{\text{del by TB}} = - \int_{0.001 \text{ [s]}}^{0.002 \text{ [s]}} 240 \text{ [V]} \cdot (0.120 \text{ [A]} - 60 \left[ \frac{\text{A}}{\text{s}} \right] t) dt$$

time requires +6

$$- \int_{0.003 \text{ [s]}}^{0.004 \text{ [s]}} 180 \text{ [V]} \cdot (0.120 \text{ [A]} - 60 \left[ \frac{\text{A}}{\text{s}} \right] (t - 0.003 \text{ [s]})) dt$$

First integral is

$$-240 \int_{0.001 \text{ [s]}}^{0.002 \text{ [s]}} (0.120 - 60t) dt = -7.2 \times 10^{-3} \text{ [J]}$$

Second integral is


$$-180 \int_{0.003 \text{ [s]}}^{0.004 \text{ [s]}} (0.120 - 60t + 0.18) dt = -1.62 \times 10^{-2} \text{ [J]}$$

So

$$W_{\text{del by TB}} = -7.2 \times 10^{-3} - 1.62 \times 10^{-2} = -2.34 \times 10^{-2} \text{ [J]}$$

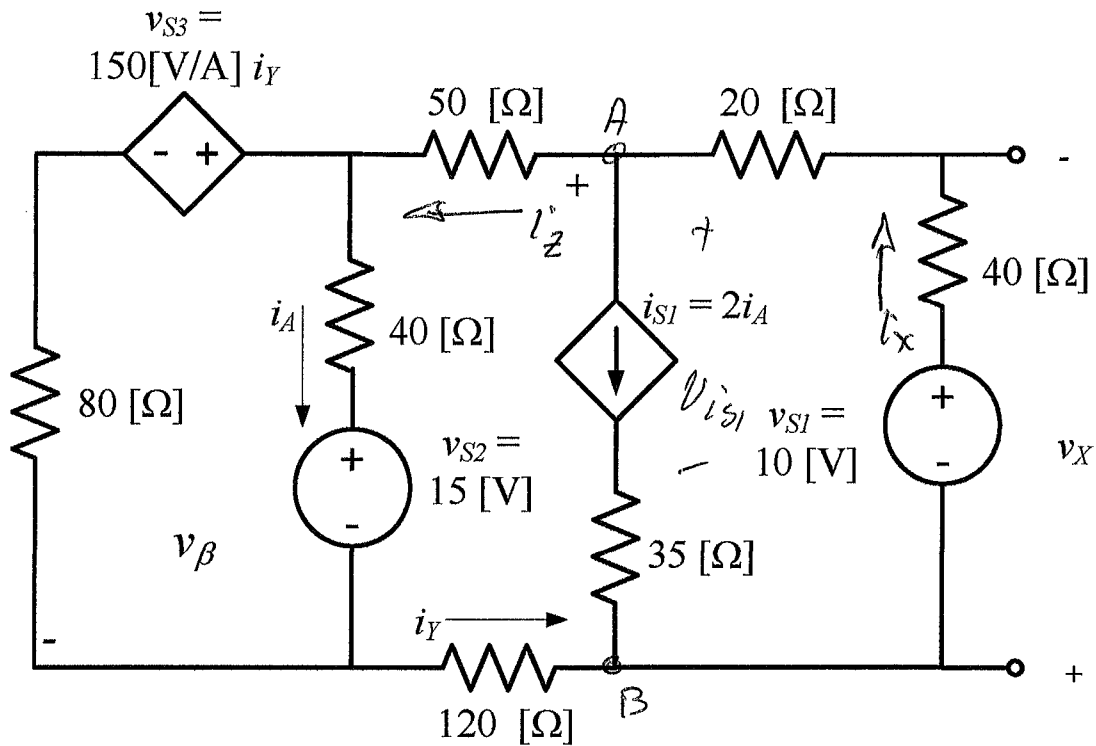2. (40 points) In the circuit below,  $v_x$  is known to be  $-14.60$  [V].

- Find the power delivered by the dependent current source.
- Find  $v_\beta$ .



Knowing  $v_x$  allows us to find  $i_x$ :

$$40 i_x - v_x - 10 = 0 \Rightarrow i_x = \frac{v_x + 10}{40} = -0.115 \text{ [A]}$$

$$\text{KCL at A: } i_x = 2i_A + i_Z$$

$$\text{KVL: } v_x + 20i_x + 50i_Z + 40i_A + 15 + 120i_Y = 0$$

$$\text{KCL at B: } i_x = 2i_A + i_Y$$

Comparing the KCL equations, we see that  $i_Z = i_Y$ .

Then we can solve these equations to find ...

Room for extra work

$$i_A' = -0,0715 \text{ [A]} \quad i_Y = i_Z' = 28,00 \text{ [mA]} = 0,0280 \text{ [A]}$$

$$a) \quad v_{i_{s1}} + 35(2i_A') + v_x + 20i_x' = 0$$

$$\Rightarrow \boxed{v_{i_{s1}} = 21,90 \text{ [V]}}$$


$$\boxed{\therefore P_{\text{del by } i_{s1}} = -2i_A' \cdot v_{i_{s1}} = 3,132 \text{ [W]}}$$

$$b) \quad -v_B - 20i_x' - v_x - 120i_Y' = 0$$

$$\Rightarrow \boxed{v_B = 13,55 \text{ [V]}}$$

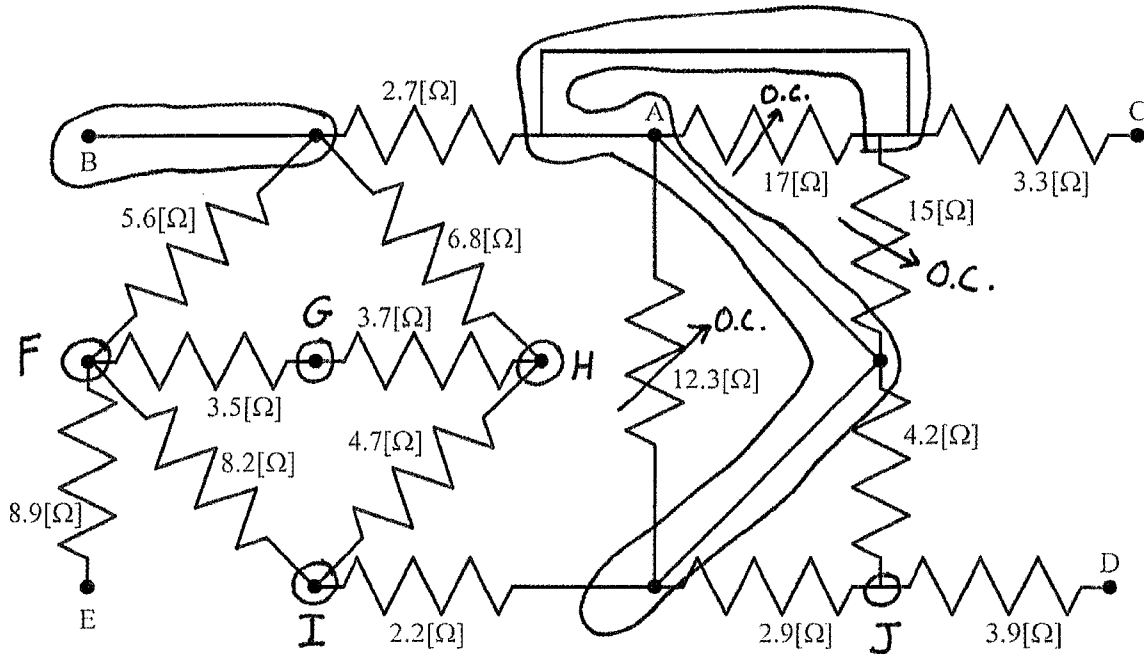3. (30 points) Use the circuit shown below to solve. In your work, show your work clearly enough so that a well-prepared ECE 2201 student would be able to follow your steps. Redraw the circuit diagram as needed.

- Find the equivalent resistance as seen from terminals D and C.
- Find the equivalent resistance with respect to terminals B and E.




We begin by indicating and naming the nodes, on the diagram above. We can see that the  $12.3\{\Omega\}$  resistor, the  $17\{\Omega\}$  resistor, and the  $15\{\Omega\}$  resistor, all are shorted; that is, they each have a wire across them. Thus, we can replace each with an open circuit.

We have series resistors and parallel resistors,

$$3.5\{\Omega\} + 3.7\{\Omega\} = 7.2\{\Omega\}, \text{ and}$$
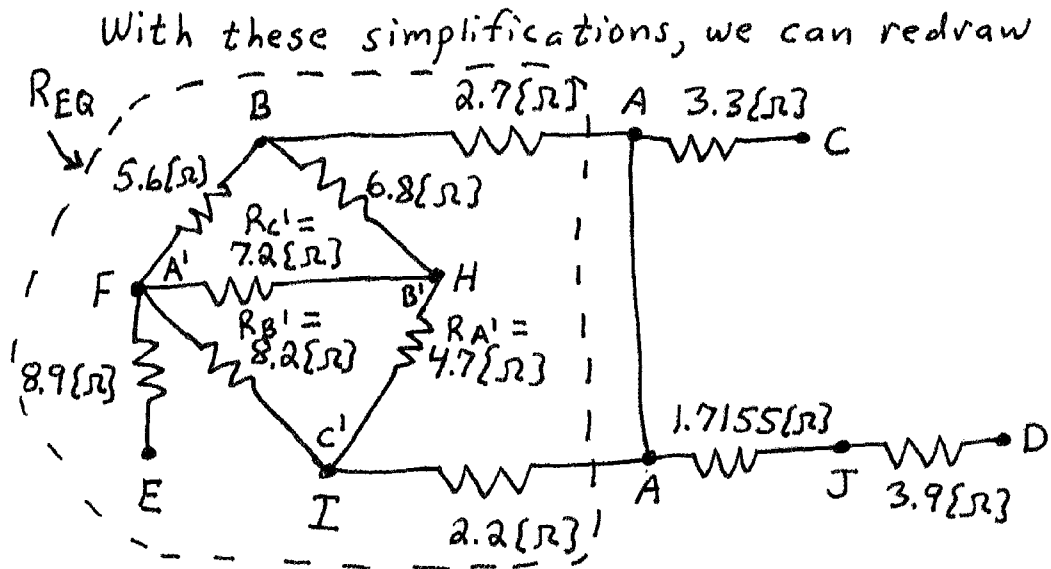
$$4.2\{\Omega\} \parallel 2.9\{\Omega\} = 1.7155\{\Omega\}. \text{ (see next page)}$$



- a) Looking from terminals C and D, the equivalent resistance shown as  $R_{EQ}$  is in parallel with a wire which is node A. So we can replace it with an open circuit. Thus the resistance seen from C and D,  $R_{CD}$ , is

$$R_{CD} = 3.3\{\Omega\} + 1.7155\{\Omega\} + 3.9\{\Omega\} = \boxed{8.9155\{\Omega\}}$$

- b) With respect to B and E, the three resistors  $R_{CD}$  are all open circuited, and can be replaced with short circuits. We have two series resistors,  $2.2\{\Omega\} + 2.7\{\Omega\} = 4.9\{\Omega\}$ .

see next page

We can perform a delta-to-woye transformation,

$$R_1 = \frac{R_{B'} R_{C'}}{R_{A'} + R_{B'} + R_{C'}} = \frac{8.2[\Omega](7.2[\Omega])}{4.7[\Omega] + 8.2[\Omega] + 7.2[\Omega]} =$$

$$R_1 = 2.9373[\Omega].$$


$$R_2 = \frac{R_{A'} R_{C'}}{R_{A'} + R_{B'} + R_{C'}} = \frac{4.7[\Omega](7.2[\Omega])}{4.7[\Omega] + 8.2[\Omega] + 7.2[\Omega]} =$$

$$R_2 = 1.6836[\Omega].$$

$$R_3 = \frac{R_{A'} R_{B'}}{R_{A'} + R_{B'} + R_{C'}} = \frac{4.7[\Omega](8.2[\Omega])}{4.7[\Omega] + 8.2[\Omega] + 7.2[\Omega]} =$$

$$R_3 = 1.9174[\Omega].$$

Redrawing, we have:

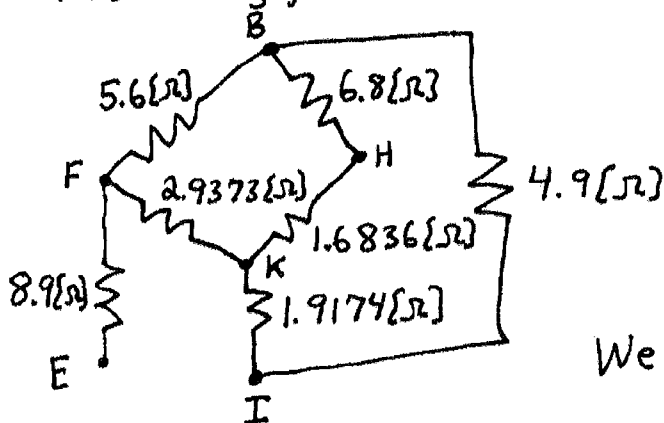


We have

$$(6.8[\Omega] + 1.6836[\Omega]) \parallel (4.9 + 1.9174)[\Omega] = 3.7799[\Omega].$$

see next page




We can redraw again to obtain:

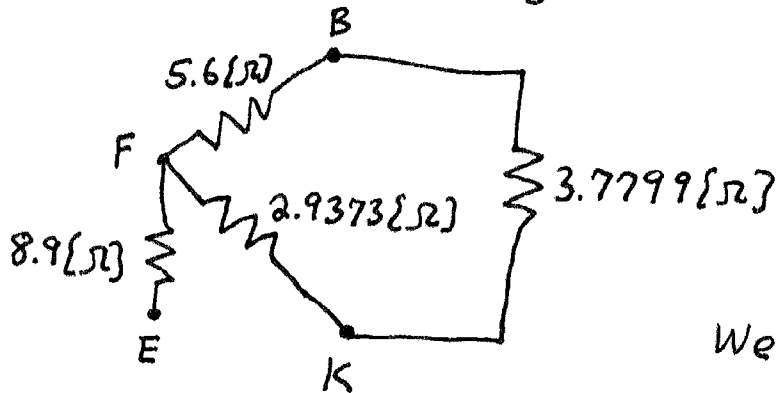

We have

$$(2.9373 + 3.7799 \{\Omega\}) \parallel 5.6 \{\Omega\} = 3.054 \{\Omega\}.$$

We redraw one more time to obtain

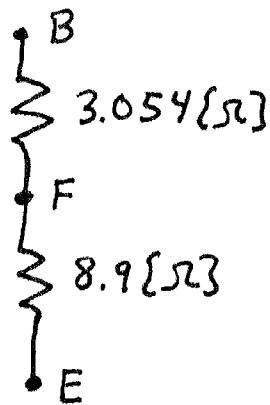

the diagram, from which we see the resistance with respect to B and E,  $R_{BE}$ , is

$$R_{BE} = 3.054 \{\Omega\} + 8.9 \{\Omega\}$$

$$R_{BE} = 11.954 \{\Omega\}.$$