

Name: _____ (please print)

Signature: _____

ECE 2201 – Quiz #1
February 7, 2023




- This quiz is closed book, closed notes.
- Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution which is not given in a reasonable order will lose credit.
- Show all units in solutions, intermediate results, and figures. Units in the quiz will be included between square brackets.
- If the grader has difficulty following your work because it is messy or disorganized, you will lose credit.
- Do not use red ink. Do not use red pencil.
- You will have 30 minutes to work on this quiz.

_____ /25

Room for extra work

A new electronic device called the TrombettaMax is shown in the diagram and labeled 'TM'. The voltage v_{TM} and current i_{TM} for the TrombettaMax are plotted in the graphs below. Reference polarities are shown in the figure.

- Find the power delivered by the TrombettaMax at $t = 16$ [ms].
- Find the energy delivered by the TrombettaMax from 5 [ms] to 15 [ms].
- If the charge carriers are positive, state whether they are gaining or losing energy at $t = 16$ [ms]. In a few words, explain how you know this.
- If the charge carriers are electrons, state whether they are gaining or losing energy at $t = 16$ [ms]. In a few words, explain how you know this.

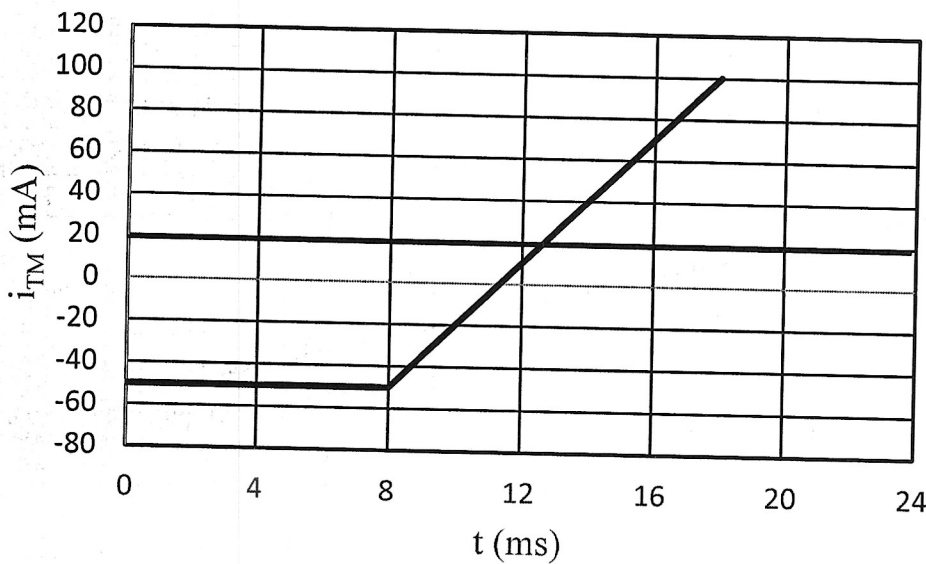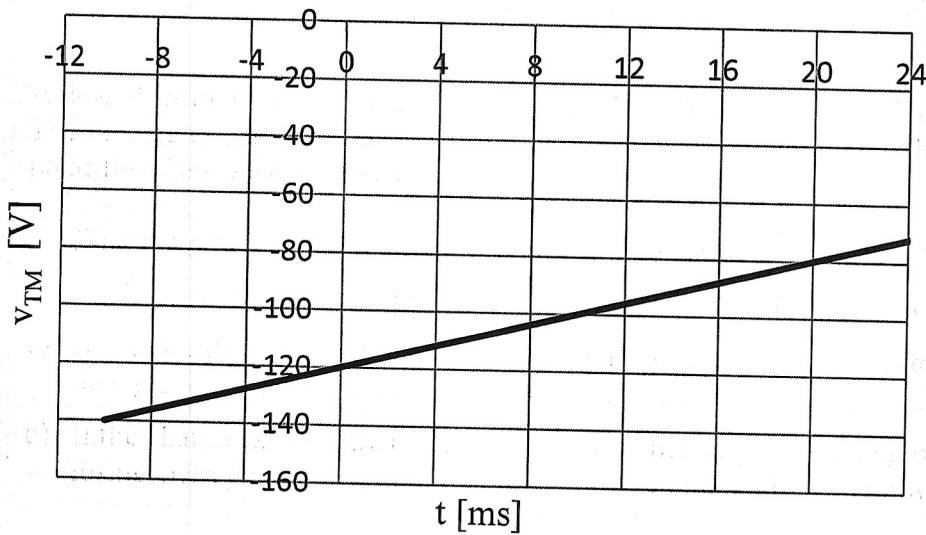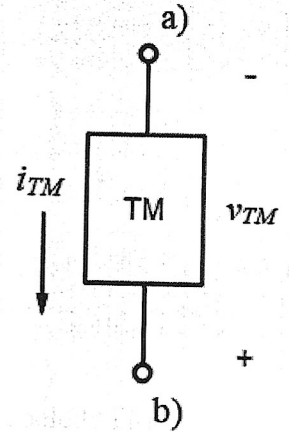

Room for extra work

Room for extra work

Room for extra work

We can simply read v_{TM} & i_{TM} from the graph at $t = 16 \text{ ms}$ but we need equations for these at part b), so...

$$+3 \quad v_{TM} = 2 \left[\frac{\text{V}}{\text{ms}} \right] t - 120 \text{ [V]}$$

$$i_{TM} = -50 \text{ [mA]} \quad 5 \leq t \leq 8 \text{ [ms]}$$

$$+3 \quad i_{TM} = 15 \left[\frac{\text{mA}}{\text{ms}} \right] (t - 8 \text{ [ms]}) - 50 \text{ [mA]} = 15 \left[\frac{\text{mA}}{\text{ms}} \right] t - 170 \text{ [mA]} \quad t \geq 8 \text{ [ms]}$$

a) The diagram is active sign relationship, so...

$$+3 \quad P_{\text{del by TM}} = + v_{TM} \cdot i_{TM} \quad \text{Convert to [V], [A], [s]}:$$

$$P_{\text{del by TM}} = (2000 \left[\frac{\text{V}}{\text{s}} \right] t - 120 \text{ [V]}) (15 \left[\frac{\text{A}}{\text{s}} \right] t - 0.170 \text{ [A]})$$

$$= 30000 \left[\frac{\text{W}}{\text{s}^2} \right] t^2 - 2140 \left[\frac{\text{W}}{\text{s}} \right] t + 20.4 \text{ [W]}$$

$$+2 \quad \underline{P_{\text{del by TM}} (0.016 \text{ [s]}) = -6.16 \text{ [W]}}$$

$$b) \quad W_{\text{del by TM}} = \int_{0.005 \text{ [s]}}^{0.008 \text{ [s]}} (-0.05 \text{ [A]}) (2000 \left[\frac{\text{V}}{\text{s}} \right] t - 120 \text{ [V]}) dt$$

$$+4 \quad + \int_{0.008 \text{ [s]}}^{0.015 \text{ [s]}} (30000 \left[\frac{\text{W}}{\text{s}^2} \right] t^2 - 2140 \left[\frac{\text{W}}{\text{s}} \right] t + 20.4 \text{ [W]}) dt$$

$$= 16.05 \text{ [mJ]} - 0.840 \text{ [mJ]}$$

$$+2 \quad \underline{W_{\text{del by TM}} = 15.21 \text{ [mJ]}}$$



Room for extra work

$$\therefore W_{\text{del by TM}} = -66.27 \text{ mJ}$$

- +2
c) At 16 ms , power delivered by TM is negative, so power is being absorbed. That power is coming from the positive charge carriers, so they are losing energy.

Alternative explanation: i_{TM} is positive so positive carriers are moving top to bottom in the diagram. v_{TM} is negative, so potential is higher at the top. So positive carriers are moving toward the more negative potential. Therefore they are losing energy.

- +2
d) The sign of the charge carriers makes no difference, so electrons are also losing energy.