

Signature

Name (print, please)

Student No.

**ECE 2300 Circuit Analysis
Summer 2009**

Quiz 5

DO NOT OPEN THIS QUIZ BOOKLET UNTIL INSTRUCTED TO DO SO


This quiz has 4 pages including this cover page. If you are missing any pages, raise your hand. You have 30 minutes to complete the quiz.

Notes

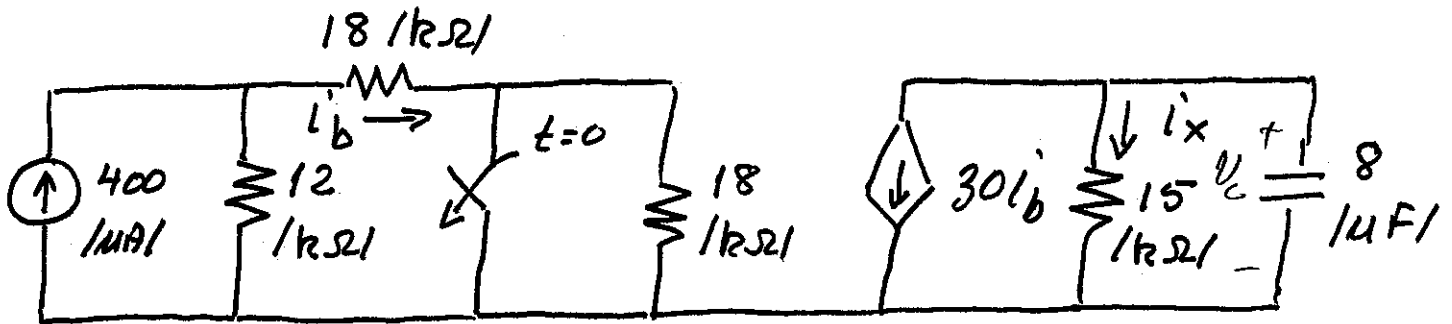1. Be sure your name and signature appear above.
2. The quiz is closed-book. You may have a calculator and one 8 ½" x 11" crib sheet.
3. To receive full credit for a problem, you must:
 - Show all work necessary to solve the problem;
 - Define all variables and parameters and label them on circuit diagrams;
 - Use the proper notation for all variables.
 - Show all units explicitly in intermediate and final results;
 - Indicate clearly whether power being calculated is absorbed or delivered;

_____ /20

The switch in the circuit shown was closed for a long time, and then opened at $t = 0$. Find $i_x(t)$ for $t > 0$.



$t < 0$:

$$I_b = 400 \times 10^{-6} \cdot \frac{12}{18 + 12} = 160 \mu\text{A}$$

$\times 6$

$$\therefore V_C(0^-) = V_C(0^+) = -30 I_b \cdot 15 \times 10^3 = -72 \text{ V}$$

$t > 0$: For $t \rightarrow \infty$, $C \rightarrow$ open. Then:

$$I_b = 400 \times 10^{-6} \cdot \frac{12}{36 + 12} = 100 \mu\text{A}$$

$\times 6$

$$\therefore V_C(\infty) = -30 I_b \cdot 15 \times 10^3 = -45 \text{ V}$$

$$\times 4 \quad R_{th} = 15 \text{ k}\Omega \Rightarrow \tau = R_{th} \cdot C = (15 \times 10^3)(8 \times 10^{-6}) = 0.12 \text{ s}$$

$$V_C(t) = V_C(\infty) + [V_C(0^+) - V_C(\infty)] e^{-t/\tau}$$

$\times 2$

$$= -45 + [-72 - (-45)] e^{-t/0.12} \text{ V} \quad t \geq 0 \text{ s}$$

$$= -45 - 27 e^{-t/0.12} \text{ V} \quad t \geq 0 \text{ s}$$

$\times 2$

∞

$$I_x(t) = \frac{V_C(t)}{15 \times 10^3} = -3 - 1.8 e^{-t/0.12} \text{ mA} \quad t > 0 \text{ s}$$