

Signature

Name (print, please)

## ECE 2300 Circuit Analysis

Summer 2011

Quiz 1

**DO NOT OPEN THIS QUIZ BOOKLET UNTIL INSTRUCTED  
TO DO SO**




*This quiz has 3 pages including this cover page. If you are missing any pages, raise your hand. You have 30 minutes to complete the quiz.*

### *Notes*

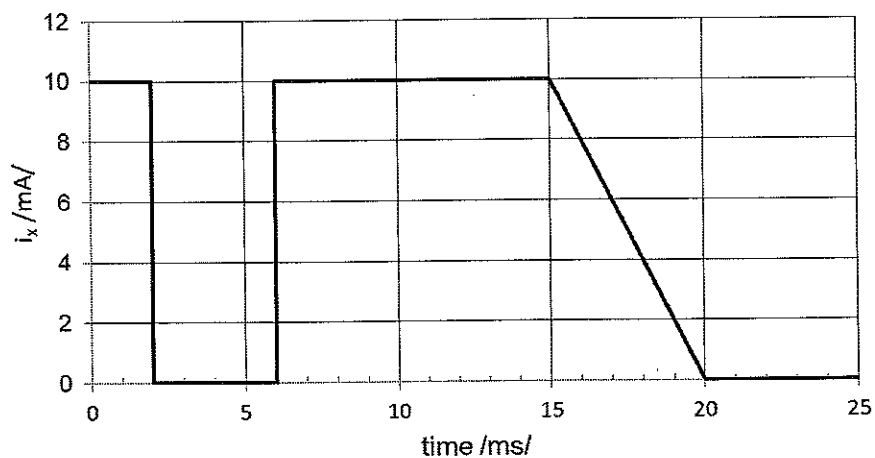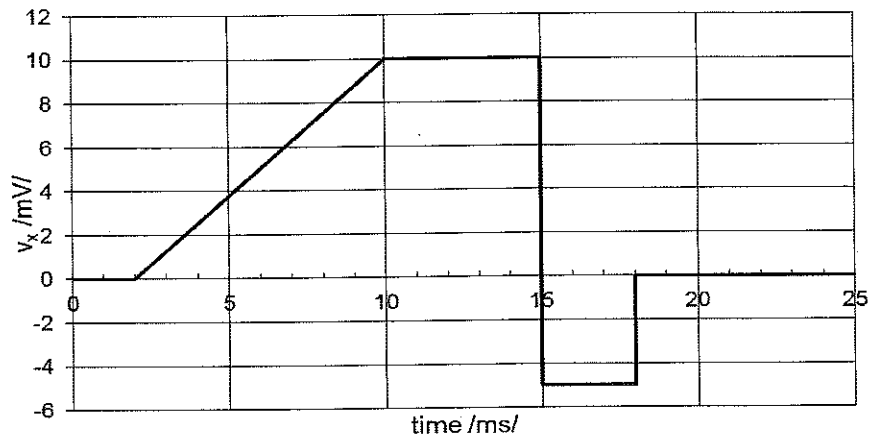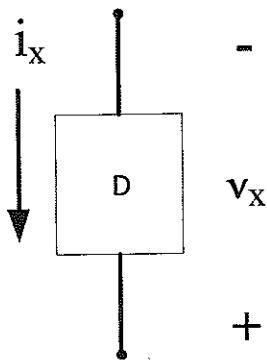1. Be sure your name and signature appear above.
2. The quiz is closed-book. You may have a calculator and one 8 ½ " x 11" crib sheet.
3. To receive full credit for a problem, you must:
  - Show all work necessary to solve the problem;
  - Define all variables and parameters and label them on circuit diagrams;
  - Use the proper notation for all variables.
  - Show all units explicitly in intermediate and final results;
  - Indicate clearly whether power being calculated is absorbed or delivered;

The plots in the figures below show the voltage  $v_x$  across and the current  $i_x$  through the device D.

- $\times 30$  i. Find the energy absorbed by the device over the time period 0 to 10 /ms/.
- $\times 20$  ii. Find the power delivered by the device at 17 /ms/.



2) Energy absorbed by D:  $w_{abs,D} = \int_0^{10 \text{ /ms/}} P_{abs,D} dt$

$P_{abs,D} = -i_x v_x$  so we need an equation for  $v_x(t)$ . Since  $v_x = 0$  for  $0 \leq t \leq 2 \text{ /ms/}$ , we need  $v_x(t)$  for  $2 \leq t \leq 10 \text{ /ms/}$ , I will convert everything to /s/ and /V/ and /A/ to reduce errors in units.

Room for Extra Work

$$V_x(t) = a + bt$$

$$t = 0.002 \text{ s} \Rightarrow V_x = 0 \quad \therefore 0 = a + 0.002b \quad (1)$$

$$t = 0.010 \text{ s} \Rightarrow V_x = 0.01 \text{ V} \quad \therefore 0.01 = a + 0.010b \quad (2)$$

Solving these eqns. together gives  $a = -0.0025 \text{ V}$  /  $b = 1.25 \text{ V/s}$

$$x^{10} \quad V_x(t) = 1.25t - 0.0025 \text{ V} \quad 0.002 \leq t \leq 0.010 \text{ s}$$

Now  $i_x(t) = 0$  until  $t = 0.006 \text{ s}$  so...

$$x^{15} \quad W_{abs,D} = - \int_{0.006 \text{ s}}^{0.010 \text{ s}} (0.010) (-0.0025 + 1.25t) dt$$

$$= \left( 2.15 \times 10^{-5} t - \frac{1}{2} 1.25 \times 10^{-2} t^2 \right) \Big|_{0.006 \text{ s}}^{0.010 \text{ s}}$$

$$x^5 \quad \underline{W_{abs,D} = -3 \times 10^{-7} \text{ J} = -0.3 \text{ } \mu\text{J}}$$

$$ii \quad P_{del,D} = -P_{abs,D} = -(-i_x)(V_x)$$

We could find a general expression for  $P_{del,D}$  if we had  $i_x(t)$ . Alternatively we can try to read a value for  $i_x$  at  $t = 17 \text{ ms}$  but this invites error, so...

$$i_x(t) = c + dt \quad t = 0.015 \text{ s} \Rightarrow i_x = 0.010 \text{ A}$$

$$\therefore 0.01 = c + 0.015d \quad (1)$$

$$t = 0.020 \text{ s} \Rightarrow i_x = 0 \quad \therefore 0 = c + 0.020d \quad (2)$$

$$x^{10} \Rightarrow i_x(t) = 0.04 - 2.0t \text{ A} \quad 0.015 \leq t \leq 0.020 \text{ s}$$

✓

$$P_{del, D} \Big|_{t=0.017 \text{ s}} = i_x \Big|_{t=0.017 \text{ s}} \cdot v_x \Big|_{t=0.017 \text{ s}}$$

$$= [0.04 - 2.0(0.017)] [-5 \times 10^{-3}]$$

$\times 10$

$$P_{del, D} \Big|_{t=0.017 \text{ s}} = -0.03 \times 10^{-3} \text{ W} = -30 \text{ } \mu\text{W}$$

---