

Name: \_\_\_\_\_ (please print)

Signature: \_\_\_\_\_


ECE 2300 – Quiz #6  
July 21, 2016

**Keep this quiz closed and face  
up until you are told to begin.**

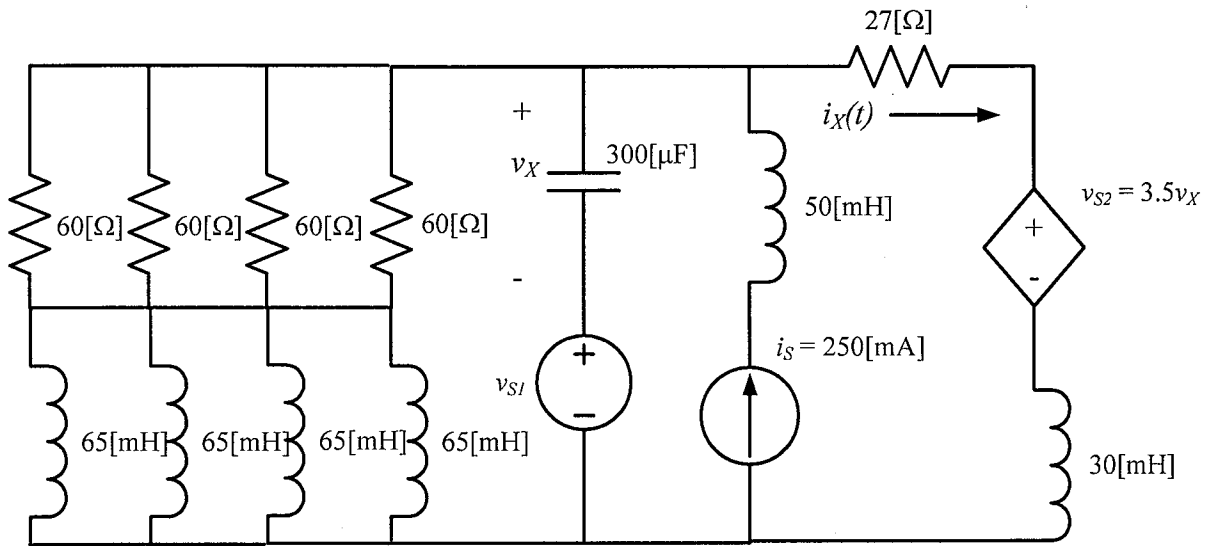1. This quiz is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution which is not given in a reasonable order will lose credit.
3. Show all units in solutions, intermediate results, and figures. Units in the quiz will be included between square brackets.
4. If the grader has difficulty following your work because it is messy or disorganized, you will lose credit.
5. Do not use red ink. Do not use red pencil.
6. You will have 30 minutes to work on this quiz.

Room for extra work

In the circuit below,  $v_{s1}(t) = 30 \cos(377t + 20^\circ)$  [V]. Find the steady state value of  $i_X(t)$ .



Room for extra work

Name: \_\_\_\_\_ (please print)


Signature: \_\_\_\_\_

ECE 2300 – Quiz #6  
July 21, 2016

**Keep this quiz closed and face  
up until you are told to begin.**

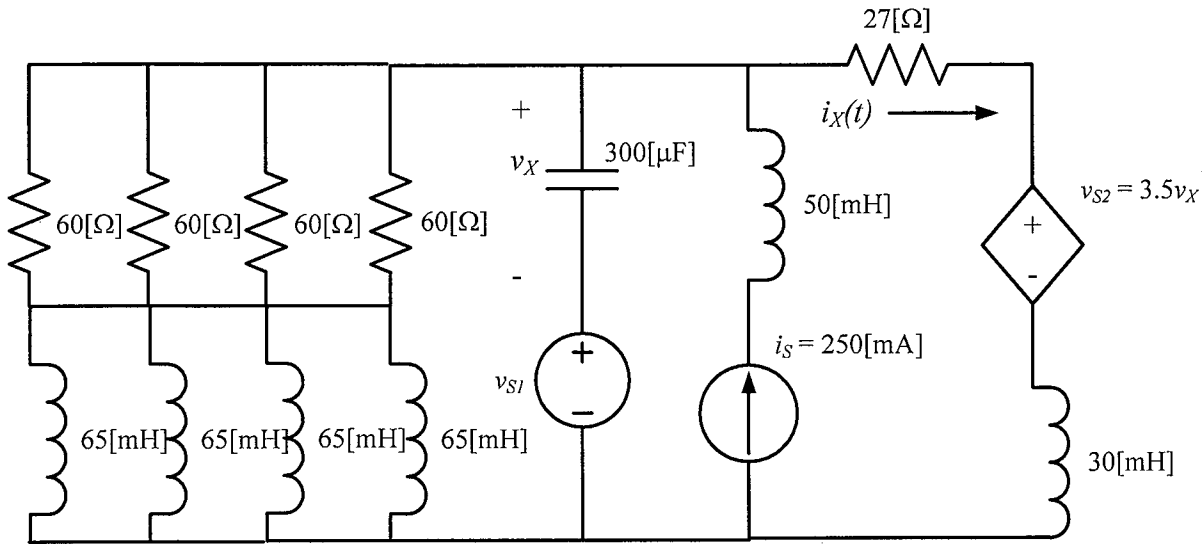1. This quiz is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution which is not given in a reasonable order will lose credit.
3. Show all units in solutions, intermediate results, and figures. Units in the quiz will be included between square brackets.
4. If the grader has difficulty following your work because it is messy or disorganized, you will lose credit.
5. Do not use red ink. Do not use red pencil.
6. You will have 30 minutes to work on this quiz.

In the circuit below,  $v_{s1}(t) = 30 \cos(377t + 20^\circ)$  [V]. Find the steady state value of  $i_X(t)$ .



It seems clear that we want to simplify the network on the left:


Four  $60 [\Omega]$  resistors in parallel is  $15 [\Omega]$ .

Four  $65 [\text{mH}]$  inductors in parallel is  $16.25 [\text{mH}]$ .

Next: We need superposition because our sources do not have the same frequency.

We treat  $v_{s1}$  first, in which case  $i_S \rightarrow$  open circuit.

$$\omega = 377 [\text{rad/s}]$$

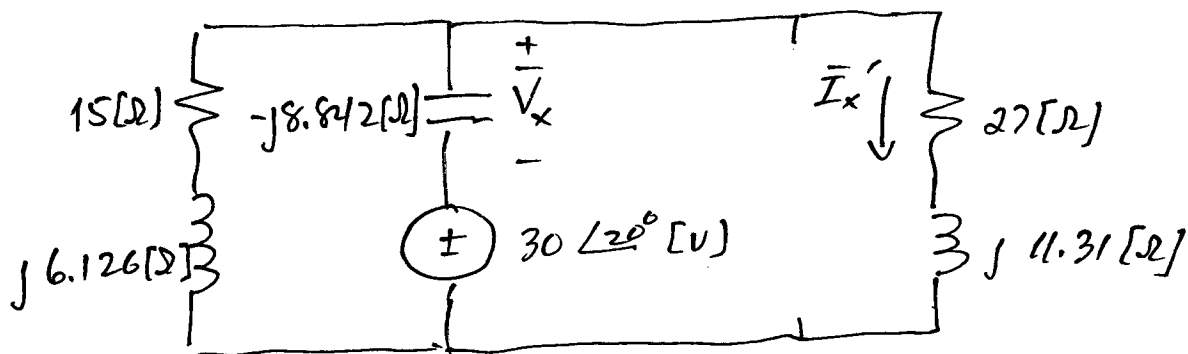

$$\frac{\bar{V}_X + 30 \angle 20^\circ}{15 + j6.126} + \frac{\bar{V}_X}{-j8.842} + \frac{\bar{V}_X + 30 \angle 20^\circ - 3.5 \bar{V}_X}{27 + j11.31} = 0$$


Room for extra work

$$\hat{V}_x = 23.08 \angle 77.61^\circ \text{ [V]}$$

$$\hat{I}_x' = \frac{\hat{V}_x + 30 \angle 20^\circ - 3.5 \hat{V}_x}{27 + j11.31} = 1.66 \angle -93.8^\circ \text{ [A]}$$

$$\therefore i_x'(t) = 1.66 \cos(377 \left[ \frac{\text{rad}}{\text{s}} \right] t - 93.8^\circ) \text{ [A]}$$

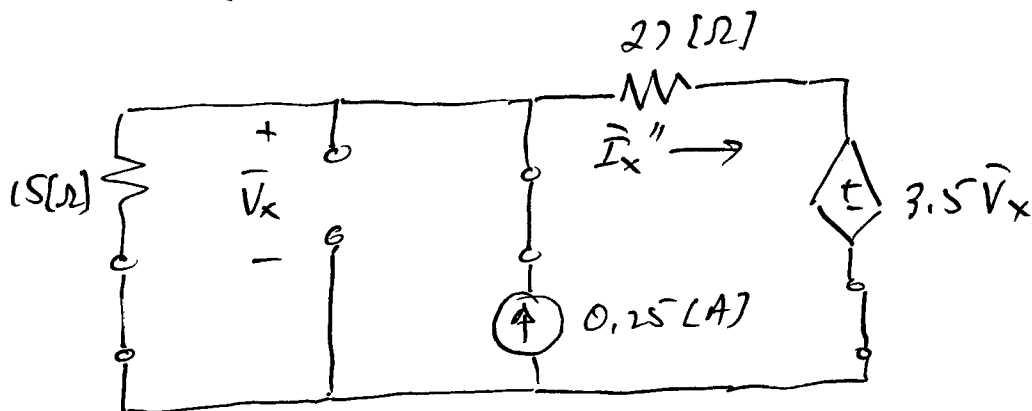The frequency of  $i_s = 0$  so the capacitor is an open circuit and the inductors are shorts.



$$\frac{\hat{V}_x}{15} + \frac{\hat{V}_x - 3.5 \hat{V}_x}{27} - 0.25 = 0 \Rightarrow \hat{V}_x = -9.643 \text{ [V]}$$

$$\hat{I}_x'' = \frac{\hat{V}_x - 3.5 \hat{V}_x}{27} = 0.8929 \text{ [A]}$$

$$i_x'' = 0.8929 \text{ [A]}$$

$$\text{So } i_x(t) = i_x'(t) + i_x''(t) = 1.66 \cos(377 \left[ \frac{\text{rad}}{\text{s}} \right] t - 93.8^\circ) + 0.8929 \text{ [A]}$$