



ECE 2300

Circuit Analysis

CIRCUIT ANALYSIS MADE EASY

PART II: KIRCHHOFF'S VOLTAGE LAW

University of Houston

Len Trombetta


de la Rosa-Pohl




UNIVERSITY OF HOUSTON
Learning. Leading.

Review: Ohm's Law

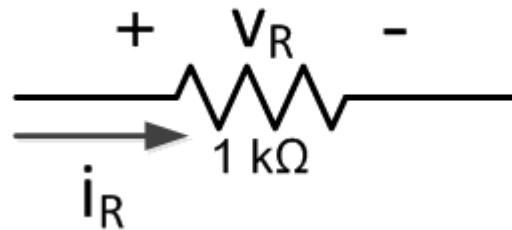Ohm's Law depends on how we label current and voltage:




$$v_R = i_R R$$

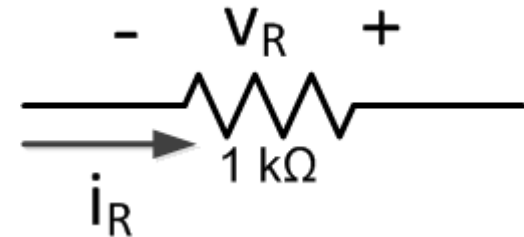


$$v_R = -i_R R$$

These are of course the same things...

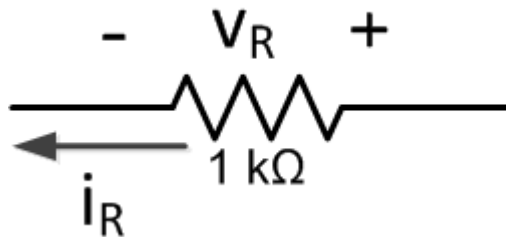

$$v_R = i_R R$$

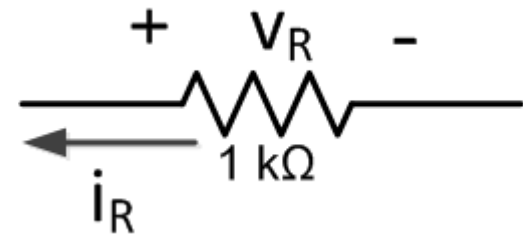

$$v_R = -i_R R$$



KIRCHHOFF'S VOLTAGE LAW


de la Rosa-Pohl



UNIVERSITY OF HOUSTON
Learning. Leading.

A Simple Circuit

- We want to “solve” this circuit...

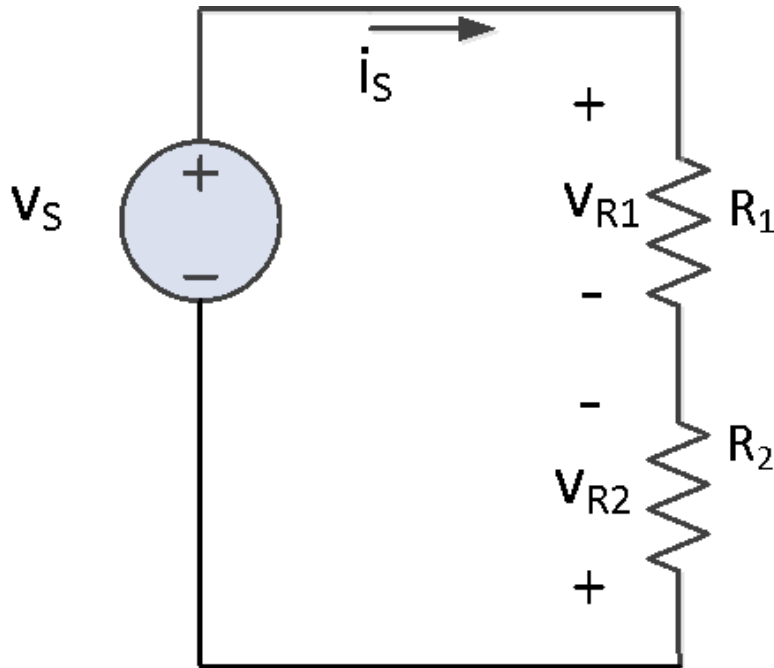

Solve??


- We want to know all of the voltages (v_{R1} , v_{R2}) and currents (i_s).
- We will assume the source (v_s) and resistances are known.

Why did I label the voltages that way?

Because I can. And anyway, it's my class.

Kirchhoff's Voltage Law

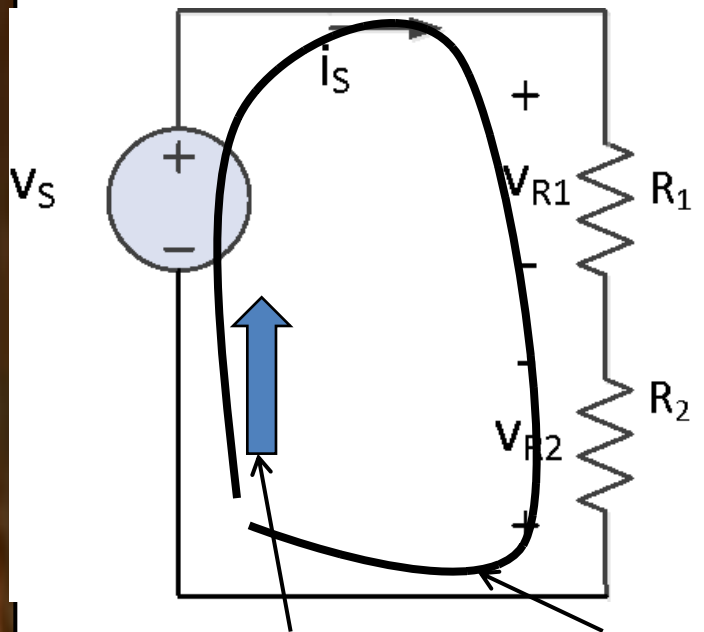KVL: The algebraic sum of the voltages around a closed loop is 0.



Direction of KVL path
(either way is fine).

KVL path

Closed Loop: We will trace a path around the circuit, accounting for all the voltages as we go. It doesn't matter which way the path goes.


Algebraic: we need to be aware of the sign of the voltage.

$$-v_S + v_{R1} - v_{R2} = 0$$

$$v_S = v_{R1} - v_{R2}$$

My Rule: When we trace a path through a voltage from '-' to '+', we put a minus sign in front of the voltage; otherwise not.

Substitute Ohm's Law for v_R 's

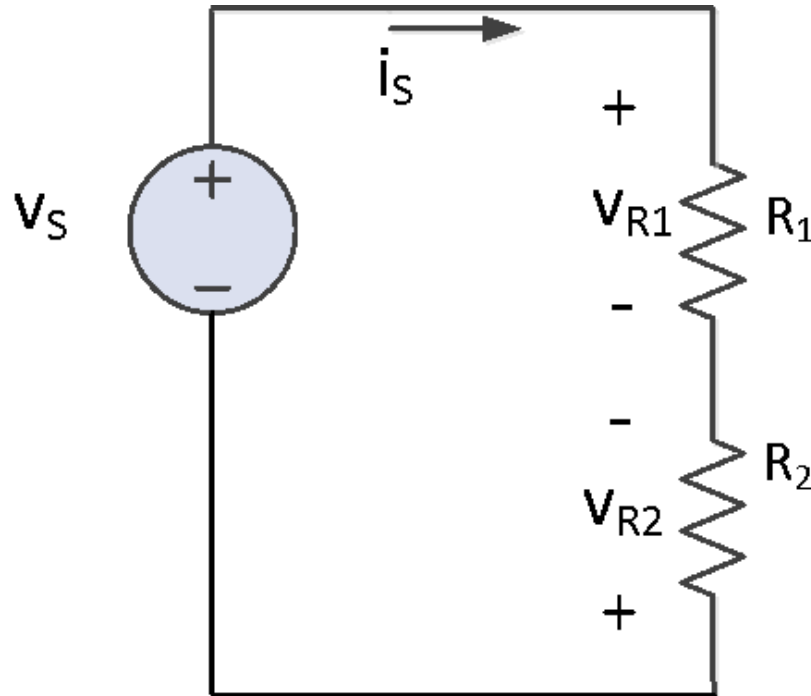

KVL

$$v_S = v_{R1} - v_{R2}$$

Ohm's Law


$$v_{R1} = i_S R_1 \quad v_{R2} = -i_S R_2$$

Algebra...

$$v_S = i_S R_1 + i_S R_2$$

$$i_S = \frac{v_S}{R_1 + R_2}$$

Now You Do It!

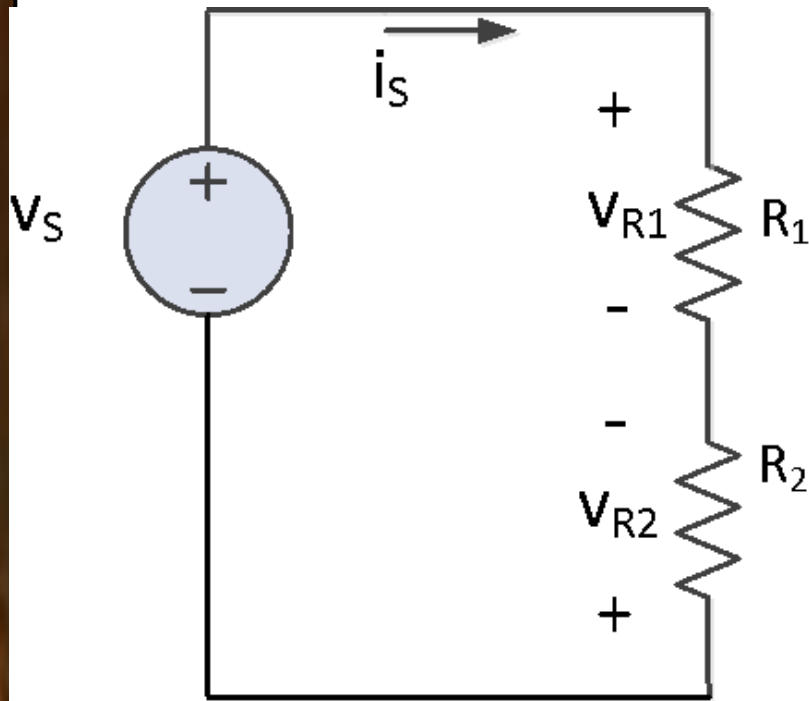

KVL

$$v_S = v_{R1} - v_{R2}$$


Ohm's Law

$$v_{R1} = i_S R_1 \quad v_{R2} = -i_S R_2$$

Algebra

$$i_S = \frac{v_S}{R_1 + R_2}$$

Now You Do It!

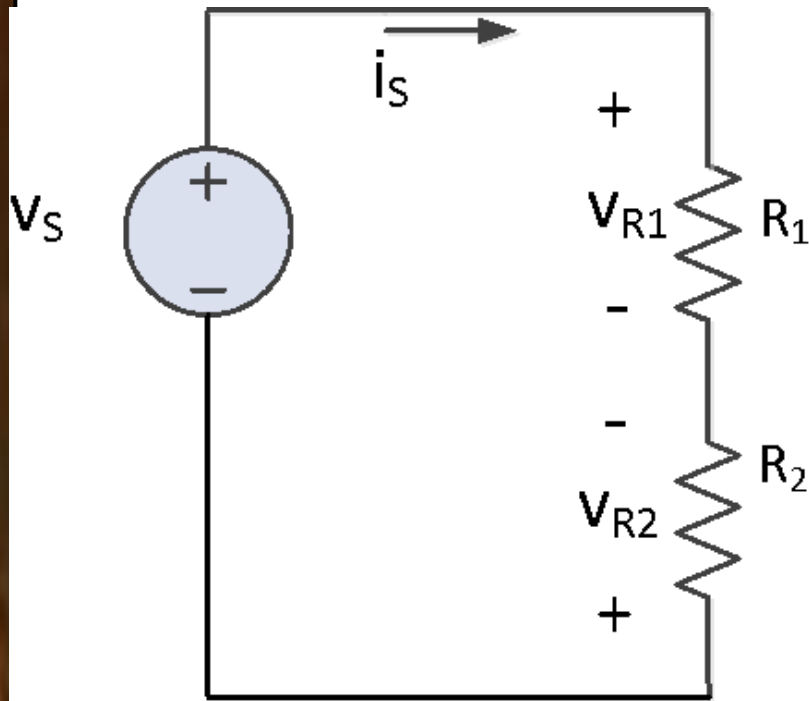

Given:

$$R_1 = 1.5 \text{ [k}\Omega\text{]}$$

$$R_2 = 2.2 \text{ [k}\Omega\text{]}$$

$$v_S = 9 \text{ [V]}$$

Find:

$$i_S$$

$$v_{R1}$$

The End

de la Rosa-Pohl



UNIVERSITY OF HOUSTON
Learning. Leading.