



---

*ECE 2300*

*Circuit Analysis*

**CIRCUITS MADE EASY PART I:  
LABELING AND OHM'S LAW**


*University of Houston*

*Len Trombetta*

*de la Rosa-Pohl*



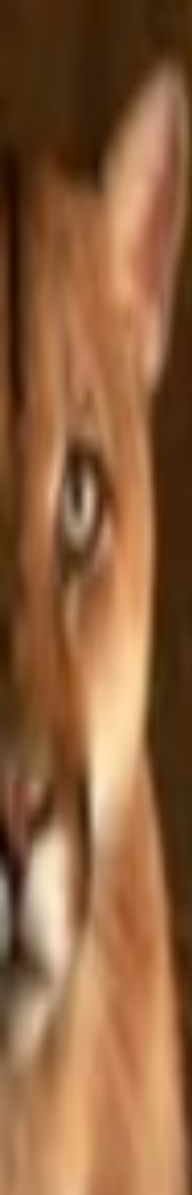UNIVERSITY OF HOUSTON  
Learning. Leading.




# OHM'S LAW

*de la Rosa-Pohl*



UNIVERSITY OF HOUSTON  
Learning. Leading.

# Ohm's Law

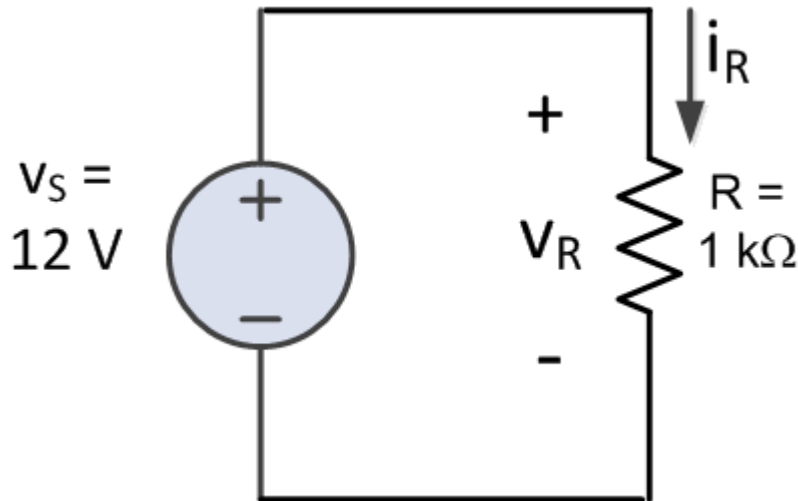

Ohm's Law gives the relationship between the voltage and the current for a resistor...

$$v_R = i_R R$$

...but there are some details we need to worry about.

Current direction and voltage polarity: how do we know what these are? How did I decide to label them that way? We can of course measure them, but to do circuit analysis we will need to label them on circuit diagrams, even if we don't have a multimeter!

We need to know some labeling conventions...



# VOLTAGE AND CURRENT LABELS



*de la Rosa-Pohl*



UNIVERSITY OF HOUSTON  
Learning. Leading.

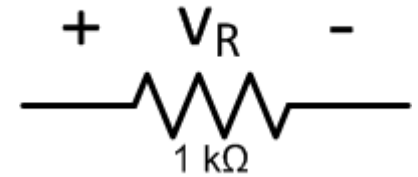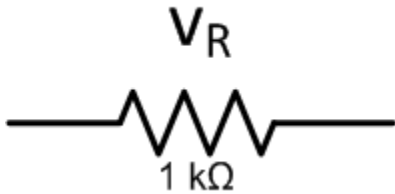
# Voltage Label Rules

- Voltage labels get a 'v' with a subscript (e.g.,  $v_R$ ), and a '+' and '-'.
- A ' $v_R$ ' without a '+' and a '-' means **nothing**.
- A '+' and a '-' without a ' $v_R$ ' mean **nothing**.



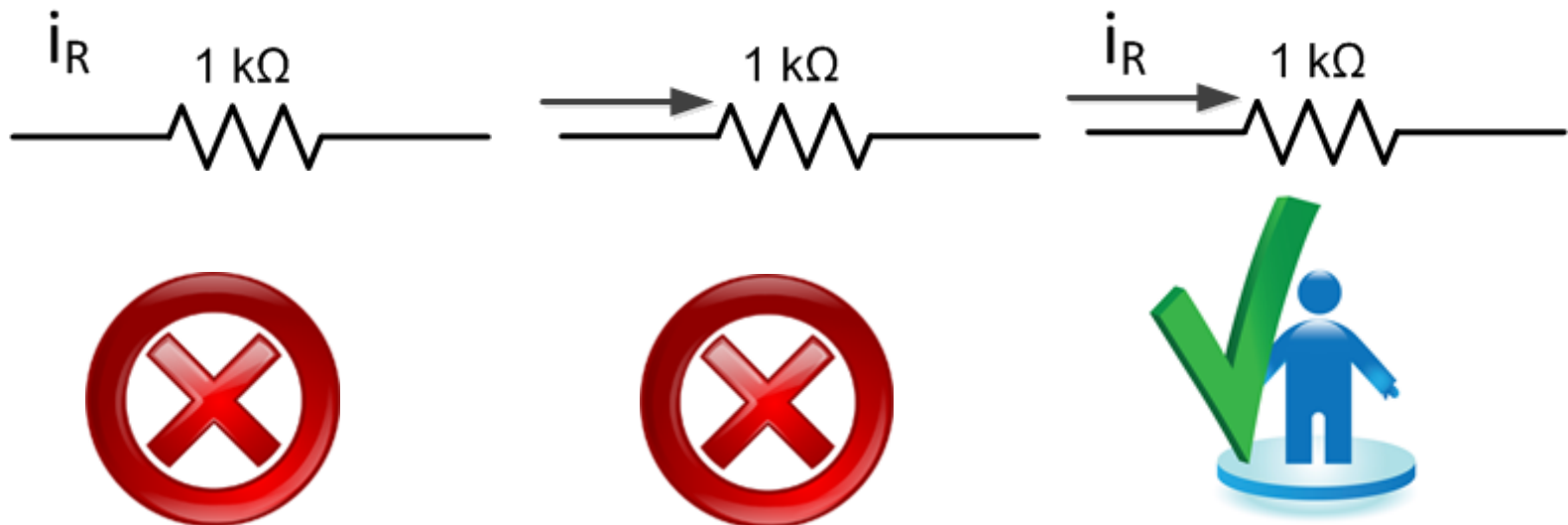
# Current Label Rules

- Current labels get an 'i' with a subscript (e.g.,  $i_R$ ), and an arrow.
- An ' $i_R$ ' without an arrow means **nothing**.
- An arrow without an ' $i_R$ ' means **nothing**.



# Voltage and Current Labels

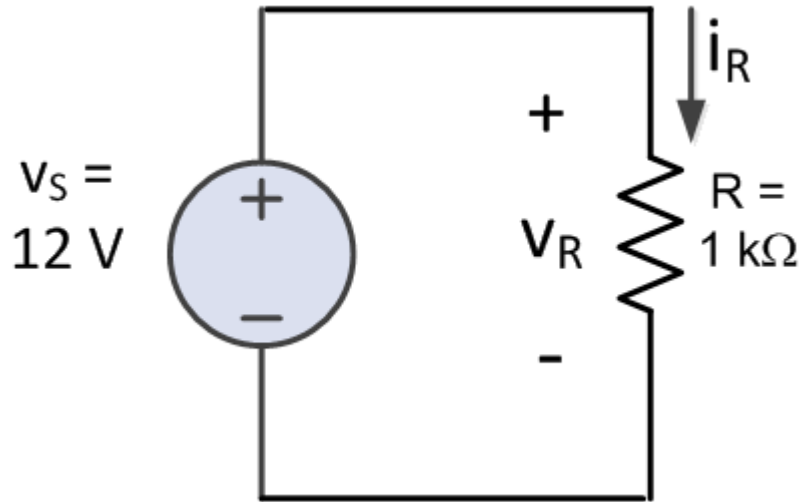


You can probably see that  $v_R = 12\text{ V}$ .

We could easily prove this using KVL (which we will do later).

We also have Ohm's Law:  $v_R = i_R R$

...which means that (by Ohm's Law)  $i_R = 12\text{ mA}$

# Voltage and Current Labels

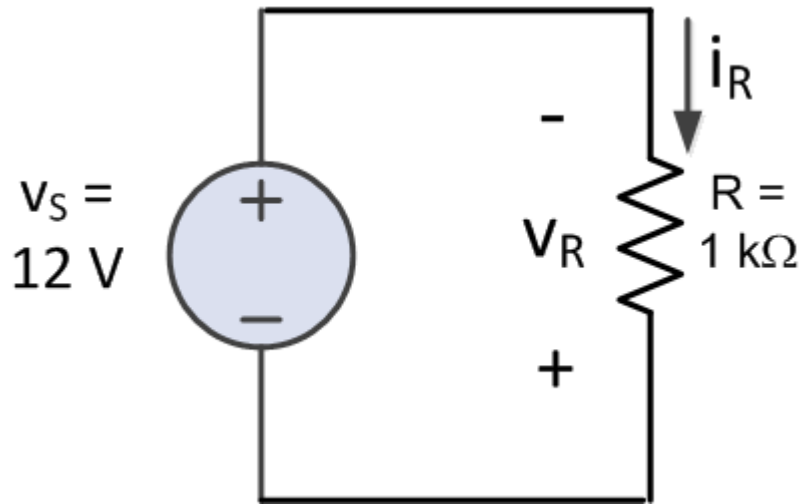

NOW what's  $v_R$ ??

$$V_R = -12\text{ V.}$$

Again, we could prove this using KVL.


Q: Does it matter that I changed the label showing the voltage polarity?

A: No. I can label the voltage polarity any way I like (well, there are only two choices, after all).



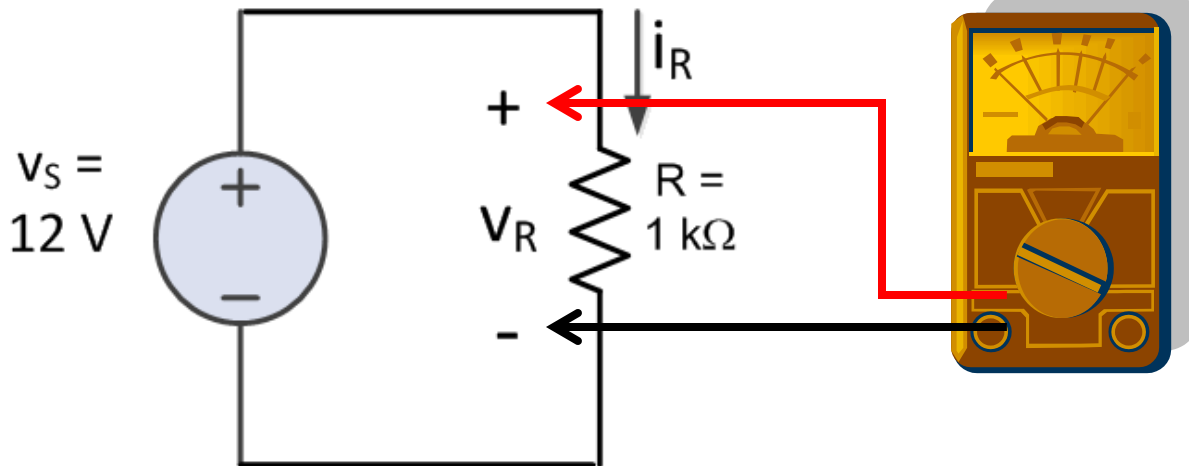
# Voltage and Current Labels

If you find this strange or confusing, think about this: you already knew it!!




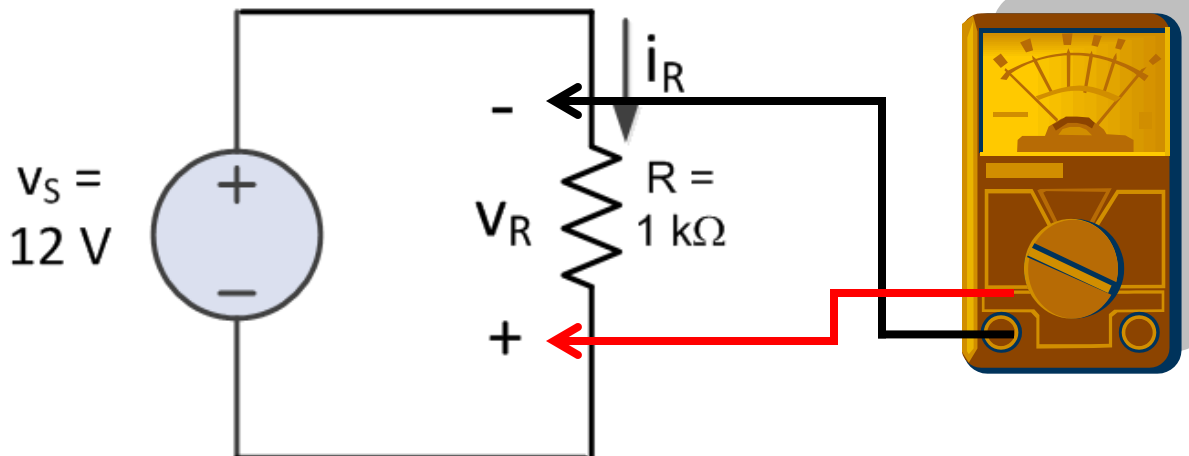With RED at the top, you were measuring the voltage drop from top to bottom.



With RED at the bottom, you were measuring the voltage drop from bottom to top.

# Voltage and Current Labels

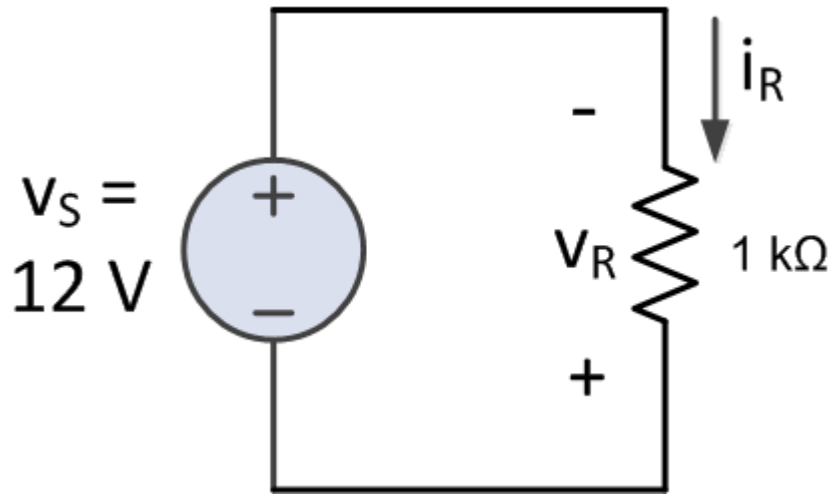

We have  
 $V_R = -12\text{ V}$

So...what about the  
current?


All we did was change a label - the circuit is exactly  
the same...

...which means  $i_R$  must still be = 12 mA

...which means that the correct form of Ohm's Law  
here is...

$$v_R = -i_R R$$

# Voltage and Current Labels

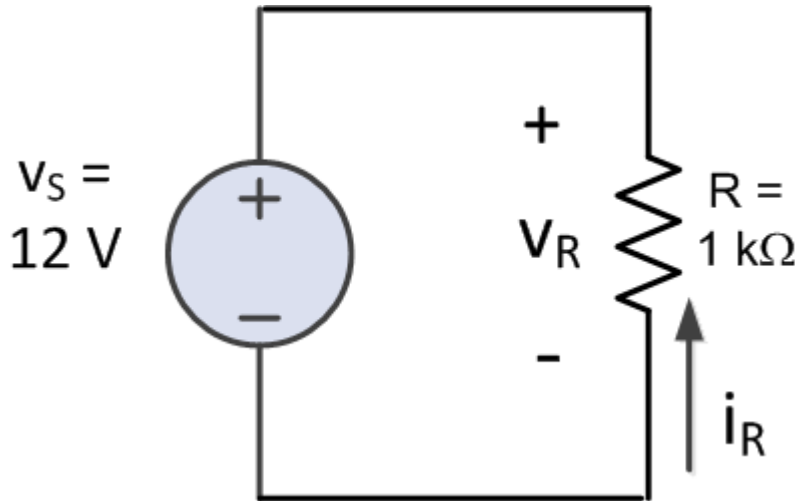

Back to the first drawing with  $v_R = 12\text{ V}$ .


...but with the current direction changed.

Q: Does it matter that I changed the label showing the current direction?

A: No. I can label the current any way I like (well, there are only two choices, after all).

So...what is the current?

# Voltage and Current Labels

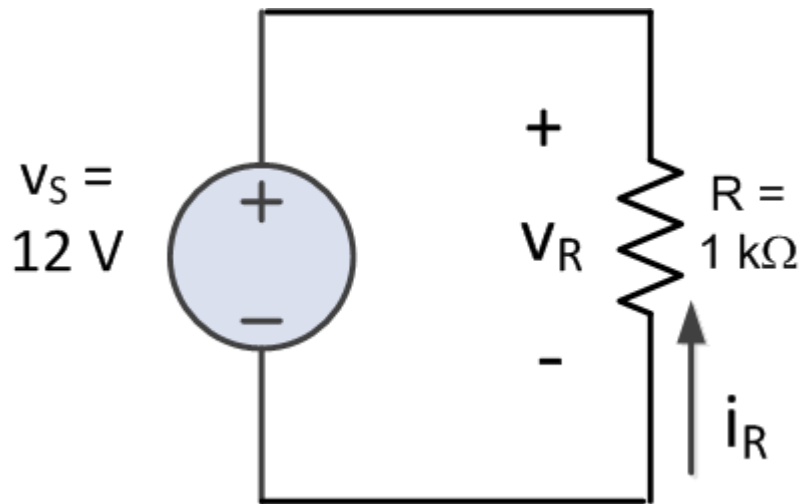

We have again  
 $V_R = 12\text{ V} \dots$


So...what about the  
current?

All we did was change a label - the circuit is exactly  
the same...

...which means  $i_R$  must be =  $-12\text{ mA}$

...which again means that the correct form of  
Ohm's Law here is...

$$v_R = -i_R R$$

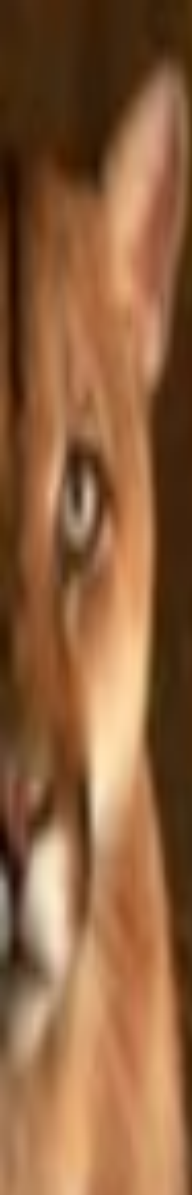

# OHM'S LAW REVISITED


*de la Rosa-Pohl*




UNIVERSITY OF HOUSTON  
Learning. Leading.
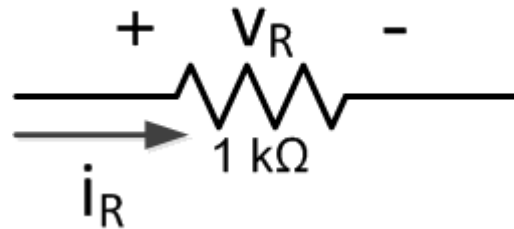
# Ohm's Law Revisited

Ohm's Law depends on how we label current and voltage:




$$v_R = i_R R$$

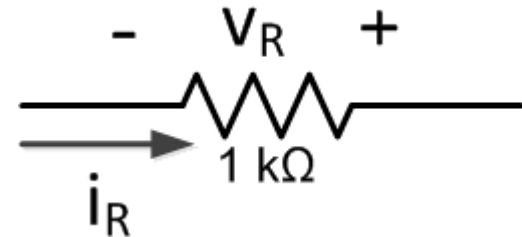


$$v_R = -i_R R$$

These are of course the same things...

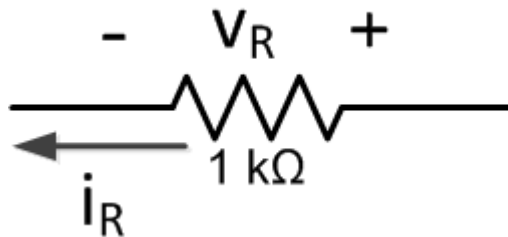


$$v_R = i_R R$$

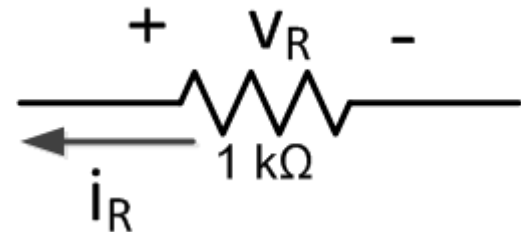


$$v_R = -i_R R$$

# Let's Try Some

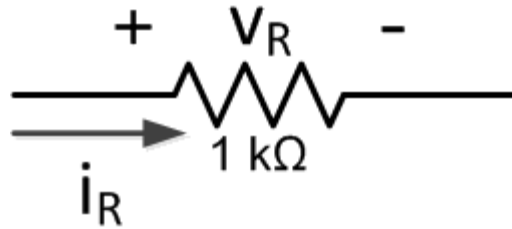


$$V_R = 7\text{ V}$$

$$i_R = ??$$

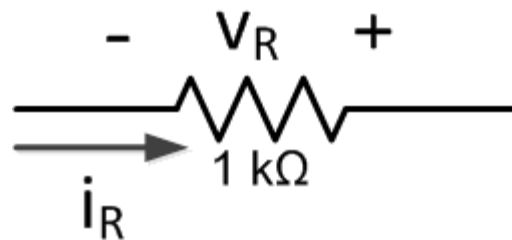

$$V_R = 120\text{ V}$$

$$i_R = ??$$

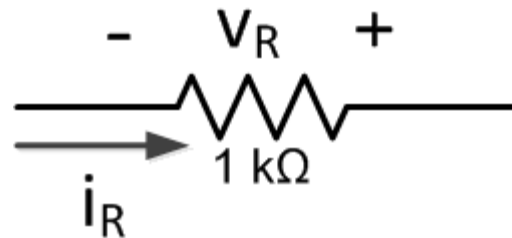


$$V_R = -120\text{ V}$$

$$i_R = ??$$

de la Rosa-Pohl




# Let's Try Some

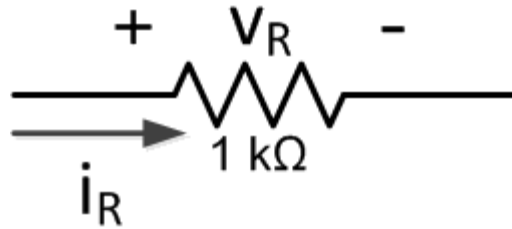


$$i_R = 7\text{ mA}$$

$$V_R = ??$$

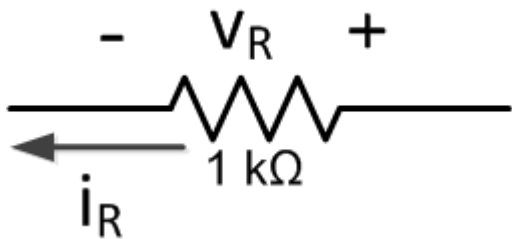

$$i_R = -12\text{ mA}$$

$$V_R = ??$$

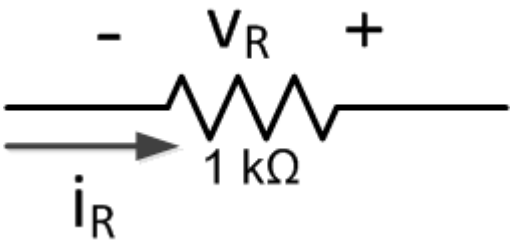

$$i_R = 50\text{ mA}$$

$$V_R = ??$$




# Actual vs. Reference Polarity

---

Because of this, we distinguish between:

*Reference Polarity or Reference Direction:* This refers to the polarity we label on a circuit diagram. We are free to put the +/ – in either direction, and to have the arrow point either way. We don't need to know which way the current is going or what the sign of the voltage really is.

*Actual Polarity or Actual Direction:* This refers to which way the current is really going, and which side of the device really has the higher potential. We do not have to label voltages and polarities with actual directions if we don't feel like it. When we calculate or measure the voltage or current, we will know from the sign whether the actual polarity is the same as the reference polarity we chose.

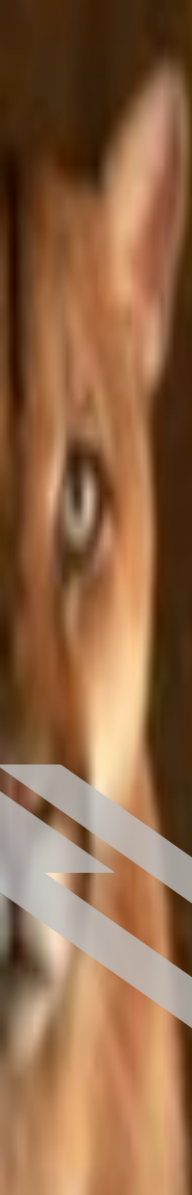

---

# The End

*de la Rosa-Pohl*

