
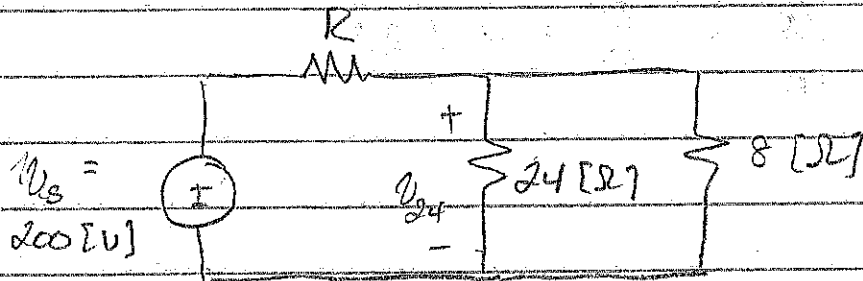


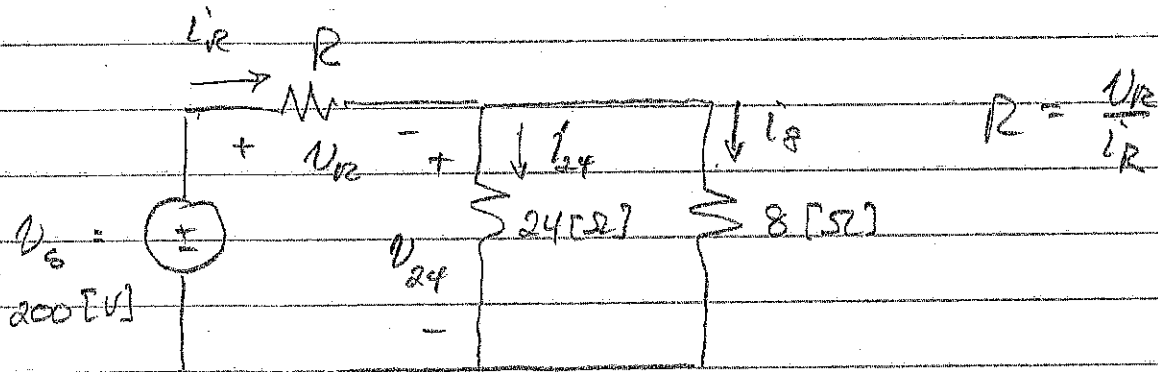Example 2.1 KVL, KCL, Ohm's Law
 - From Nilsson & Riedel 8ed. Pg. 42



Find: R , Given: $V_{24} = 120 [V]$

Approach: If we know the ratio of voltage to current in R , we can find R . We will need to label these variables, as well as some others...



Ohm: $I_{24} = \frac{V_{24}}{24} = 5 [A]$

KVL: $24 I_{24} - 8 I_8 = 0 \Rightarrow I_8 = \frac{24 I_{24}}{8} = \frac{V_{24}}{8} = 15 [A]$


KCL: $I_R = I_{24} + I_8 = 20 [A]$

$$\text{KVL: } V_R + V_{df} - 200 = 0 \Rightarrow V_R = 80 \text{ [V]}$$


$$\therefore R = \frac{V_R}{i_R} = \frac{80}{20} = 4 \text{ [}\Omega\text{]}$$

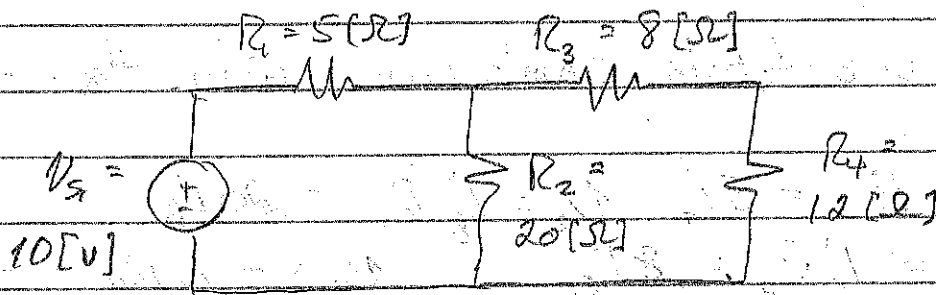Example 2.7

Solve the circuit shown by finding values for all unknown currents.



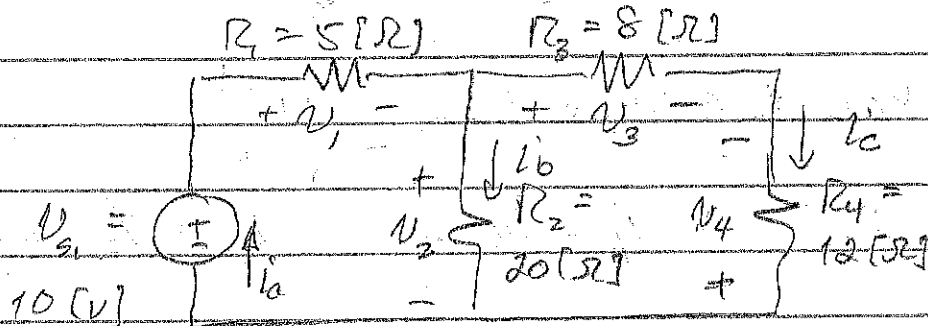Idea: There are 3 unknown currents, which have been labeled on the diagram below. Resistor voltages have also been labeled, although as we will see, we don't need to do this - there's a shortcut!



We can write 1 independent KCL and 2 independent KVLs:

KCL:
$$I_1 = I_2 + I_3 + I_4$$

KVL

$$V_1 + V_2 - V_3 = 0$$

KVL

$$V_3 - V_4 - V_2 = 0$$

*

We now substitute Ohm's Law into the KVL's:

$$V_1 = i_a R_1 = 5i_a \quad V_2 = i_b R_2 = 20i_b$$

$$V_3 = i_c R_3 = 8i_c \quad V_4 = -i_c R_4 = -12i_c$$

Then the KVL's become: (and using $V_s = 10$ [V])

$$5i_a + 20i_b - 10 = 0$$

$$8i_c - (-12i_c) - 20i_b = 0$$

Solving KCL & 2 KVL's:

$$i_a = \frac{2}{3} \text{ [A]}$$

$$i_b = \frac{1}{3} \text{ [A]}$$


$$i_c = \frac{1}{3} \text{ [A]}$$

We could have written the last two KVL's directly, without having to label resistor voltages. See Trombetta's notes, Chapter 2.

* We have written V_4 differently from the others (to illustrate the use of Ohm's Law with the active sign relationship).

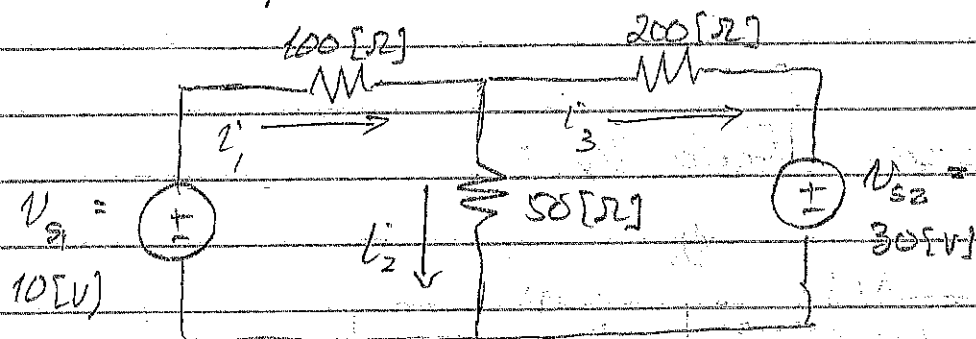Example 2.3

Find the power delivered by each of the voltage sources in the circuit below.



Approach: We'll find the unknown currents, which have been labeled on the diagram. We will need to solve simultaneous equations to find them, but once we have them, we can find anything else, including source power, with a single equation.

KCL

$$i_1 = i_2 + i_3$$

KVL

$$200 i_3 + 30 - 50 i_2 = 0$$

KVL

$$100 i_1 + 50 i_2 - 10 = 0$$

Solving gives

$$i_1 = 28.57 \text{ mA}$$

$$i_2 = 142.86 \text{ mA}$$


$$i_3 = -114.29 \text{ mA}$$

↗

$$P_{del \text{ by } V_{S1}} = V_{S1} \cdot I_1' = 285.7 \text{ [mW]}$$

$$P_{del \text{ by } V_{S2}} = -V_{S2} \cdot I_3 = 3.429 \text{ [W]}$$

Something else: Find V_x :

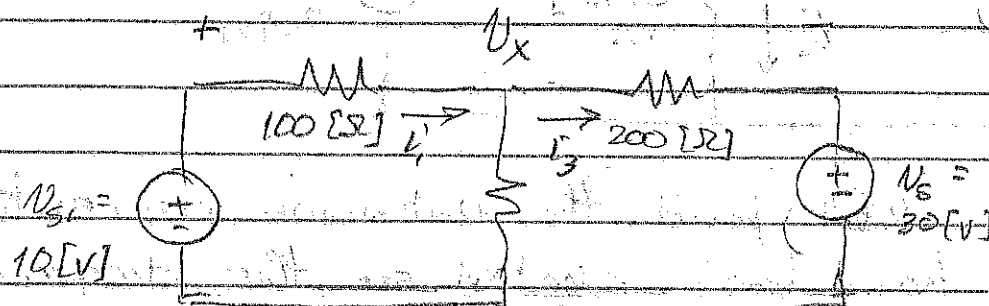

We can use V_x in a KVL:

$$V_x - 200 I_3 - 100 I_1 = 0$$


$$\Rightarrow V_x = -20 \text{ [V]}$$

Also: $V_x + V_{S2} - V_{S1} = 0$


$$\Rightarrow V_x = -20 \text{ [V]}$$

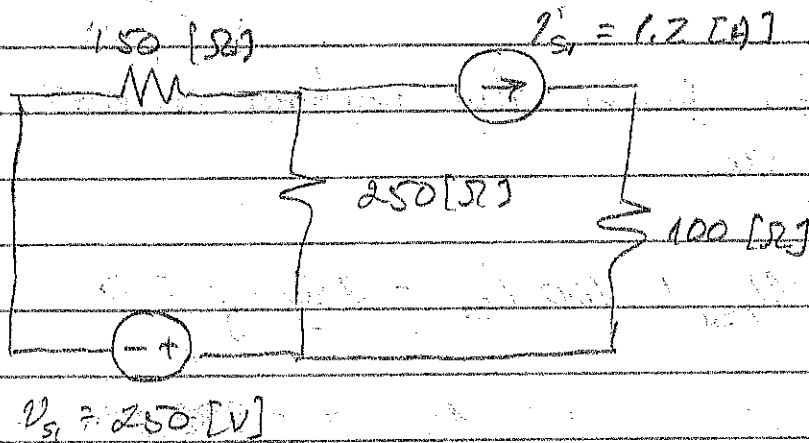Example 2.4

In the circuit below, find the power delivered by the sources i_s and v_s .



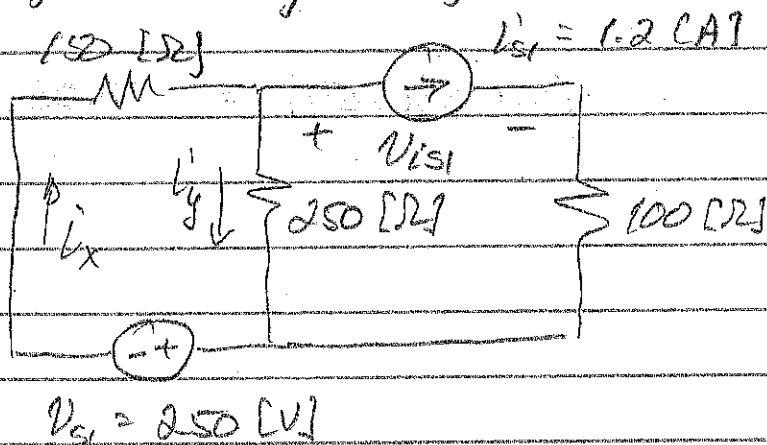We can find the two unknown currents, which we have labeled below, with two simultaneous equations. Once we have all the branch currents (the third one, i_s , is known), we can find anything else we need.



branch currents i_x , i_y , i_s

$$\left. \begin{array}{l} \text{KCL: } i_x = i_y + 1.2 \\ \text{KVL: } 150 i_x + 250 i_y + 250 = 0 \end{array} \right\} \begin{array}{l} i_x = 0.125 \text{ [A]} \\ i_y = -1.025 \text{ [A]} \end{array}$$


Now we can find the voltage across the current source:

$$\begin{aligned} \text{KVL: } V_{i_{s1}} + 100 i_{s1} - 250 i_y &= 0 \\ \Rightarrow V_{i_{s1}} &= -388.75 \text{ [V]} \end{aligned}$$

$$\begin{aligned} \therefore P_{\text{del by } i_{s1}} &= -i_{s1} \cdot V_{i_{s1}} \\ &= -(1.2)(-388.75) = 466.5 \text{ [W]} \end{aligned}$$

$$\begin{aligned} P_{\text{del by } V_{s1}} &= -i_x \cdot V_{s1} \\ &= -(0.125)(250) = -31.25 \text{ [W]} \end{aligned}$$

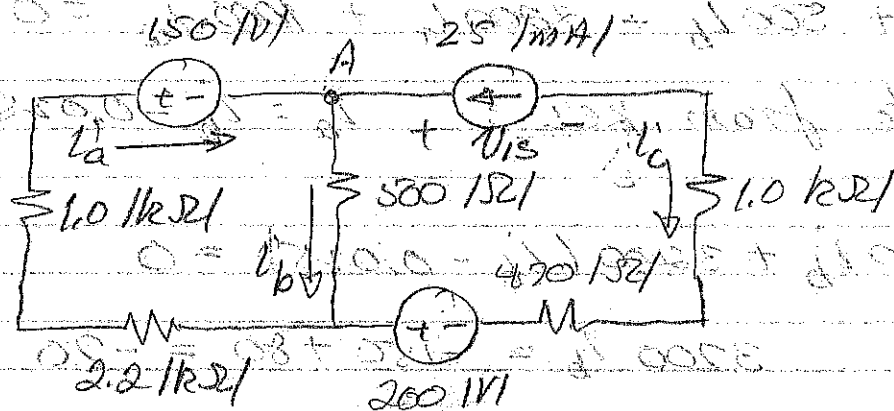Example 2.5: KVL, KCL with current source



FIND the power delivered by the current source.

We have 3 branches and therefore 3 unknown currents: i_a , i_b , i_c . However, our work is simplified because one of the currents is obvious from the diagram.

$$i_c = -2.5 \text{ mA}$$

So we need two more equations.

KCL at A: $i_a - i_b - i_c = 0$

$$-i_a + i_b + i_c = 0$$

KVL?

Important note: I do not know the voltage across the current source v_{is} . Therefore I will not use a KVC in the right-hand branch, because it will introduce another unknown (v_{is}).

So I will do my KVL around the left-hand loop: going clockwise from the top-left corner I have ...

(Ex 2.5 p.2)

$$150 + 500i_b + 2200i_a + 1000i_c = 0$$

Substitute from KCL: $i_a = i_b + 0.025$

$$150 + 500i_b + 3200i_b - 0.025 = 0$$

$$\Rightarrow 3700i_b = -150 + 80 = -70$$

$$i_b = -18.92 \text{ mA}$$

$$i_a = i_b + i_c = -43.92 \text{ mA}$$

Now the circuit is "solved" and I can do the right-hand KVL to find V_s .

$$V_s + 1470i_c = 200 - 500i_b$$

$$V_s = 200 + 500(-0.01892) - 1470(-0.025)$$

$$\therefore V_s = 222.3 \text{ V}$$

The absorbed power is $P_{abs} = V_s i_c$

$$P_{abs} = (222.3)(-0.025) = -5.682 \text{ W}$$

So the power delivered is


$$P_{del} (25 \text{ mA}) = +5.682 \text{ W}$$

Example 2.6 KVL, KCL, Ohm's Law, Dependent Source

For the circuit below ...

a) ... write a KCL and one KVL to solve for i_1 , i_2 , i_3

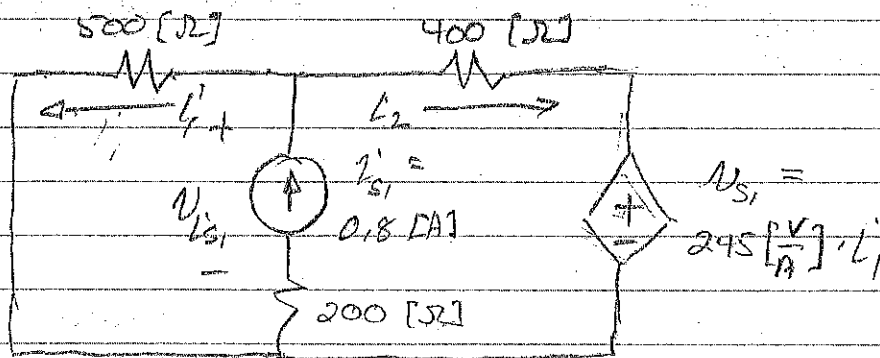b) ... find the power delivered by the current source.



a) KCL: $i_{S1}' = i_1' + i_2'$


KVL: $400 i_2' + 245 i_1' - 500 i_1' = 0$

Note that a KVL through the current source means we have to include v_{S1} , which we don't know. So I avoid the current source by going around the outside loop.

Now I have two equations in two unknowns. Solving gives:

$$i_1' = 0.4885 \text{ [A]}$$

$$i_2' = 0.3115 \text{ [A]}$$

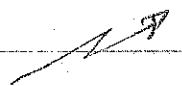


Now that I have V_1 and i_2 , I can do a single KVL to find V_{i_1} :

$$400i_2 + 245i_1 + 200i_{s1} - V_{i_1} = 0$$

$$V_{i_1} = 404.28 \text{ [V]}$$

$$\therefore \boxed{P_{del \text{ by } i_{s1}} = i_{s1}' \cdot V_{i_1} = 323.4 \text{ [W]}}$$

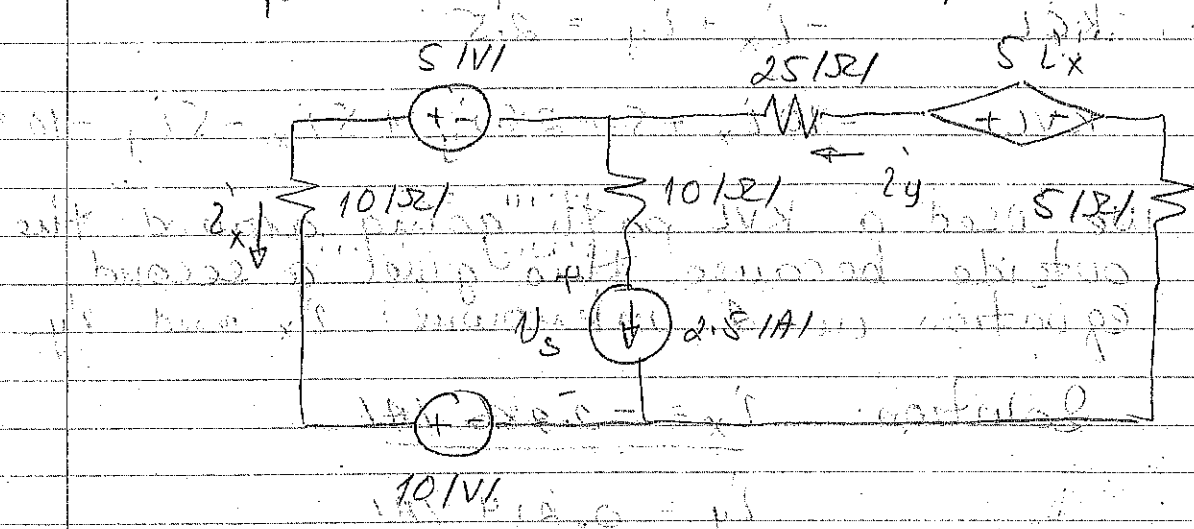Example 2.2.3 (KVL, KCL w/ Dependent Voltage Source)



Note that although there are three branches, we have only two unknown currents since the current in the center branch is known - to be 2.5 A.

We need only label current in the right-hand branch (i_y) since current in the left-hand branch is already labelled (i_x).

Be careful not to confuse the current-controlled dependent voltage source ($5i_x$) - it is a voltage source, not a current source.

Find a) all branch currents

b) power delivered by 2.5 A source.

→

(Ex 2.7 p. 2)

KCL $-i'_x + i'_y = 2.5$

KVL $= 10i'_x + 5 - 25(i'_y) + 5i'_x - 5i'_y - 10 = 0$

We used a KVL path going around the outside because this gives a second equation in i'_x and i'_y .

Solution: $i'_x = -2.286 \text{ A}$

$i'_y = 0.214 \text{ A}$

Note that although there are three meshes, we need a KVL for only two meshes since the current in the third mesh is known.


the current in the mesh is $i'_x = -2.286 \text{ A}$ (so the current in the branch is 2.286 A downward).
 the current in the mesh is $i'_y = 0.214 \text{ A}$ (so the current in the branch is 0.214 A downward).
 $P = 2.5 V_s = -107.15 \text{ W}$ (delivered)

- the power delivered is 107.15 W .
 if it is a voltage source, the current is 2.5 A .

find all power delivered

(b) power delivered by 2.5 A source

Example: 2.8

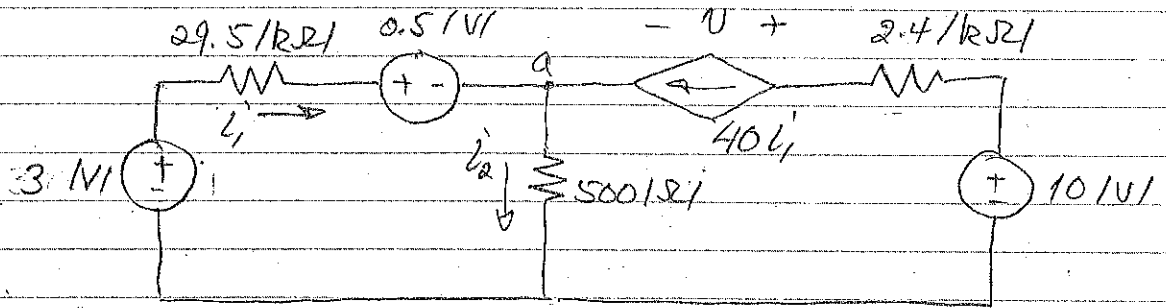

Find a) i_1 in microamps and b) V in volts

$$\text{KCL at a): } i_2 - i_1 - 40i_1 = 0$$

$$i_2 = 41i_1 \quad (1)$$

$$\text{KVL: } -3 + 29500 i_1 + 0.5 + 500 i_2 = 0 \quad (2)$$

$$(1) \Rightarrow (2) \Rightarrow$$

$$-3 + 29500 i_1 + 0.5 + 500(41i_1) = 0$$

$$50,000 i_1 = 2.5$$


$$\underline{i_1 = 5 \times 10^{-5} \text{ A} = \underline{\underline{50 \mu\text{A}}}}$$

KVL:

$$-3 + 29500 i_1 + 0.5 - V - 2400 \cdot (40i_1) + 10 = 0$$

$$V = 7.5 - 66500 i_1 = 4.95 \text{ V}$$

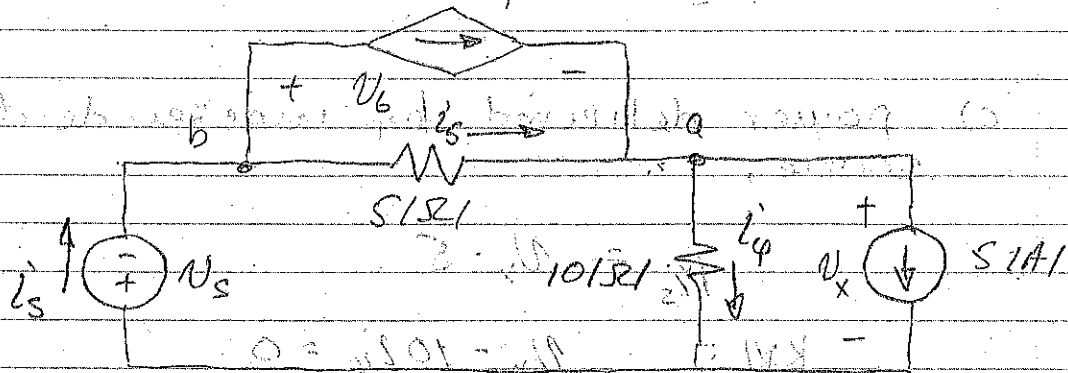Example 2.9: KVL, KCL with a dependent current source



GIVEN: $I_\phi = 5 \text{ A}$

CALCULATE: $U_s = ? \text{ V}$

a) U_s is unknown with sign not known with KVL around left loop

KVL: $U_s + 5I_s + 10I_\phi = 0$

We need $I_s = ?$

KCL at a): $-I_s - 6I_\phi + I_\phi + 5 = 0$

$I_s = 5 - 5I_\phi = -20 \text{ A}$

$\therefore U_s = -5I_s - 10I_\phi = 100 - 50 = \underline{\underline{50 \text{ V}}}$

b) power absorbed by independent voltage source:

$P_{U_s} = U_s \cdot I_s$


KCL at b): $-I_s + 6I_\phi + I_s = 0$

$I_s = 6I_\phi + I_s = 30 - 20 = 10 \text{ A}$

(Ex 2-11 p. 2)

$\therefore P_{N_s} = 50 \cdot 10 = 1 \text{ W} \text{ absorbed}$

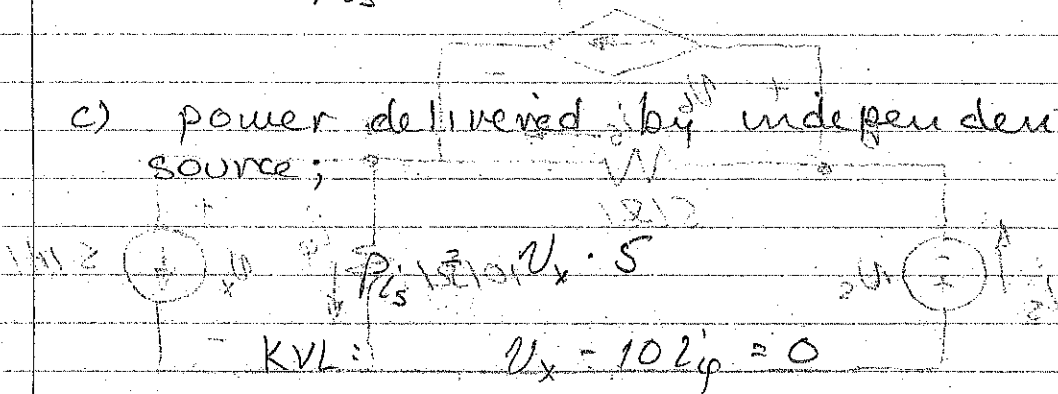c) power delivered by independent current source;



KVL: $V_x - 10 \text{ V} = 0$

$V_x = 10 \text{ V}$

$\therefore P_{i_s} = 50 (5) = 250 \text{ W (delivered)}$

This result is positive, so power is being absorbed. Therefore the power = delivered.

$P_{i_s} \text{ (delivered)} = 250 \text{ W/W}$

d) power delivered by the controlled current source;

$P_{6\Omega} = 100 \cdot 6 = 600 \text{ W}$

KVL: $V_6 - 5I_s = 0$

$V_6 = 5I_s = 100 \text{ V}$

$\therefore P_{6\Omega} = 100(6)(5) = 3000 \text{ W absorbed}$

$\Rightarrow P_{6\Omega} \text{ (delivered)} = +3000 \text{ W/W}$

e) total power dissipated in two resistors

$P = 25^2 \cdot 5 + 10^2 \cdot 10 = 400(5) + 25(10) = 2250 \text{ W}$