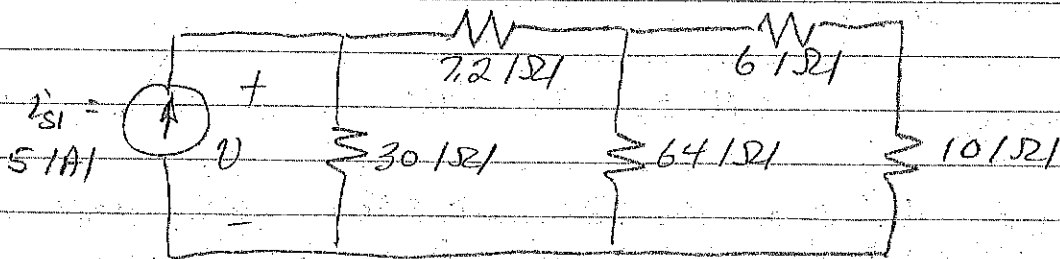


Example 3.1

10 WCTK5117 - 1


For the circuit shown we want to find
 a) V , b) power delivered by i_{s1} , c) power
 dissipated by the 10Ω resistor.



$$R_{eq1} = 6 + 10 = 16 \Omega$$

$$R_{eq2} = 16 \parallel 64 = \frac{16 \cdot 64}{16 + 64} = 12.8 \Omega$$


We re-draw the circuit now, for clarity.

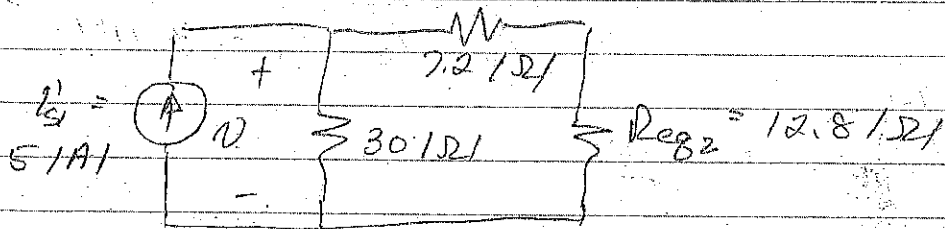

$$R_{eq3} = 7.2 + 12.8 = 20 \Omega$$

$$R_{eq4} = 30 \parallel 20 = \frac{30 \cdot 20}{30 + 20} = 12 \Omega$$

A final re-draw gives

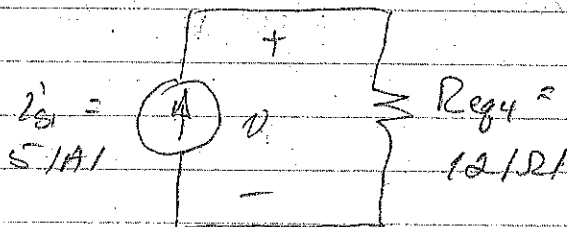


Note that because our series and parallel combinations are equivalent to the original network of resistors, the voltage v does not change.

a) $v = i_{s1} R_{eq} = 60 \text{ V}$


b) $P_{del, i_{s1}} = i_{s1} \cdot v = 300 \text{ W}$

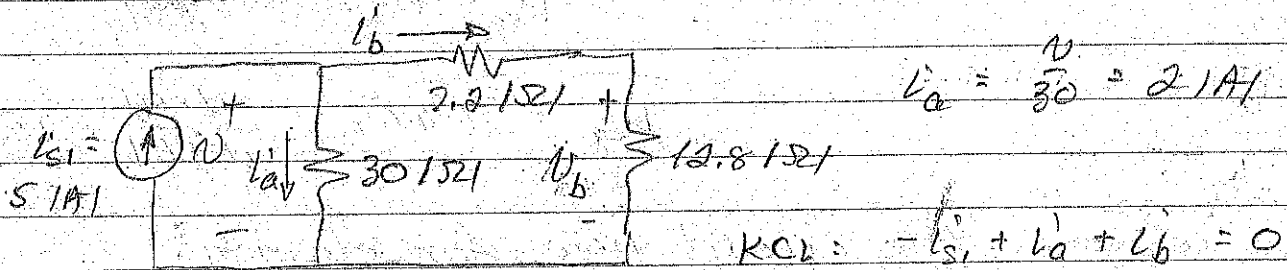c) To get to the 10Ω resistor, we need to "unfold" the circuit. But let's use what we know:




$\Rightarrow i_b = i_{s1} - i_a = 3 \text{ A}$

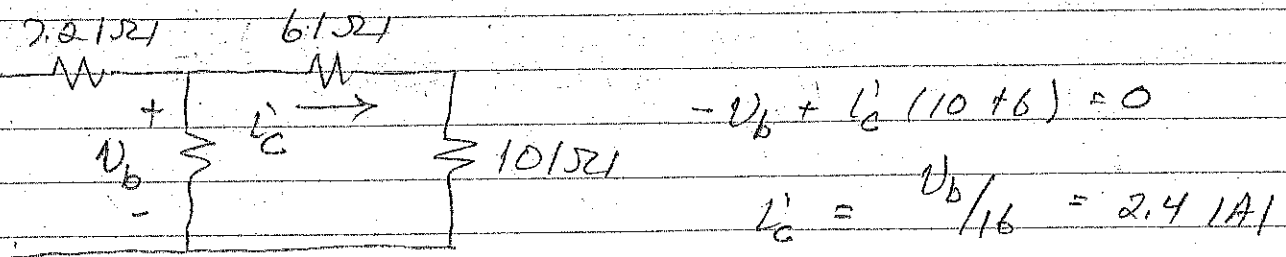$\therefore v_b = (12.8)(3) = 38.4 \text{ V}$



d) Finally $P_{abs, 10} = i_c^2 \cdot 10 = 57.6 \text{ W}$

Example 3.2

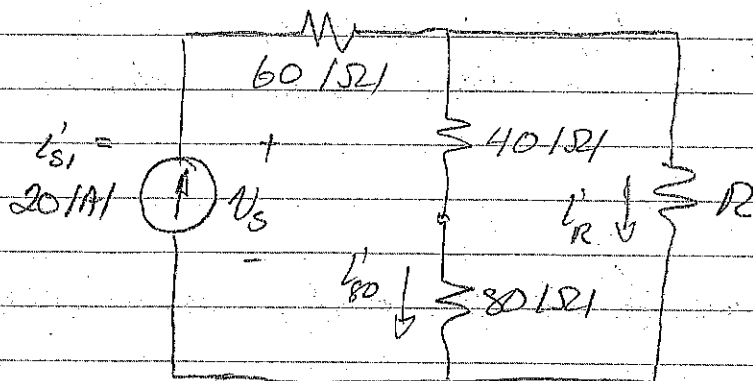

a) Find R so that $i_{80}' = 4 \text{ A}$.

CDR \Rightarrow

$$i_{80}' = 20 \cdot \frac{R}{(40+80)+R} = 4$$

We need to solve for R :

$$\frac{R}{120+R} = 0.2 \Rightarrow R = 24 + 0.2R$$

$$0.8R = 24 \Rightarrow \underline{\underline{R = 30 \text{ } \Omega}}$$

b) Find the power absorbed by R .

i) CDR:

$$i_R' = 20 \cdot \frac{(40+80)}{(40+80)+30} = 16 \text{ A}$$

(Alternatively, $i_R' = 20 - i_{80}' = 16 \text{ A}$)

Then

$$P_{\text{abs},R} = i_R'^2 \cdot (30) = 7680 \text{ W}$$

(This is a large value compared with power dissipation in your typical lab kit resistors. These are rated for a max power dissipation of $\frac{1}{4}$ W !)

c) Find V_{s1} and I_{s1} by using parallel
To do this, we first simplify using resistor
series combinations.


$$R_{eq} = 60 + [(40 + 80) \parallel 30]$$

$$= 60 + 24 = 84 \Omega$$

$$\text{So } V_s = 20 \cdot 84 = 1680 \text{ V}$$

$$P_{del, I_{s1}} = I_{s1} \cdot V_s = 33,600 \text{ W}$$

Example 3.3

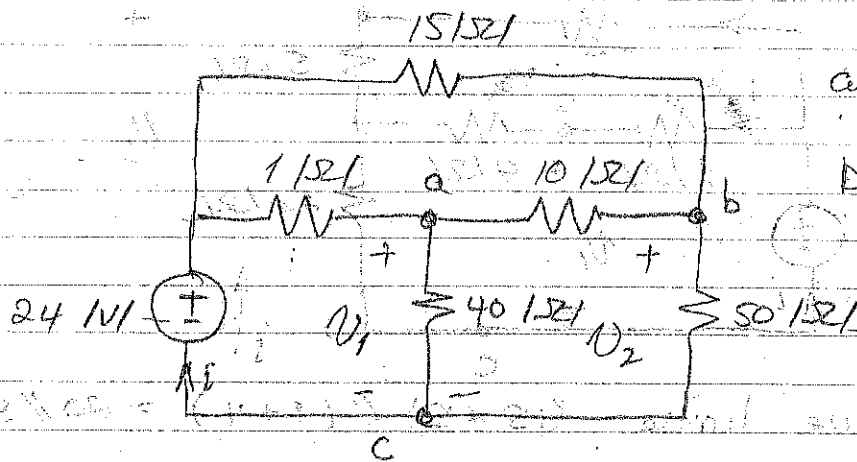


a) Find i .

b) Find V_1, V_2

a) We have $R_a = 50 \Omega$, $R_b = 40 \Omega$, $R_c = 10 \Omega$

Transformation:

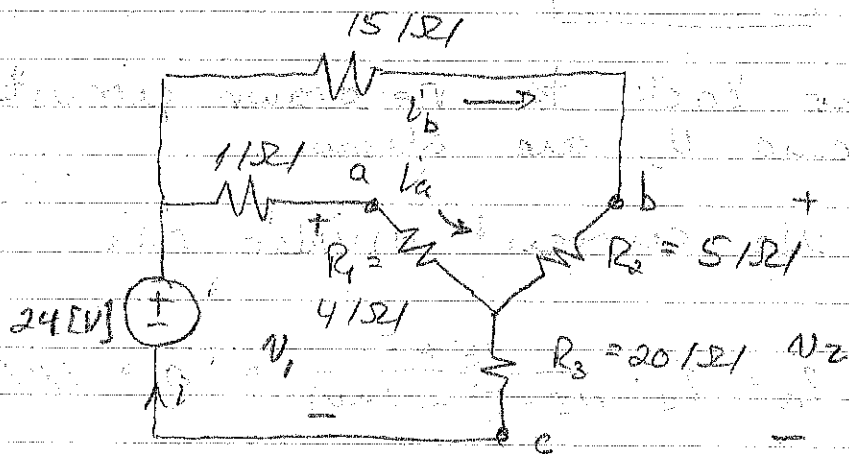


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{40(10)}{100} = 4 \Omega$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c} = \frac{10(50)}{100} = 5 \Omega$$


$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{40(50)}{100} = 20 \Omega$$

Example 3.3

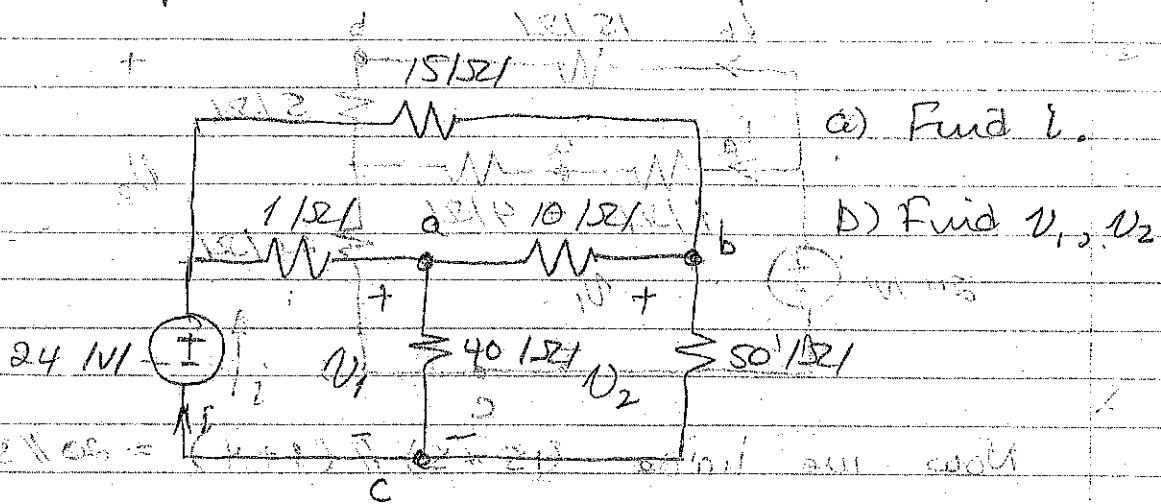

a) We have: $R_a = 50 \Omega$, $R_b = 40 \Omega$, $R_c = 10 \Omega$

Transformation:

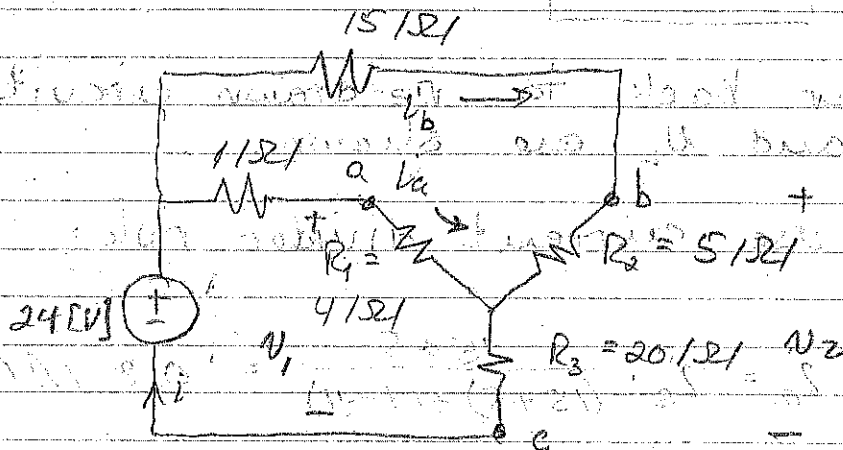


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{40(10)}{100} = 4 \Omega$$


$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c} = \frac{10(50)}{100} = 5 \Omega$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{40(50)}{100} = 20 \Omega$$

Re-draw

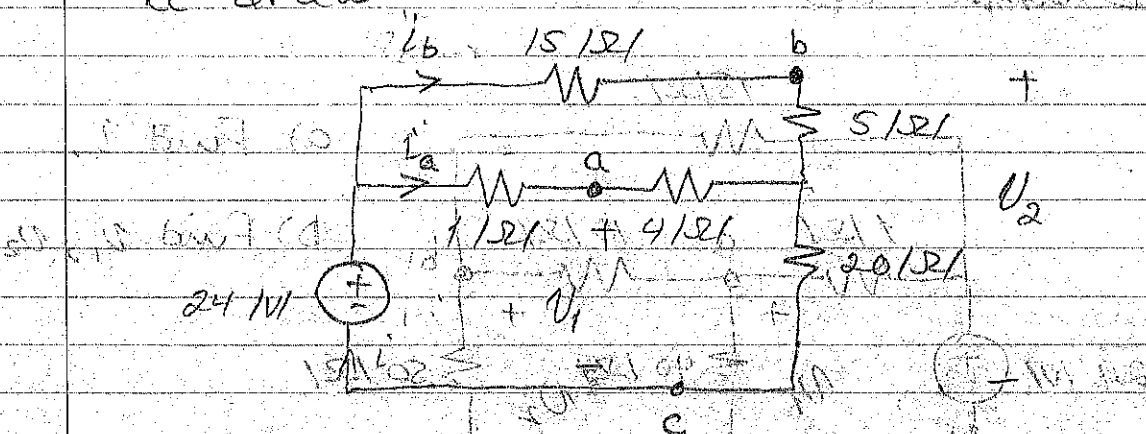

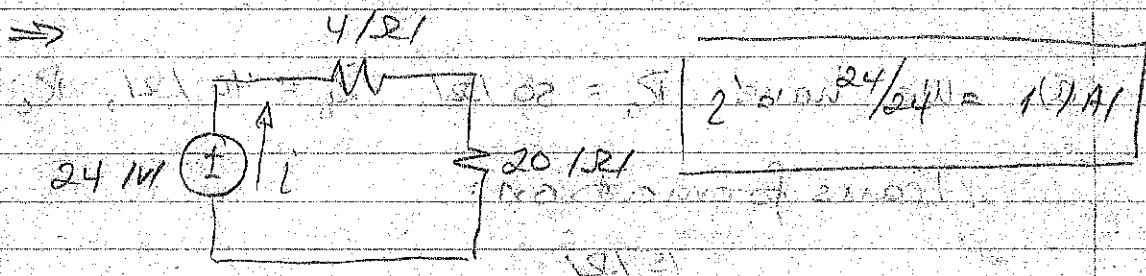Now we have $(15+5) \parallel (1+4) = 20 \parallel 5 = 4 \Omega$



b) Refer back to re-drawn circuit where U_1 and U_2 are shown

Then use current divider rule:

$$I_a = 2s \cdot \frac{5}{(15+5) + (1+4)} = 0.8 \text{ A}$$

$$I_b = 2s \cdot \frac{1+4}{(15+5) + (1+4)} = 0.2 \text{ A}$$

KVL: $-24 + 1 \cdot I_a + U_1 = 0 \Rightarrow U_1 = 23.2 \text{ V}$


KVL: $-24 + 15 I_b + U_2 = 0 \Rightarrow U_2 = 21 \text{ V}$

Example 3.4 Device Modeling

This problem is taken from Nilsson & Riedel, 8 ed. p. 42.


The device shown below can be modeled by a voltage source in series with a resistor. The table shows the measured terminal voltage and current for several cases.

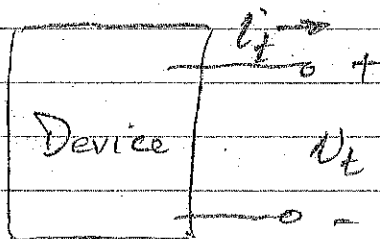Find the model parameters, that is, the values of the voltage source and resistance.



v_T [V]	i_T [A]
25	0
15	0.1
5	0.2
0	0.25

We begin by drawing the proposed model:

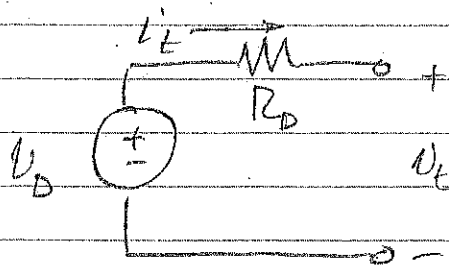

We need to find v_D and R_D .

For the data in this particular case, the problem is easy, because they give us values for the case where v_T and i_T are 0.

○ (Ex 3.4 p.2)

- For $i_t = 0$, v_t is the same as v_D .
- For $v_t = 0$, $i_t = v_D / R_D$.

From these two cases, it is clear that

$$\boxed{v_D = 25 \text{ [V]}} \quad \text{and} \quad R_D = \frac{v_D}{i_t} = \frac{25}{0.25} = 100$$

$$\boxed{R_D = 100 \text{ [}\Omega\text{]}}$$

○ We could also do this problem even if we had only been given the 2nd and 3rd table entries. But for that we need a general formula:

Looking at our model, we have

$$v_t - v_D + i_t R_D = 0$$

Now we have v_t and i_t in terms of v_D and R_D .

$$v_t = 15 \text{ [V]} \Rightarrow i_t = 0.1 \text{ [A]} \Rightarrow 15 - v_D + 0.1 R_D = 0 \quad \textcircled{1}$$

$$v_t = 5 \text{ [V]} \Rightarrow i_t = 0.2 \text{ [A]} \Rightarrow 5 - v_D + 0.2 R_D = 0 \quad \textcircled{2}$$


○ Solving gives $\boxed{v_D = 25 \text{ [V]}}$ and $\boxed{R_D = 100 \text{ [}\Omega\text{]}}$

Example 3.5 Device Modeling


The device shown below can be modeled by a current source in parallel with a resistor.

When a $100 [\Omega]$ resistor is connected to the device terminals, the voltage across it is $30 [V]$. When a $400 [\Omega]$ resistor is connected, the voltage across it is $-60 [V]$.

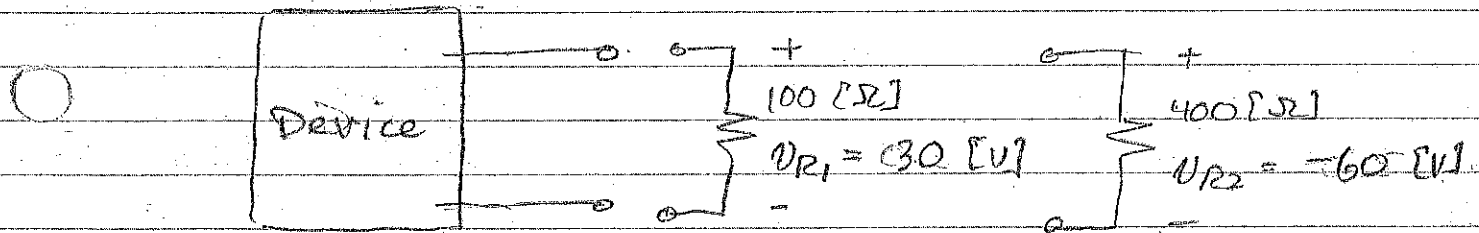Find the model parameters, that is, the values of the current source and resistance.



We start by drawing the proposed model:

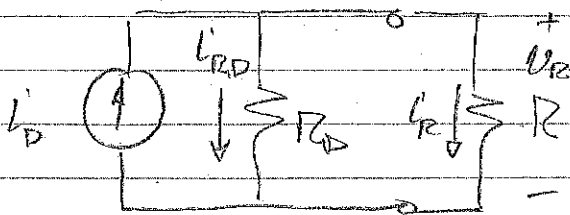

We need to find R_D and I_D .

As for Example 2.4, we need a formula to describe this circuit. We have by KCL

$$I_D = I_{RD} + I_R$$

○ (Ex 3.8 p.2)

But the information we are given is in terms of $V_R = I'_D R$. So we re-write this as

$$I'_D = \frac{V_R}{R_D} + \frac{V_R}{R}$$

Now we have I'_D and R_D , which we are looking for, in terms of V_R and R , which we have.

$$R = 100 [\Omega] \Rightarrow V_R = 303 [V]$$

$$\Rightarrow I'_D = \frac{303}{R_D} + \frac{303}{100} \quad (1)$$

$$R = 400 [\Omega] \Rightarrow V_R = -605 [V]$$

$$\Rightarrow I'_D = \frac{-605}{R_D} + \frac{-605}{400} \quad (2)$$

Solving gives $I'_D = 150 [mA]$ and $R_D = -200 [\Omega]$

WAIT! WHAT?? How can we have a negative R_D ??

Remember that I'_D in parallel with R_D is a model only. We are not saying that inside the box there is a current source and a resistor. We are saying that whatever is inside, which may be quite complicated, can be modeled with

○ I'_D and R_D . So R_D in that case can be negative.

But just to be clear: actual resistors have a positive resistance.