

Name: _____ (please print)

Signature: _____

ECE 2202 –Exam 1
October 10, 2020

Online

1. This quiz is open book, open notes.
2. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution which is not given in a reasonable order will lose credit.
3. Show all units in solutions, intermediate results, and figures. Units in the quiz will be included between square brackets.
4. If the grader has difficulty following your work because it is messy or disorganized, you will lose credit.
5. Do not use red ink. Do not use red pencil.
6. You will have 90 minutes to work on this exam, and 15 minutes to download/print, scan and submit.

_____ /30


_____ /40

_____ /30

_____ /100


Room for extra work

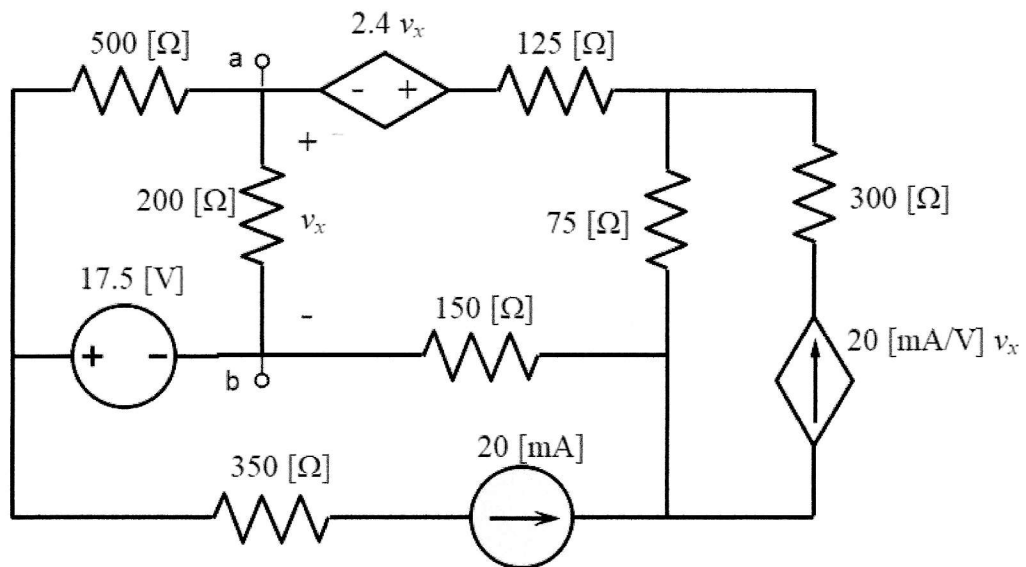1. [30 points] Find the Norton equivalent as seen by the $200\ \Omega$ resistor in the circuit below.



Room for extra work

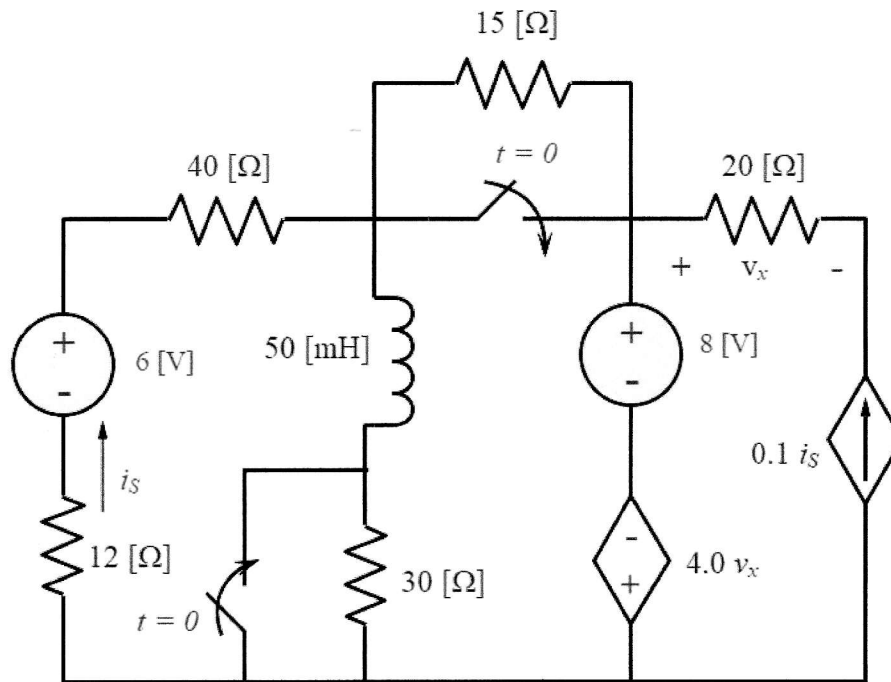
2. [40 points] In the circuit below, both switches were open for a long time, and then closed at $t = 0$. Find the energy stored in the inductor at $t = 10$ [ms].



Room for extra work

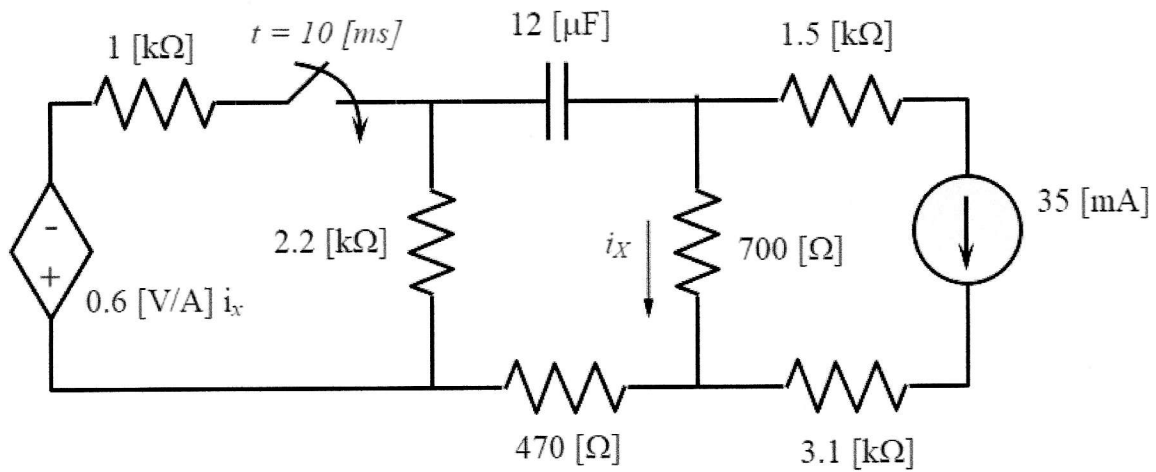
3. [30 points] The switch in the circuit below was open for a long time and then closed at $t = 10$ [ms].

- Find $i_X(10 \text{ [ms]}^+)$.
- Find the Thevenin equivalent resistance seen by the capacitor for $t > 10$ [ms].




Room for extra work

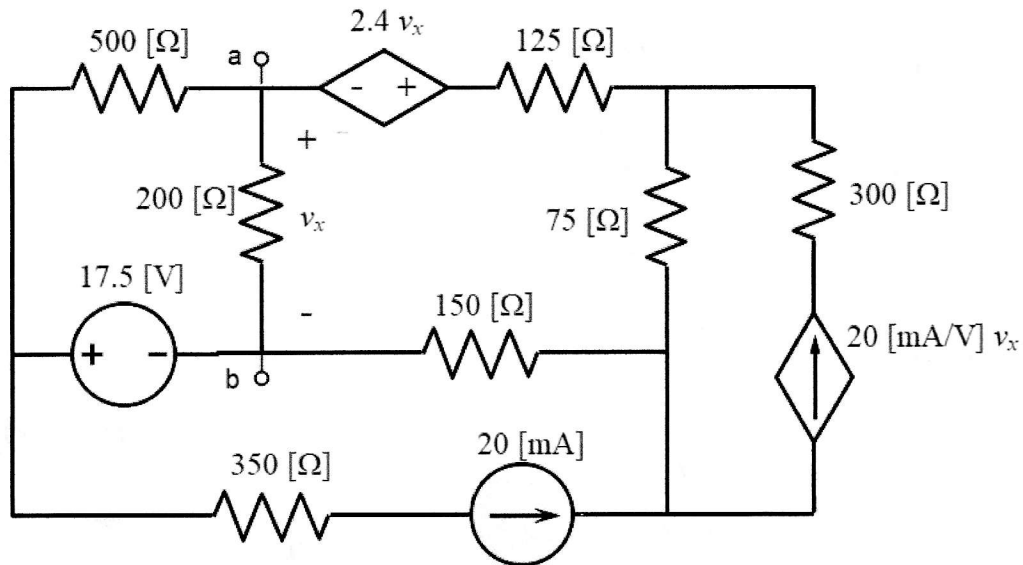1. [30 points] Find the Norton equivalent as seen by the 200 [Ω] resistor in the circuit below.



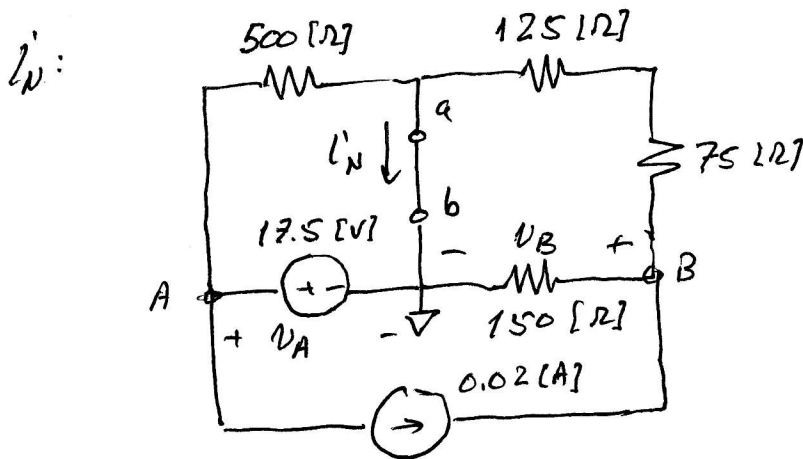After removing the 200 [Ω] resistor, we need 2 of V_{oc} , i_N , or test source to find Norton resistance. Finding $i_N = i_{sc}$ will make $v_x = 0$ and simplify considerably. Using a test source will also simplify the circuit. But we will do all three here.



$$\frac{v_B}{150} - 0.02 + \frac{v_B}{200} = 0$$

$$\Rightarrow v_B = 1.714 \text{ [V]}$$

$$i_N = \frac{17.5}{500} + \frac{v_B}{200} = 43.57 \text{ [mA]}$$




$i_N = 14$

$R_{Th} = 14, V_{oc} = 14$

Model = 2

Room for extra work

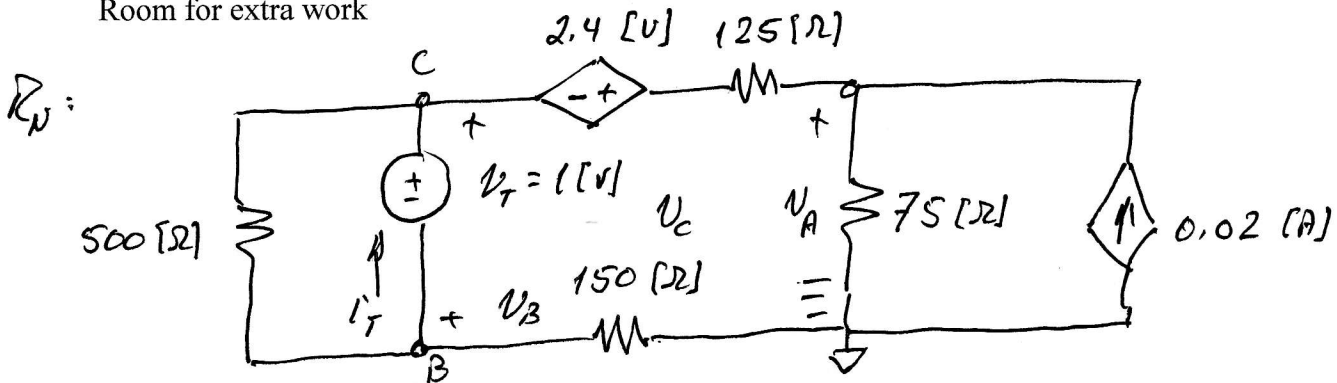

$$V_x = 1 \text{ [V]} \Rightarrow 2.4 V_x = 2.4 \text{ [V]}, \quad 20 \left[\frac{\text{mA}}{\text{V}} \right] V_x = 0.02 \text{ [A]}$$

$$\frac{V_A}{75} - 0.02 + \frac{V_A - V_C - 2.4}{125} = 0$$


$$\frac{V_C - V_A + 2.4}{125} + \frac{V_B}{150} = 0 \quad V_C - V_B = 1 \text{ [V]}$$

$$V_A = 1.907 \text{ [V]} \quad V_B = -0.8143 \text{ [V]} \quad V_C = 0.1857 \text{ [V]}$$

$$I_T' = \frac{1}{500} + \frac{V_C - V_A + 2.4}{125} = 7.4296 \text{ [mA]}$$


$$\Rightarrow R_N = \frac{1}{I_T'} = 134.6 \text{ [}\Omega\text{]}$$

Thus the Norton equivalent is:

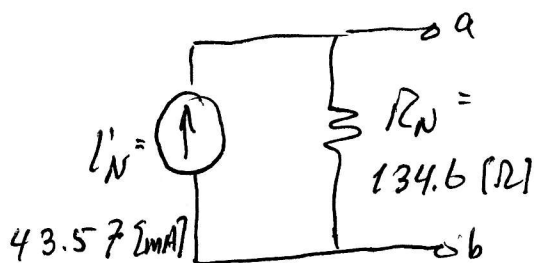Just for a check,
let's do V_{oc} :

p.2

Room for extra work

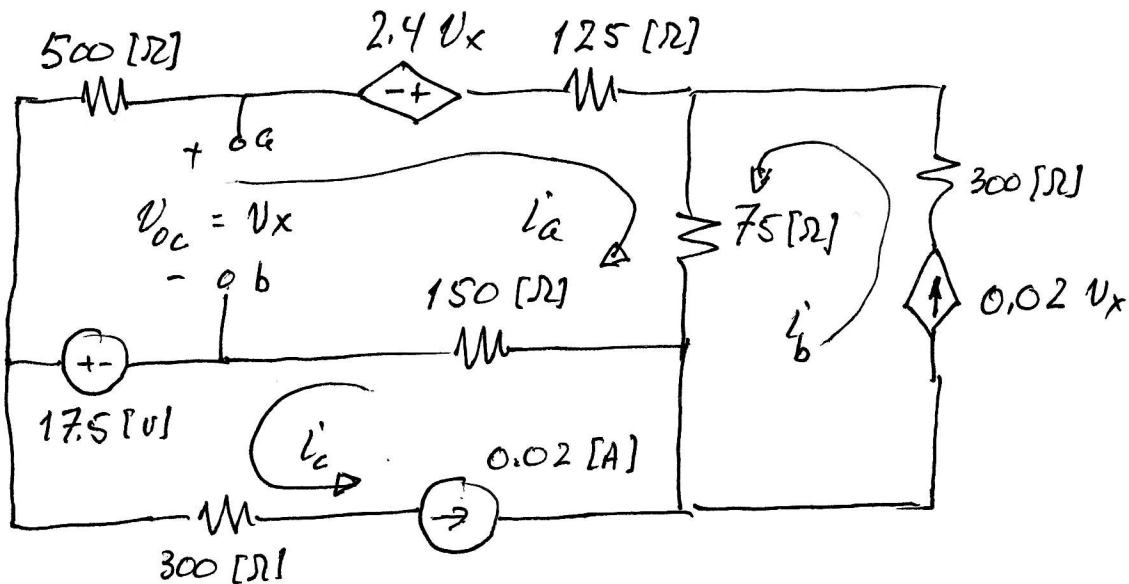

Since we have current sources on two mesh edges, mesh-current seems like the way to go here.

$$625 i'_a - 2.4 V_x + 75(i'_a + i'_b) + 150(i'_a + i'_c) - 17.5 = 0$$


$$i'_c = 0.02 \text{ [A]} \quad i'_b = 0.02 V_x \quad \left| \quad \begin{array}{l} i'_a = 23.27 \text{ [mA]} \\ i'_b = 117.31 \text{ [mA]} \\ i'_c = 20 \text{ [mA]} \end{array} \right.$$

$$V_x - 17.5 + 500 i'_a = 0$$


This gives $V_x = V_{oc} = 5.865 \text{ [V]}$

Then $\frac{V_{oc}}{i'_a} = 134.6 \text{ [}\Omega\text{]}$ so this checks.

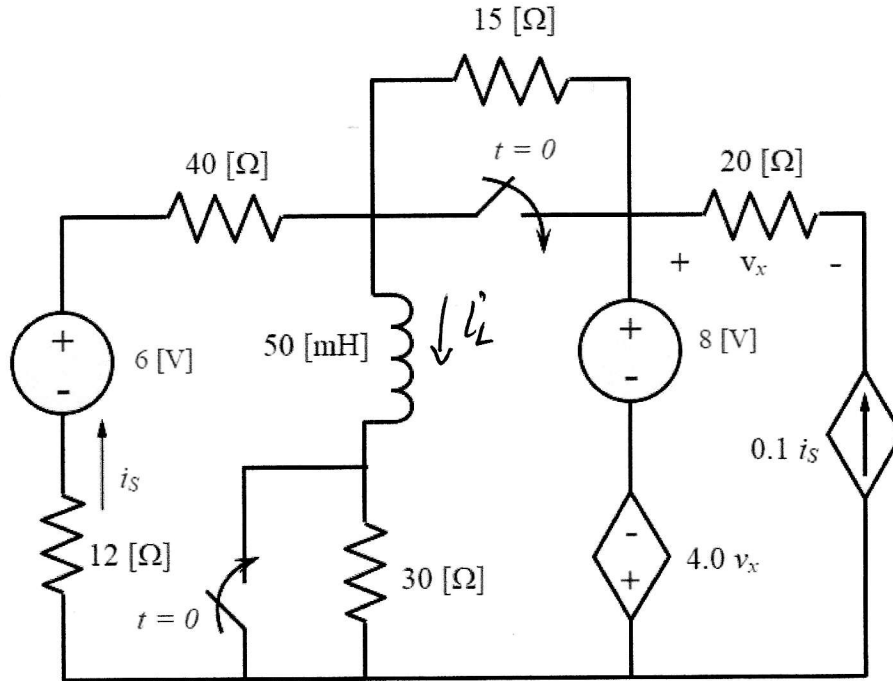2. [40 points] In the circuit below, both switches were open for a long time, and then closed at $t = 0$. Find the energy stored in the inductor at $t = 10$ [ms].



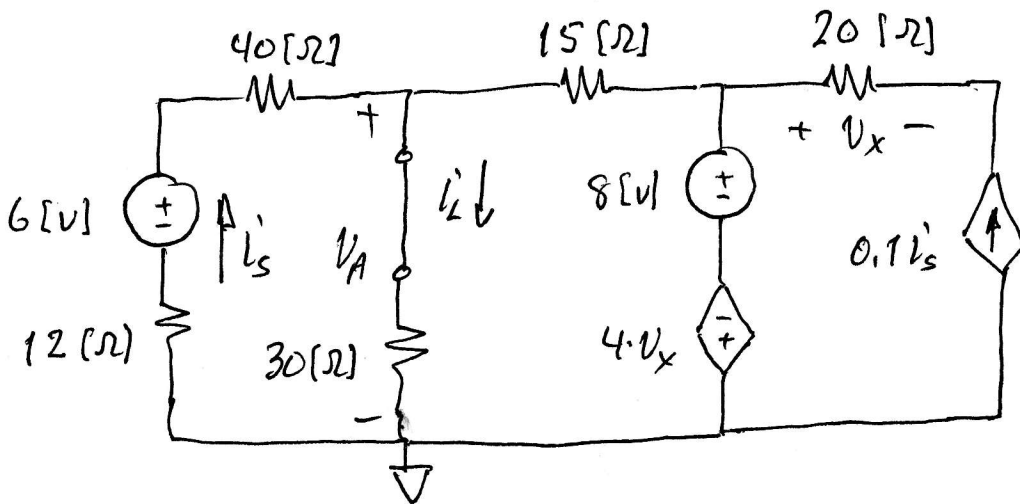Current i_L has been defined. Draw for $t < 0$



+ 4

$$\frac{V_A}{30} + \frac{V_A - 6}{52} + \frac{V_A - 8 + 4V_x}{15} = 0 \quad V_x = -2i_s \quad (+3)$$

+ 7


$$V_A = 5.485 \text{ [V]} \quad V_x = -19.80 \text{ [mV]}$$

$$i_L(0) = \frac{V_A}{30} = 182.8 \text{ [mA]} \quad 5$$

+ 2

Room for extra work

Draw for $t > 0$

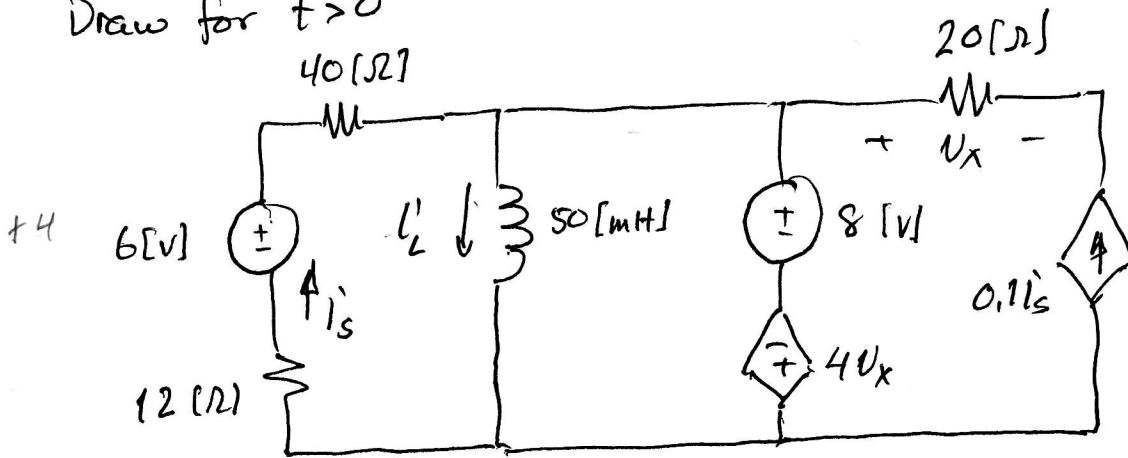

We have a voltage source (two, in fact) in parallel with the inductor, so we have to integrate.

+6 integration

$$i_L' = \frac{1}{0.05} \int_0^{0.01 \text{ [s]}} (8 - 4V_x) dt + i_L(0) \quad i_L(0) = 182.8 \text{ [mA]}$$

+8 integrated

$$V_x = -2i_s' \quad 52i_s' - 6 + 8 - 4(-2i_s') = 0 \Rightarrow i_s' = -33.33 \text{ [mA]}$$

$$\Rightarrow V_x = 66.67 \text{ [mV]} \Rightarrow -4V_x = -266.67 \text{ [mV]}$$

+2 limits

$$i_L' = \frac{1}{0.05} \int_0^{0.01 \text{ [s]}} (7.7333) dt + 182.8 \text{ [mA]}$$

+3


$$i_L'(10 \text{ [ms]}) = 1.730 \text{ [A]}$$

+4

$$W_L(10 \text{ [ms]}) = \frac{1}{2} L i_L^2(10 \text{ [ms]}) = 74.77 \text{ [mJ]}$$

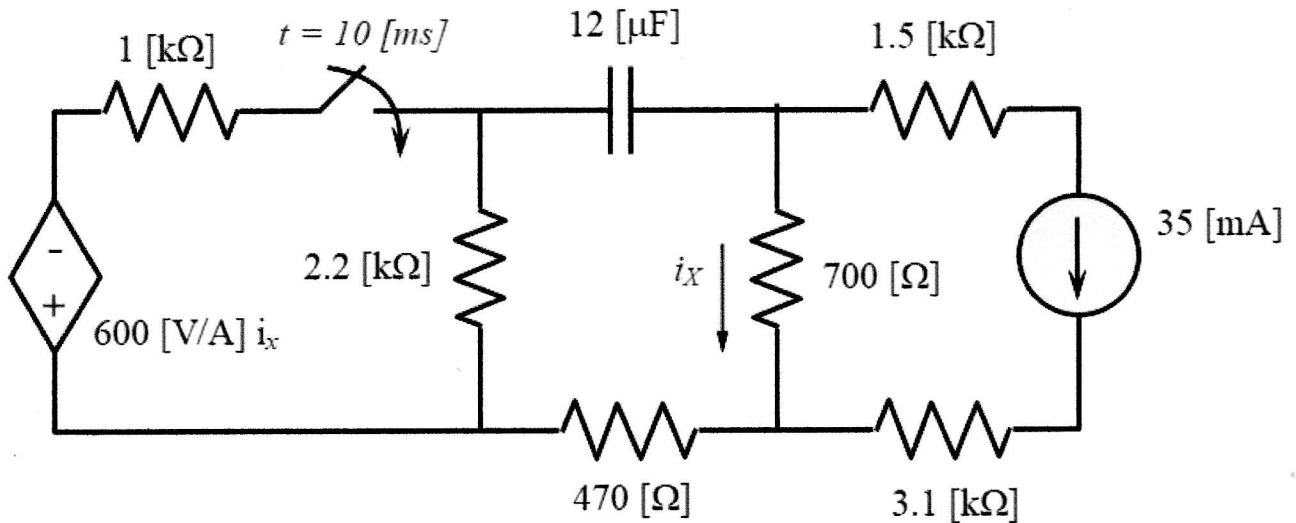
3. [30 points] The switch in the circuit below was open for a long time and then closed at $t = 10$ [ms].

- Find $i_X(10 \text{ [ms]}^+)$.
- Find the Thevenin equivalent resistance seen by the capacitor for $t > 10$ [ms].



a) To find $i'_X(10^+ \text{ [ms]})$, will need $v_C(10^+ \text{ [ms]})$.

Draw for $t < 10$ [ms]:

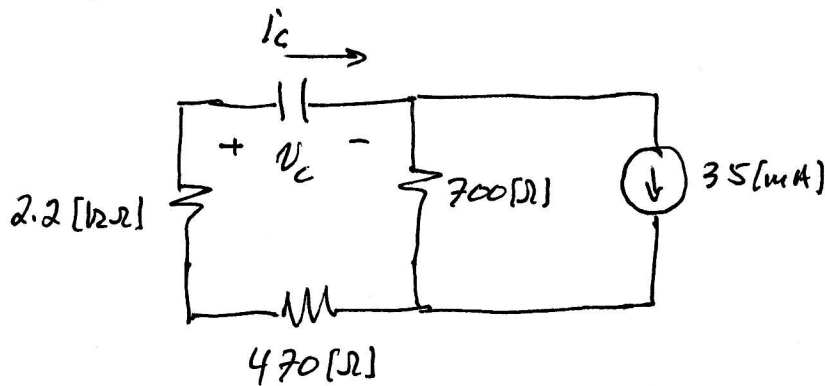


$C \rightarrow$ open-ckt
 $\Rightarrow i'_C \rightarrow 0$

$$\boxed{v_C(10^- \text{ [ms]}) = v_C(10^+ \text{ [ms]}) = 700 \cdot 0.035 = \underline{24.5 \text{ [V]}}}$$

Draw for $t > 10$ [ms]:

\rightarrow


Room for extra work

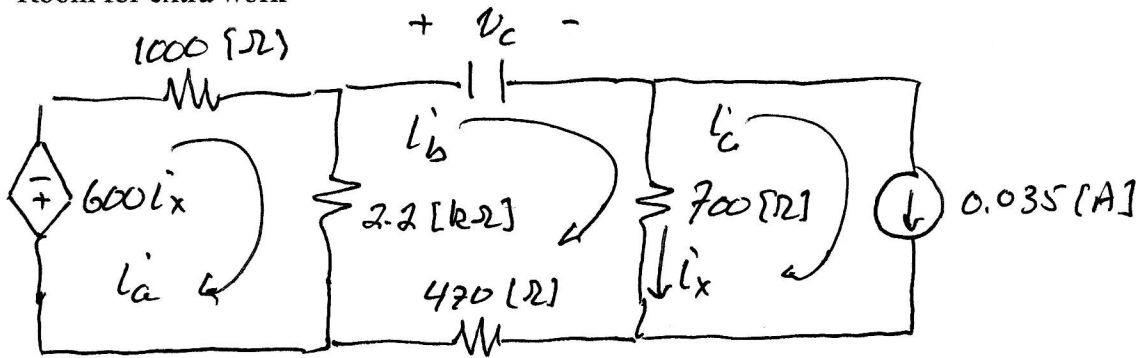Key information: $V_c = 24.5 \text{ [V]}$

$$1000i_a + 2200(i_a - i_b) + 600i_x = 0 \quad i_c = 0.035 \text{ [A]}$$

$$24.5 + 700(i_b - i_c) + 470i_b + 2200(i_b - i_a) = 0 \quad i_x = i_b - i_c$$

$$\text{Solve: } i_x = -28.64 \text{ [mA]} \Rightarrow \boxed{i_x (10^3 \text{ [ms]}) = -28.64 \text{ [mA]}}$$

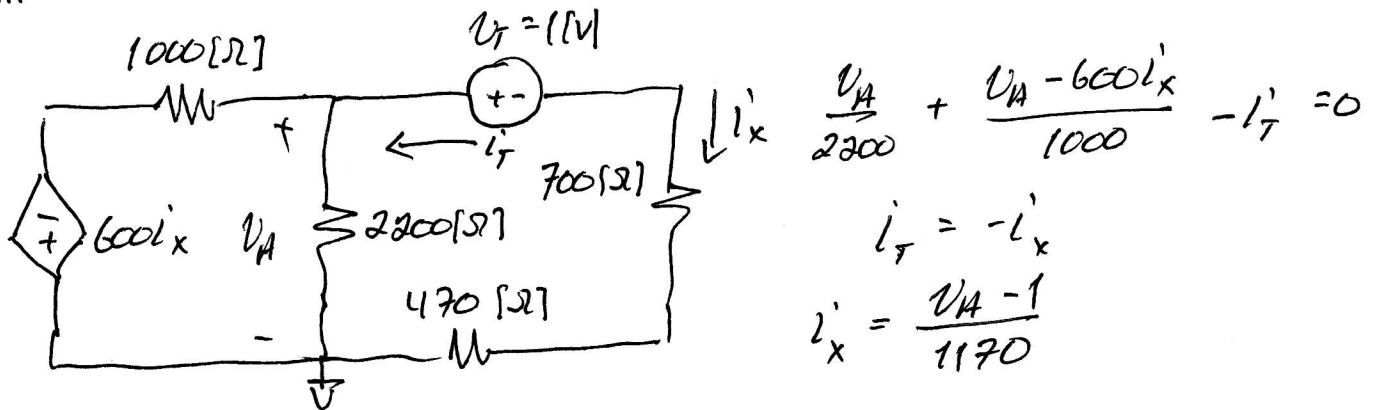b) R_{Th} does not depend on time. Let's use a test source:

$$\frac{V_A}{2200} + \frac{V_A - 600i_x}{1000} - i_T = 0$$

$$i_T = -i_x$$

$$i_x = \frac{V_A - 1}{1170}$$

$$V_A = 0.1903 \text{ [V]} \quad i_x = -0.6920 \text{ [mA]}$$

$$\therefore i_T = 0.6920 \text{ [mA]} \Rightarrow \boxed{R_{Th} = \frac{1}{i_T} = 1445 \text{ [}\Omega\text{]}}$$