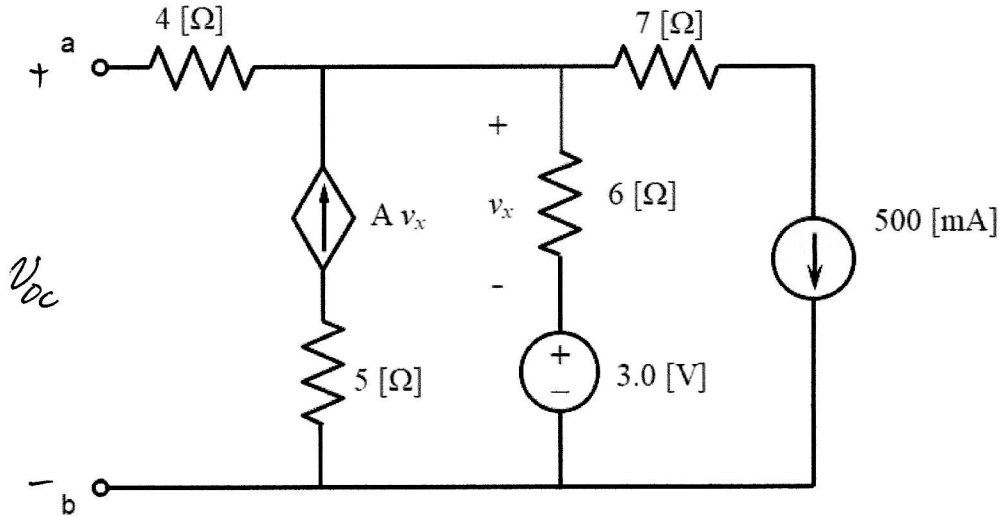


1. [35 points] For the circuit below, do the following.

- a) Find the Thevenin equivalent of the circuit at terminals a, b, if the parameter $A = 0.5$.
- b) Find an expression for the Thevenin equivalent resistance as a function of the parameter A. That is, find R_{TH} in terms of A.
- c) Find the value of A that results in a Thevenin equivalent resistance of $-1 [\Omega]$.




Find V_{oc} : $\frac{v_x}{6} - 0.5 v_x + 0.5 = 0 \Rightarrow v_x = 1.5 [V]$

a)

$V_{oc} = v_x + 3 = 4.5 [V]$

Apply a test source: $A = 0.5$

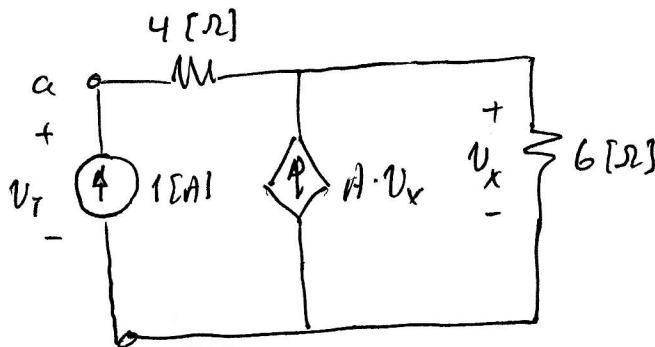


$-1 - 0.5 v_x + \frac{v_x}{6} = 0$

$\Rightarrow v_x = -3 [V]$

$V_T = 1 \times 4 + v_x = 1 [V]$

$R_{TH} = 1 [\Omega]$

So we have

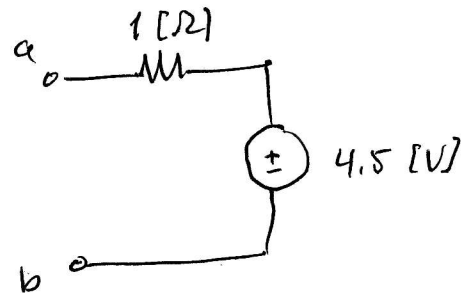

Room for extra work

b) For arbitrary A , we have... (previous circuit)

$$-1 - A \cdot V_x + \frac{V_x}{6} = 0 \quad \text{and} \quad R_{TH} = 4 + V_x$$

$$\text{So } V_x = R_{TH} - 4 \Rightarrow -1 + \frac{R_{TH} - 4}{6} - A \cdot (R_{TH} - 4) = 0$$

$$\text{Solving for } R_{TH} \text{ gives } \boxed{R_{TH} = \frac{1}{\frac{1}{6} - A} + 4}$$

c) Solving for A we have


$$A = -\frac{1}{R_{TH} - 4} + \frac{1}{6}$$

If we want $R_{TH} = -1 [\Omega]$, we need $A = 0.3666?$


2. [60 points] In the circuit below, the switch SW1 was in position 'a' for a long time. At $t = 0$ it moved to position 'b', as indicated by the dashed line. At $t = 2$ [s] it moved back to position 'a'. Switch SW2 was open for a long time, and closed at $t = 3$ [s]. The current source i_{SI} has the value $i_{SI} = 39 \text{ [mA/s}^2] t^2$.

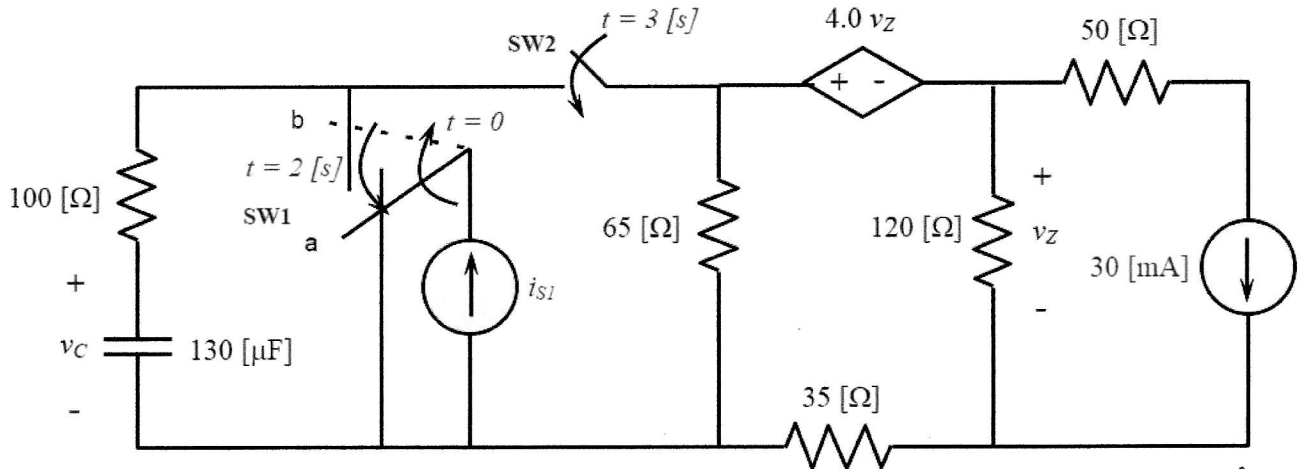0.39

- Find the capacitor voltage $v_C(t)$ for $t \geq 0$ [s].
- Make a rough plot of $v_C(t)$ for $t \geq 0$ [s]. You can use the graph given below or you can create your own graph. High accuracy and many calculated points are not required. You will get full credit if your graph is clearly labeled, and shows a few specific values.




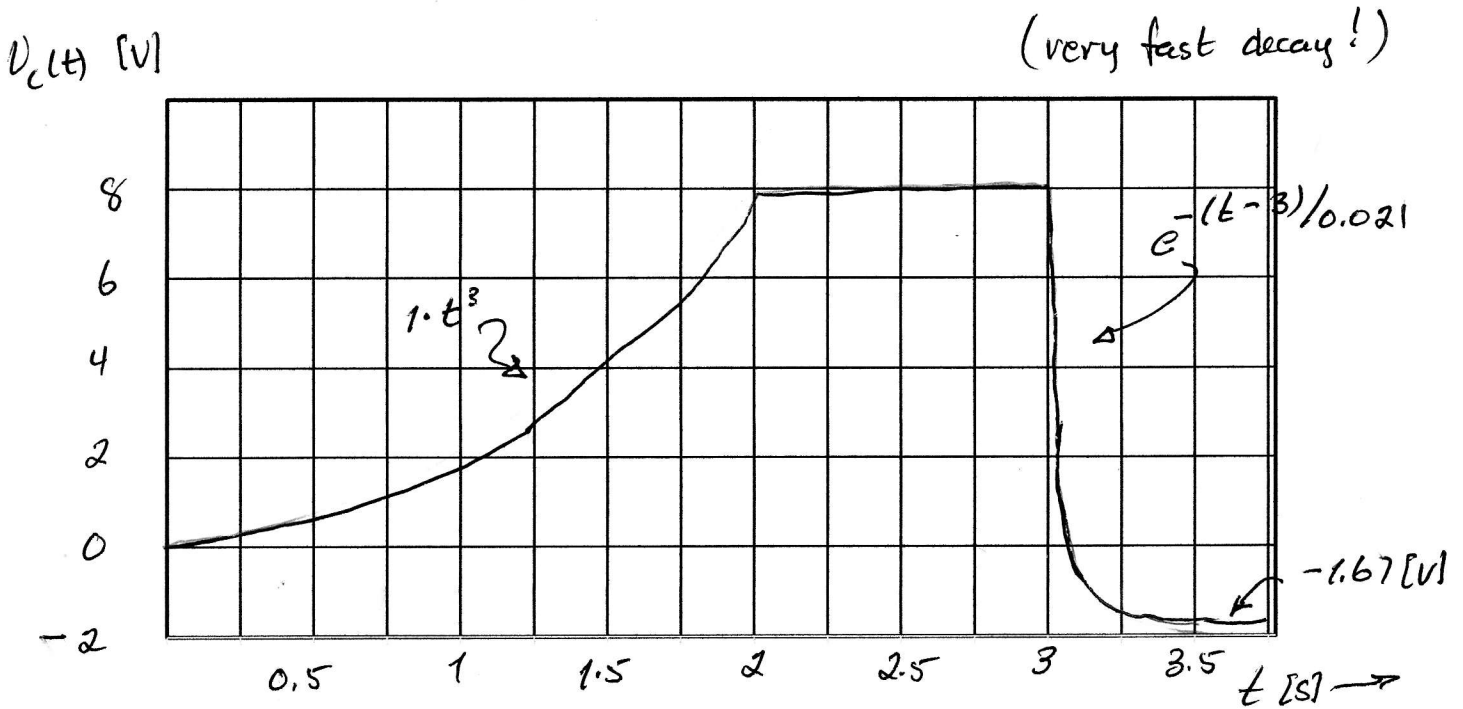a) For $t < 0$, SW1 is at 'a' and SW2 is open. So the capacitor is isolated and $v_C(0) = 0$.



Room for extra work

$0 < t < 2$ [s] Sw1 at 'b', Sw2 open

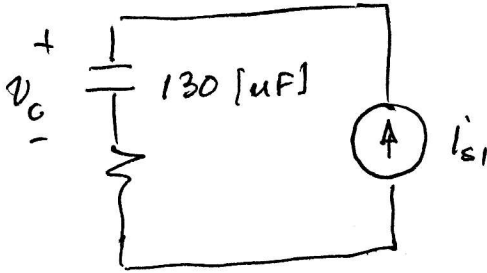

$$V_c(t) = \frac{1}{C} \int_0^t i_{s1}(t) dt + V_c(0)$$

$$V_c(t) = \frac{1}{130 \times 10^{-6}} \int_0^t (0.39 \times 10^{-3}) t^2 dt + 0$$


$$V_c(t) = \frac{1}{3} \frac{0.39 \times 10^{-3}}{130 \times 10^{-6}} t^3 = 1 \cdot t^3 \text{ [V]} \quad 0 \leq t \leq 2 \text{ [s]}$$

↗
This has units $\left[\frac{V}{s^3}\right]$

$2 < t < 3$ [s] Sw1 at 'a', Sw2 open

Capacitor is again isolated so $V_c(t) = 1 \cdot 2^3 = 8 \text{ [V]}$
 $2 \leq t \leq 3 \text{ [s]}$

$t > 3$ [s] Sw1 at 'a', Sw2 closed.

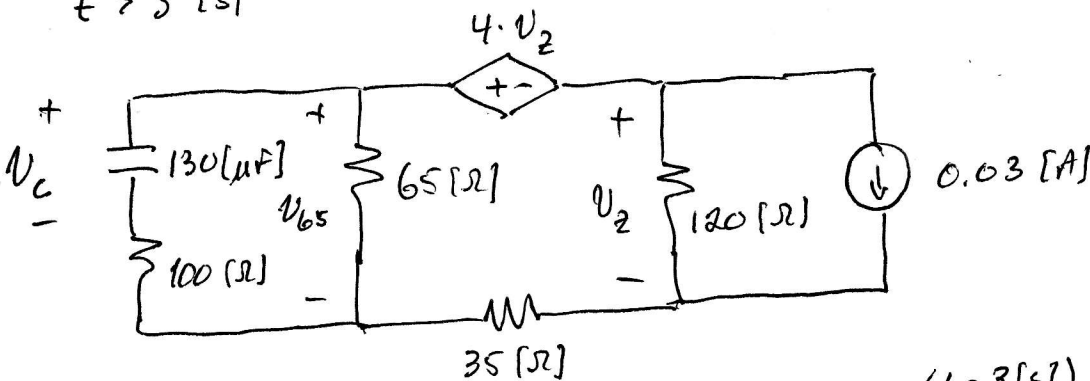

$$V_c(t) = V_{c,f} + (V_c(3[s]) - V_{c,f}) e^{-(t-3[s])/T_c} \quad t \geq 3 \text{ [s]}$$

$$V_c(3[s]) = 8 \text{ [V]}$$


Room for Extra Work

$V_{c,f}$: At steady-state, $C \rightarrow$ open so $V_{c,f} = V_{65}$.

$$\frac{V_2}{120} + 0.3 + \frac{V_2 + 4V_2}{100} = 0 \quad V_2 = -0.5143 \text{ [V]}$$

$$V_{c,f} = V_{65} = 65 \cdot \frac{V_2 + 4V_2}{100} = \underline{\underline{-1.67 \text{ [V]}}}$$

Test source:

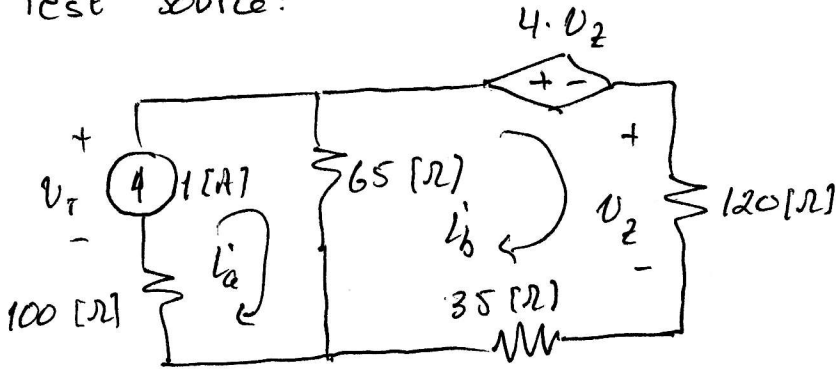

$$i_a = 1 \text{ [A]}$$

$$65(i_b - i_a) + 5V_2 + 35i_b = 0$$

$$V_2 = 120 i_b$$

$$V_T = 65(i_a - i_b) + 100i_a$$

$$V_T = 158.96 \text{ [V]} \Rightarrow R_{TH} = 158.96 \text{ [}\Omega\text{]}$$

$$\tau_c = R_{TH} C = 20.66 \text{ [ms]}$$

So...

$$V_c(t) = -1.67 + (8 + 1.67)e^{-\frac{(t-3 \text{ [s]})}{0.02066 \text{ [s]}}} \text{ [V]} \quad t \geq 3 \text{ [s]}$$

$$V_c(t) = -1.67 + 9.67e^{-\frac{(t-3 \text{ [s]})}{0.02066 \text{ [s]}}} \text{ [V]} \quad t \geq 3 \text{ [s]}$$

Summary:


$$V_c(t) = \begin{cases} 0 & t < 0 \\ 1 \cdot t^3 \text{ [V]} & 0 \leq t \leq 2 \text{ [s]} \\ 8 \text{ [V]} & \cancel{0 \leq t \leq 2 \text{ [s]}} \\ -1.67 + 9.67e^{-\frac{(t-3)}{0.02066}} \text{ [V]} & 2 \leq t \leq 3 \text{ [s]} \\ & t \geq 3 \text{ [s]} \end{cases}$$

3. [55 points] The circuit below is operating in steady state. Find the voltage $v_L(t)$. The values of the sources are given as follows.

$$v_{S1}(t) = 15 \text{ [V]} \cos(600t) - 37 \text{ [V]} \cos(1200t - 20^\circ)$$

$$v_{S2}(t) = 6.5 \text{ [V]} \sin(1200t)$$

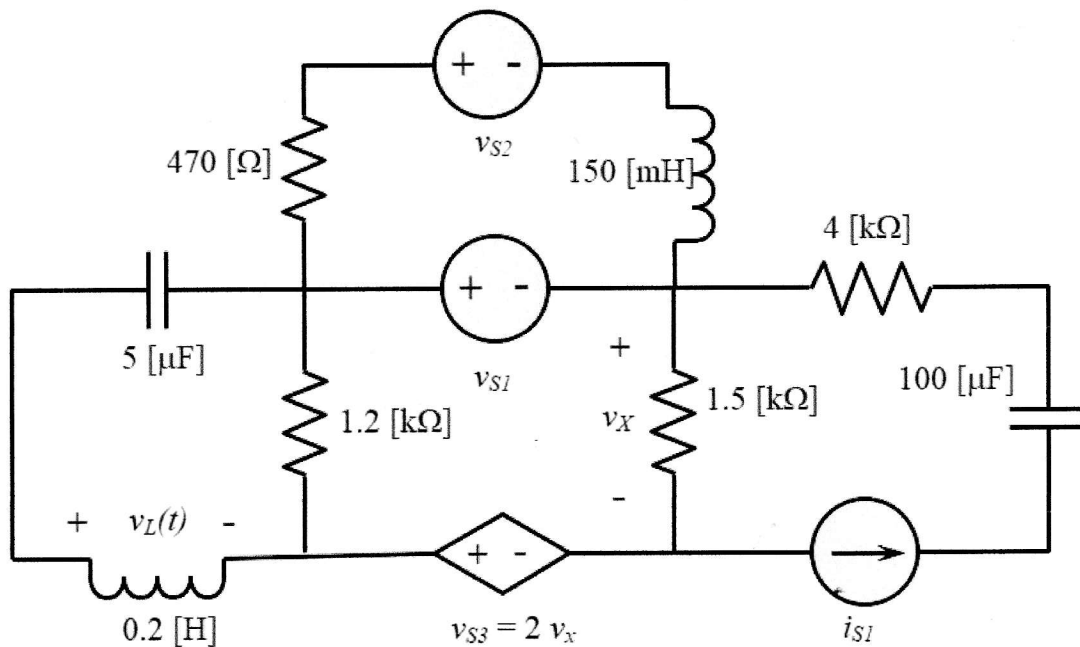
$$i_{S1}(t) = 30 \text{ [mA]} \sin(600t) = 0.03 \text{ [A]} \cos(600t - 90^\circ)$$



We need superposition, but note that v_{S2} , $470[\Omega]$, and 150 [mH] are in parallel with a voltage source and will not be "seen" by 0.2 [H] , so we can ignore them. We also note that v_{S1} has two frequency components, and we need to consider only one at a time.

Consider first $\omega = 600 \text{ [rad/s]}$. We need that component of v_{S1} and i_{S1} :

Room for extra work

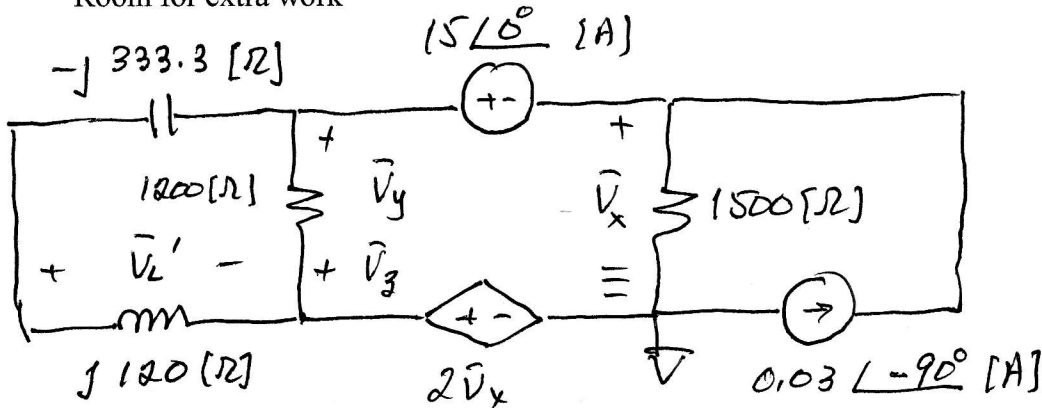

$$\frac{\bar{V}_x}{1500} - 0.03 \angle -90^\circ + \frac{\bar{V}_y - \bar{V}_z}{1200} + \frac{\bar{V}_y - \bar{V}_z}{j(120 - 333.3)} = 0$$

$$\bar{V}_x - \bar{V}_y = 15 \quad \bar{V}_z = 2\bar{V}_x$$

$$\bar{V}_x = -8.6839 + j2.3579 \text{ [V]}$$

$$8.998 \angle 164.81^\circ$$

$$\bar{V}_y = -23.684 + j2.3579 \text{ [V]}$$

$$23.801 \angle 174.31^\circ$$


$$\bar{V}_z = -17.368 + j4.7158 \text{ [V]}$$

$$18.60 \angle 164.81^\circ$$

$$\bar{V}_L' = \frac{\bar{V}_y}{j(120 - 333.3)} \cdot j120 = 13.322 - j1.2263 \text{ [V]}$$

$$13.388 \angle -5.685^\circ$$

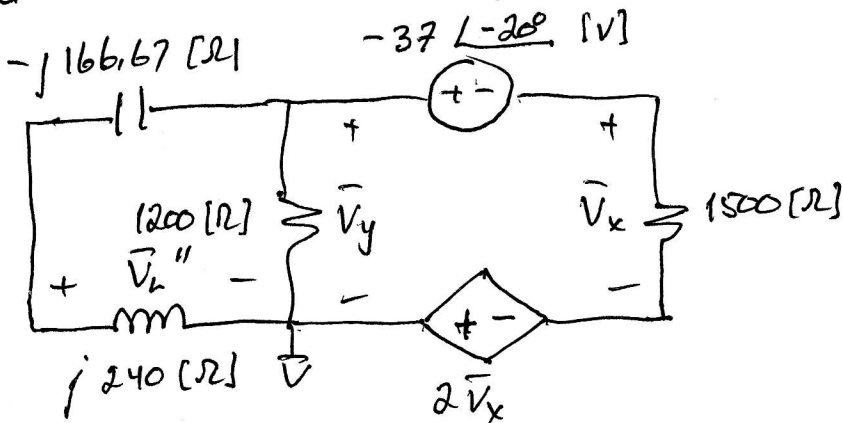The $\omega = 1200 \frac{\text{rad}}{\text{s}}$ component is in V_s :



27
p. 2

Room for extra work

$$\frac{\bar{V}_y}{j(240 - 166.67)} + \frac{\bar{V}_y}{1200} + \frac{\bar{V}_y + 37 \angle -20^\circ + 2\bar{V}_x}{1500} = 0$$

$$\bar{V}_y + \bar{V}_x + 37 \angle -20^\circ = 0$$

$$\bar{V}_x = 0.7470 + j2.1338 \quad [V]$$

$$2.2608 \angle 70.706^\circ$$

$$\bar{V}_y = -35.516 + j10.521 \quad [V]$$

$$37.042 \angle 163.5^\circ$$

$$\bar{V}_x'' = \frac{\bar{V}_y}{j(240 - 166.67)} \cdot j240 = -116.24 + j34.434 \quad [V]$$

$$121.23 \angle 163.50^\circ$$

Converting to time domain for each \bar{V}_x & \bar{V}_x''

$$v_x(t) = 13.388 \cos(\omega t - 5.685^\circ) [V]$$

$$+ 121.23 \cos(\omega t + 163.50^\circ) [V]$$

4. [50 points] The circuit below is operating in steady state and at a frequency of 30 [Hz]. The voltage across load 3 is known and is shown in the diagram. The loads are specified as follows.


Load 1 absorbs 2.5 [kVAR] at a power factor of 0.8 leading.

Load 2 is a 30 [Ω] resistor in parallel with a 120 [μ F] capacitor.

Load 3 absorbs 3.5 [kW] and 4.0 [kVAR].

a) Find the source voltage \bar{V}_s necessary to produce the voltage indicated across L3.

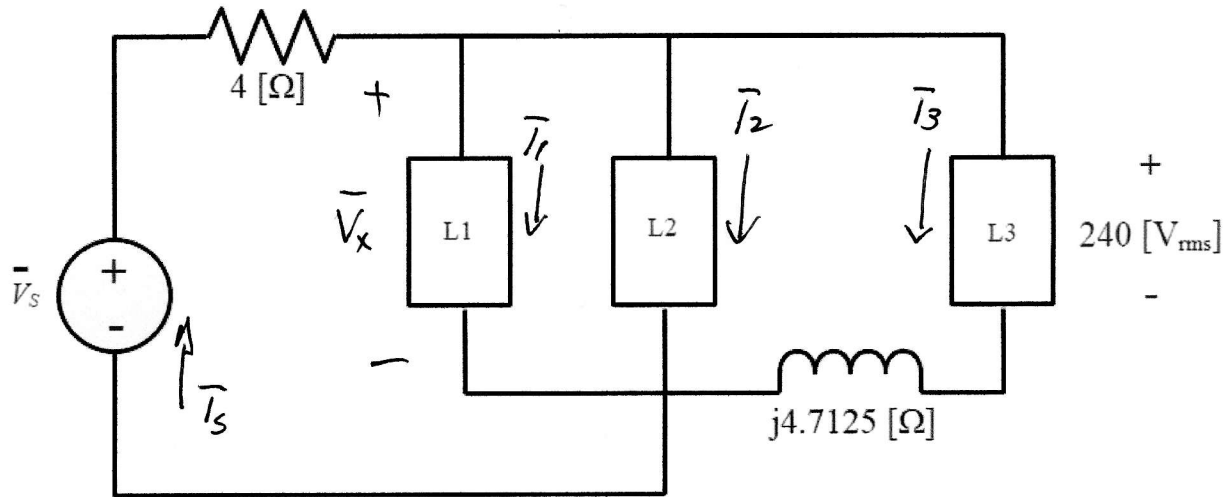b) Find the complex power delivered by the source.



$$L1: \text{pf} = 0.8 \Rightarrow \text{rf} = \sqrt{1 - 0.8^2} = 0.6$$

$$|S_1| = \frac{2500}{0.6} = 4166.7$$

$$\Rightarrow S_1 = 4166.7 \cdot (0.8) \overset{\text{leading}}{\angle -} j 4166.7 (0.6) = 3333.4 - j 2500 \text{ [VA]}$$

$$L2: 120 [\mu\text{F}] \rightarrow -j / (2\pi \cdot 30 \cdot 120 \times 10^{-6}) = -j 44.21 [\Omega]$$

$$Z_2 = 30 \parallel (-j 44.21) = 20.541 - j 13.939 [\Omega]$$

$$24.824 \angle -34.16^\circ$$

$$L3: S_3 = 3500 + j 4000 \text{ [VA]}$$

Room for extra work

Game plan: We'll find the three load currents and sum them to find \bar{I}_s . This will require knowing $\bar{V}_x \dots$

$$\bar{I}_3^* = \frac{S_3}{240} = 14.583 + j16.667 \text{ [Arms]} \Rightarrow \bar{I}_3 = \frac{14.583 - j16.667}{22.146 \angle -48.815^\circ} \text{ [Arms]}$$

$$\bar{V}_x = \bar{I}_3 \cdot j4.7125 + 240 = \frac{161.46 + j68.724}{175.48 \angle 23.057^\circ} \text{ [Vrms]}$$

$$\bar{I}_2 = \frac{\bar{V}_x}{Z_2} = \frac{3.8274 + j5.9430}{7.0688 \angle 57.218^\circ} \text{ [Arms]}$$

$$\bar{I}_1^* = \frac{S_1}{\bar{V}_x} = 11.899 - j20.548 \text{ [Arms]} \Rightarrow \bar{I}_1 = \frac{11.899 + j20.548}{23.745 \angle -59.926^\circ} \text{ [Arms]}$$

$$\bar{I}_s = \bar{I}_1 + \bar{I}_2 + \bar{I}_3 = \frac{30.309 - j31.272}{43.550 \angle -48.89^\circ} \text{ [Arms]}$$

$$\text{KVL: } \bar{V}_s = \bar{V}_x + \bar{I}_s \cdot 4 = \frac{282.70 - j56.363}{288.26 \angle -11.275^\circ} \text{ [Vrms]}$$

$$S_{\text{del by } \bar{V}_s} = \bar{V}_s \cdot \bar{I}_s^* = \frac{10332 + j7131.3}{12554 \angle 34.615^\circ} \text{ [VA]}$$