

Name: \_\_\_\_\_ (please print)

Signature: \_\_\_\_\_

# ECE 2202 – Exam 1

October 7, 2023

**Keep this exam closed until you are  
told to begin.**

1. This exam is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution that is not given in a reasonable order will lose credit. Clearly indicate your answer (for example by enclosing it in a box).
3. Show all units in solutions, intermediate results, and figures. Units in the exam will be included between square brackets.
4. If the grader has difficulty following your work because it is messy or disorganized, you will lose credit.
5. Do not use red ink. Do not use red pencil.
6. You will have 90 minutes to work on this exam.

1. \_\_\_\_\_/35

2. \_\_\_\_\_/35

3. \_\_\_\_\_/30


Total = 100

Room for extra work

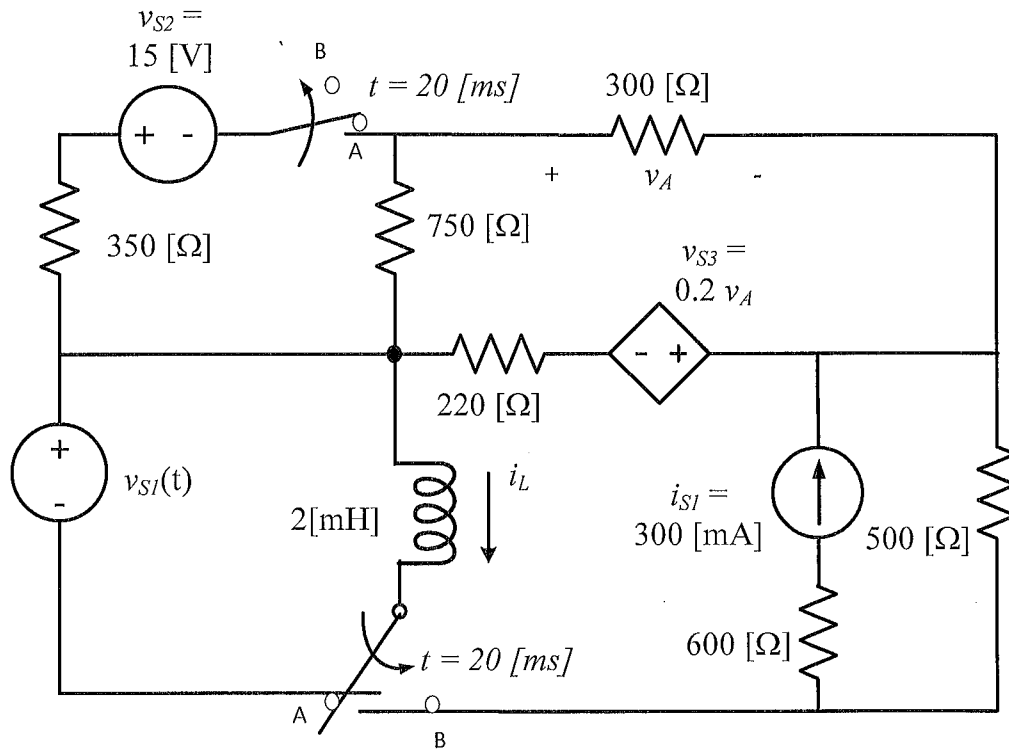1. {35 Points} In the circuit shown, both switches were in position ‘A’ for a long time, and moved to position ‘B’ at  $t = 20$  [ms]. At  $t = 0$ , the current in the inductor  $i_L$  was 1.8 [mA]. The source  $v_{S1}(t)$  has the value

$$v_{S1}(t) = 0.6 \left[ \frac{\text{V}}{\text{s}^2} \right] t^2 \quad 0 \leq t \leq 20 \text{ [ms]}$$



Find the power delivered by the current source  $i_{S1}$  at  $t = 20$  [ms]<sup>+</sup>.



Room for extra work

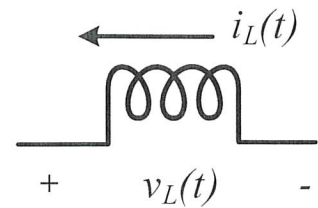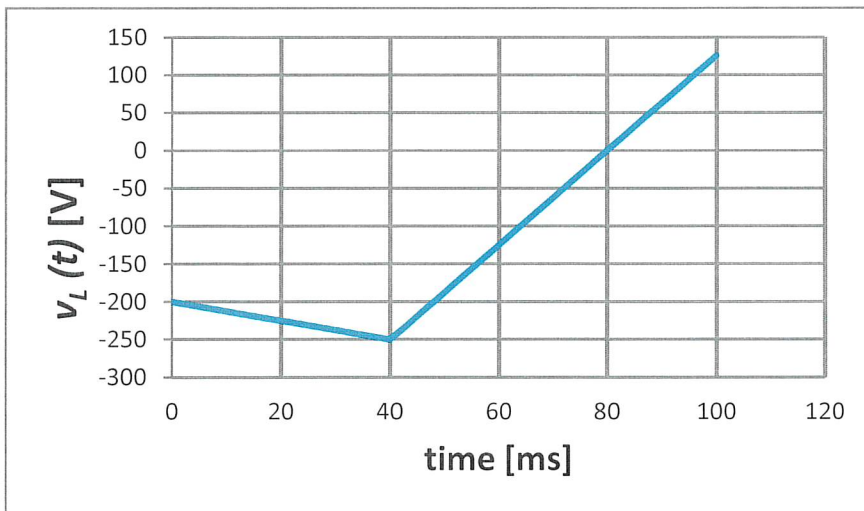
2. {35 Points} The voltage  $v_L(t)$  across a 500 [mH] inductor is given in the graph below. It is known that  $i_L(60 \text{ [mS]}) = 21.5 \text{ [A]}$ . The value of the inductor current at  $t = 0$  is not known.

Find  $i_L$  at 80 [mS]. The inductor voltage polarity and current direction are shown in the figure.



Room for extra work

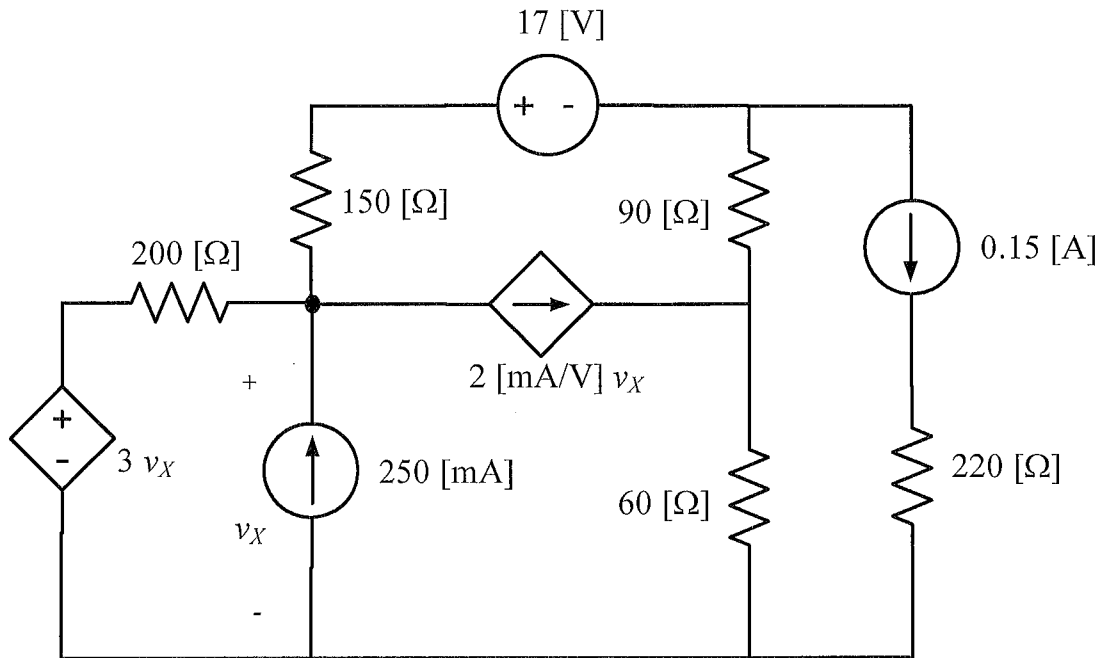3. {30 Points} For the circuit below, do the following.
- Find the Thevenin equivalent seen by the 250 [mA] current source.
  - Find the power delivered by the 250 [mA] current.




Room for extra work



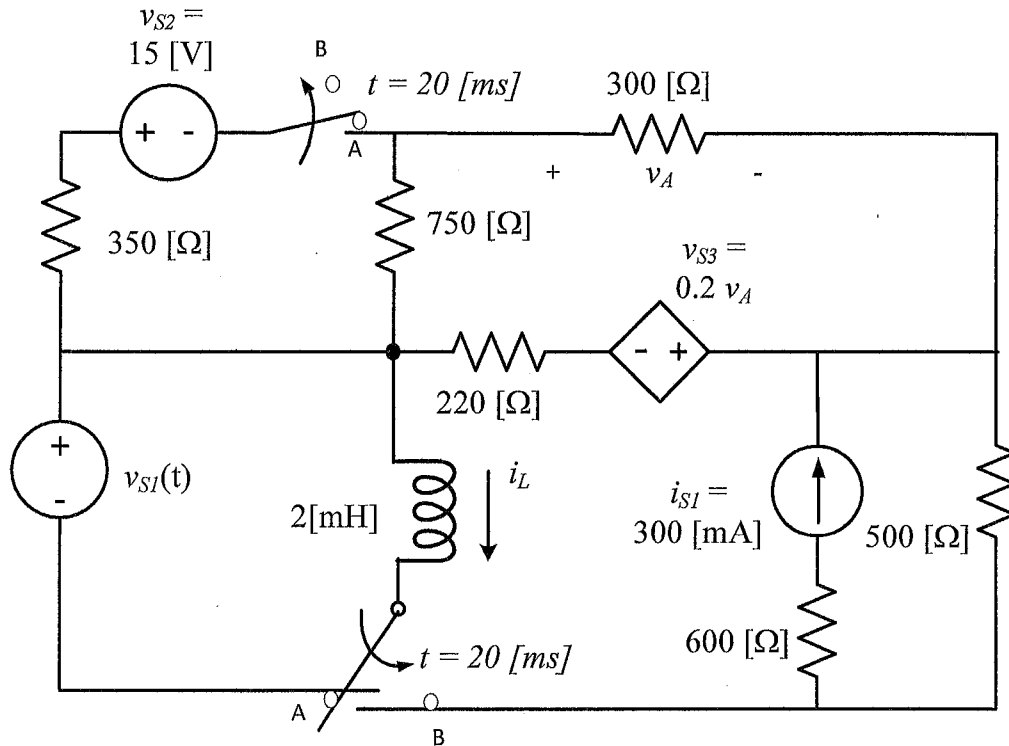
1. {35 Points} In the circuit shown, both switches were in position 'A' for a long time, and moved to position 'B' at  $t = 20$  [ms]. At  $t = 0$ , the current in the inductor  $i_L$  was 1.8 [mA]. The source  $v_{S1}(t)$  has the value

$$v_{S1}(t) = 0.6 \left[ \frac{\text{V}}{\text{s}^2} \right] t^2 \quad 0 \leq t \leq 20 \text{ [ms]}$$

Find the power delivered by the current source  $i_{S1}$  at  $t = 20$  [ms]<sup>+</sup>.



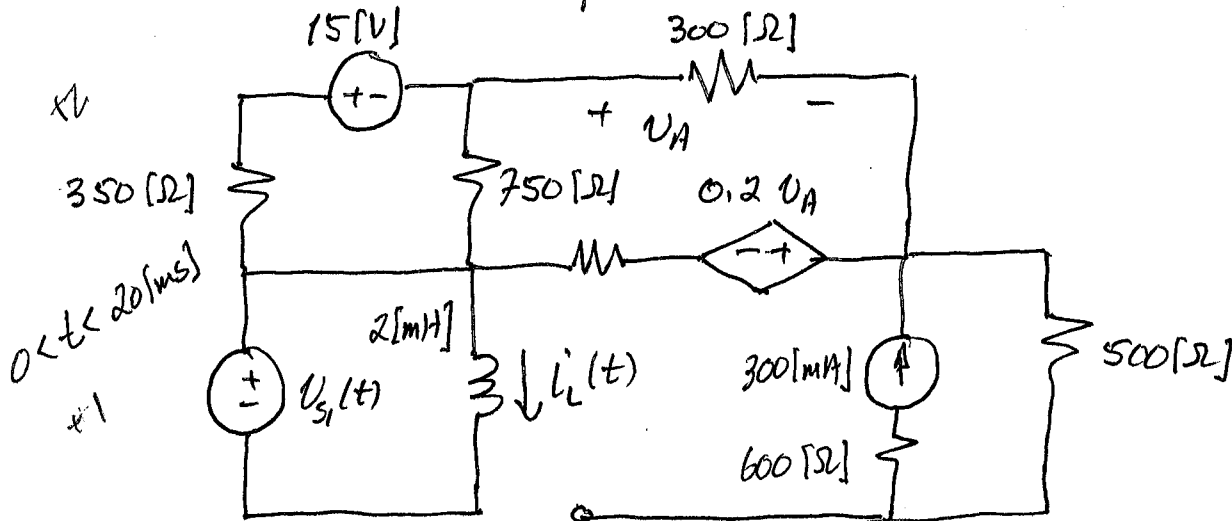With switches in position A, the circuit is ...




Room for extra work

The only relevant thing here is that the inductor is in parallel with  $v_{S1}$ . So...

$$+9 \quad i_L'(t) = \frac{1}{L} \int_0^t v_{S1}(t) dt + i_L'(0)$$

$$+2 \quad i_L'(0.02 [s]) = \frac{1}{0.002} \int_0^{0.02 [s]} 0.6 t^2 dt + 0.0018 [A] = 2.6 [mA]$$

After the switch moves...

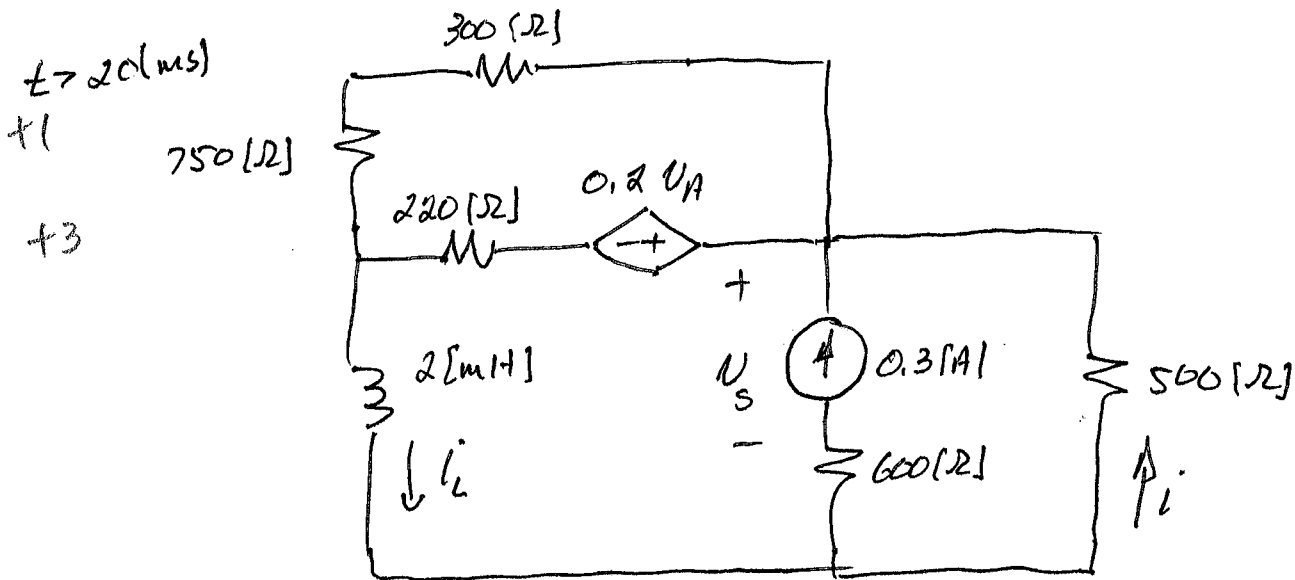

With  $i_L' = 2.6 [mA]$ , this circuit is valid for  $20 [ms]^+$ , we need  $v_S(20 [ms])^+$ :



$$+12 \quad 0.0026 = 0.3 + i \Rightarrow i' = -0.2994 [A]$$

$$+3 \quad v_S - 600(0.3) + 500i = 0 \Rightarrow v_S = 328.7 [V]$$

$$+3 \quad \boxed{P_{del \text{ by } i_{S1}} = (328.7)(0.3) = 98.61 [W] \quad t = 20 [ms]^+}$$

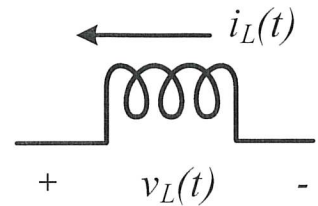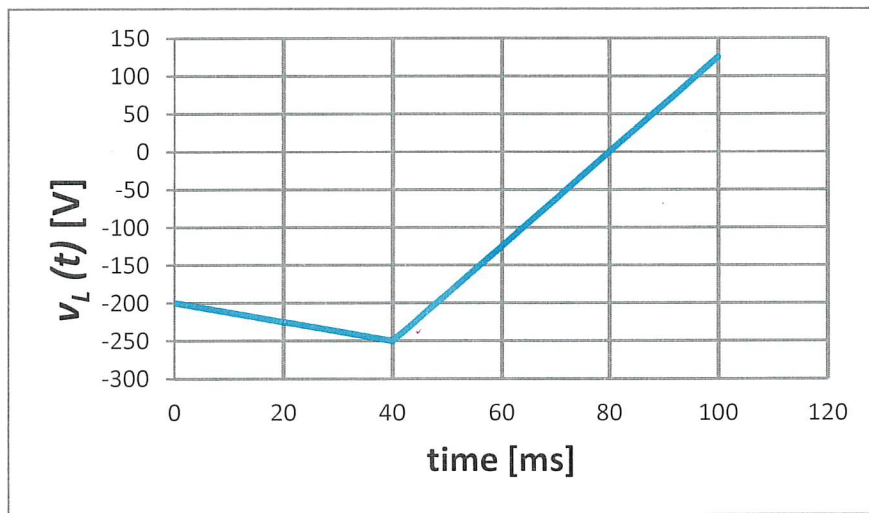2. {35 Points} The voltage  $v_L(t)$  across a 500 [mH] inductor is given in the graph below. It is known that  $i_L(60 \text{ [ms]}) = 21.5 \text{ [A]}$ . The value of the inductor current at  $t = 0$  is not known. [ms]

Find  $i_L$  at 80 [ms]. The inductor voltage polarity and current direction are shown in the figure.



Although we could integrate from 0 to 40 [ms], and then 40 [ms] to 60 [ms], and finally from 60 [ms] to 80 [ms], it's easier than that:

$$i_L(t) = -\frac{1}{L} \int_{t_0}^t v_L(t) dt + i_L(t_0)$$

With  $t_0 = 60 \text{ [ms]}$  and  $i_L(t_0) = 21.5 \text{ [A]}$ , we have

$$v_L(t) = mt + b \quad 40 \text{ [ms]} \leq t \leq 100 \text{ [ms]}$$

$$v_L(40 \text{ [ms]}) = -250 \text{ [V]} \quad v_L(80 \text{ [ms]}) = 0$$

$$\Rightarrow v_L(t) = 6250 \left[ \frac{\text{V}}{\text{s}} \right] t - 500 \text{ [V]}$$


Room for extra work

Then


$$i_L'(80 \text{ [ms]}) = -\frac{1}{0.15} \int_{0.06 \text{ [s]} + 2}^{0.08 \text{ [s]} + 2} (6250t - 500) dt + 21.5 \text{ [A]} + 3$$

$$\boxed{i_L'(80 \text{ [ms]}) = 24 \text{ [A]}}$$

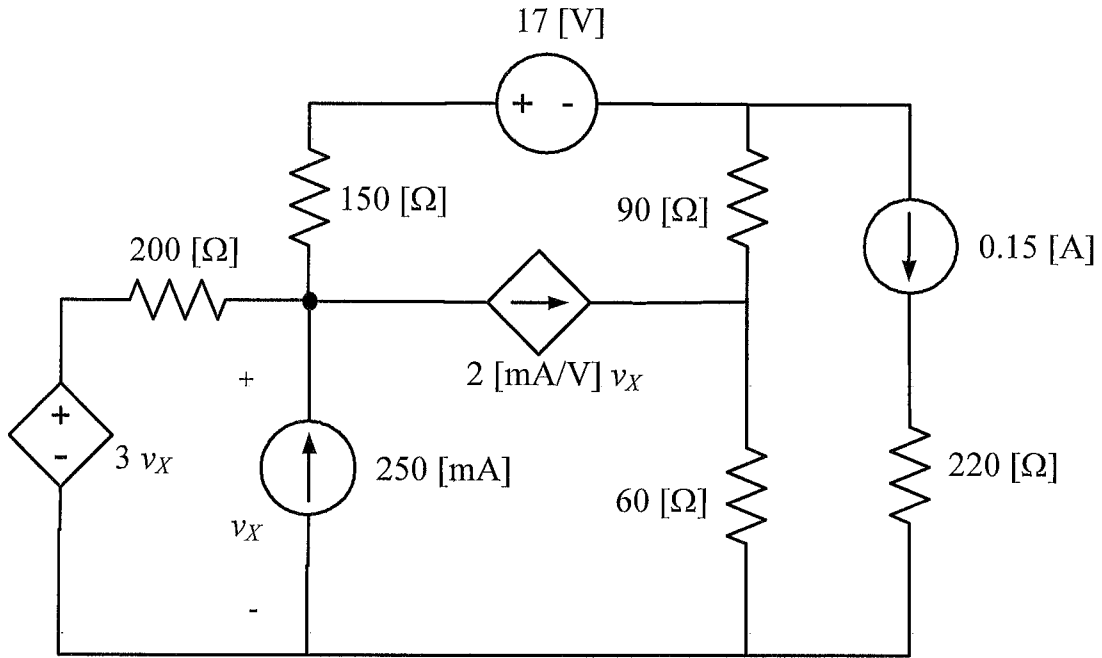3. {30 Points} For the circuit below, do the following.  
 a. Find the Thevenin equivalent seen by the 250 [mA] current source.  
 b. Find the power delivered by the 250 [mA] current.



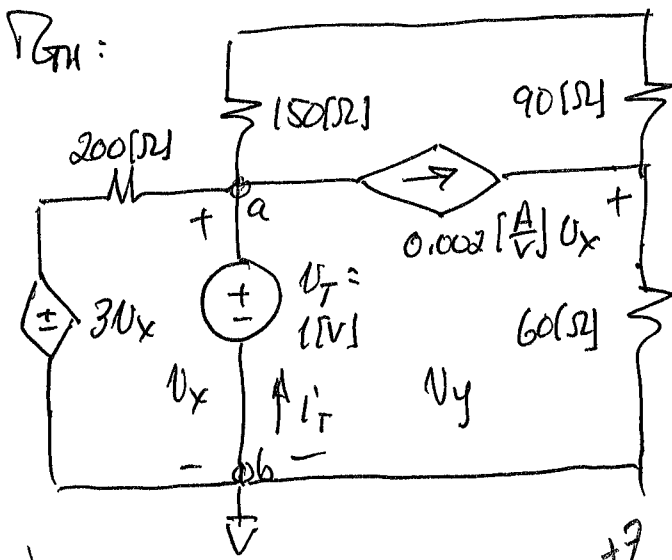We need two of  $i_{sc}$ ,  $V_{oc}$ ,  $V_{Th}$ . We'll do all three here.  
 Finding  $i_{sc}$  simplifies things because with the short,  $v_x = 0$ .  
 Finding  $V_{Th}$  also simplifies things. Finding  $i_{sc}$  is hardest.



$$v_x = 1[V]$$

$$\frac{v_y}{60} - 0.002 + \frac{v_y - 1}{240} = 0 \Rightarrow v_y = 0.296[V]$$

$$-i_T + \frac{v_x - 3v_x}{200} + 0.002v_x + \frac{v_x - v_y}{240} = 0$$

$$v_y = 0.296[V] \quad i_T = -5.0667[mA]$$


$$\Rightarrow R_{Th} = -197.4[\Omega]$$

+4

analysis +7

+2  
7

Room for extra work

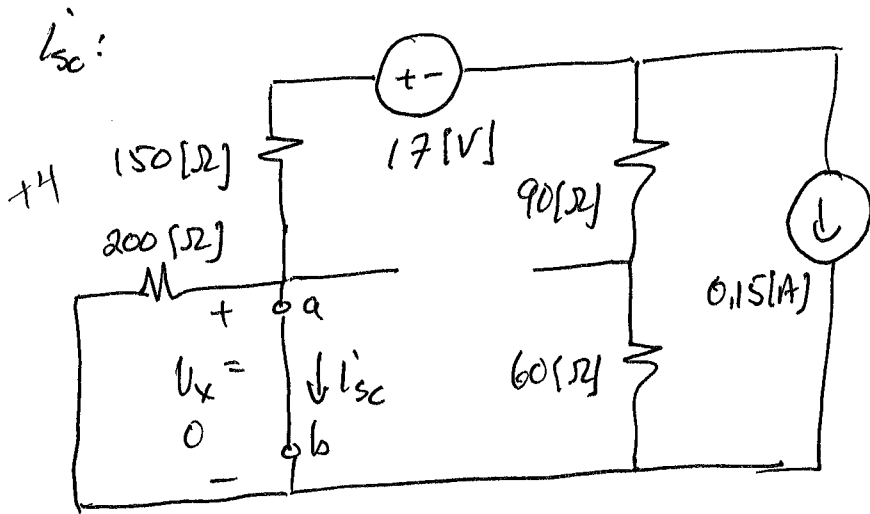


$U_x = 0$  analysis +7  
 $200[\Omega]$  is shorted.

$$(i_{sc}' + 0.15)(150) - 17 + 150i_{sc}' = 0$$


$$i_{sc}' = -18.333 \text{ [mA]}$$
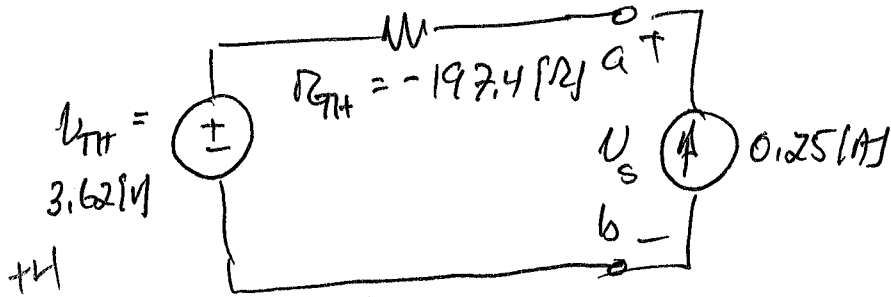
$$U_{TH} = i_{sc}' \cdot R_{TH} = 3.62 \text{ [V]} \quad +2$$



$$U_s = -45.73 \text{ [V]}$$
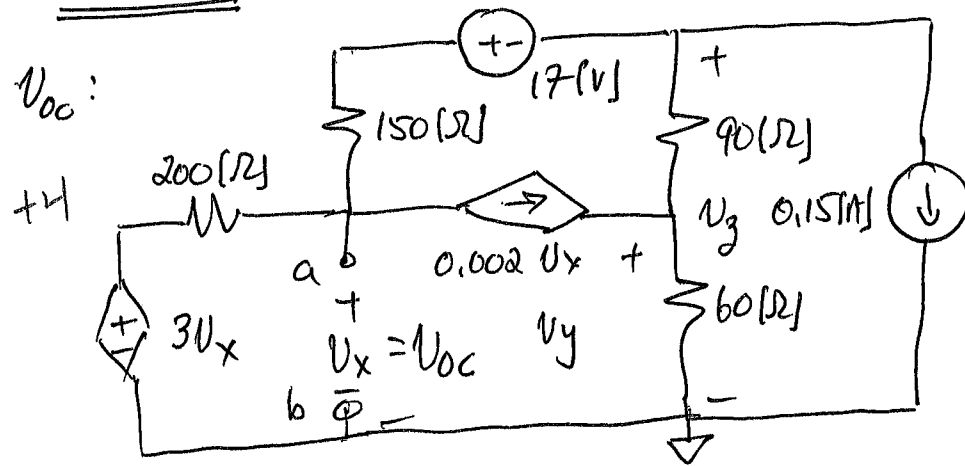
$$P_{del \text{ by } 0.25 \text{ [A]}} = 0.25 U_s = -11.43 \text{ [W]}$$



So this checks!

$$\frac{U_x - 3U_x}{200} + \frac{U_x - U_y - 17}{150} + 0.002 U_x = 0$$

$$\frac{U_y}{60} + \frac{U_y - U_z}{90} - 0.002 U_x = 0$$

$$\frac{U_z - U_y}{90} + 0.15 + \frac{U_z - U_x + 17}{150} = 0$$

$$U_x = 3.62 \text{ [V]} = U_{TH} \quad \checkmark$$

$$U_y = -6.83 \text{ [V]} \quad +2$$

$$U_z = -17.72 \text{ [V]}$$