


Name: _____ (please print)

Signature: _____


ECE 2300 – NOT Quiz #5
July 14, 2015

This quiz is “take-home”. Dr. Trombetta will grade it for you if you wish, but it will not count for a grade in the course. You should be able to work it in 30 minutes without help and without aids except for a one-page crib sheet.

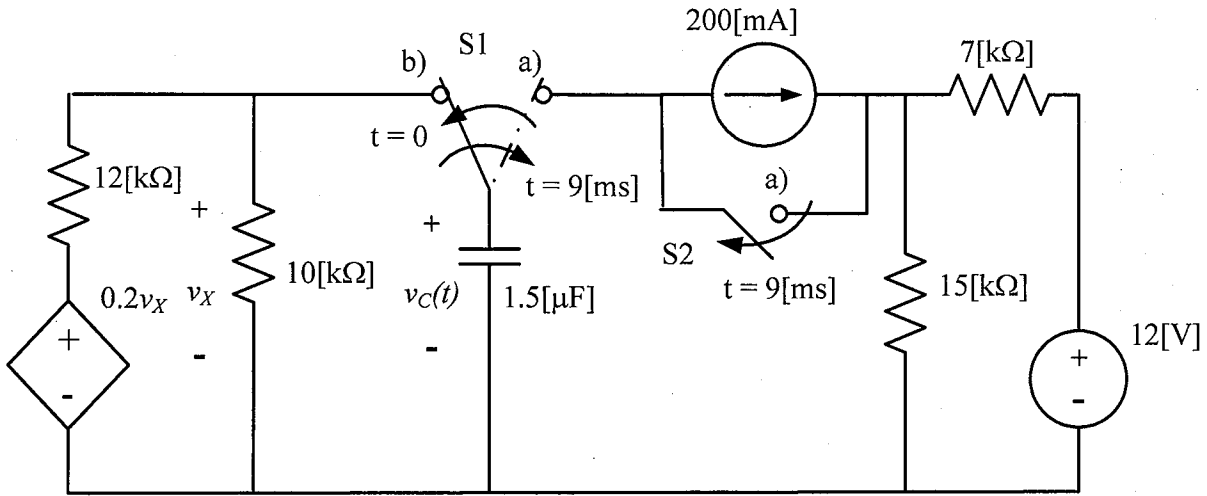Switches S1 and S2 were in position a) for a long time, and then moved to b) at $t = 0$. At $t = 9$ [ms], switch S1 moved back to position a), and switch S2 opened. Find the voltage across the capacitor $v_C(t)$ at $t = 12$ [ms].




Re-draw for $t < 0$:

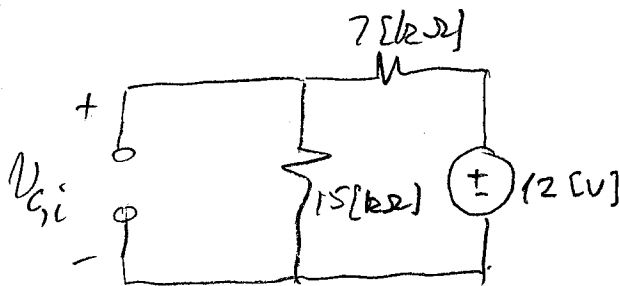

$$v_{Ci} = 12 \cdot \frac{15}{22} = 8.182 \text{ [V]}$$

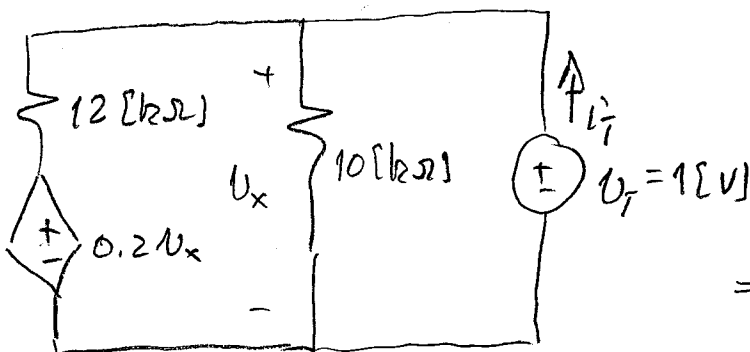Re-draw for $0 < t < 9$ [ms] and insert a test source:



$$i'_T = \frac{1}{10^4} + \frac{1 - 0.2v_x}{12000}$$

$$v_x = 1 \text{ [V]}$$

$$\Rightarrow i'_T = 10^{-4} + 6.667 \times 10^{-5} = 0.1667 \text{ [mA]}$$


$$R_{TH} = \frac{1}{i'_T} = 6 \text{ [k}\Omega] \Rightarrow \tau = R_{TH} C = 9 \text{ [ms]}$$

Room for extra work

$$\therefore 0 < t < 9 \text{ [ms]} \Rightarrow V_C(t) = 8,182 \text{ [V]} e^{-t/9 \text{ [ms]}}$$

$$\text{at } t = 9 \text{ [ms]}, V_C = 8,182 e^{-1} = 3,01 \text{ [V]}$$

Re-draw for $t > 9 \text{ [ms]}$:

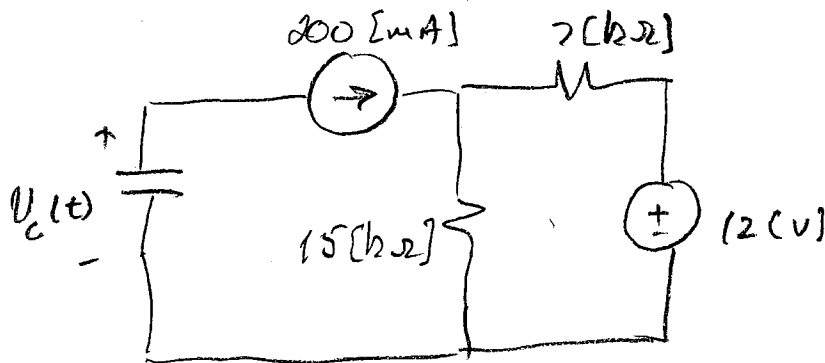

$$V_C(t) = -\frac{1}{C} \int_{9 \text{ [ms]}}^t 0,2 \text{ [A]} dt + V_C(9 \text{ [ms]})$$

$$= -\frac{0,2 \text{ [A]}}{1,5 \times 10^{-6} \text{ [F]}} (t - 9 \text{ [ms]}) + 3,01 \text{ [V]} \quad t \geq 9 \text{ [ms]}$$

$$\begin{aligned} \text{At } t = 12 \text{ [ms]}, \quad V_C &= -1,333 \times 10^5 \left[\frac{\text{A}}{\text{F}} \right] \cdot 3 \times 10^{-3} \text{ [s]} + 3,01 \\ &= -400 + 3,01 = \underline{\underline{-397 \text{ [V]}}} \end{aligned}$$