

Name: _____ (please print)

Signature: _____

ECE 2202 – Final Exam
August 4, 2020
Online

1. This quiz is open book, open notes.
2. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution which is not given in a reasonable order will lose credit.
3. Show all units in solutions, intermediate results, and figures. Units in the quiz will be included between square brackets.
4. If the grader has difficulty following your work because it is messy or disorganized, you will lose credit.
5. Do not use red ink. Do not use red pencil.
6. You will have 150 minutes to work on this quiz, and 20 minutes to download/print, scan and submit.
7. You **MUST** use lower case letters for time domain quantities, and upper-case letters with overbars for phasor quantities.

1. _____ /35

2. _____ /45

3. _____ /45



4. _____ /40

5. _____ /35

_____ /200

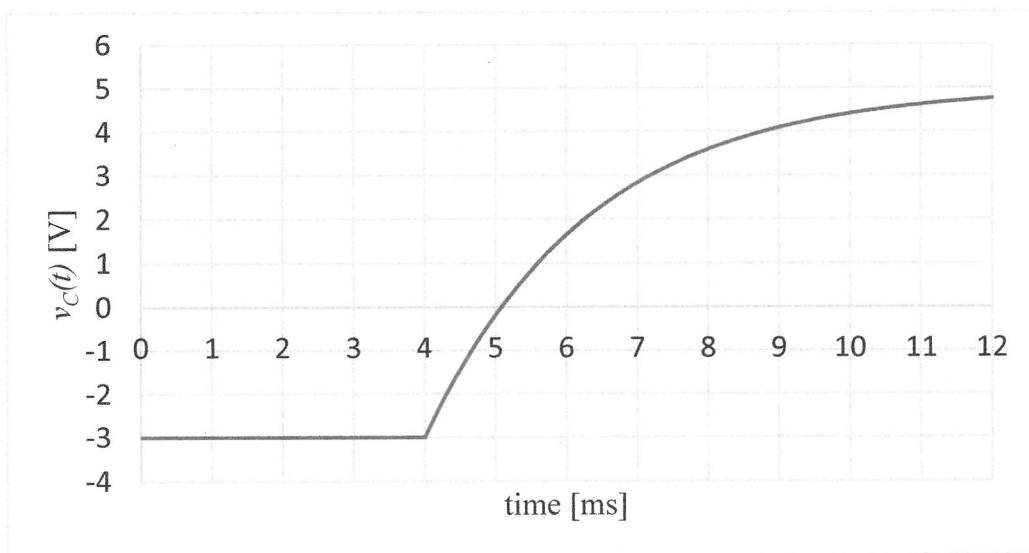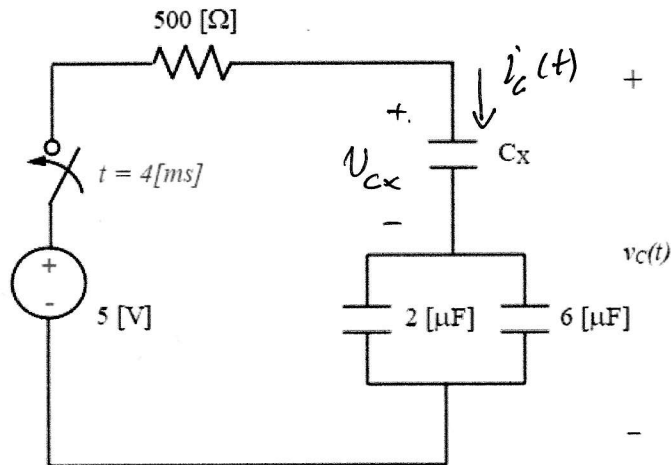1. [35 points] The circuit shown was set up as an experiment to determine the value of the unknown capacitance C_X . The switch had been open for a long time and closed at $t = 4$ [ms]. It is known that before the switch closed, the capacitor C_X had no energy stored in it. A plot of $v_C(t)$ is shown in the graph.

- From the graph, estimate the time constant τ_C .
- Find the unknown capacitance C_X .
- Write an equation for $v_C(t)$ for $t > 4$ [ms]. Clearly indicate initial and final values, and τ_C .
- Find the energy stored in C_X for $t \rightarrow \infty$.



We define an equivalent capacitance C_{eq} , with voltage $v_C(t)$. Then

$$v_C(t) = v_{C,f} + (v_C(t_0) - v_{C,f}) e^{-\frac{(t-4 \text{ [ms]})}{\tau_C}} \quad t \geq 4 \text{ [ms]}$$

Room for extra work

So we have $t_0 = 4 \text{ [ms]}$ at which point $v_c(t_0) = -3 \text{ [V]}$.

From the circuit it's also clear that $v_{sf} = 5 \text{ (V)}$.

a) We can find τ_c in several ways. Here are two...

1. From the graph we see that $v_c = 0$ at $t \approx 5.05 \text{ [ms]}$.
($t = 5 \text{ [ms]}$ is close enough!) So we have

$$v_c = 0 = 5 + (-3 - 5) e^{-(5-4)/\tau_c} \quad \tau_c \text{ in [ms]}$$

$$\text{So } e^{-1/\tau_c} = \frac{5}{8} \Rightarrow \tau_c \approx 2.13 \text{ [ms]}$$

2. At the time $(t-4) = \tau_c$, we have

$$v_c = 5 - 8 e^{-1} \approx 2.06 \text{ [V]}.$$

At this voltage, $t \approx 6.2 \text{ [ms]}$ So $\tau_c \approx 2.2 \text{ [ms]}$.

So this gives a slightly different answer.

+ 8
+ 4
we will use $\tau_c = 2.15 \text{ [ms]}$ (a compromise). For full credit,
any answer in the vicinity of 2 [ms] is acceptable.


b) We have $\tau_c = 2.15 \text{ [ms]} = R_{TH} C_{eq}$

$$R_{TH} = 500 \text{ [\Omega]} \Rightarrow C_{eq} = 4.4 \text{ [\mu F]} \Rightarrow \underline{C_x = 9.8 \text{ [\mu F]}}$$


$$c) \quad v_c(t) = 5 - 8 e^{-(t-4 \text{ [ms]})/2.15 \text{ [ms]}} \quad t \geq 4 \text{ [ms]}$$

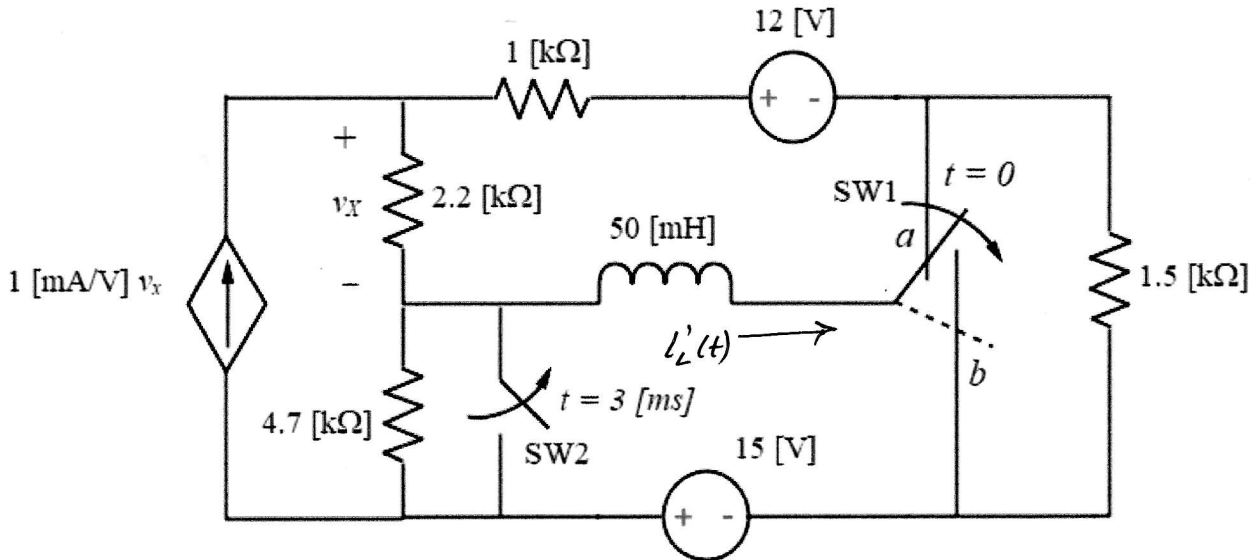2. [45 points] In the circuit below, switch SW1 was in position 'a' for a long time, and switch SW2 was closed for a long time. At $t = 0$, SW1 moved to position 'b' (indicated by the dashed line) and remained there. After 3 [ms], SW2 opened and remained open.

Find the energy stored in the inductor at $t = 3.5$ [ms].



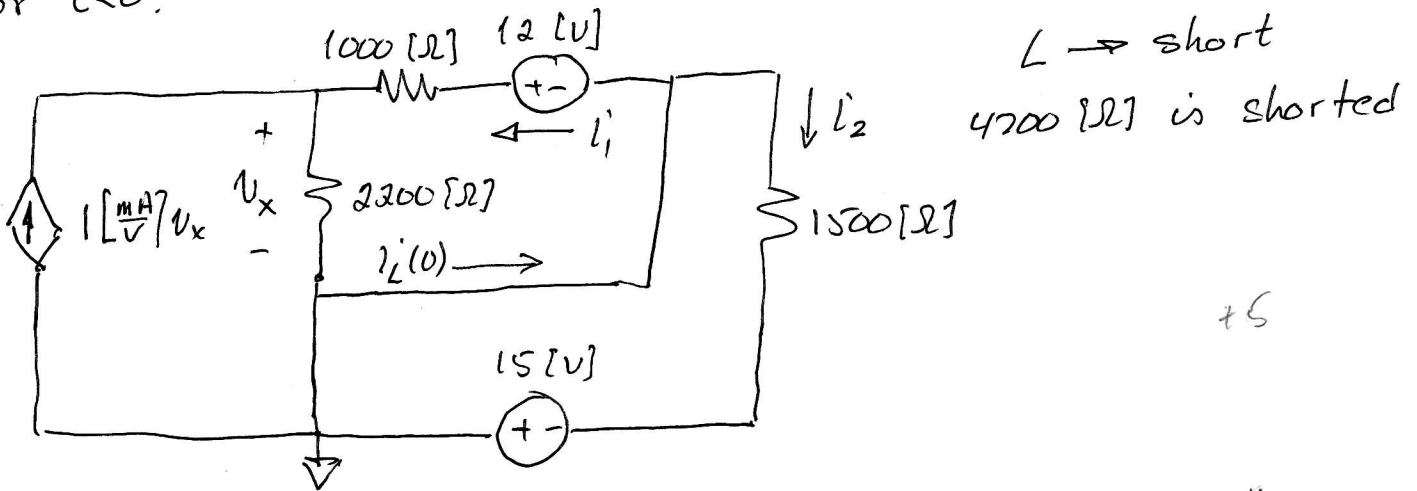We will need $i_L'(t)$... start by finding the initial current for $t < 0$:




$$\frac{v_x}{2200} - 0.001 v_x + \frac{v_x - 12}{1000} = 0 \Rightarrow v_x = 26.4 \text{ [V]}$$

$$i_L'(0) = i_1 + i_2 = -\frac{v_x - 12}{1000} + \frac{15}{1500} = -4.4 \text{ [mA]}$$

Room for extra work

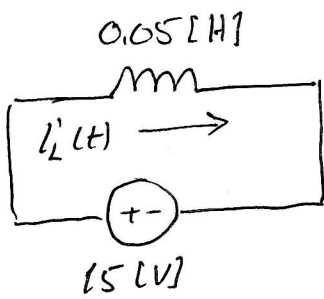For $0 < t < 3$ [ms], the inductor is in parallel with a voltage source, so nothing else matters!




$$i_L'(t) = \frac{1}{0.05} \int_0^{3 \times 10^{-3}} 15 dt - 4.4 \text{ [mA]}$$

$$i_L'(t) = \frac{15}{0.05} 3 \times 10^{-3} - 4.4 \text{ [mA]}$$

$$i_L'(3 \text{ [ms]}) = 895.6 \text{ [mA]}$$

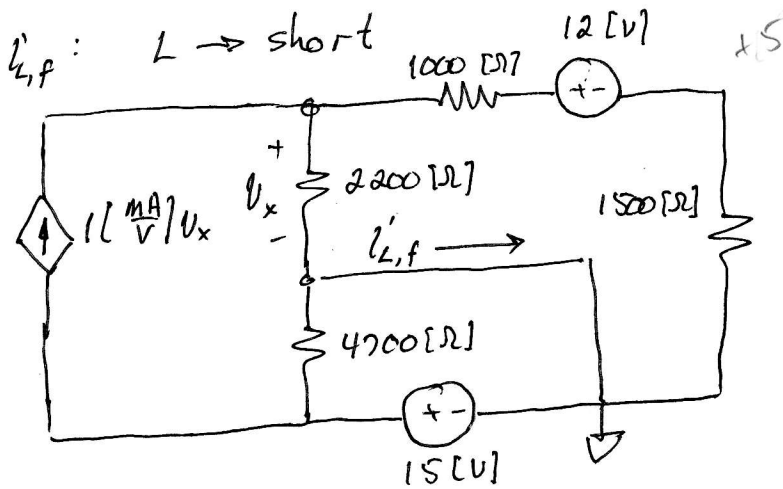
For $t > 3$ [ms] we need $i_{L,f}$ and \mathcal{E}_L :



$$-0.001 V_x + \frac{V_x}{2200} + \frac{V_x - 12}{2500} = 0$$

$$V_x = -33.0 \text{ [V]}$$
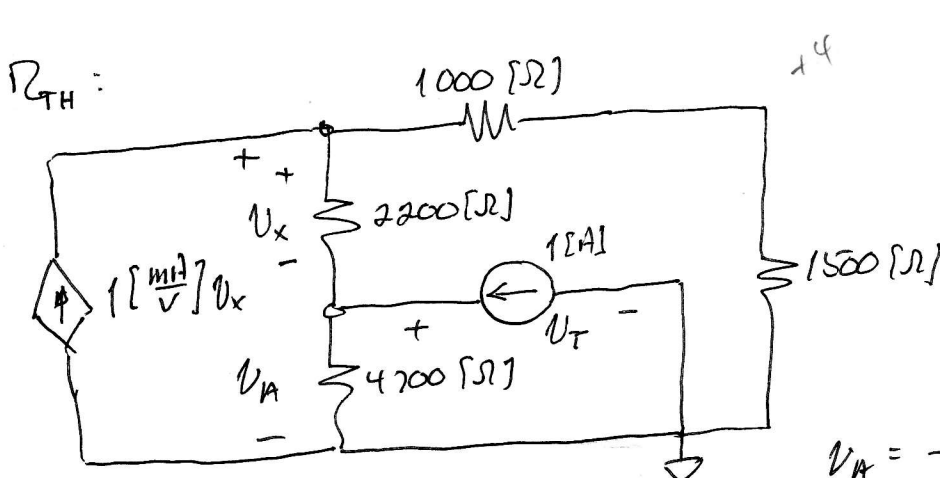
$$i_{L,f} = \frac{V_x}{2200} + \frac{15}{4700} = -11.81 \text{ [mA]}$$



$$\frac{V_T}{4700} - 1 + \frac{V_T - V_A}{2700} = 0$$

$$\frac{V_A - V_T}{2200} + \frac{V_A}{2500} - 0.001 V_x = 0$$

$$V_x = V_A - V_T$$

$$V_A = -3615.4 \text{ [V]} \quad V_x = -2651.3 \text{ [V]}$$

$$V_T = -964.1 \text{ [V]}$$

Room for extra work

Prob 1: d) we need the voltage across C_x ...

$$+b \quad i_c(t) = C_{eq} \frac{dV_c(t)}{dt} = (4.4 \times 10^{-6})(-8) \left(e^{-(t-4[ms])/2.15[ms]} \right) \left(\frac{-1}{2.15 \times 10^{-3}} \right)$$

$$= 0.0164 e^{-(t-4[ms])/2.15[ms]} \quad [A]$$

$$V_{C_x}(t) = \frac{1}{C_x} \int_{4[ms]}^{\infty} i_c(t) dt + V_{C_x}(4[ms])$$

We were given that there was no energy stored in C_x before the switch closed, so $V_{C_x}(4[ms]) = 0$.

$$+b \quad V_{C_x}(t) = \frac{1}{9.8 \times 10^{-6}} \int_{4[ms]}^{\infty} 0.0164 e^{-(t-4[ms])/2.15[ms]} dt = 3.564 [V]$$

$$+1 \quad \therefore \boxed{W_{\text{stored } C_x} = \frac{1}{2} (9.8 \times 10^{-6}) (3.564)^2 = 62.26 [\mu J]}$$

$$\text{Prob 2: } V_T = -964.1 [V] \Rightarrow R_{TH} = -964.1 [\Omega]$$

$$\tau_L = L/R_{TH} = -0.05/964.1 = -0.052 [ms]$$

$$\text{So we have... } i_L(t) = 895.6 [mA] + (-11.81 - 895.6) [mA] e^{+(t-3)/0.052} \quad t \geq 3 [ms]$$

at $t = 3.5 [ms]$,


$$i_L'(t=3.5 [ms]) = -13.6 \frac{kA}{ms} \quad (\text{unrealistically large, but...})$$

$$+2 \quad W = \frac{1}{2} L i_L'^2 = 4.63 \times 10^{-6} [J] \quad (\text{yikes!})$$

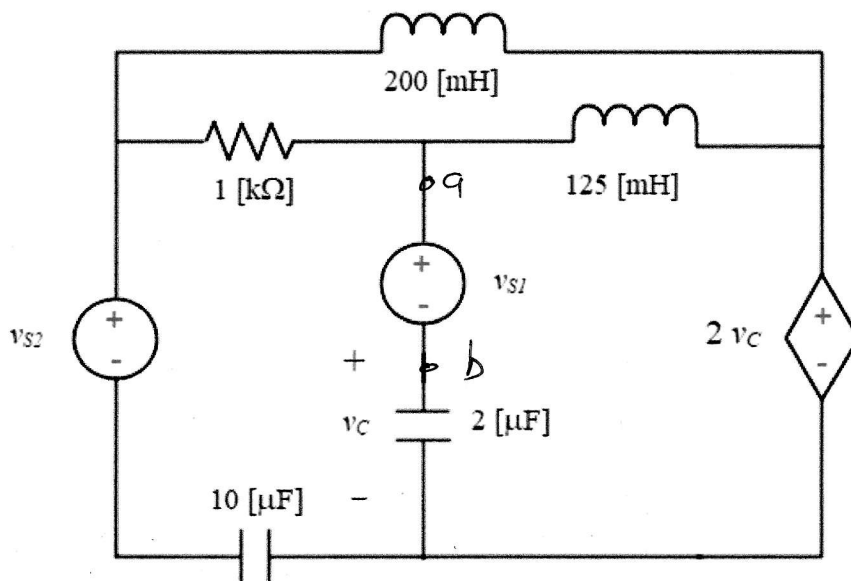
3. [45 points] For the circuit below, the voltage sources are as follows.

$$v_{s1}(t) = 110 \cos(377 t + 20^\circ) \text{ [V]}; \quad v_{s2}(t) = 52 \cos(1000 t) \text{ [V]}$$

- Find the Thevenin equivalent impedance of the circuit below **as seen by the voltage source v_{s1}** at $\omega = 1000$ [rad/s].
- Find the Thevenin equivalent voltage seen by the voltage source v_{s1} .
- Draw the Thevenin equivalent circuit **in the time domain**, using appropriate time domain circuit elements to represent the Thevenin impedance. Clearly label the values of the circuit elements, and the terminals at which you are calculating the equivalent circuit.



Test current source:

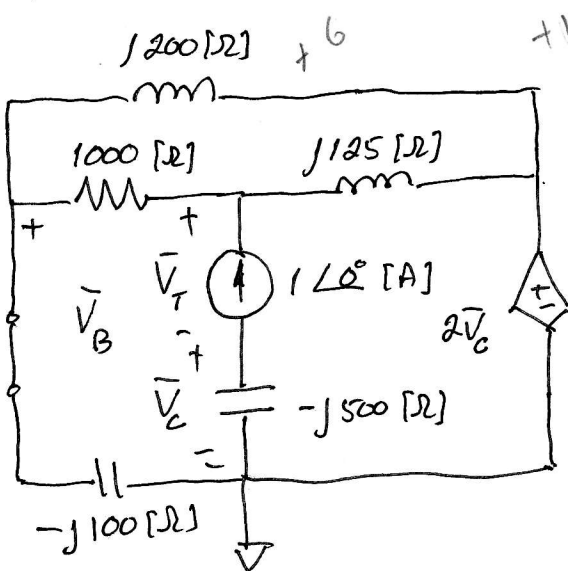

$$\frac{\bar{V}_T + \bar{V}_C - \bar{V}_B}{1000} - 1 + \frac{\bar{V}_T + \bar{V}_C - 2\bar{V}_C}{j125} = 0$$

$$\frac{\bar{V}_B}{-j100} + \frac{\bar{V}_B - \bar{V}_C - \bar{V}_T}{1000} + \frac{\bar{V}_B - 2\bar{V}_C}{j200} = 0$$

$$\bar{V}_C = -(1)(-j500) = j500$$

$$\bar{V}_B = 1056.5 \angle -66.4^\circ \text{ [V]}$$


$$\bar{V}_T = 696.8 \angle 67.2^\circ \text{ [V]}$$

$$\Rightarrow Z_{TH} = 696.8 \angle 67.2^\circ \text{ [}\Omega\text{]}$$

$$= 264.2 + j644.7^\circ \text{ [}\Omega\text{]}$$

Room for extra work

b) \bar{V}_{TH} :

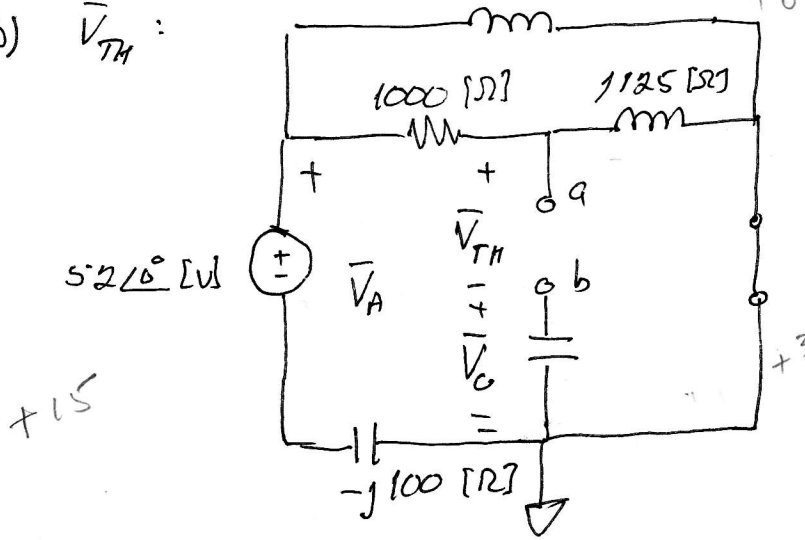

$$\bar{V}_C = 0.$$


$$\frac{\bar{V}_A}{1000 + j125} + \frac{\bar{V}_A}{j200} + \frac{\bar{V}_A - 5.2 \angle 0^\circ}{-j100} = 0$$

$$\bar{V}_A = 104.5 \angle 11.41^\circ \text{ [V]}$$

$$\bar{V}_{TH} = \bar{V}_A \cdot \frac{j125}{j125 + 1000} = 12.96 \angle 94.28^\circ \text{ [V]} \\ = -0.967 + j12.92 \text{ [V]}$$

c)

+10.

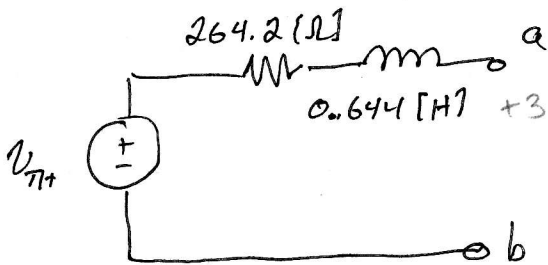

$$V_{TH} = 12.96 \cos(1000t + 94.28^\circ) \text{ [V]}$$

4. [40 points] In this problem, a source V_s is connected to three loads by way of a transmission line with impedance $Z_{Line} = R + jX$. The following is known about the circuit.

Load 1 is absorbing 600 [W] and delivering 750 [VAR].


Load 2 is absorbing 2500 [VA] at a power factor of 0.7 lagging.

Load 3 is a 50 [Ω] resistor in parallel with an impedance of $j200$ [Ω].

$$= 24586 + j 88654 \text{ (VA)}$$

The load voltage V_{L12} is $120\angle-120^\circ$ [V]rms. The source V_s delivers $92\angle74.5^\circ$ [kVA] of power to the line and the three loads combined, and operates at a frequency of 377 [rad/s].

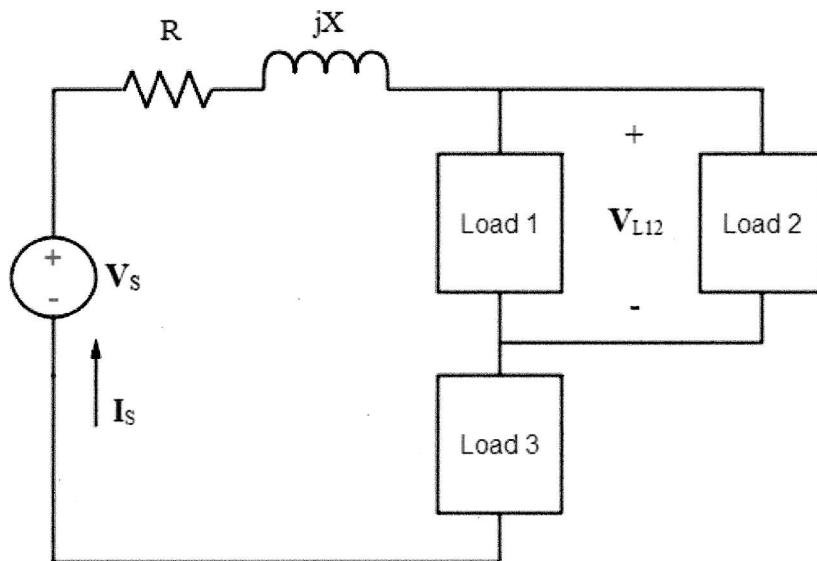- Find I_s .
- Find the complex power absorbed by the transmission line.
- Find the values of the line resistance R and inductance L .



a) we will deal with S absorbed unless otherwise stated.

$$+5 \quad S_1 = 600 - j750 \text{ [VA]}$$

$$= 960.5 \angle -5.34^\circ \text{ [VA]}$$

$$+5 \quad \vec{I}_1^* = \frac{600 - j750}{120 \angle -120^\circ} = 8 \angle 68.87^\circ \text{ [A]}_{rms} \Rightarrow \vec{I}_1 = 8 \angle -68.87^\circ \text{ [A]}_{rms}$$

$$= 2.884 - j7.462$$

$$S_2: \cos(\theta) = 0.7 \Rightarrow \sin(\theta) = \sqrt{1 - 0.7^2} = 0.714$$

$$+5 \quad S_2 = 2500(0.7) + j2500(0.714) = 2500 \angle 45.57^\circ \text{ [VA]}$$

$$\vec{I}_2^* = \frac{2500 \angle 45.57^\circ}{120 \angle -120^\circ} = 20.83 \angle 165.6^\circ \text{ [A]}_{rms}$$

$$+5 \quad \vec{I}_2 = 20.83 \angle -165.6^\circ \text{ [A]}_{rms} \quad 9$$

$$= -20.18 - j5.18 \text{ [A]}_{rms}$$



+2

Room for extra work

$$\vec{I}_3 = \vec{I}_1 + \vec{I}_2 = 21.42 \angle -143.8^\circ \text{ [A]}_{\text{rms}}$$

$$= -17.28 - j12.65 \text{ [A]}_{\text{rms}}$$

b) Find S_3 , then subtract total load power from delivered power to find S_{abs} by line:

+1 $Z_3 = j200 // 50 = 48.57 \angle 14.04^\circ \text{ [\Omega]} = 47.06 + j11.77 \text{ [\Omega]}$

+5 $S_3 = |\vec{I}_3|^2 Z_3 = 22257.2 \angle 14.04^\circ \text{ [VA]} = 21592 + j5399.6 \text{ [VA]}$

+4 $S_{\text{Line}} = S_{\text{del by } V_s} - S_1 + S_2 + S_3 = 82,222 \angle 89.55^\circ \text{ [VA]}$
 $= 643.5 + j82219 \text{ [VA]}$


c) $Z_{\text{Line}} = \frac{S_{\text{Line}}}{|\vec{I}_3|^2} = 179.2 \angle 89.55^\circ \text{ [\Omega]} = 1.403 + j179.2 \text{ [\Omega]}$

+4

+4 $\Rightarrow \left[R = 1.4 \text{ [\Omega]} \right] \quad \left[L = \frac{179.2}{\omega} = 475 \text{ [mH]} \right]$

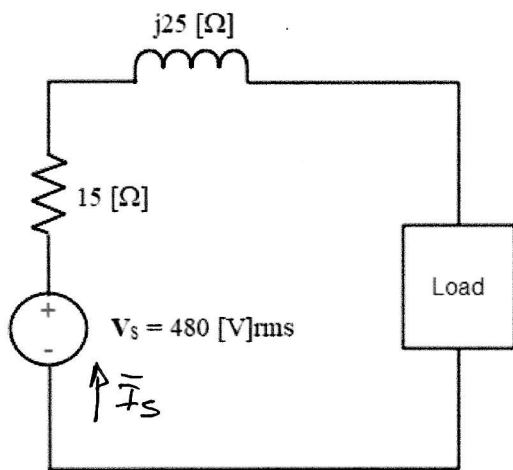5. [35 points] In the circuit below, the power source V_s operates at $\omega = 377$ [rad/s]. The Load is a 100 [Ω] resistor in series with a 300 [mH] inductor.

- Find the ^{complex} power delivered by the source V_s .
- Find the power factor of the load.
- A 20 [μ F] capacitor is added in parallel with the load to adjust the load power factor. Find the new load power factor.
- After adding the capacitor in part c, what now is the power supplied by V_s ?



$$300 \text{ [mH]} \rightarrow j(377)(0.3) = j113.1 \text{ [\Omega]}$$

+5
a)
$$\vec{I}_s = \frac{480}{15 + j25 + 100 + j113.1} = 2.671 \angle -50.22^\circ \text{ [A]}_{\text{rms}}$$

$$= 1.709 - j2.053 \text{ [A]}_{\text{rms}}$$

+5
$$\therefore S_{\text{del by } V_s} = \bar{V}_s \vec{I}_s^* = (480)(2.671 \angle 50.22^\circ) = 1282.1 \angle 50.22^\circ \text{ [VA]}$$

$$= 820.3 + j985.2 \text{ [VA]}$$

b)
$$Z_{\text{Load}} = 100 + j113.1 \text{ [\Omega]} = 150.97 \angle 48.52^\circ \text{ [\Omega]}$$

+3
$$\Rightarrow \text{pf} = \cos(48.52^\circ) = 0.6624$$

c)
$$20 \text{ [\mu F]} \rightarrow -j/\omega c = -j132.6 \text{ [\Omega]}$$

+3 putting this in parallel with $150.97 \angle 48.52^\circ \text{ [\Omega]}$ gives

+4
$$Z'_{\text{Load}} = \frac{(-j132.6)(150.97 \angle 48.52^\circ)}{-j132.6 + 150.97 \angle 48.52^\circ} = 196.5 \angle -30.45^\circ \text{ [\Omega]} = 169.4 + j99.58 \text{ [\Omega]}$$

$$\Rightarrow \text{pf} = \cos(30.45^\circ) = 0.862$$

Room for extra work

+ 5

$$\bar{I}_6' = \frac{480}{15 + j25 + 196.5 \angle -30.45^\circ} = 2.413 \angle 22.02^\circ \text{ [A]}_{\text{rms}}$$
$$= 2.24 + j0.905$$

d)

$$S'_{\text{del by } V_s} = \bar{V}_s \bar{I}_6'^* = 480 (2.413 \angle -22.02^\circ)$$

+ 6

$$= 1158.2 \angle -22.02^\circ \text{ [VA]}$$

+ 2

e) The power delivered by source has been reduced,
so this configuration saves money!