

### EXAMPLE 9.1

For the function  $v(t)$ , find the indicated quantities.

frequency  $v(t) = 40 \cos(2513.27t + 36.87^\circ)$  V

a)  $f = \frac{\omega}{2\pi} = \frac{2513.27}{2\pi} = 400$  Hz

period b)  $T = \frac{1}{f} = 0.002500 = 2.5$  ms

amplitude c)  $V_m = 40$  V

$v(t=0)$  d)  $v(0) = 40 \cos(36.87^\circ) = 32$  V

Phase e)  $\phi = 36.87^\circ \rightarrow \frac{2\pi}{360} \times 36.87 = 0.643$  rad

f) time at which  $v(t) = 0$

$$\cos(2513.27t + 36.87^\circ) = 0$$

$$2513.27t + 0.643 = 1.5708$$

$$t = \frac{1.5708 - 0.643}{2513.27} = 368.96 \mu\text{s}$$

g) time at which  $\frac{dv}{dt} = 0$

$$\frac{dv}{dt} = -40(2513.27) \sin(2513.27t + 36.87^\circ) = 0$$

$$2513.27t + 0.643 = 0$$

$$t = -255.84 \mu\text{s}$$

or  $2513.27t + 0.643 = 3.1415$

$$t = 994.16 \mu\text{s}$$

### Example 9.2

Find the phasor transform of each time-domain function.

a)  $v(t) = 170 \cos(377t - 40^\circ) \text{ V}$

$$v(t) = \operatorname{Re} \{ 170 e^{j377t} e^{-j40^\circ} \}$$

$$\therefore \bar{V} = 170 \angle -40^\circ \text{ V}$$

b)  $i(t) = 10 \sin(1000t + 20^\circ) \text{ A}$

Since our transforms are being defined in terms of cosine and not sine, we need to convert:

$$i(t) = 10 \cos(1000t + 20^\circ - 90^\circ) \text{ A}$$

$$= 10 \cos(1000t - 70^\circ) \text{ A}$$

$$\therefore \bar{I} = 10 \angle -70^\circ \text{ A}$$

c)  $i(t) = 5 \cos(\omega t + 36.87^\circ) + 10 \cos(\omega t - 53.13^\circ) \text{ A}$

$$\bar{I} = 5 \angle 36.87^\circ + 10 \angle -53.13^\circ \text{ A}$$

We could add these directly with a calculator but let's do it manually to see what's involved.

$$5 \angle 36.87^\circ = 5 \cos 36.87^\circ + j 5 \sin 36.87^\circ$$

$$= 4.0 + j 3.0$$

$$\begin{aligned} 10 \angle -53.13^\circ &= 10 \cos(-53.13^\circ) + j 10 \sin(-53.13^\circ) \\ &= 6.0 - j 8.0 \end{aligned}$$

Adding real and imaginary parts gives

$$\bar{I} = (4.0 + j 3.0) + (6.0 - j 8.0) = 10.0 - j 5.0 \text{ A}$$

Now we transform back:

$$\phi = \tan^{-1} \frac{-5}{10} = -26.57^\circ$$

$$r = \sqrt{10^2 + 5^2} = 11.18 \text{ A}$$

$$\therefore \bar{I} = 11.18 \angle -26.57^\circ \text{ A}$$

We can go back to the time domain:

$$i(t) = 11.18 \cos(\omega t - 26.57^\circ) \text{ A}$$

### Example 9.3

Find the equivalent impedance at a, b.



Solution: Transform to phasor domain:

$$C \rightarrow \frac{1}{j\omega C} = -j/\omega C$$

$$L \rightarrow j\omega L$$


$$R \rightarrow R$$

a)  $\omega = 1000 \text{ [rad/s]}$

$$10 \mu\text{F} : -j/\omega C = -j/(1000 \cdot 10 \times 10^{-6}) = -j 10^2 \Omega$$

$$50 \text{ mH} : j\omega L = j(1000 \cdot 50 \times 10^{-3}) = j 50 \Omega$$

so we have

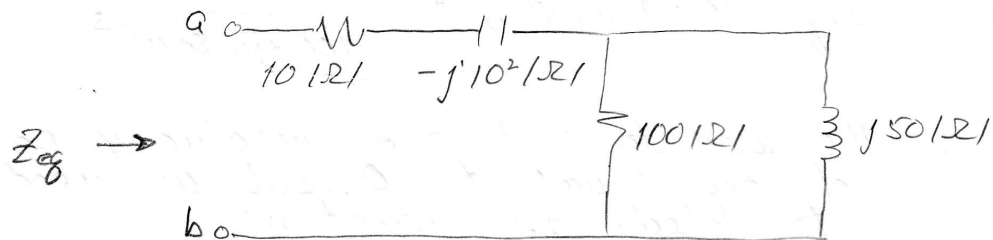

$$\begin{aligned}
 \text{and } Z_{eq} &= 10 + (-j10^3) + 100 \parallel j50 \\
 &= 10 - j100 + \frac{100(j50)}{100 + j50} \\
 &= 10 - j100 + (20 + j40) \\
 &= 30 - j60 \text{ } \Omega
 \end{aligned}$$

$$\omega = 4000 \text{ rad/s}$$

$$\begin{aligned}
 \text{b) } 10 \mu\text{F} &= -j/\omega C = -j/(4000 \cdot 10 \times 10^{-6}) = -j25 \text{ } \Omega \\
 50 \text{ mH} &= j\omega L = j(4000 \cdot 10 \times 10^{-3}) = j200 \text{ } \Omega
 \end{aligned}$$

$$Z_{eq} = 10 - j25 + \frac{100(j200)}{100 + j200}$$

$$\begin{aligned}
 &= 10 - j25 + (80 + j40) \\
 &= 90 + j15 \text{ } \Omega
 \end{aligned}$$

At what  $\omega$  is  $Z_{eq}$  purely resistive?

c) Purely resistive  $\Rightarrow Z = R + jX \rightarrow 0$  i.e. there is no imaginary part. Thus

$$Z_{eq} = 10 - j/10 \times 10^{-6} \omega + \frac{100(j\omega 50 \times 10^{-3})}{100 + j\omega 50 \times 10^{-3}}$$

We need to set the imaginary part of  $Z_{eq}$  equal to 0, but we need to clear the fraction:

(Example 9.3 cont)

$$\frac{100(j\omega 50 \times 10^{-3})}{100 + j\omega 50 \times 10^{-3}} \cdot \frac{100 - j\omega 50 \times 10^{-3}}{100 - j\omega 50 \times 10^{-3}}$$

$$= \frac{j\omega 50 \cdot (100 - j\omega 50 \times 10^{-3})}{100^2 + (\omega 50 \times 10^{-3})^2}$$

$$= \frac{j\omega 5000 + \omega 0.250}{10^4 + \omega^2 2.5 \times 10^{-3}}$$

$$\text{So } \Im\{z_{eq}\} = -1/\omega 10 \times 10^{-6} + \frac{\omega 5000}{10^4 + \omega^2 2.5 \times 10^{-3}} = 0.$$

$$-(10^4 + \omega^2 2.5 \times 10^{-3}) + \omega^2 5.0 \times 10^{-3} = 0$$


$$\omega^2 (2.5 \times 10^{-3}) = 10^4$$

$$\omega^2 = 4 \times 10^6$$

$$\omega = \underline{\underline{2 \times 10^3 \text{ rad/s}}}$$

Example 9.4

Find  $v_o(t)$ .

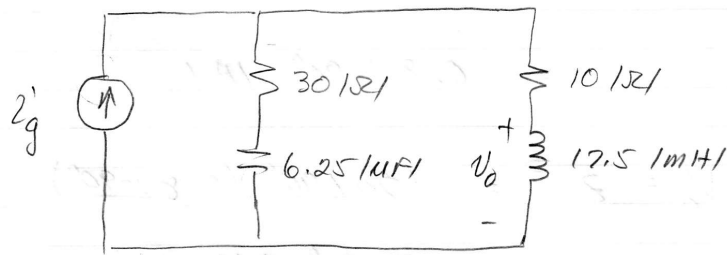

GIVEN:  $i_g = 0.8 \cos 4000t \text{ A}$


SOLUTION: Transform to phasor domain:

$$i_g: \bar{I}_g = 0.8 \angle 0^\circ \text{ A}$$

$$C: -j/\omega C = -j/(4000 \times 6.25 \times 10^{-6}) = -j40 \Omega$$

$$L: j\omega L = j(4000 \times 17.5 \times 10^{-3}) = j70 \Omega$$

so we have:

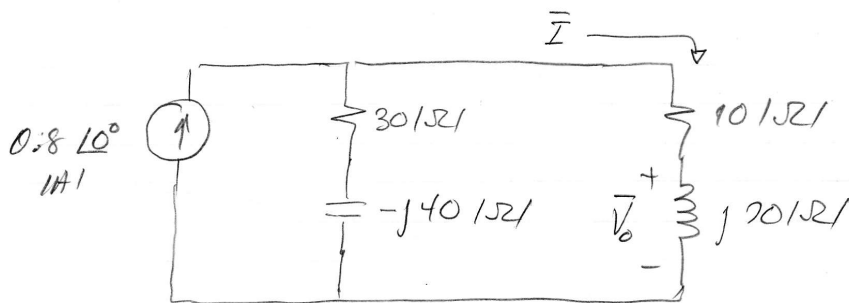

$$\bar{I} = 0.8 \angle 0^\circ \cdot \frac{30 - j40}{(10 + j70) + (30 - j40)}$$

$$\bar{I} = 0.8 \angle 0^\circ \cdot \frac{30 - j40}{40 + j30}$$

$$= 0.8 \angle -90^\circ \text{ A}$$

$$\bar{V}_0 = Z \bar{I} = (70 \angle 90^\circ)(0.8 \angle -90^\circ)$$


$$= 56 \angle 0^\circ \text{ V}$$

Inverse Transform:

$$v_0(t) = 56 \cos(4000t + 0^\circ) \text{ V}$$




### Example 9.5

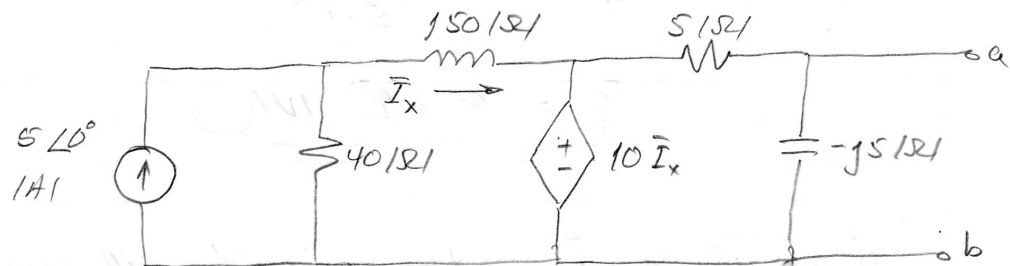

Find the Thevenin Equivalent circuit at a, b.

Source transformation:

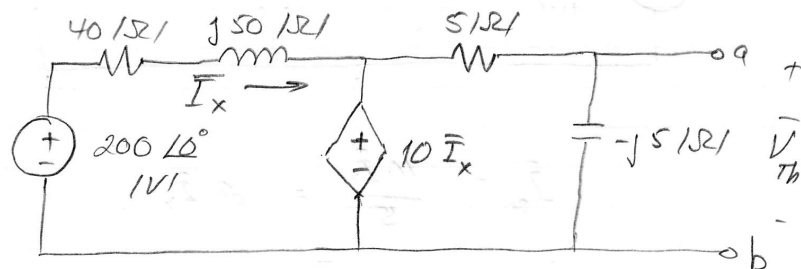

Voltage divider rule applies here:

$$\vec{V}_{Th} = 10 \vec{I}_x \cdot \frac{-j5}{5-j5} \quad (1)$$

$$-\vec{I}_x = \frac{10 \vec{I}_x - 200}{40+j50} \quad (2)$$


$$(2) \Rightarrow -(40+j50) \vec{I}_x = 10 \vec{I}_x - 200$$

$$\vec{I}_x = \frac{80-j100}{45-j5} = 2.83 \angle -45^\circ \text{ A}$$

Then 
$$\bar{V}_{Th} = \frac{(28.3 \angle -45^\circ) \times 5 \angle -90^\circ}{5 - j5}$$

$$\bar{V}_{Th} = \underline{20 \angle -90^\circ \text{ V}}$$

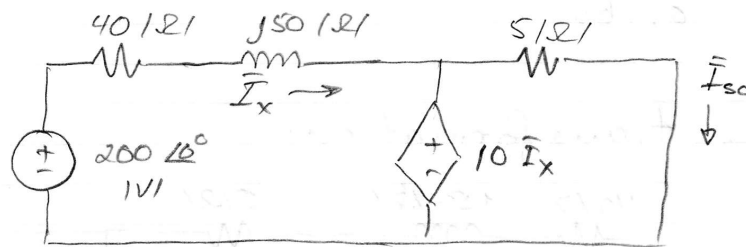If we find  $\bar{I}_{sc}$ , the circuit will simplify because  $-j5$  will be shorted out:



$$\bar{I}_{sc} = \frac{10 \bar{I}_x}{5} = 2 \bar{I}_x$$

$$-\bar{I}_x = \frac{10 \bar{I}_x - 200}{40 + j50} \quad (\text{same as before})$$

$$= 2.83 \angle -45^\circ \text{ A}$$

$$\bar{I}_{sc} = 5.66 \angle -45^\circ \text{ A}$$

$$\therefore \underline{\underline{Z_{Th}}} = \frac{\bar{V}_{Th}}{\bar{I}_{sc}} = \frac{20 \angle -90^\circ}{5.66 \angle -45^\circ} = \underline{\underline{2.5 - j2.5 \ \Omega}}$$

Note the use of  $Z_{Th}$  as a generalization of  $R_{Th}$ .