
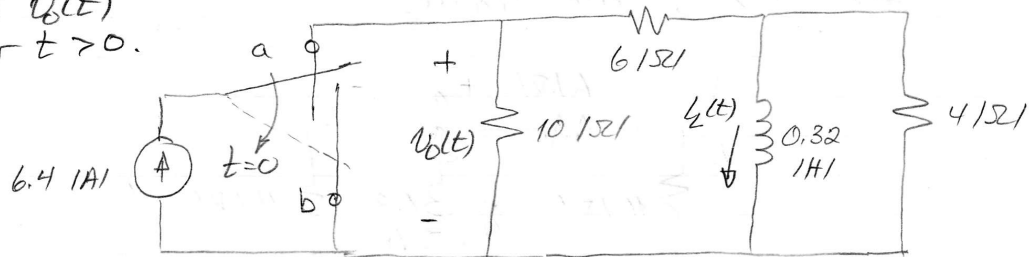


PROBLEM 7.1

a) Find $v(t)$ for $t > 0$.

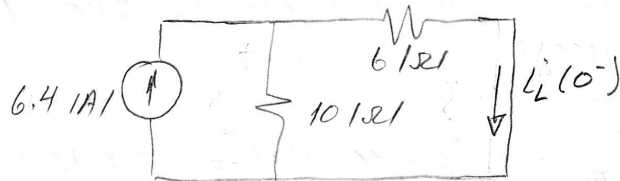

a) For $t < 0$ the inductor acts like a short, so the equivalent circuit is




We solve for current in the inductor first, then find $v(t)$.

Reason: We can find inductor current for $t = 0^+$ because we know there is no instantaneous change in inductor current. We have no such restriction on v_0 so finding v_0 for $t = 0^+$ is tricky.

$$\text{So, } i_L(0^-) = i_L(0^+) = 6.4 \cdot \frac{10}{10+6} = 4 \text{ A}$$

For $t > 0$, we have

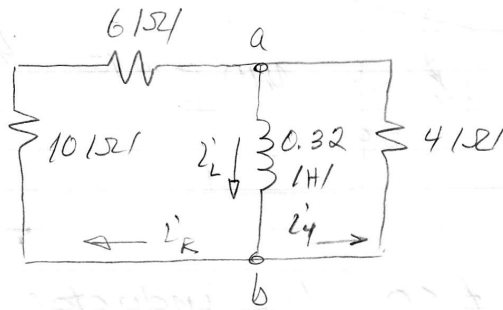

Inductor "sees" a resistance at the terminals a, b which is the Thevenin resistance:

$$R_{Th} = (6 + 10) \parallel 4 = 3.2 \Omega$$

$$\therefore \tau = L/R_{Th} = 0.32/3.2 = 0.1 \text{ s}$$

$$i_L(0^+) = i_L(0^-) = 1 \text{ A}, \text{ and } i_L(t) = 1 \text{ A} e^{-t/\tau}$$

$$\therefore i_L(t) = 4 e^{-10t} \text{ A} \quad t \geq 0 \text{ s}$$

Now, CDR \Rightarrow

$$i_R' = i_L' \cdot \frac{4}{16+4} = 0.8 e^{-10t} \text{ A}$$

$$\text{So } \underline{\underline{V_o(t) = -10 i_R' = -8 e^{-10t} \text{ V} \quad t \geq 0 \text{ s}}}$$

(PROBLEM 7.1 cont)

Let's look at $v_o(0^-)$ and $v_o(0^+)$:

Note that before $t=0$, we had

$$v_o(0^-) = 10 \left[6.4 \times \frac{6}{16} \right] = 24.0 \text{ V}$$

This is $v_o(0^-)$. From our solution above,

$$v_o(0^+) = -8 \text{ V}$$

So clearly $v_o(0^-) \neq v_o(0^+)$!

b) Find the percent of the initial inductor energy that is dissipated in the $4 \text{ }\Omega$ resistor.

$$w_L = \frac{1}{2} L i_L(0^+)^2 = \frac{1}{2} (0.32)(4)^2 = 2.56 \text{ J}$$

in $4 \text{ }\Omega$ resistor

$$i_4 = i_L \frac{16}{20} = 3.2 e^{-10t} \text{ A} \quad t \geq 0 \text{ s}$$

$$\therefore P_{\text{diss}} = i_4^2 R = (10.24)(4) e^{-20t} \text{ W} \quad t \geq 0 \text{ s}$$

Total energy dissipated in $4 \text{ }\Omega$ is


$$W = \int_0^{\infty} 40.96 e^{-20t} dt = 2.048 \text{ J}$$

So % dissipated in $4 \text{ }\Omega$ is

$$\frac{2.048}{2.56} = 0.8 \Rightarrow \underline{\underline{80\%}}$$

↗

Another approach:

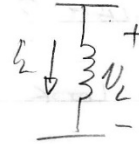


$$\begin{aligned}V_L(t) &= L \frac{di_L}{dt} = 0.32 \frac{d}{dt} (4e^{-10t}) \\&= -3.2 (4) e^{-10t} \\&= -12.8 e^{-10t} \text{ V} \quad t > 0 \text{ s}\end{aligned}$$

Now by VDR:

$$\begin{aligned}V_0 &= V_L \cdot \frac{10}{10+6} \\&= -8 e^{-10t} \text{ V} \quad t > 0 \text{ s}\end{aligned}$$

PROBLEM 7.2

a) Find $V_0(t)$ for $t > 0$.

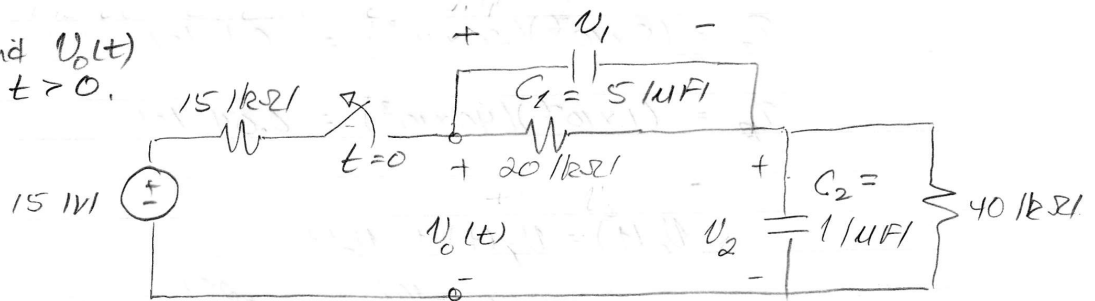


a) For $t < 0$, there is no current in the capacitors, so

$$V_1(0^-) = V_1(0^+) = 15 \cdot \frac{20}{20 + 40 + 15} = 4 \text{ V} \equiv V_{01}$$

$$V_2(0^-) = V_2(0^+) = 15 \cdot \frac{40}{20 + 40 + 15} = 8 \text{ V} \equiv V_{02}$$

Now for $t \geq 0$, we have

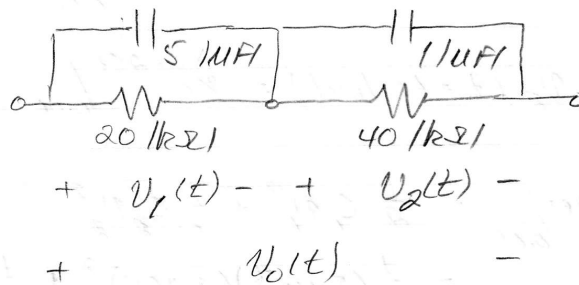

We can treat this problem as two separate RC circuits, i.e.

→

$$\tau_1 = (5 \times 10^{-6})(20 \times 10^3) = 0.1 \text{ s}$$

$$\tau_2 = (1 \times 10^{-6})(40 \times 10^3) = 0.04 \text{ s}$$

$$\begin{aligned} V_0(t) &= V_1(t) + V_2(t) \\ &= 4e^{-10t} + 8e^{-25t} \text{ V} \quad t \geq 0 \text{ s} \end{aligned}$$

b) Find the percent of the initial energy in the capacitors that is dissipated after 60 ms.

$$\begin{aligned} W &= \frac{1}{2} C_1 V_{01}^2 + \frac{1}{2} C_2 V_{02}^2 \\ &= \frac{1}{2} (5 \times 10^{-6})(4)^2 + \frac{1}{2} (1 \times 10^{-6})(8)^2 \\ &= 7.2 \times 10^{-5} \text{ J} \end{aligned}$$

After 60 ms:

$$V_1(t=60 \text{ ms}) = 4e^{-10t} \Big|_{0.06} = 2.195 \text{ V}$$

$$V_2(t=60 \text{ ms}) = 8e^{-25t} \Big|_{0.06} = 1.785 \text{ V}$$


$$\begin{aligned} \therefore w \Big|_{0.06} &= \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 \\ &= \frac{1}{2} (5 \times 10^{-6})(2.195)^2 + \frac{1}{2} (1 \times 10^{-6})(1.785)^2 \\ &= 1.364 \times 10^{-5} \text{ J} \end{aligned}$$

So percent dissipated is

$$1 - \frac{1.364}{7.200} = \underline{\underline{81.06\%}}$$

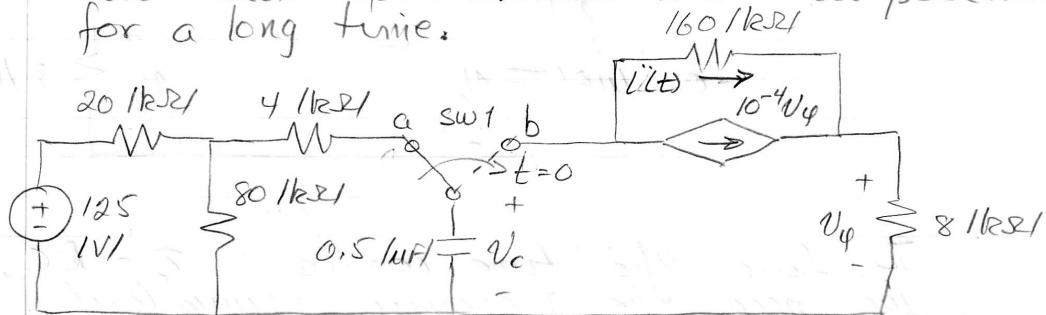
PROBLEM 7.3

For the circuit shown, find $v_c(t)$ and $i(t)$ for $t > 0$. SW1 was in position a for a long time.



We will find $v_c(t)$ first, and use this information to find $i(t)$.

Find initial conditions:

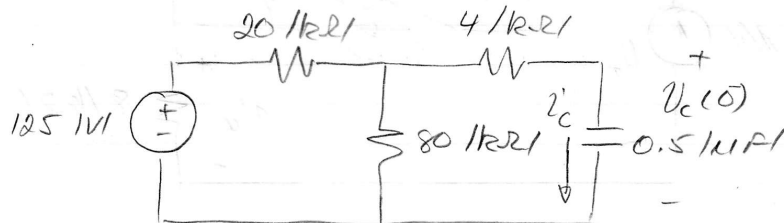


Since SW1 was in position a for a long time, $i'_c = 0$, so


$$v_c(0^+) = v_c(0) = 125 \cdot \frac{80 \times 10^3}{(80 + 20) \times 10^3} = 100 \text{ V}$$

Now for $t > 0$...

$t > 0$

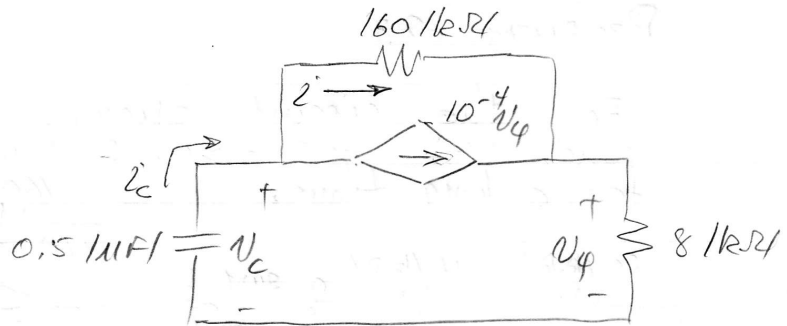

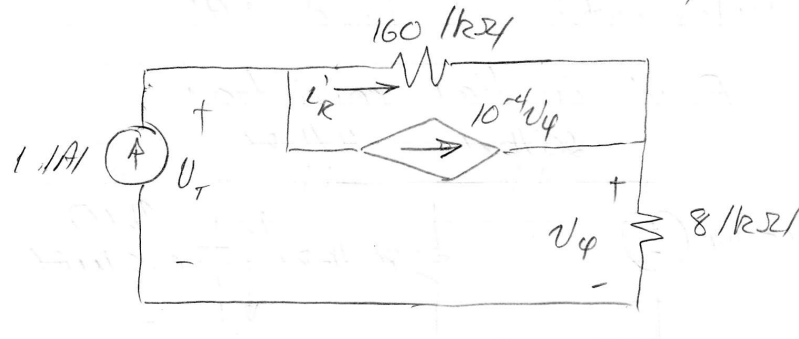To find the time constant $\tau_c = RC$, we need the Thevenin equivalent resistance as seen at the capacitor terminals: Use a test source for this:



$$\text{Thus } V_p = 8 \times 10^3 \cdot 1 \text{ V}$$

$$i'_R + 10^{-4} V_p = 1$$

$$i'_R = 1 - 0.8 = 0.2 \text{ A}$$

$$\therefore V_T = 160 \times 10^3 i'_R + V_p$$

$$= 3.2 \times 10^4 + 8 \times 10^3 = 4 \times 10^4 \text{ V}$$

$$\therefore R_{Th} = V_{T/1} = 40 \text{ k}\Omega$$

PROBLEM 7.3

$$\tau = R_{Th} \cdot C = (4 \times 10^4)(0.5 \times 10^{-6}) = 20 \text{ ms}$$

Thus

$$V_c(t) = 100 e^{-t/20 \times 10^{-3}} \text{ [V]}$$

⇒

$$V_c(t) = 100 e^{-50t} \text{ V} \quad |t| \geq 0 \text{ s}$$

Now referring back to the $t > 0$ figure,

$$\begin{aligned} i_c' &= -C \frac{dV_c}{dt} \\ &= -(5 \times 10^{-7})(-5000) e^{-50t} \\ &= 0.0025 e^{-50t} \text{ A} \quad |t| > 0 \text{ s} \end{aligned}$$


$$\text{Thus } V_q = 8000 i_c' = 20 e^{-50t} \text{ V}$$

$$i_c'(t) + 10^{-4} V_q = i_c'$$


$$\begin{aligned} \therefore i_c'(t) &= i_c' - 10^{-4} (20 e^{-50t}) \\ &= (2.5 - 2.0) \times 10^{-3} \times e^{-50t} \end{aligned}$$

$$i_c'(t) = 5 \times 10^{-4} e^{-50t} \text{ A} \quad |t| \geq 0 \text{ s}$$

PROBLEM 7.4
 a) Find $v_C(t=0^+)$.

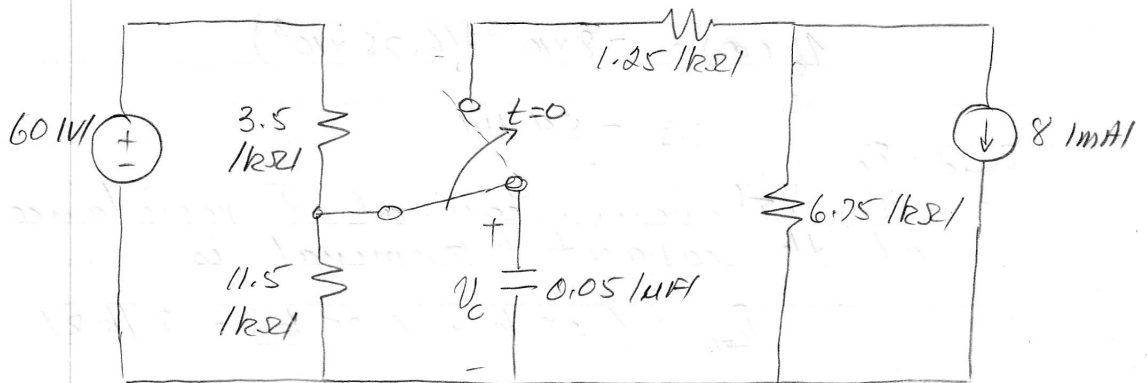


a) For $t < 0$, we have

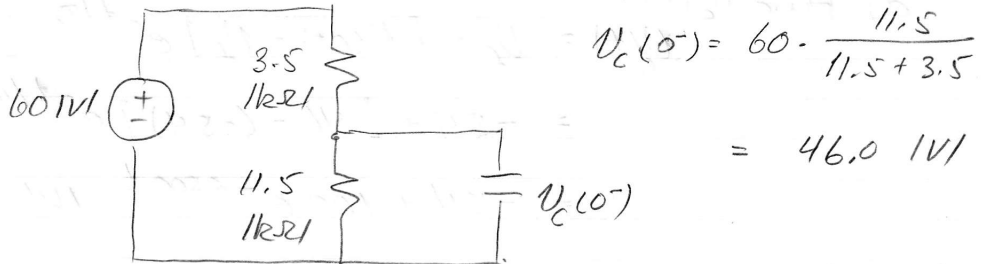

So $v_C(t=0^+) = v_C(t=0^-) = 46 \text{ V}$

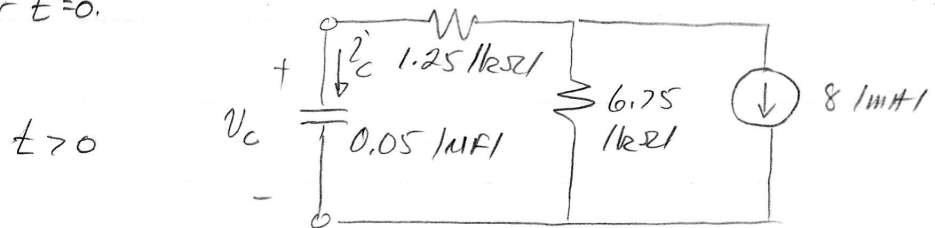b) Find $v_C(\infty)$, i.e., the steady state value of v_C , after $t=0$.



After a long time, $i_c \rightarrow 0$, so

$$V_c(\infty) = -8 \times 10^{-3} \cdot (6.75 \times 10^3) \\ = -54 \text{ V}$$

c) Find τ_c .

The Thevenin equivalent resistance at the capacitor terminals is

$$R_{Th} = (1.25 \text{ k} + 6.75 \text{ k}) = 8 \text{ k}\Omega$$

$$\therefore \tau = R_{Th} C = 8000 (0.05 \times 10^{-6}) \\ = 400 \text{ }\mu\text{s}$$

d) Find $V_c(t)$.

$$V_c(t) = V_f + [V(0^+) - V_f] e^{-t/\tau_c} \\ = -54 + [46 - (-54)] e^{-t/400 \times 10^{-6}} \\ = -54 + 100 e^{-2500t} \text{ V} \quad t \geq 0 \text{ s}$$


So $V_c(t) = 0$

$$\Rightarrow -54 + 100 e^{-2500t} = 0$$




$$t = -\frac{\ln(54/100)}{2500} = 246.5 \text{ }\mu\text{s}$$

PROBLEM 7.5

Find $i(t)$.

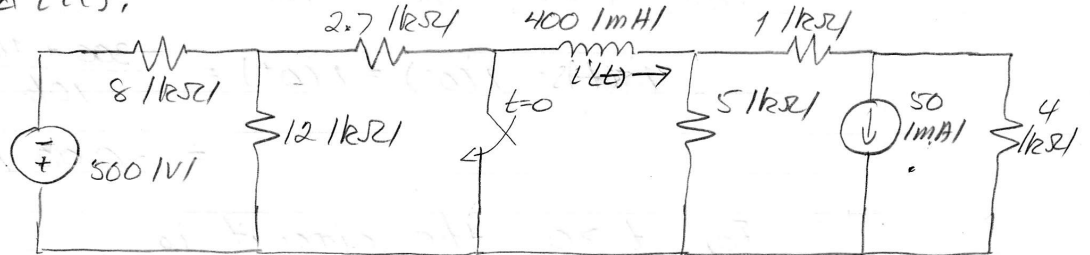

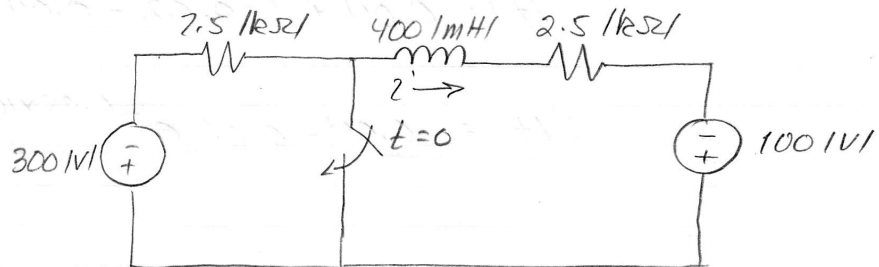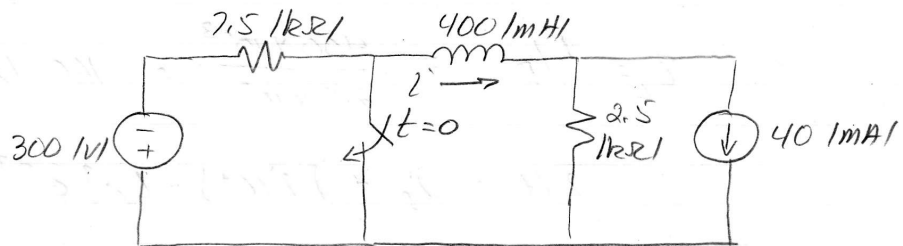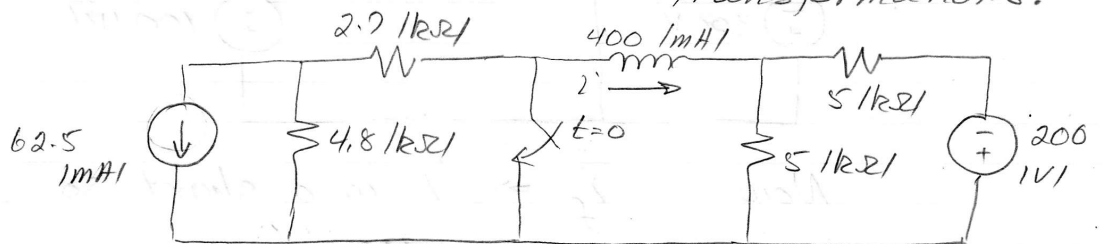This looks like a job for source transformations!




For $t < 0$, we have

$$i'(t) = i'(0^-) = i'(0^+) = \frac{-300 + 100}{10k}$$

$$= -0.02 \text{ A}$$

For $t > 0$ the circuit is

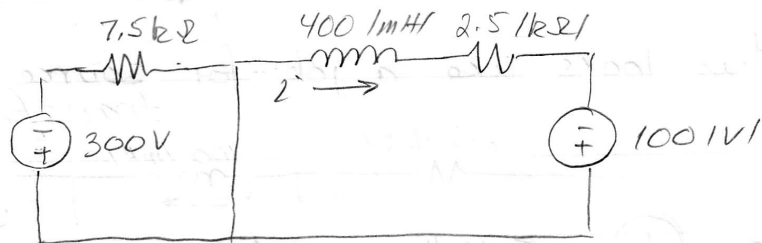

Now $i'_f \Rightarrow L$ is a short so

$$i'_f = \frac{100}{2.5k} = 0.04 \text{ A}$$

$$\tau_L = L/R = \frac{400 \times 10^{-3}}{2.5 \times 10^3} = 160 \text{ μs}$$

$$i'(t) = i'_f + [i'(0^+) - i'_f] e^{-t/\tau_L}$$

$$i'(t) = 0.04 + (-0.02 - 0.04) e^{-t/160 \times 10^{-6}} \quad \text{A} \quad t > 0 \text{ s}$$

$$i'(t) = 0.04 - 0.06 e^{-6.25 \times 10^3 t} \quad \text{A} \quad t > 0 \text{ s}$$