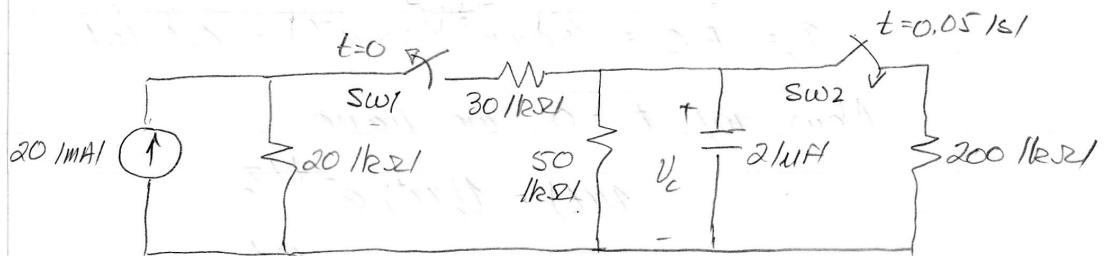



PROBLEM 7.6



SW1 has been closed and SW2 open for a long time.

a) Find $v_c(t)$ for $0 \leq t \leq 0.05$ s

Draw circuit for $t < 0$:

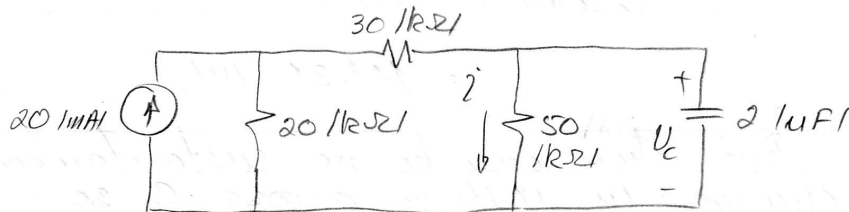

C is an open circuit, so $v_c = 50 \times 10^3 \cdot i$

CDR:

$$i = (20 \times 10^{-3}) \cdot \frac{20 \text{ k}}{20 \text{ k} + 80 \text{ k}} = 4 \times 10^{-3} \text{ A}$$

$$\therefore v_c(0^-) = v_c(0^+) = i \cdot 50 \text{ k}\Omega = 200 \text{ V}$$

Re-draw for $0 \leq t \leq 0.05$ s:



$$\tau_c = RC = (50 \times 10^3)(2 \times 10^{-6}) = 0.1 \text{ s}$$

Now w/ $t_0 = 0$ we have

$$V(t) = V_c(0^+) e^{-t/\tau_c}$$

$$V(t) = 200 e^{-10t} \text{ V}, \quad 0 \leq t \leq 0.05 \text{ s}$$

b) Find $V_c(t)$ for $t \geq 0.05 \text{ s}$

Just before $t = 0.05 \text{ s}$, we have


$$V_c(0.05^-) = 200 e^{-10(0.05)}$$

$$= 121.31 \text{ V}$$

But there can be no instantaneous change in voltage across C so

$$V_c(0.05^+) = 121.31 \text{ V}$$

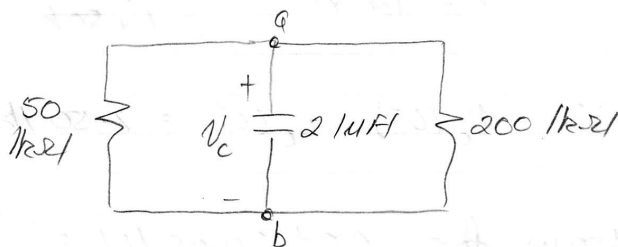Now for $t \geq 0.05 \text{ s}$ the circuit is



Now R at the capacitor terminals is

$$R = 200 \text{ k} \parallel 50 \text{ k} = 40 \text{ k}\Omega$$

$$\therefore \tau_c = RC = 0.08 \text{ s}$$

(PROBLEM 7.6 cont)

$$\text{So ... } V_c(t) = 121.31 e^{-(t-0.05)/0.08} \text{ V,} \\ t \geq 0.05 \text{ s}$$

c) Find total energy dissipated in 50 k Ω

$$P_{abs} = V_c^2 / 50 \times 10^3$$

$$W = \int_0^{0.05} \frac{(200)^2}{50 \times 10^3} e^{-20t} dt + \int_{0.05}^{\infty} \frac{(121.31)^2}{50 \times 10^3} e^{-25(t-0.05)} dt$$

$$= 0.8 \int_0^{0.05} e^{-20t} dt + 0.294 e^{1.25} \int_{0.05}^{\infty} e^{-25t} dt$$

$$= -4 \times 10^{-2} e^{-20t} \Big|_0^{0.05} - \frac{1.03}{25} e^{-25t} \Big|_{0.05}^{\infty}$$

$$= 25.28 \text{ mJ} + 11.75 \text{ mJ}$$

$$= 37.03 \text{ mJ}$$

d) Find total energy dissipated in 200 k Ω


$$W = \int_{0.05}^{\infty} \frac{(121.31)^2}{200 \times 10^3} e^{-25(t-0.05)} dt$$

$$= (2.36 \times 10^{-2}) e^{1.25} \int_{0.05}^{\infty} e^{-25t} dt$$

$$= \frac{-0.257}{25} e^{-25t} \Big|_{0.05}^{\infty}$$

$$= 2.94 \text{ mJ}$$


PROBLEM 7.7

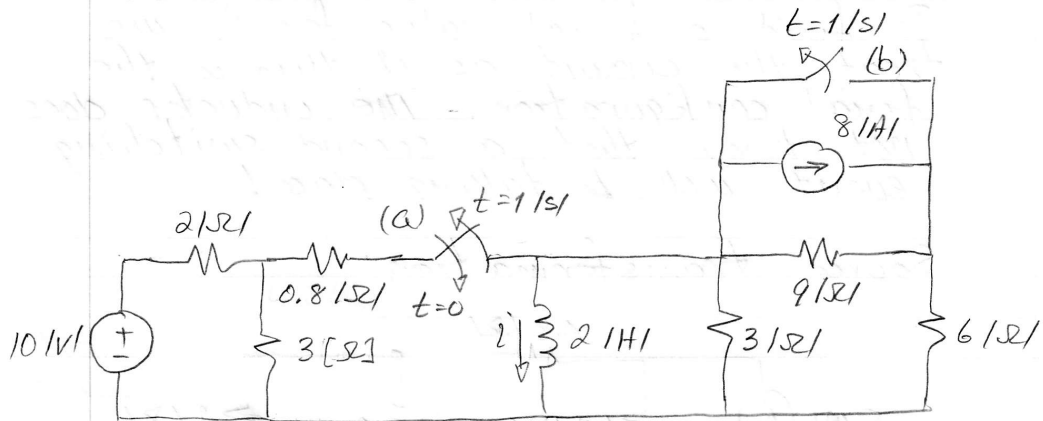

Switch a was open and b closed for a long time.


a) Find $i(t)$ for $0 \leq t \leq 1/s$

For $t < 0$ we have

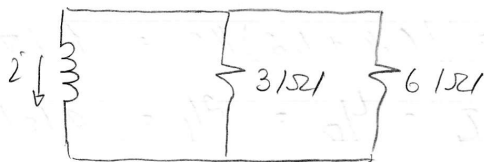

So $i(0^-) = i(0^+) = 0$.


For $0 \leq t \leq 1/s$ we re-draw:

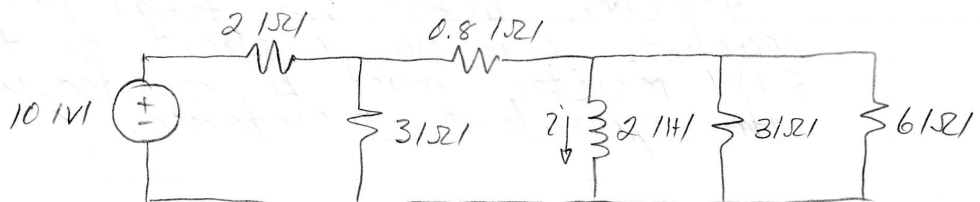

Note: This is a step-response problem!

To find a final value for i , we treat the circuit as if this is the final configuration. The inductor does not know that a second switching event will be taking place!

Source transformation:

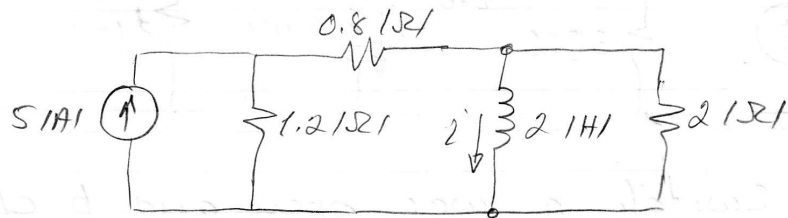

"Final value" \Rightarrow L becomes a short.

Then,

$$i_f = 5 \cdot \frac{1.2}{1.2 + 0.8} = 3 \text{ A}$$

$$R = (0.8 + 1.2) \parallel 2 = 1 \text{ ohm}$$

$$\therefore \tau = L/R = 2 \text{ H} = 2 \text{ s}$$

Note: In calculating i_f , L is a short so the 2 ohm resistor is shorted out.

However, before the final value is reached, L is not a short, so the 2 ohm resistor must be counted in the equivalent resistance.

(PROBLEM 7.7 con't)

Finally,

$$i(t) = i_f + [i(0^+) - i_f] e^{-t/\tau}$$

$$i(t) = 3 + (0 - 3) e^{-t/2}$$


$$i(t) = 3(1 - e^{-0.5t}) \text{ A}, \quad 0 \leq t \leq 1 \text{ s}$$

b) Find $i(t)$ for $t \geq 1 \text{ s}$.

At $t = 1 \text{ s}$ we have

$$i(t) = 3(1 - e^{-0.5(1)}) = 1.18 \text{ A} = i(1^+)$$

Re-draw for $t \geq 1 \text{ s}$

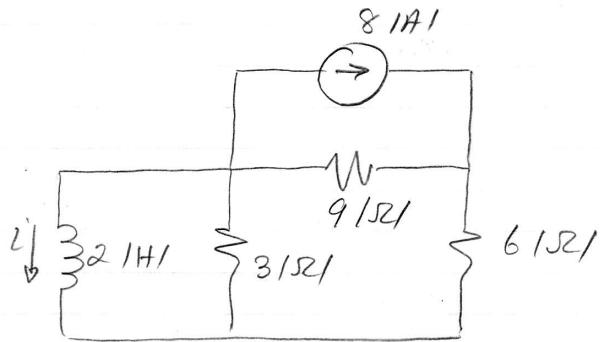

Final value $\Rightarrow L$ becomes a short \Rightarrow
 3 ohm is shorted out and:

$$i = -8 \cdot \frac{9}{9+6} = -\frac{72}{15} = -4.8 \text{ A}$$

$$R = (9+6) \parallel 3 = 2.5 \text{ } \Omega$$

$$\tau_L = L/R = 0.8 \text{ s}$$

$$i(t) = i_f + [i_f' - i(t)] e^{-(t-1)/\tau_L}$$


$$i(t) = -4.8 + [1.18 - (-4.8)] e^{-(t-1)/0.8}$$

$$i(t) = -4.8 + 5.98 e^{-1.25(t-1)} \text{ A}$$

$$1 \leq t \text{ s}$$

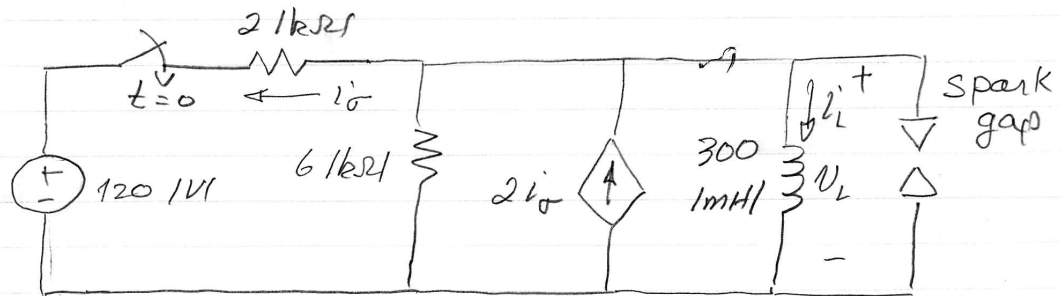
Problem 7.8

The switch in the circuit below was open for a long time and then closed at $t=0$. The spark gap will break down (i.e., arc over and create a short) when the voltage across it reaches 36 kV. How long after the switch closes will arcing occur?



$$i_L(0^-) = i_L(0^+) = 0$$

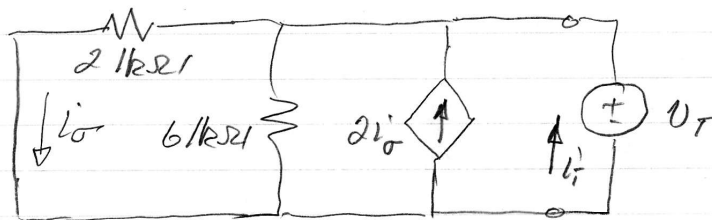
Theremin resistance at the terminals of the inductor for $t > 0$.



$$\begin{aligned} i_σ &= \frac{V_T}{2000} ; & i_T &= -2i_σ + 2i_σ + \frac{V_T}{6000} \\ & & &= -\frac{V_T}{2000} + \frac{V_T}{6000} \\ & & &= -V_T (-3.333 \times 10^{-4}) \end{aligned}$$

$$\therefore R_{Th} = \frac{U_T}{I_T} = -3 \text{ k}\Omega \Rightarrow \tau = -10^{-4} \text{ s}$$

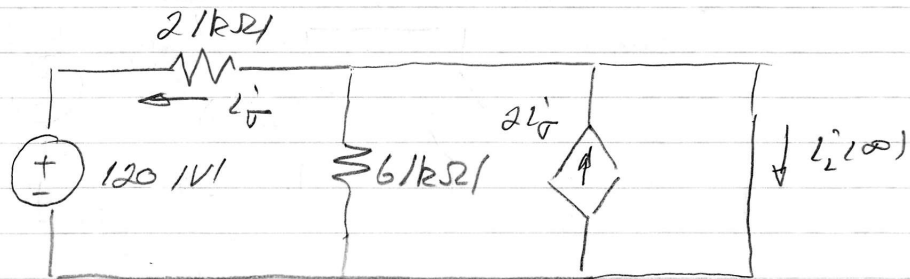To find $i_L(\infty)$ we set L to a short:



$$i_T = -\frac{120}{2000} = -60 \text{ mA}$$

$$i_L(\infty) = 2i_T - i_T = -60 \text{ mA}$$

$$\therefore i_L(t) = -60 + (0 - (-60)) e^{+t/100 \mu\text{s}} \text{ mA}$$

$$= -60(1 - e^{t/100 \mu\text{s}}) \quad t \geq 0 \text{ }\mu\text{s}$$

Now
$$v_L(t) = L \frac{di_L}{dt} = L \frac{60 \times 10^{-3}}{100 \times 10^{-6}} e^{t/100 \mu\text{s}} \text{ V}$$

$$v_L(t) = 1.8 \times 10^2 e^{t/100 \mu\text{s}} \text{ V} \quad t \geq 0 \text{ }\mu\text{s}$$

So the inductor voltage is growing exponentially. The spark gap will arc at


$$1.8 \times 10^2 e^{t/100 \times 10^{-6}} = 36000$$

$$e^{t/100 \times 10^{-6}} = 200$$


$$t = 100 \times 10^{-6} \cdot \ln 200 = 529.8 \text{ }\mu\text{s}$$

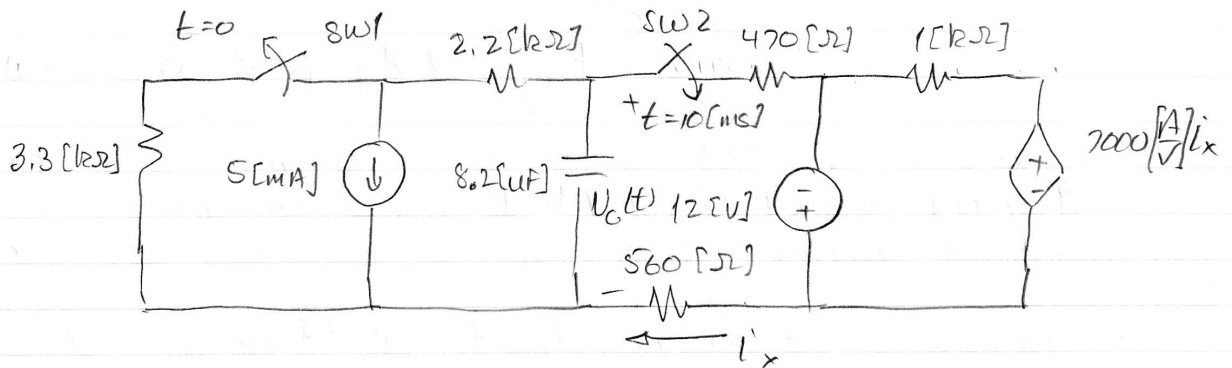PROBLEM 2.9

SW1 was closed for a long time and SW2 was open for a long time. At $t=0$, SW1 opened. At $t=10$ [ms], SW2 closed. Find $i_x(t)$ for $t>0$. *



Start by drawing circuit for $t < 0$:

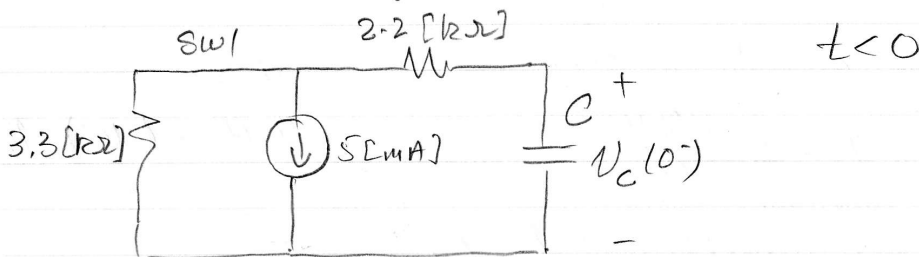


Since SW1 has been closed for a long time, we are in steady state and $C \rightarrow$ open circuit. So...

$$V_C(0^-) = V_C(0^+) = -(0.005)(3300) = -16.5 \text{ [V]}$$

Now SW1 opens...

○ We will find $V_C(t)$ first, and then worry about i_x

$$0 < t < 10 \text{ [ms]}$$

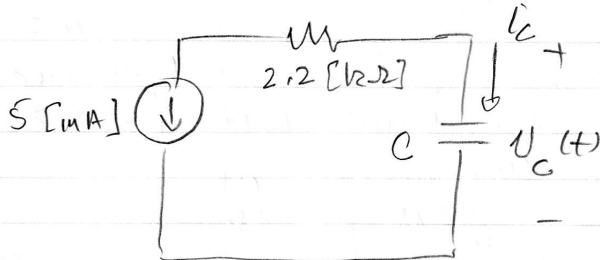

This is not a single-time-constant response!!

Why not?

- There is no "steady state": if we open-circuit the cap, we will violate KCL because we will have a current source going into an open ckt.
- There is no time constant: putting a test source at the capacitor terminals and setting the current source to 0 $\Rightarrow R_{TH} = \infty$!

So this is a job for...

$$i_C = C \frac{dV_C(t)}{dt}$$

$$V_C(t) = \frac{1}{C} \int_{t_0}^t i_C(t) dt + V_C(t_0)$$

$$t_0 = 0$$

$$i_C(t_0) = i_C(0^-) = i_C(0^+)$$


$$= \frac{1}{8.2 \times 10^{-6}} \int_0^t (0.005) dt + (-16.5) \text{ [V]}$$

$$V_C(t) = -609.8 t - 16.5 \text{ [V]} \quad 10 > t > 0 \text{ [ms]}$$

The second switching event is at $t = 10$ [ms].
At this time,

$$V_C(t=10 \text{ [ms]}) = -609.8 (0.01) - 16.5 = -22.6 \text{ [V].}$$

PROBLEM 7.9 (cont)

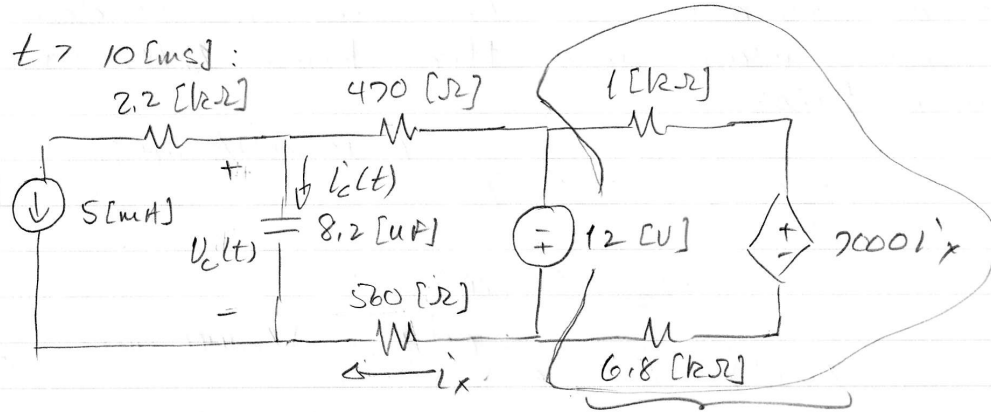

these components are in parallel with a voltage source and can be ignored.

$R_{TH} :$

if we remove C and insert a test source, $5 \text{ [mA]} \rightarrow$ open and $12 \text{ [V]} \rightarrow$ short, so

$$R_{TH} = 470 + 560 = 1030 \text{ [}\Omega\text{]}.$$

$v_{C,f} :$ Open-circuit C to find $v_{C,f}$, which is the steady-state (final) value of v_C .

$$-v_{C,f} + (0.005)560 + 12 + (0.005)470 = 0$$

$$v_{C,f} = -12.15 \text{ [V]}$$

So
$$v_C(t) = v_{C,f} + [v_C(t=10 \text{ [ms]}) - v_{C,f}] e^{-t/\tau_C}$$

$$\tau_C = R_{TH} C = 8.446 \text{ [ms]}$$

So
$$v_C(t) = -12.15 + [-22.6 - (-12.15)] e^{-(t-10 \text{ [ms]})/8.446 \text{ [ms]}}$$

[V] $t \geq 10 \text{ [ms]}$

But we were asked for i_x . This can be done in several ways now that we know $v_c(t)$. One way is this:

$$i_c'(t) = C \frac{dv_c(t)}{dt} = 5.29 e^{-(t-10\text{ms})/8.446\text{ms}} \quad [\text{mA}]$$

$$\text{KCL:} \quad -i_x' - i_c' - 5\text{mA} = 0$$

$$i_x'(t) = 5.29 e^{-(t-10\text{ms})/8.446\text{ms}} - 5 \quad [\text{mA}] \quad t > 10\text{ms}$$

of course for $0 < t < 10\text{ms}$, SW 2 is open and...

$$i_x(t) = 0 \quad 0 < t < 10\text{ms}.$$