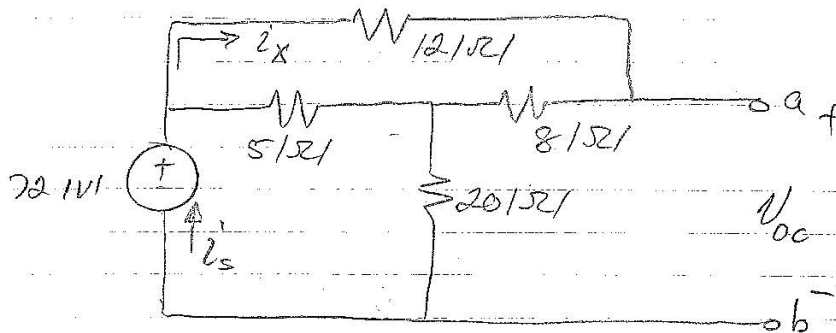



PROBLEM 4.1 (Nilsson & Riedel 8 ed.)

- Find the Thevenin Equivalent at a, b.



Note that a, b is open circuit \Rightarrow
 $12\ \Omega$ is in series with $8\ \Omega$.
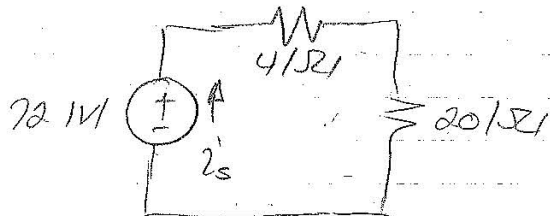
$$\text{So ... } (12 + 8) \parallel 5 = \frac{20 \cdot 5}{25} = 4\ \Omega$$



Of course now we have lost terminals a, b so we need to "unfold" this circuit:

$$i'_s = \frac{72}{24} = 3\ \text{A}$$

In original circuit we can use current divider to find i_x :


$$i_x = i'_s \cdot \frac{5}{(12+8) + 5} = i'_s \cdot \frac{5}{25} = 0.6\ \text{A}$$

Now $V_{oc} - I'_s \cdot 20 - I'_x \cdot 8 = 0$

$$\underline{V_{oc}} = 20 I'_s + 8 I'_x = \underline{64.8 \text{ V}}$$

$$= V_{Th}$$

Short-circuit current:

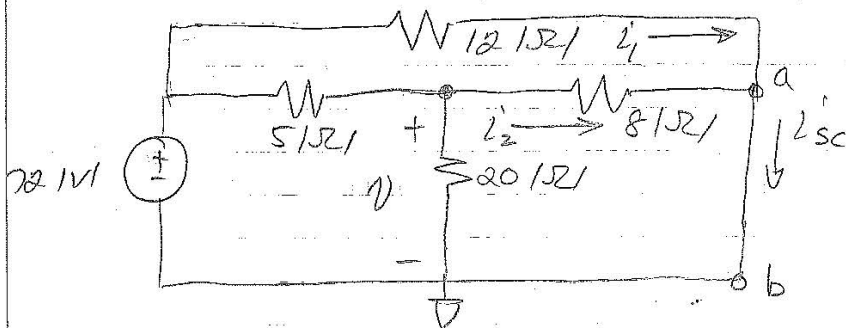

Note that we must take I'_{sc} in the direction $a \rightarrow b$ if we take V_{oc} with positive polarity at a.

$$\frac{V}{20} + \frac{V}{8} + \frac{V - 72}{5} = 0$$


$$\Rightarrow V = 38.4 \text{ V}$$

$$\therefore I'_2 = \frac{V}{8} = 4.8 \text{ A}$$

$$I'_1 = \frac{72}{12} = 6 \text{ A}$$


$$\Rightarrow I'_{sc} = I'_1 + I'_2 = 10.8 \text{ A}$$

$$\therefore \underline{R_{Th}} = \frac{V_{oc}}{I'_{sc}} = \underline{6 \Omega}$$

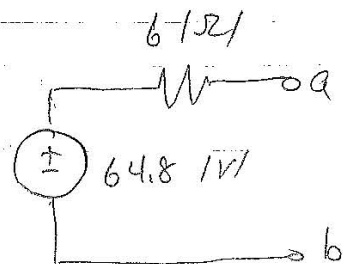


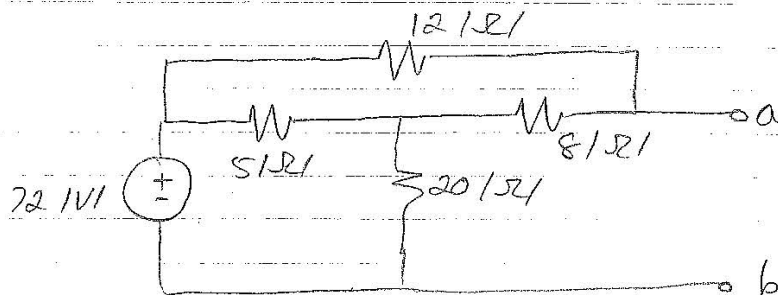PROBLEM 4.1 REVISITED : R_{TH} calculation

Use test-source idea — but here is a case where we don't need to apply the test source!




De-activate independent sources:

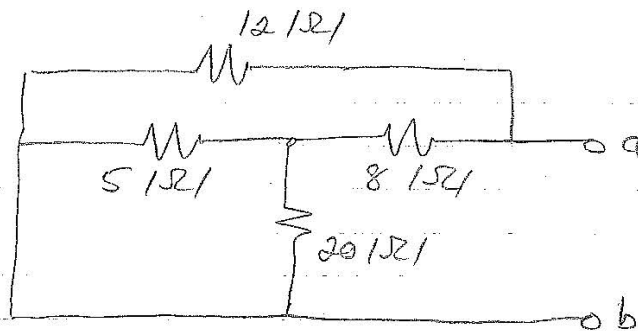

Now $R_{Th} = (20 \parallel 5 + 8) \parallel 12 = 6 \Omega$

PROBLEM 4.2 (Nilsson & Riedel 8ed)

Find the Thevenin Equivalent at a, b.

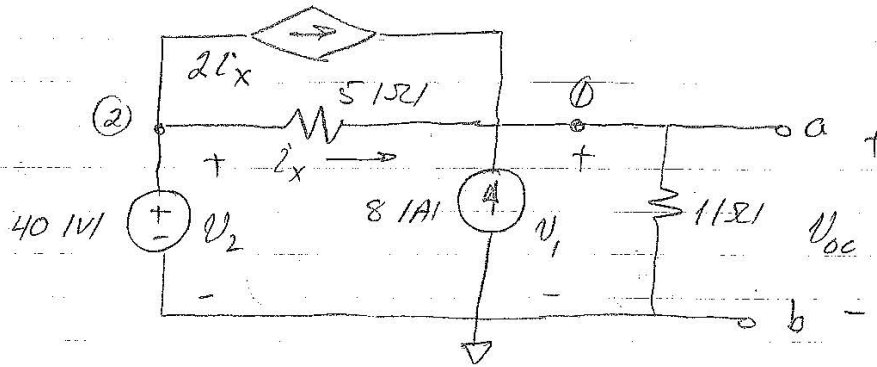

open-circuit voltage

$$\frac{V_1}{1} - 8 + \frac{V_1 - V_2}{5} - 2i'_x = 0$$

$$i'_x = \frac{V_2 - V_1}{5}$$


$$V_2 = 40 \text{ V}$$

Solution: $V_1 = 20 \text{ V}$

$$i'_x = 4 \text{ A}$$


Then $V_{oc} = \underline{\underline{V_{TH}}} = V_1 = \underline{\underline{20 \text{ V}}}$

Short-circuit current

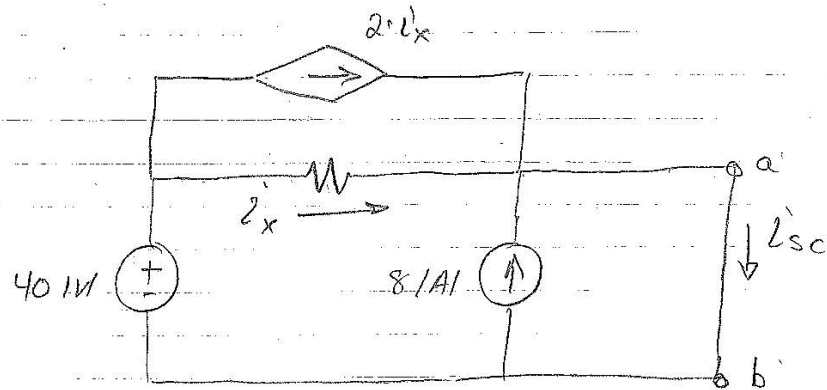

Note that i_{sc} must be taken in the direction $a \rightarrow b$ if V_{oc} has positive polarity at a .

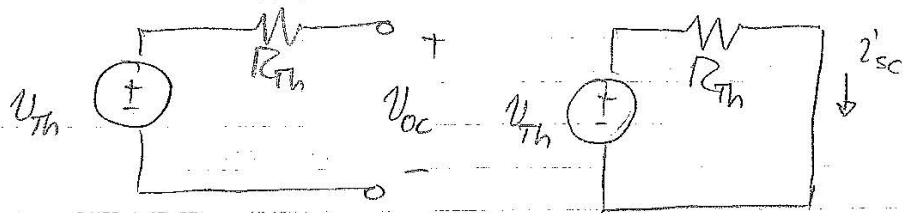Why is that? Go back to the Thevenin equivalent:



For $V_{Th} > 0$ and $R_{Th} > 0$, V_{oc} and i_{sc} are positive as indicated.

Note also that we were able to remove the 1Ω resistor because the short circuit \Rightarrow no current through it.

(PROBLEM 4.2 cont.)

$$\text{KVL: } -40 + 5i_x = 0$$


$$\text{KCL: } i_{sc} - 8 - i_x - 2i_x = 0$$

$$\text{Solution: } i_x = 8 \text{ A}$$


$$i_{sc} = 32 \text{ A}$$

$$\therefore P_{Gh} = V_{oc}/i_{sc} = 20/32 = 5/8 \text{ W}$$

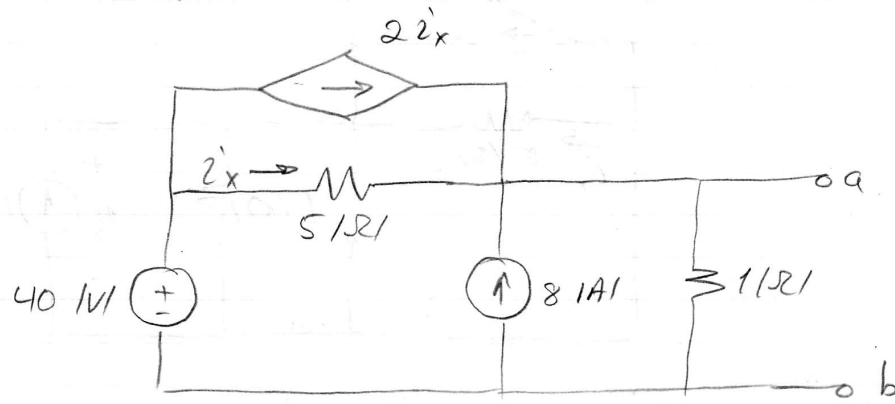PROBLEM 4.2 REVISITED: R_{TH} calculation
TEST VOLTAGE



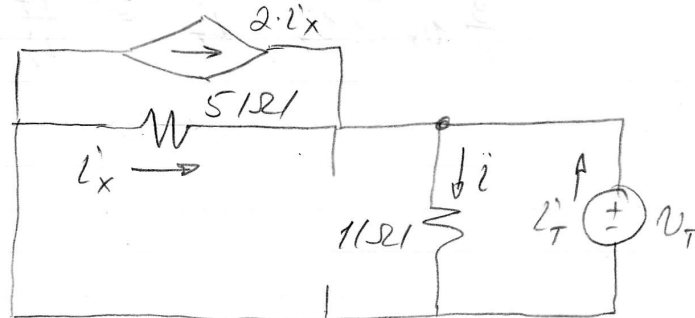Apply test voltage and de-activate independent sources:



$$\text{KCL: } -2i_T - i_x - 2i_x + i = 0$$

$$i = U_T / 1$$

$$\text{KVL: } U_T + 5i_x = 0 \Rightarrow i_x = -U_T / 5$$


$$\therefore i_T = -3i_x + \frac{U_T}{1}$$

$$= \frac{3}{5}U_T + U_T / 1 = U_T \left(\frac{3}{5} + 1 \right)$$

$$\Rightarrow \frac{U_T}{i_T} = \frac{1}{(8/5)} = \underline{\underline{5/8 \text{ } 1\Omega}} = R_{TH}$$

✓

TEST CURRENT

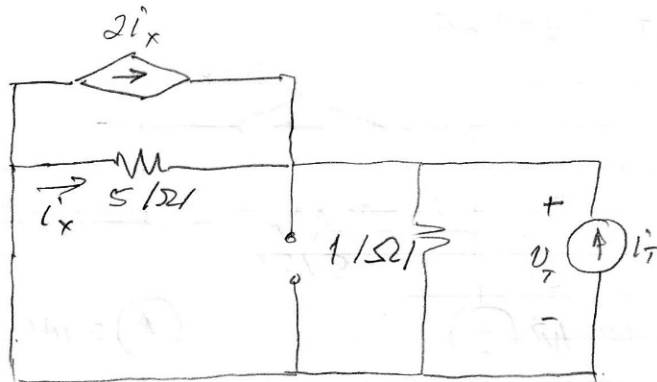

$$\text{KCL: } -2i_x - i_x + \frac{V_T}{1} - i_T = 0$$

$$i_x = -\frac{V_T}{5}$$


$$\frac{3}{5} V_T + V_T = i_T \Rightarrow \frac{V_T}{i_T} = R_{TH} = \frac{5}{8} \Omega$$

(PROBLEM 4.2 REVISITED con't)

Note that we need to find V_T/i_T so we manipulated our equations to arrive at this.

BUT: Since any test source will work, it is often useful to choose a specific value, say 1 V (or 1 A).

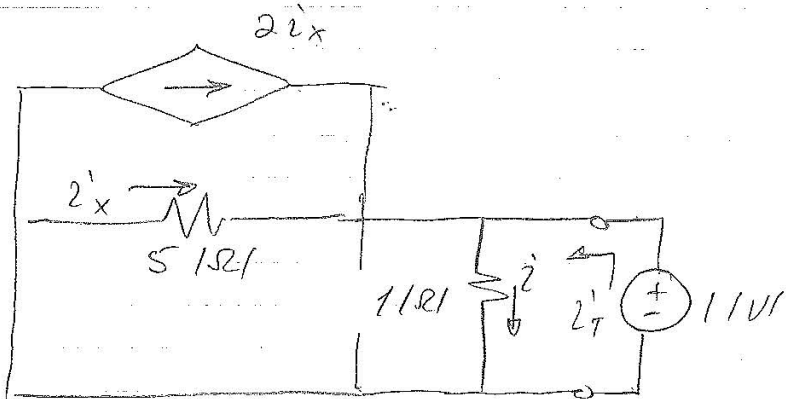Looking again at Problem 4.2, we apply a 1 V test source:



Now

$$i_T = 1\text{ A}$$

$$1 + 5i_T' = 0 \Rightarrow i_T' = -0.2\text{ A}$$

$$\therefore i_T = -3i_T' + i_T$$


$$= +0.6 + 1 = 1.6\text{ A}$$

$$\Rightarrow R_{Th} = V_T/i_T = 1/1.6 = 0.625\ \Omega$$

(= $5/8\ \Omega$)

PROBLEM 4.3 (Nilsson & Riedel, 8ed)

Find the Thevenin Equivalent at a), b).

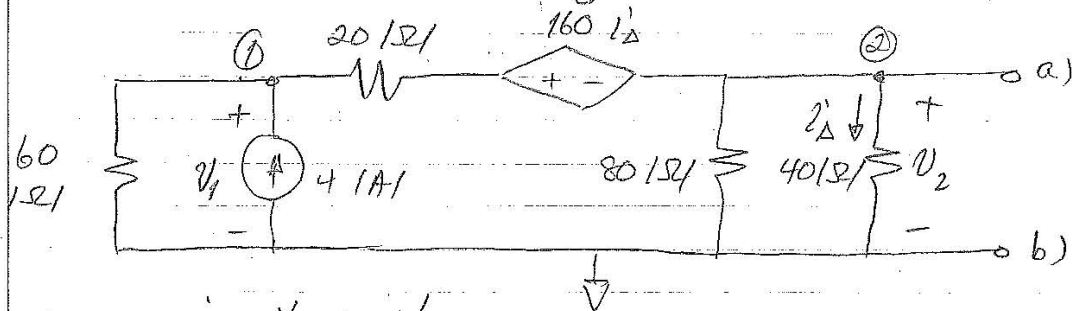

open-circuit voltage:

$$\frac{V_2}{40} + \frac{V_2}{80} + \frac{V_2 - V_1 + 160 i'_{\Delta}}{20} = 0$$

$$\frac{V_1}{60} - 4 + \frac{V_1 - V_2 - 160 i'_{\Delta}}{20} = 0$$

$$i'_{\Delta} = V_2/40$$


Solution: $V_2 = V_{oc} = \underline{V_{Th}} = 30 \text{ V}$

$$i'_{\Delta} = 0.75 \text{ A}$$

$$V_1 = 172.5 \text{ V}$$

Short-circuit current

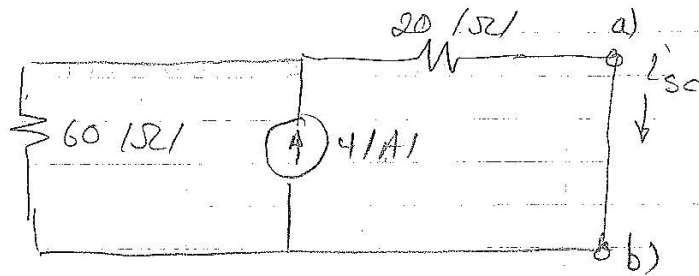with a), b) short-circuited, there is no current in the 80 ohm or 40 ohm resistors. Also, $i'_{\Delta} = 0$, so the circuit simplifies considerably:




Then $i_{sc} = 4 \cdot \frac{60}{60+20} = 3 \text{ A}$

So $R_{Th} = V_{oc}/i_{sc} = 10 \text{ } \Omega$

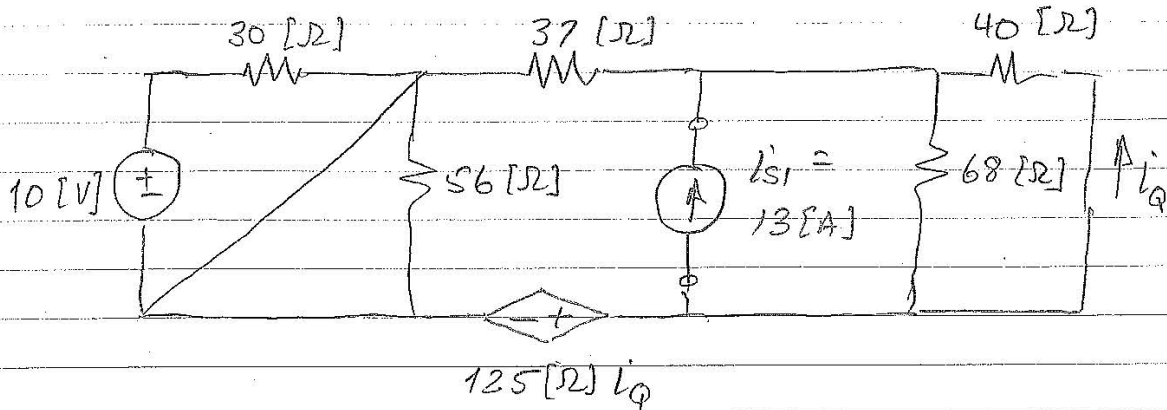
PROBLEM 4.5

- Find the Thevenin Equivalent seen by the current source.



Note: "seen by the current source" means exactly that = what equivalent circuit does the current source see? For that, we need to disconnect the current source because the current source is not part of the equivalent circuit.

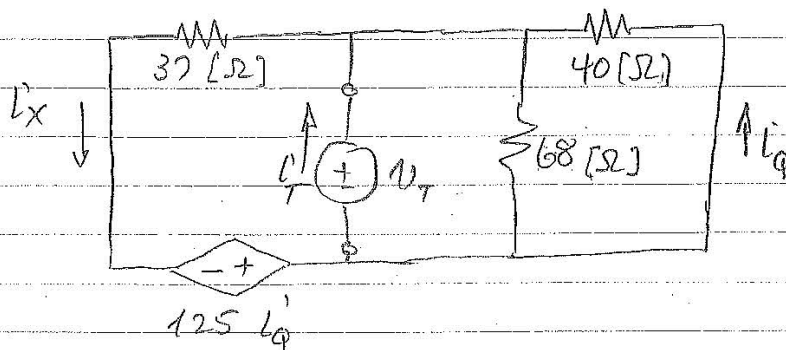Because we have no independent sources, we must find R_{TH} with a test source.



We have removed several components that were in parallel with a short.

$$\text{KVL: } -V_T - 40i_\phi = 0$$

$$\text{Set } V_T = 1 \text{ [V] (arbitrary)} \Rightarrow i_\phi = -25 \text{ [mA]}$$

$$\text{KVL: } -V_T + 37i_x - 125i_\phi = 0$$

$$\Rightarrow i_x = \frac{1 + 125(-0.025)}{37} = -57.43 \text{ [mA]}$$

$$\text{KCL: } i_T = i_x - i_\phi + \frac{1}{68} = -17.72 \text{ [mA]}$$

$$\therefore \underline{R_{TH} = -56.42 \text{ } [\Omega]}$$

Note that the terminals of the Thevenin Equivalent do not "see" any independent sources, which means...

$$V_{TH} = 0$$

So the Thevenin Equivalent is just a resistance:

