


ECE 3317

Applied Electromagnetic Waves

Prof. David R. Jackson
Fall 2023


Notes 10

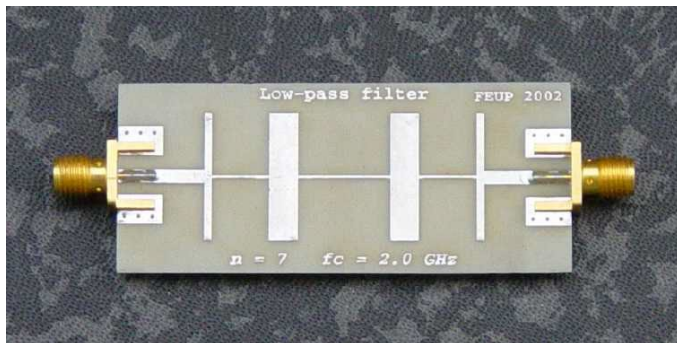Transmission Lines (Reflection and Impedance)



Reflection

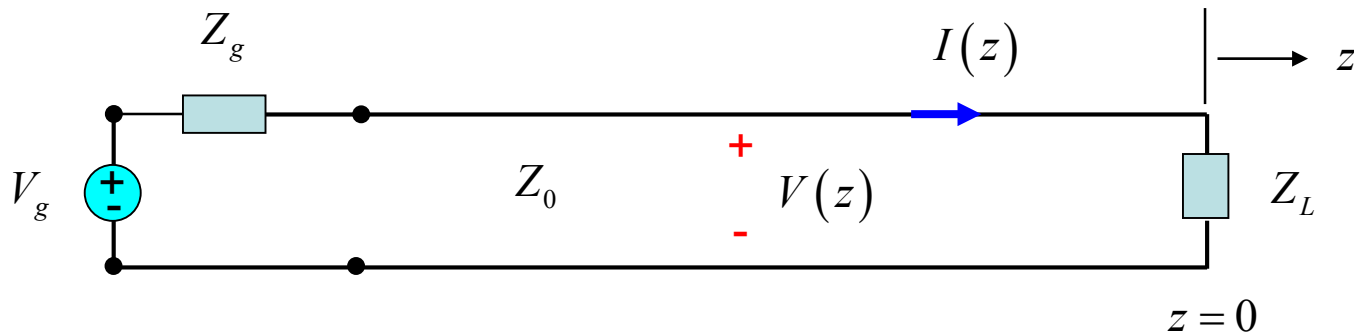Consider a transmission line that is terminated with a load:



$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Note:
In the frequency domain notes,
the load is always at $z = 0$.

Voltage and current on the line:


$$V(z) = \underbrace{A e^{-\gamma z}}_{V^+(z)} + \underbrace{B e^{+\gamma z}}_{V^-(z)}$$

$$I(z) = \underbrace{\left(\frac{A}{Z_0}\right) e^{-\gamma z}}_{I^+(z)} - \underbrace{\left(\frac{B}{Z_0}\right) e^{+\gamma z}}_{I^-(z)}$$

Reflection (cont.)

Important point:

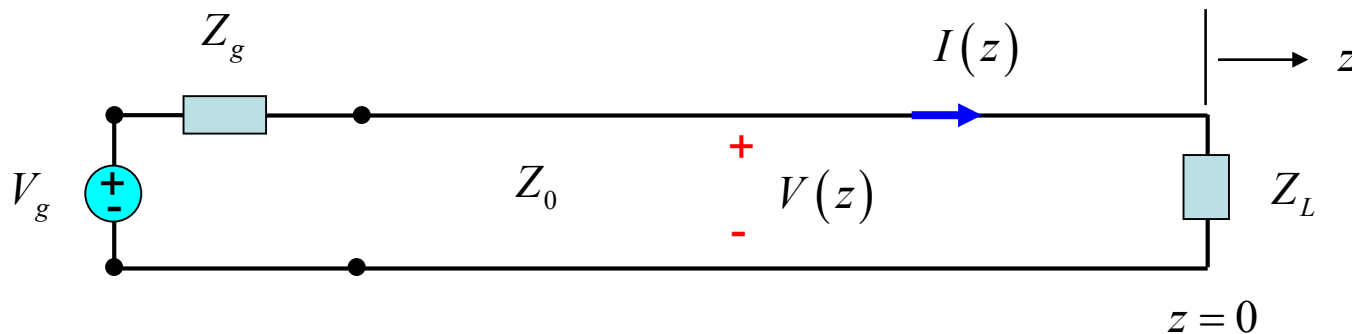The forward-traveling and backward-traveling wave amplitudes are the amplitudes that describe the two waves in sinusoidal steady-state (after all bounces have died down and we are in steady state).




$$V(z) = Ae^{-\gamma z} + Be^{+\gamma z} \quad I(z) = \left(\frac{A}{Z_0}\right)e^{-\gamma z} - \left(\frac{B}{Z_0}\right)e^{+\gamma z}$$

A = amplitude of **net** forward-traveling wave

B = amplitude of **net** backward-traveling wave

Reflection (cont.)

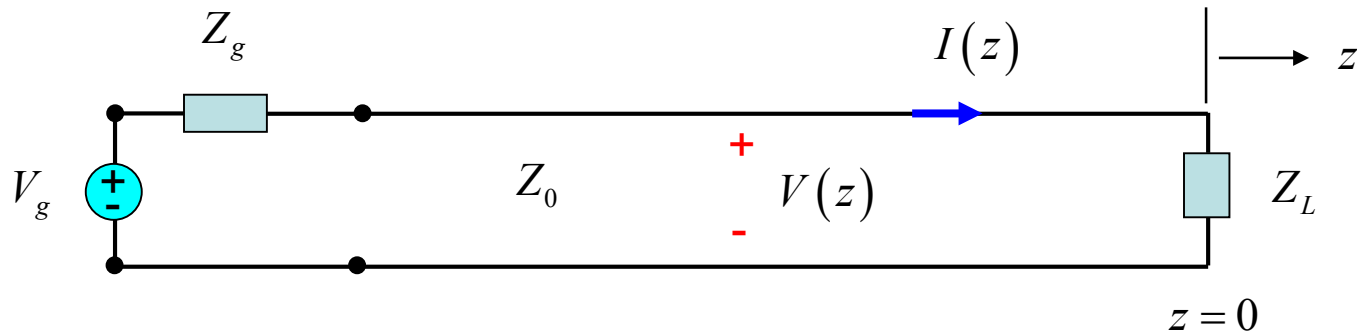

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$V(z) = Ae^{-\gamma z} + Be^{+\gamma z}$$

$$I(z) = \left(\frac{A}{Z_0}\right)e^{-\gamma z} - \left(\frac{B}{Z_0}\right)e^{+\gamma z}$$

At the load ($z = 0$): $V(0) = Z_L I(0)$

Hence, we have
$$A + B = Z_L \left(\frac{1}{Z_0} (A - B) \right)$$

or

$$B \left(1 + \frac{Z_L}{Z_0} \right) = A \left(\frac{Z_L}{Z_0} - 1 \right)$$

Reflection Coefficient

We define the load reflection coefficient:

$$\Gamma_L \equiv \frac{V^-(0)}{V^+(0)}$$

Hence $\Gamma_L = \frac{B}{A}$ ← $V(z) = Ae^{-\gamma z} + Be^{+\gamma z}$

$$V^+(z) = Ae^{-\gamma z}$$

$$V^-(z) = Be^{+\gamma z}$$

We then have, from the last slide,

$$\Gamma_L = \frac{B}{A} = \frac{\left(\frac{Z_L}{Z_0} - 1\right)}{\left(1 + \frac{Z_L}{Z_0}\right)}$$

or

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

This is the same formula that we had in the time domain, but here the load impedance and the characteristic impedance may be complex.

Voltage and Current

We can then use $B = \Gamma_L A$ to write:


$$V(z) = A \left(e^{-\gamma z} + \Gamma_L e^{+\gamma z} \right)$$
$$I(z) = \frac{1}{Z_0} A \left(e^{-\gamma z} - \Gamma_L e^{+\gamma z} \right)$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Note: The generator (source) will determine the unknown (complex) constant A .

Impedance

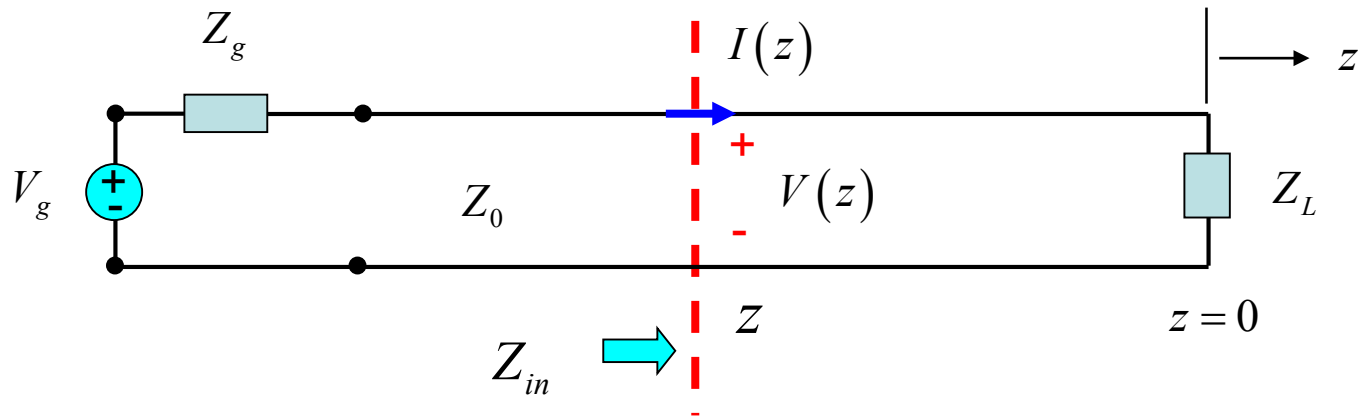
We define the **input impedance** at any point z on the line:




$$Z_{in}(z) \equiv \frac{V(z)}{I(z)}$$

The input impedance is the impedance “seen” looking to the right.

Impedance (cont.)

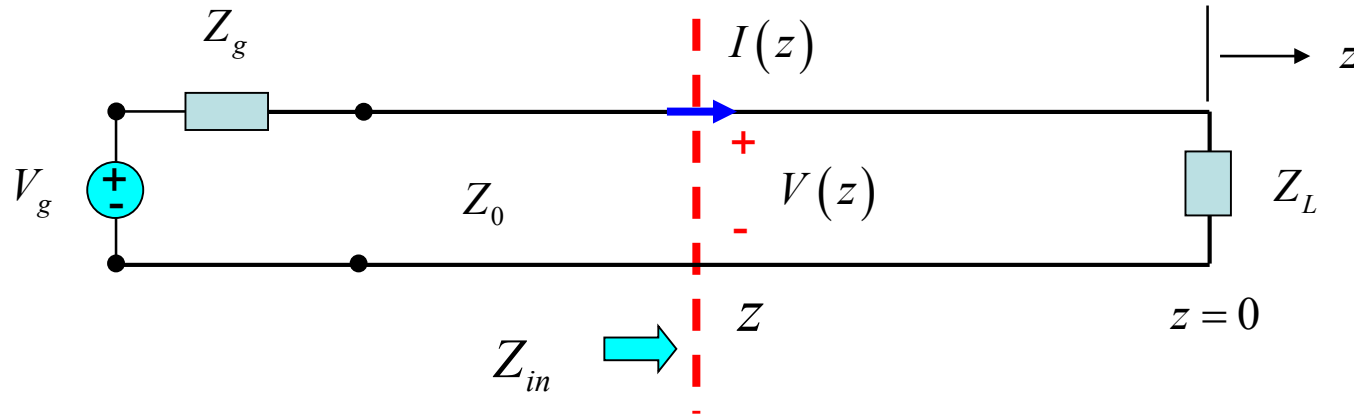

$$Z_{in}(z) \equiv \frac{V(z)}{I(z)}$$

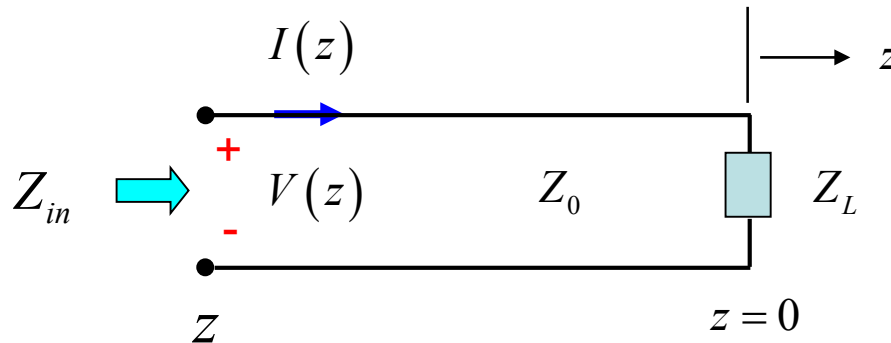

Note:

The input impedance does not care what is to the left of the point z .

We can remove everything to the left if we wish.

(What is to the left of the point z only affects the amplitude level of the voltage and current.)

Impedance (cont.)

We then have

$$Z_{in}(z) = \frac{A(e^{-\gamma z} + \Gamma_L e^{+\gamma z})}{\frac{1}{Z_0} A(e^{-\gamma z} - \Gamma_L e^{+\gamma z})}$$

Canceling the constant A , we have


$$Z_{in}(z) = Z_0 \left(\frac{e^{-\gamma z} + \Gamma_L e^{+\gamma z}}{e^{-\gamma z} - \Gamma_L e^{+\gamma z}} \right)$$

or

$$Z_{in}(z) = Z_0 \left(\frac{1 + \Gamma_L e^{+2\gamma z}}{1 - \Gamma_L e^{+2\gamma z}} \right)$$

Impedance (cont.)

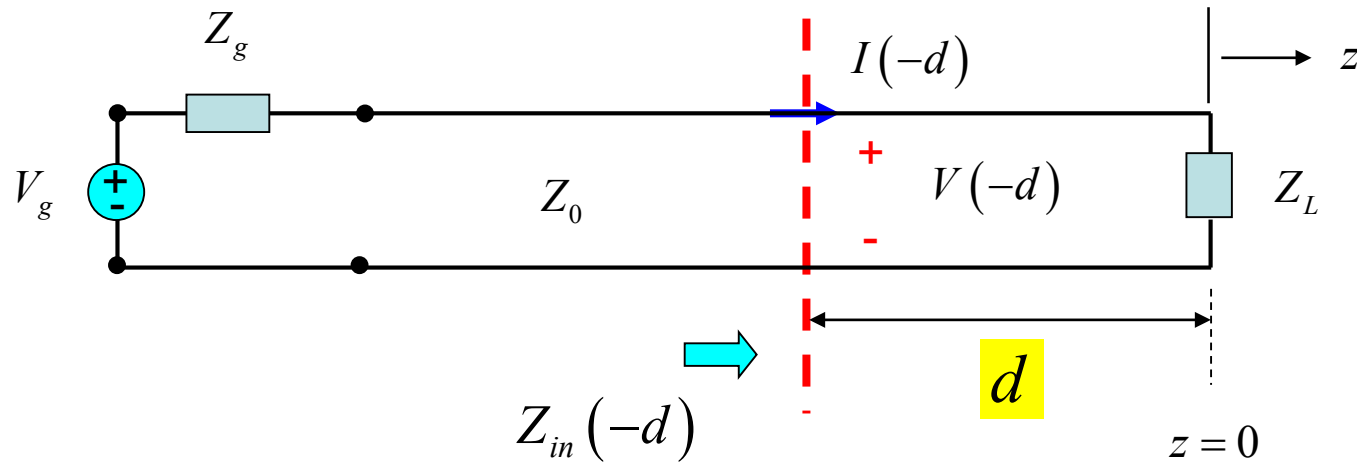Now let $z = -d$: $e^{\gamma z} = e^{-\gamma d}$ (Here d is the distance from the load.)




$$Z_{in}(-d) = Z_0 \left(\frac{1 + \Gamma_L e^{-2\gamma d}}{1 - \Gamma_L e^{-2\gamma d}} \right)$$

Impedance (cont.)

At the beginning of the line ($d = l$) we have:

$$Z_{in}(-l) = Z_0 \left(\frac{1 + \Gamma_L e^{-2\gamma l}}{1 - \Gamma_L e^{-2\gamma l}} \right)$$

$l =$ length of line

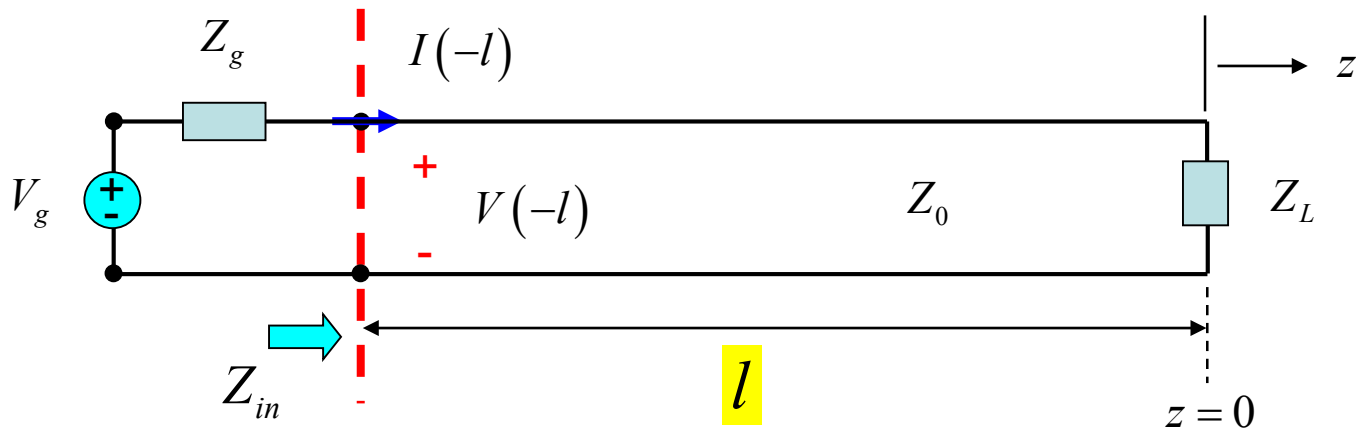

Impedance (cont.)

We can derive a new form (“tangent form”) for the input impedance.

Substituting for the load reflection coefficient, we have:

$$\begin{aligned} Z_{in}(z) &= Z_0 \left(\frac{1 + \Gamma_L e^{+2\gamma z}}{1 - \Gamma_L e^{+2\gamma z}} \right) \\ &= Z_0 \left(\frac{1 + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{+2\gamma z}}{1 - \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{+2\gamma z}} \right) \\ &= Z_0 \left(\frac{(Z_L + Z_0) + (Z_L - Z_0) e^{+2\gamma z}}{(Z_L + Z_0) - (Z_L - Z_0) e^{+2\gamma z}} \right) \\ &= Z_0 \left(\frac{(Z_L + Z_0) e^{-\gamma z} + (Z_L - Z_0) e^{+\gamma z}}{(Z_L + Z_0) e^{-\gamma z} - (Z_L - Z_0) e^{+\gamma z}} \right) \end{aligned}$$


Impedance (cont.)

Rearranging the expression, we have:

$$\begin{aligned} Z_{in}(z) &= Z_0 \left(\frac{(Z_L + Z_0)e^{-\gamma z} + (Z_L - Z_0)e^{+\gamma z}}{(Z_L + Z_0)e^{-\gamma z} - (Z_L - Z_0)e^{+\gamma z}} \right) \\ &= Z_0 \left(\frac{Z_L(e^{+\gamma z} + e^{-\gamma z}) - Z_0(e^{+\gamma z} - e^{-\gamma z})}{-Z_L(e^{+\gamma z} - e^{-\gamma z}) + Z_0(e^{+\gamma z} + e^{-\gamma z})} \right) \\ &= Z_0 \left(\frac{Z_L(2 \cosh(\gamma z)) - Z_0(2 \sinh(\gamma z))}{-Z_L(2 \sinh(\gamma z)) + Z_0(2 \cosh(\gamma z))} \right) \\ &= Z_0 \left(\frac{Z_L - Z_0 \tanh(\gamma z)}{Z_0 - Z_L \tanh(\gamma z)} \right) \end{aligned}$$

Impedance (cont.)

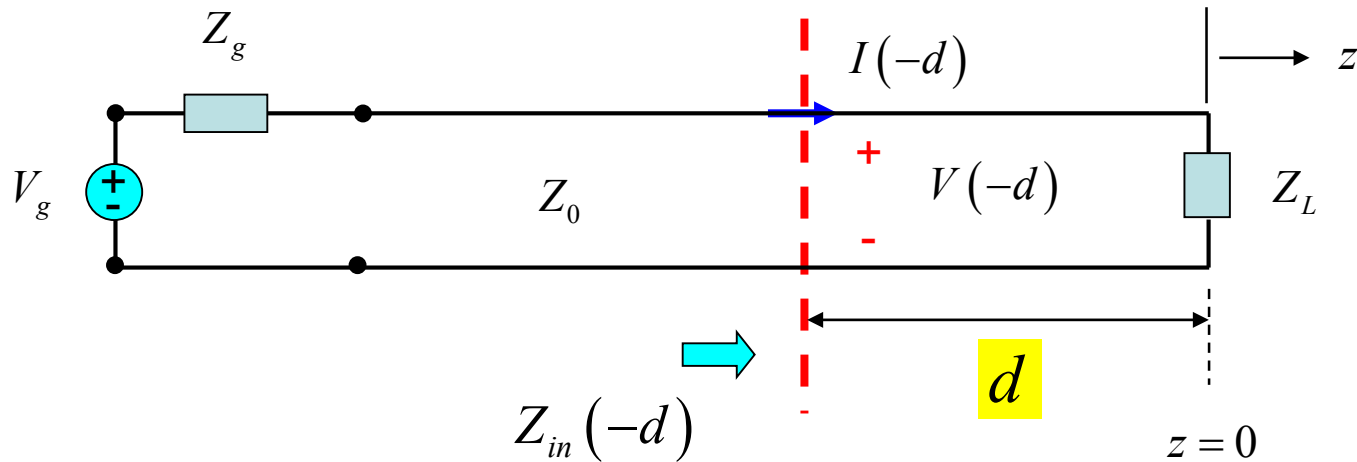Now let $z = -d$: $\tanh(\gamma z) = \tanh(-\gamma d) = -\tanh(\gamma d)$



$$Z_{in}(-d) = Z_0 \left(\frac{Z_L + Z_0 \tanh(\gamma d)}{Z_0 + Z_L \tanh(\gamma d)} \right)$$


d = distance from load

Impedance (cont.)

At the beginning of the line ($d = l$) we have:

$$Z_{in}(-l) = Z_0 \left(\frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)} \right)$$

$l = \text{length of line}$

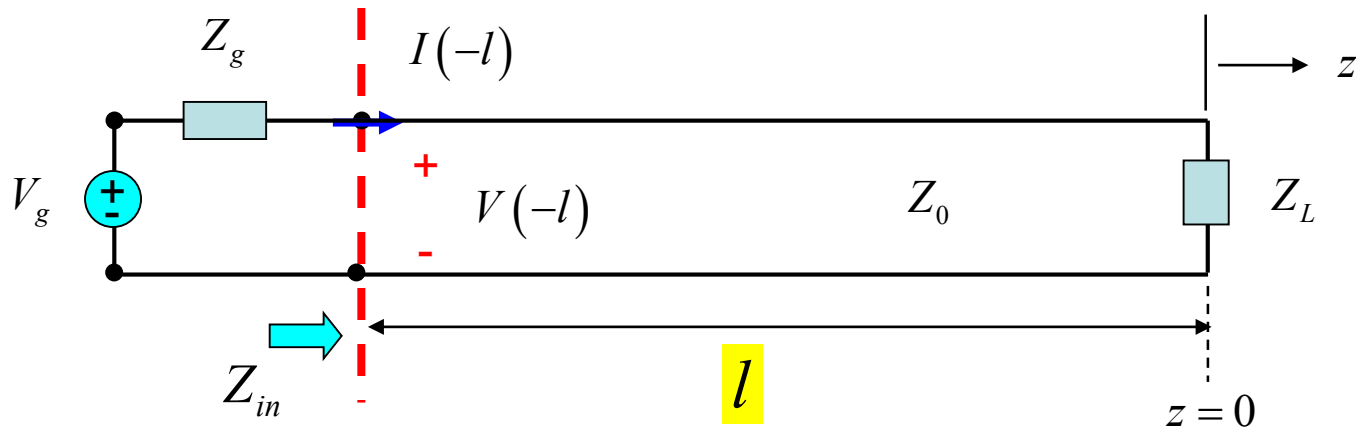

Impedance (cont.)

Limiting Cases

1) General (lossy) line: $l = 0 \rightarrow Z_{in} = Z_L$

2) Lossless line:

$$\omega = 0 \rightarrow \gamma = 0 \rightarrow Z_{in} = Z_L$$

$$\gamma = \sqrt{(\cancel{R} + j\omega L)(\cancel{G} + j\omega C)} = j\omega\sqrt{LC} \rightarrow 0$$

These limiting cases agree with circuit theory.

Impedance (cont.)

Limiting Cases (cont.)

3) Lossy infinite line: $l \rightarrow \infty \rightarrow Z_{in} = Z_0$ (complex)

Proof:

$$Z_{in} = Z_0 \left(\frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)} \right)$$

$$\gamma = \alpha + j\beta, \quad \alpha > 0$$

$$\tanh(\gamma l) \rightarrow 1$$

$$\text{Note: } \tanh(\gamma l) = \frac{\sinh(\gamma l)}{\cosh(\gamma l)} = \frac{\frac{1}{2}(e^{\gamma l} - e^{-\gamma l})}{\frac{1}{2}(e^{\gamma l} + e^{-\gamma l})} = \frac{1 - e^{-2\gamma l}}{1 + e^{-2\gamma l}} = \frac{1 - e^{-2\alpha l} e^{-j2\beta l}}{1 + e^{-2\alpha l} e^{-j2\beta l}}$$

$l \rightarrow \infty$
↓

Impedance (cont.)

Limiting Cases (cont.)

4) Matched load ($Z_L = Z_0$):

$$Z_{in} = Z_0 \left(\frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)} \right)$$



$$Z_{in} = Z_0 \left(\frac{Z_0 + Z_0 \tanh(\gamma l)}{Z_0 + Z_0 \tanh(\gamma l)} \right)$$



$$Z_{in} = Z_0 \quad (\text{independent of line length!})$$

Impedance (cont.)

Lossless Case

$$\gamma = \alpha + j\beta = \sqrt{\cancel{(R + j\omega L)}\cancel{(G + j\omega C)}} = j\omega\sqrt{LC}$$

Use $\tanh(jx) = j \tan(x)$


We then have
$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right)$$

where

$$\beta = \omega\sqrt{LC} = \omega\sqrt{\mu\varepsilon} = \frac{2\pi f}{c_d} = \frac{2\pi}{\lambda_d} \quad \lambda_d = \frac{\lambda_0}{\sqrt{\mu_r \varepsilon_r}}$$

Impedance (cont.)

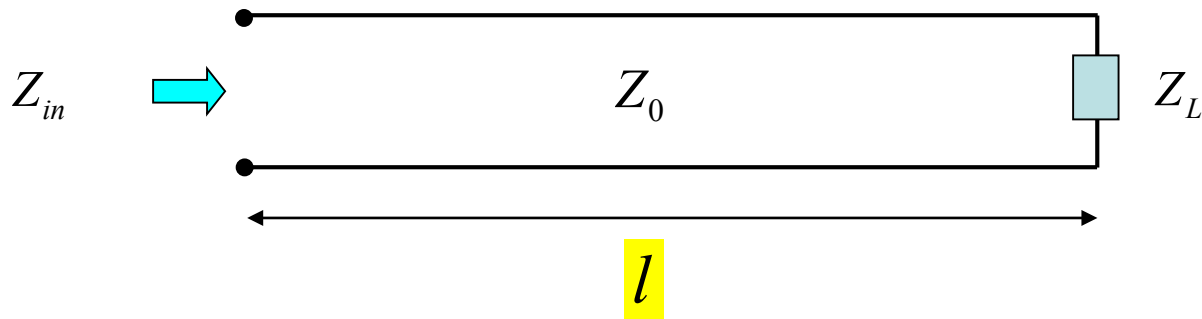Summary of final formula for a lossless line:



$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right)$$

$$\beta = \omega \sqrt{LC} = \omega \sqrt{\mu \epsilon} = \frac{2\pi f}{c_d} = \frac{2\pi}{\lambda_d}$$

$$\lambda_d = \lambda_0 / \sqrt{\mu_r \epsilon_r}$$

Impedance (cont.)

For a lossless line:

The input impedance repeats every **one-half wavelength**.

The voltage and current repeat every **wavelength**.

The voltage and current become their negatives after **one-half wavelength**.


The magnitude of the voltage and current repeat every **one-half wavelength**.

$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} \right) \quad \beta = \frac{2\pi}{\lambda_d} \quad \beta d = 2\pi \left(\frac{d}{\lambda_d} \right)$$

$$V(z) = A \left(e^{-j\beta z} + \Gamma_L e^{+j\beta z} \right) \quad I(z) = \frac{1}{Z_0} A \left(e^{-j\beta z} - \Gamma_L e^{+j\beta z} \right) \quad \beta z = 2\pi \left(\frac{z}{\lambda_d} \right)$$

Impedance (cont.)

Special Cases of Lossless Line

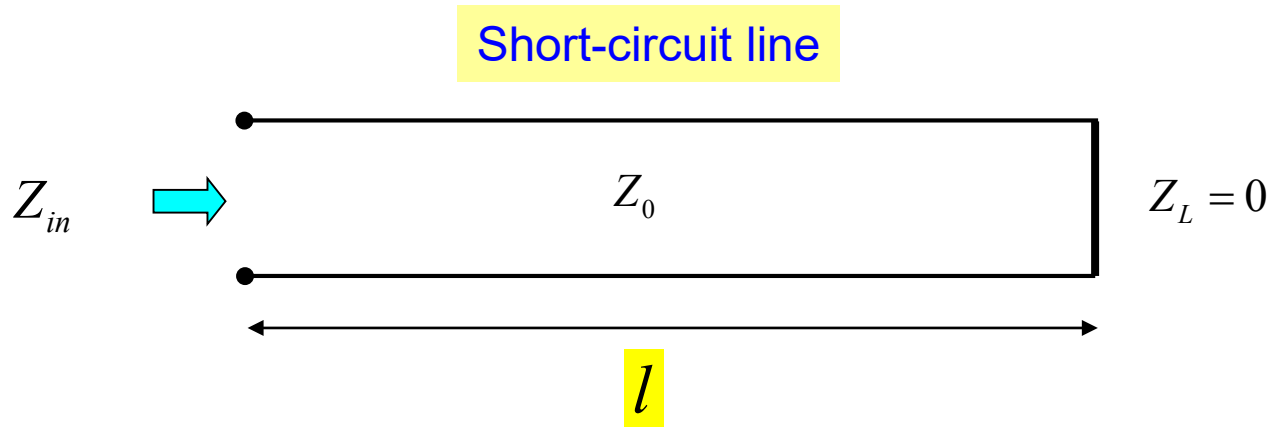

$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right)$$


$$Z_{in} = jZ_0 \tan(\beta l) \quad \text{or} \quad Z_{in} = jZ_0 \tan(2\pi l / \lambda_d)$$

Impedance (cont.)

Short-circuit line


$$X_{in} = Z_0 \tan(\beta l)$$

$$Z_{in} = jX_{in}$$

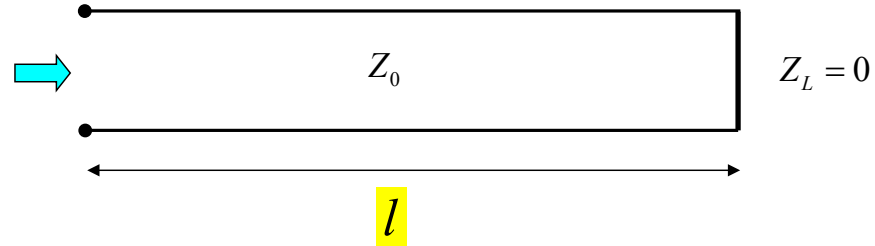

or
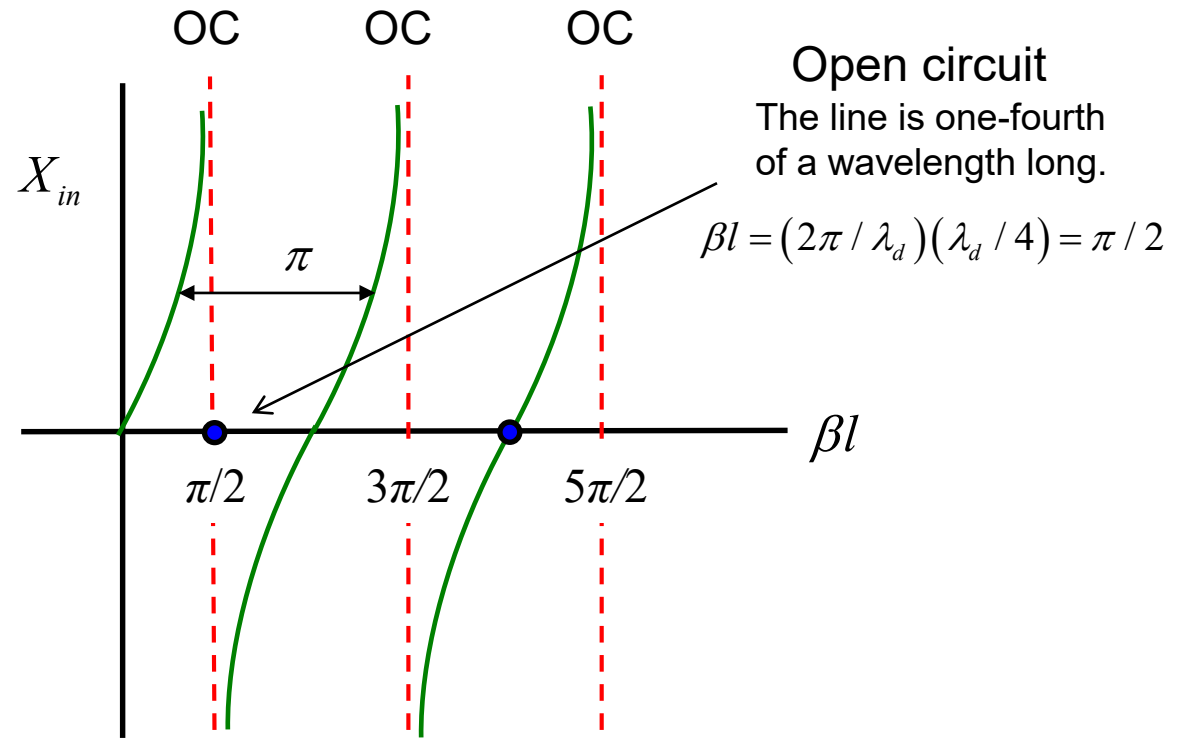
$$X_{in} = Z_0 \tan(2\pi l / \lambda_d)$$




Impedance (cont.)

Short-circuit line

$$X_{in} = Z_0 \tan(\beta l)$$

Low frequency:

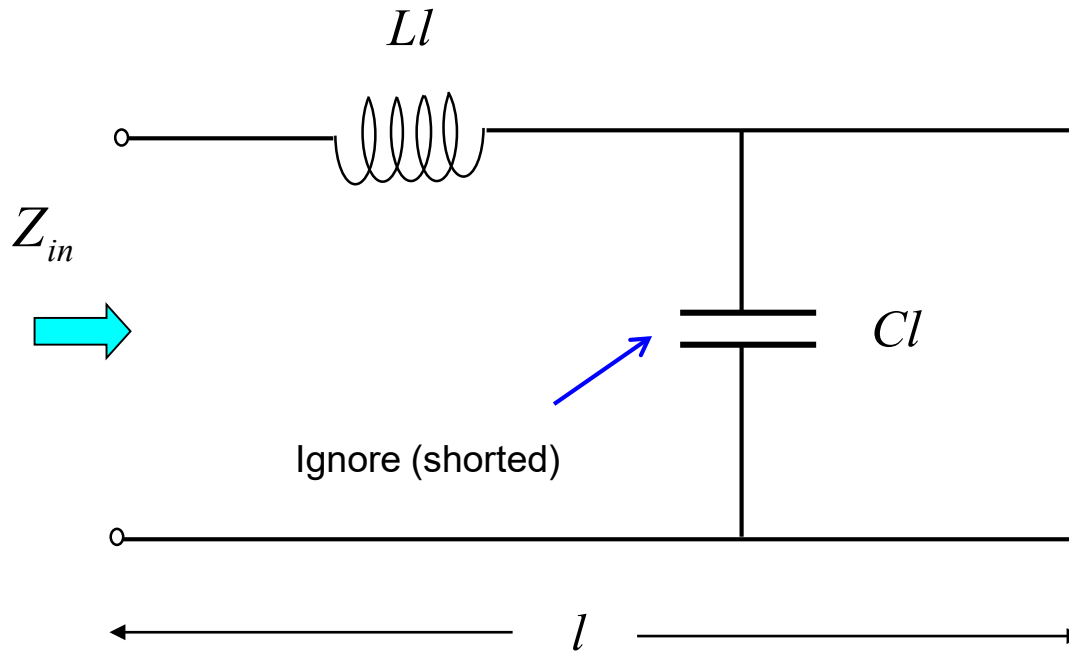
$$\begin{aligned} X_{in} &\approx Z_0 (\beta l) \\ &= \sqrt{\frac{L}{C}} (\omega \sqrt{LC} l) \\ &= \omega (Ll) \end{aligned}$$



$$X_{in} \approx \omega (Ll)$$

Impedance (cont.)

Special Cases of Lossless Line (cont.)

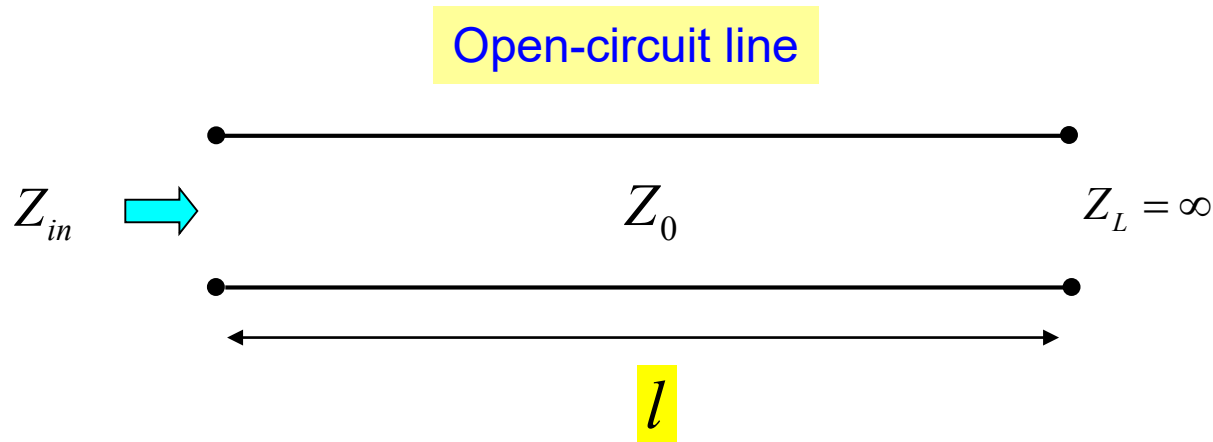

$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right) \Rightarrow Z_{in} = Z_0 \left(\frac{1 + j \cancel{(Z_0 / Z_L)} \tan(\beta l)}{\cancel{(Z_0 / Z_L)} + j \tan(\beta l)} \right)$$

$$Z_{in} = -jZ_0 \cot(\beta l)$$

or $Z_{in} = -jZ_0 \cot(2\pi l / \lambda_d)$

Impedance (cont.)

Open-circuit line



$$X_{in} = -Z_0 \cot(\beta l)$$

or

$$X_{in} = -Z_0 \cot(2\pi l / \lambda_d)$$

$$Z_{in} = jX_{in}$$

Open-circuit line

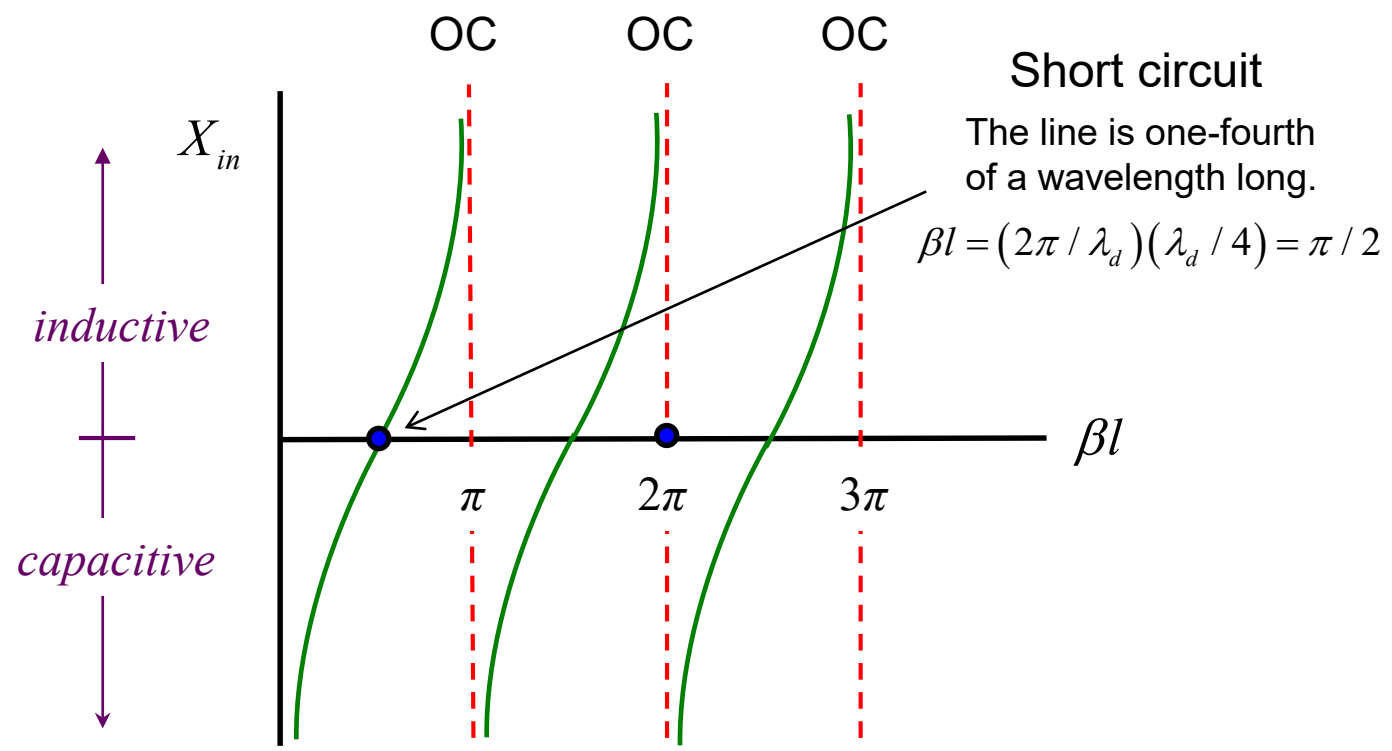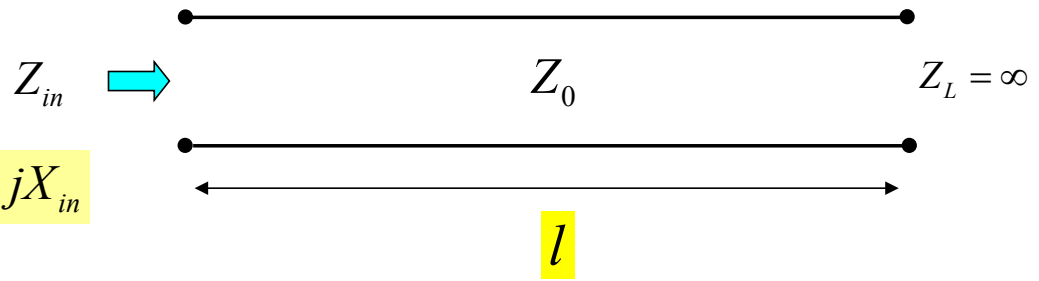


Impedance (cont.)

Open-circuit line

$$X_{in} = -Z_0 \cot(\beta l)$$

Low frequency:
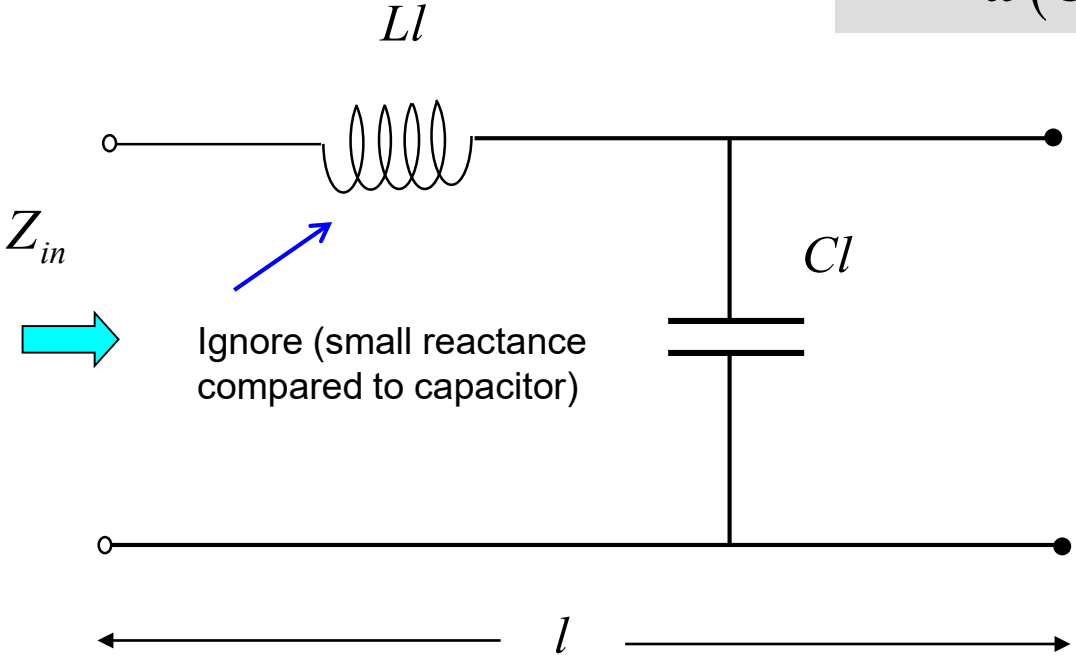
$$\begin{aligned} X_{in} &\approx -Z_0 / (\beta l) \\ &= -\sqrt{\frac{L}{C}} \left(\frac{1}{\omega \sqrt{LC} l} \right) \\ &= \frac{-1}{\omega(Cl)} \end{aligned}$$




$$B_{in} = -1 / X_{in} \quad (\text{for reactive element})$$

$$B_{in} \approx \omega(Cl)$$

Filter Application

Microstrip Filter

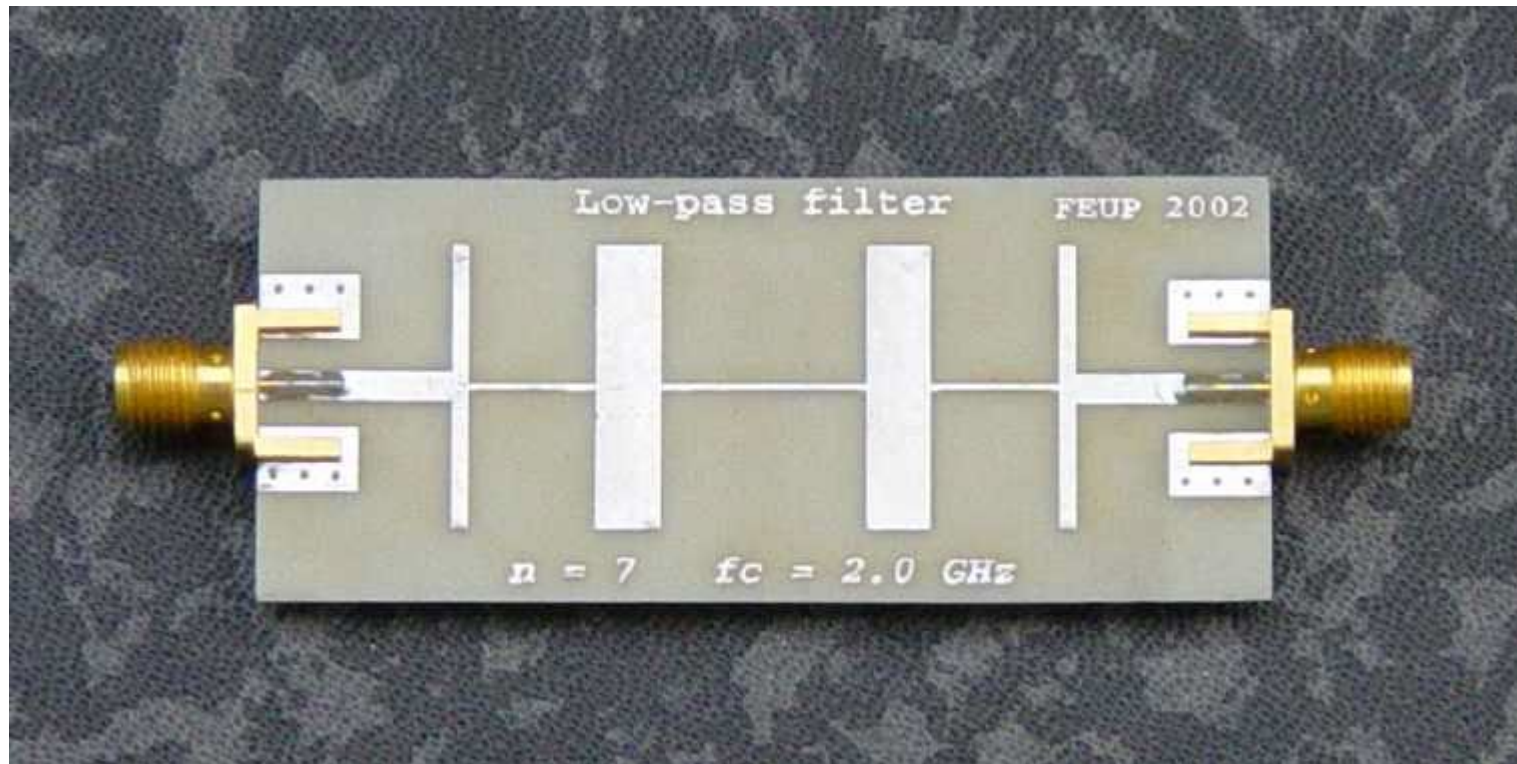(Here is an application with microstrip lines being used to realize L and C elements.)



Appendix: Summary of Formulas

General Lossy Case

$$Z_{in} = Z_0 \left(\frac{Z_L + Z_0 \tanh(\gamma d)}{Z_0 + Z_L \tanh(\gamma d)} \right)$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z_{in} = Z_0 \left(\frac{1 + \Gamma_L e^{-2\gamma d}}{1 - \Gamma_L e^{-2\gamma d}} \right)$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$V(z) = A \left(e^{-\gamma z} + \Gamma_L e^{+\gamma z} \right)$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$I(z) = \frac{1}{Z_0} A \left(e^{-\gamma z} - \Gamma_L e^{+\gamma z} \right)$$

$$\gamma = \alpha + j\beta$$

$$\lambda_g = 2\pi / \beta$$

Appendix: Summary of Formulas

Lossless Case

$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} \right)$$

$$Z_{in} = Z_0 \left(\frac{1 + \Gamma_L e^{-j2\beta d}}{1 - \Gamma_L e^{-j2\beta d}} \right)$$

$$V(z) = A \left(e^{-j\beta z} + \Gamma_L e^{+j\beta z} \right)$$

$$I(z) = \frac{1}{Z_0} A \left(e^{-j\beta z} - \Gamma_L e^{+j\beta z} \right)$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$\beta = \omega \sqrt{LC} = \omega \sqrt{\mu \epsilon} = \frac{2\pi f}{c_d} = \frac{2\pi}{\lambda_d}$$

$$\lambda_d = \lambda_0 / \sqrt{\epsilon_r \mu_r}$$

$$Z_{in}^{\text{short}} = jZ_0 \tan(\beta l)$$

$$Z_{in}^{\text{open}} = -jZ_0 \cot(\beta l)$$