

# ECE 3317


## Applied Electromagnetic Waves

Prof. David R. Jackson  
Fall 2023

### Notes 11

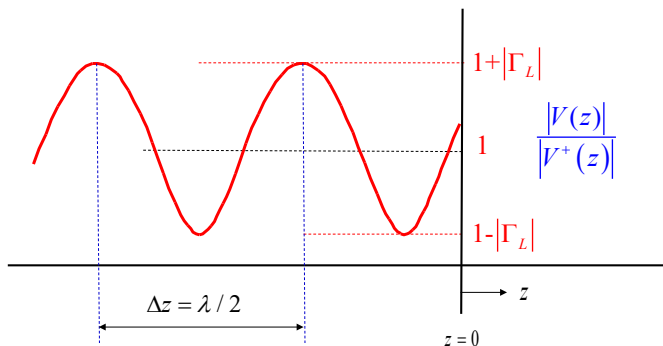
## Transmission Lines

(Standing Wave Ratio (SWR) and Generalized Reflection Coefficient)


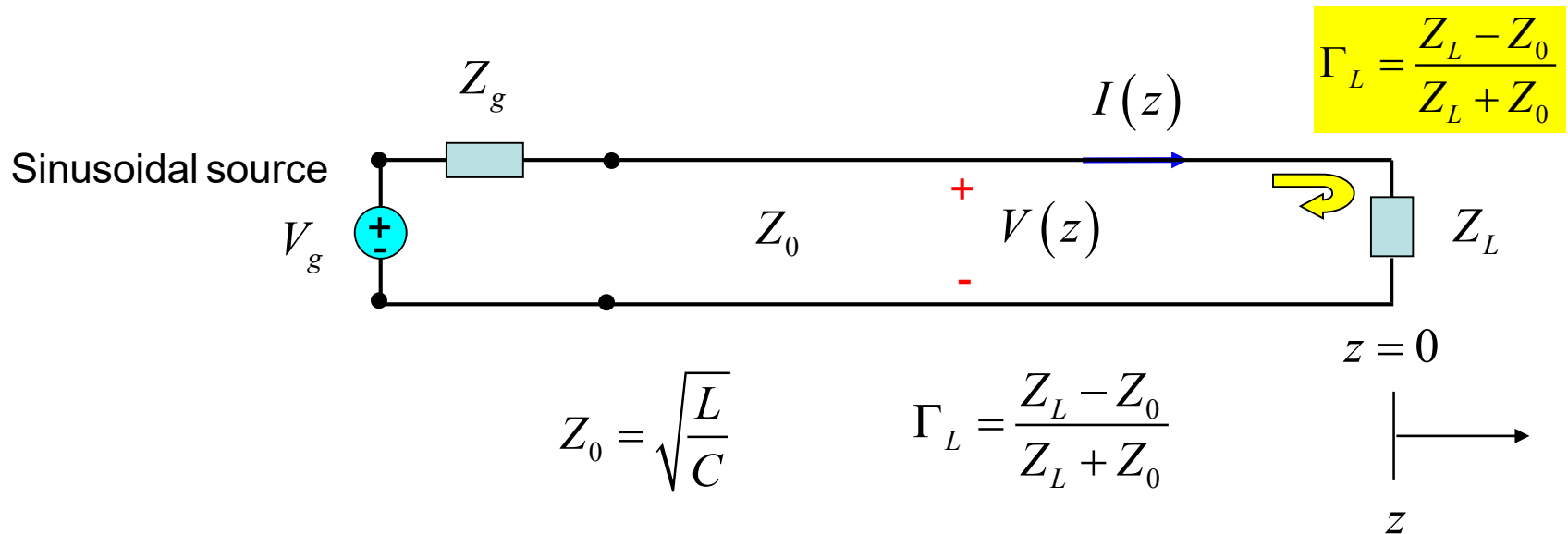
# Standing Wave Ratio

Consider a lossless transmission line that is terminated with a load:




**Lossless line:**

$$\beta = \omega\sqrt{LC} = \omega\sqrt{\mu\varepsilon} = \omega\sqrt{\mu_0\varepsilon_0}\sqrt{\mu_r\varepsilon_r} = k_0\sqrt{\mu_r\varepsilon_r} = \frac{2\pi}{\lambda_d}, \quad \lambda_d = \frac{\lambda_0}{\sqrt{\mu_r\varepsilon_r}}$$

$$k_0 \equiv \omega\sqrt{\mu_0\varepsilon_0} = \frac{\omega}{c} = \frac{2\pi}{\lambda_0} \quad \lambda_0 = \frac{c}{f} \quad c = 2.99792458 \times 10^8 \text{ [m/s]}$$

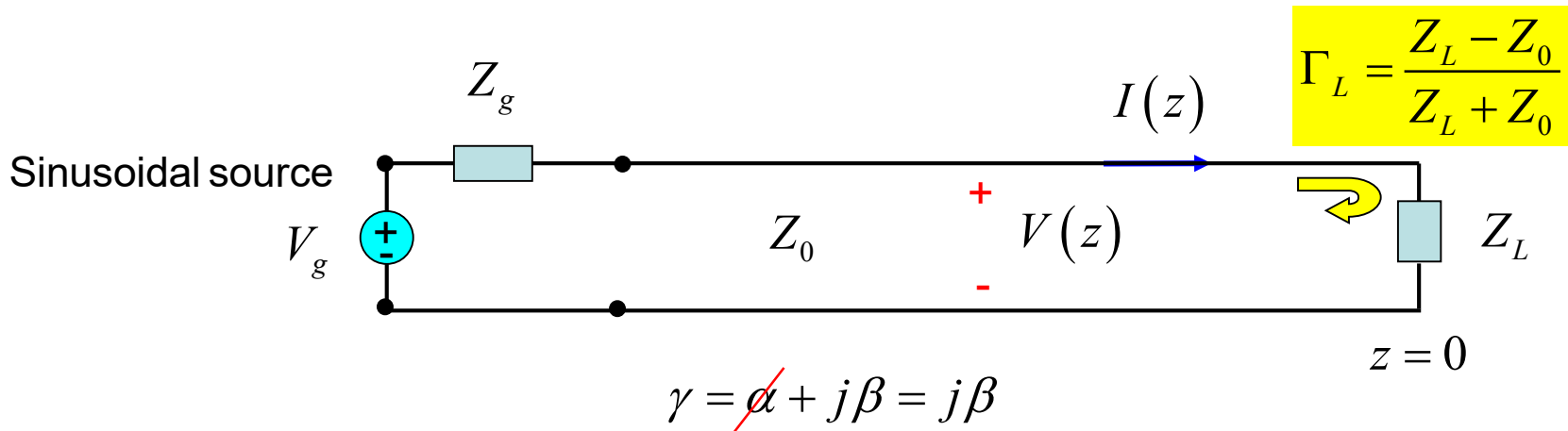
# Standing Wave Ratio (cont.)

Consider a lossless transmission line that is terminated with a load:



$$V(z) = A \left( e^{-j\beta z} + \Gamma_L e^{+j\beta z} \right)$$
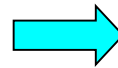
$$I(z) = \frac{1}{Z_0} A \left( e^{-j\beta z} - \Gamma_L e^{+j\beta z} \right)$$



$$V(z) = A e^{-j\beta z} \left( 1 + \Gamma_L e^{+j2\beta z} \right)$$

$$I(z) = \frac{1}{Z_0} A e^{-j\beta z} \left( 1 - \Gamma_L e^{+j2\beta z} \right)$$

$$V^+(z) = A e^{-j\beta z}$$

$$V^-(z) = A \Gamma_L e^{+j\beta z}$$

$$V^-(z) / V^+(z) = \Gamma_L e^{+j2\beta z}$$

# Standing Wave Ratio (cont.)

$$V(z) = Ae^{-j\beta z} \left( 1 + \Gamma_L e^{+j2\beta z} \right)$$

Denote  $\Gamma_L = |\Gamma_L| e^{j\phi}$  (the polar form of  $\Gamma_L$ )

Then we have  $V(z) = Ae^{-j\beta z} \left( 1 + |\Gamma_L| e^{+j(\phi+2\beta z)} \right)$

The magnitude is  $|V(z)| = |A| \left| 1 + |\Gamma_L| e^{+j(\phi+2\beta z)} \right|$

Maximum voltage:  $V_{\max} \equiv |V(z)|_{\max} = |A|(1 + |\Gamma_L|)$   $\phi + 2\beta z_{\max} = 2\pi m$

Minimum voltage:  $V_{\min} \equiv |V(z)|_{\min} = |A|(1 - |\Gamma_L|)$   $\phi + 2\beta z_{\min} = \pi + 2\pi n$

$$m, n = 0, \pm 1, \pm 2, \dots$$

# Standing Wave Ratio (cont.)

The voltage standing wave ratio is the ratio of  $V_{\max}$  to  $V_{\min}$ .

$$\text{VSWR} \equiv \frac{V_{\max}}{V_{\min}}$$

We then have:

$$\text{VSWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

$$1 \leq \text{VSWR} \leq \infty$$



Perfect match:  $\Gamma_L = 0$



Reactive load:  $|\Gamma_L| = 1$

# Standing Wave Ratio (cont.)

For the **current** we have

$$|I(z)| = |A| \left( \frac{1}{Z_0} \right) \left| 1 - |\Gamma_L| e^{+j(\phi + 2\beta z)} \right|$$

Hence we have:

$$I_{\max} \equiv |I(z)|_{\max} = |A| \left( \frac{1}{Z_0} \right) (1 + |\Gamma_L|) \quad \phi + 2\beta z_{\max} = \pi + 2\pi n$$

$$I_{\min} \equiv |I(z)|_{\min} = |A| \left( \frac{1}{Z_0} \right) (1 - |\Gamma_L|) \quad \phi + 2\beta z_{\min} = 2\pi m$$

The current standing wave ratio is thus

$$\text{ISWR} \equiv \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

Hence

$$\text{VSWR} = \text{ISWR} = \text{SWR}$$

**Note:**

The current is maximum where the voltage is minimum, and vice versa.

# Standing Wave Pattern


$$|V(z)| = |A| \underbrace{\left| 1 + |\Gamma_L| e^{+j(\phi+2\beta z)} \right|}_{\text{Plot this part.}}$$

$$|V^N(z)| \equiv \left| \frac{V(z)}{V^+(z)} \right| = \left| 1 + |\Gamma_L| e^{+j(\phi+2\beta z)} \right|$$

Plot this part.

$$2\beta z = 2 \left( \frac{2\pi}{\lambda_d} \right) z = 4\pi \left( \frac{z}{\lambda_d} \right)$$

$$\Gamma_L = |\Gamma_L| e^{j\phi}$$

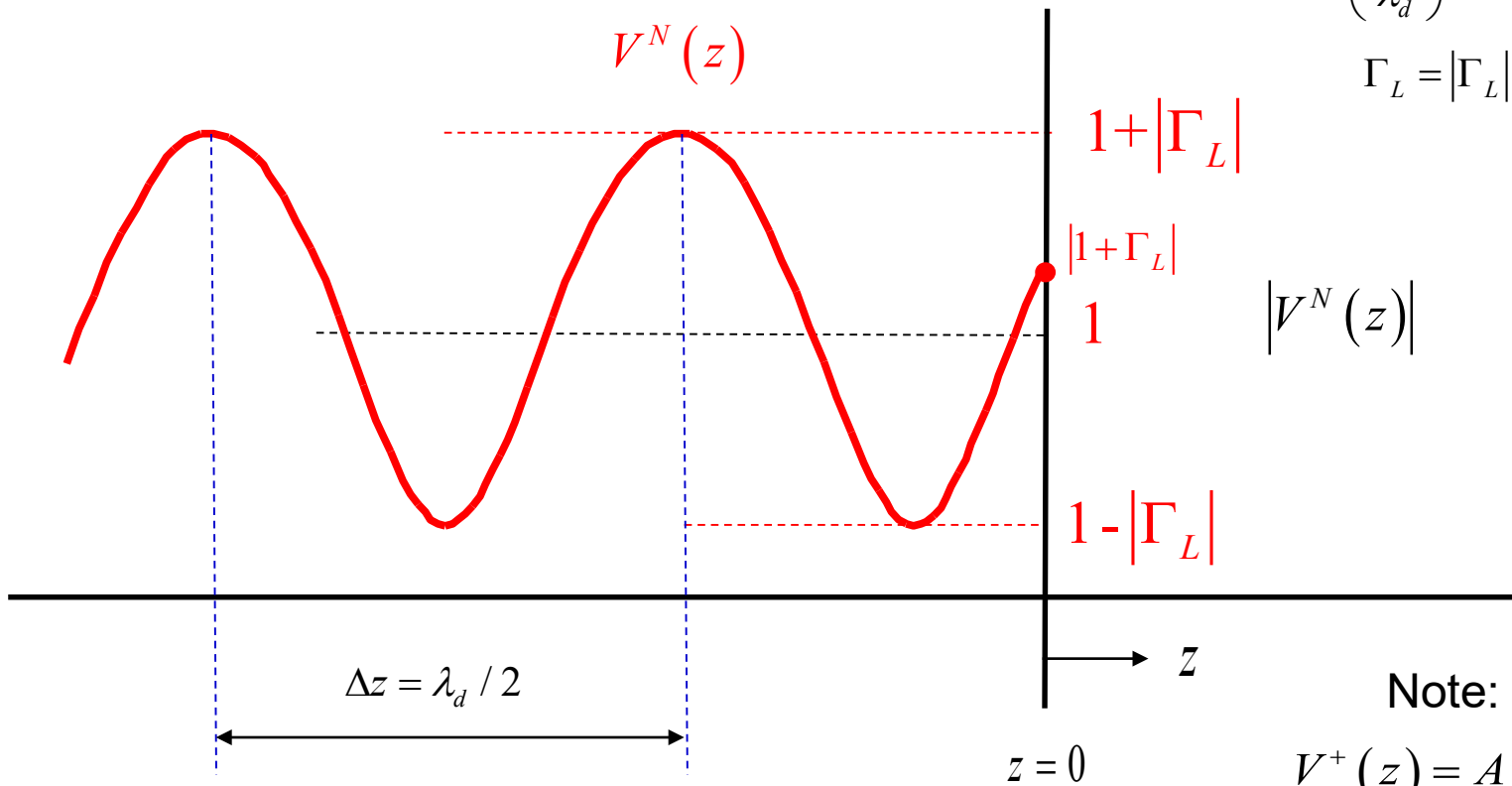

$|V^N(z)|$

Note:

$$V^+(z) = A e^{-j\beta z}$$

$$|V^+(z)| = |A|$$

( $V^+$  is the net wave going in the  $+z$  direction.)


# Standing Wave Pattern (cont.)

For a real load ( $Z_L = R_L$ ):

$\Gamma_L$  is real, and there is always a voltage maximum or minimum at the load ( $z = 0$ ).

$$R_L < Z_0 \Rightarrow \Gamma_L < 0 \Rightarrow \phi = \pi \Rightarrow \text{voltage minimum at } z = 0 \quad (\phi + 2\beta z_{\min} = \pi + 2\pi n)$$
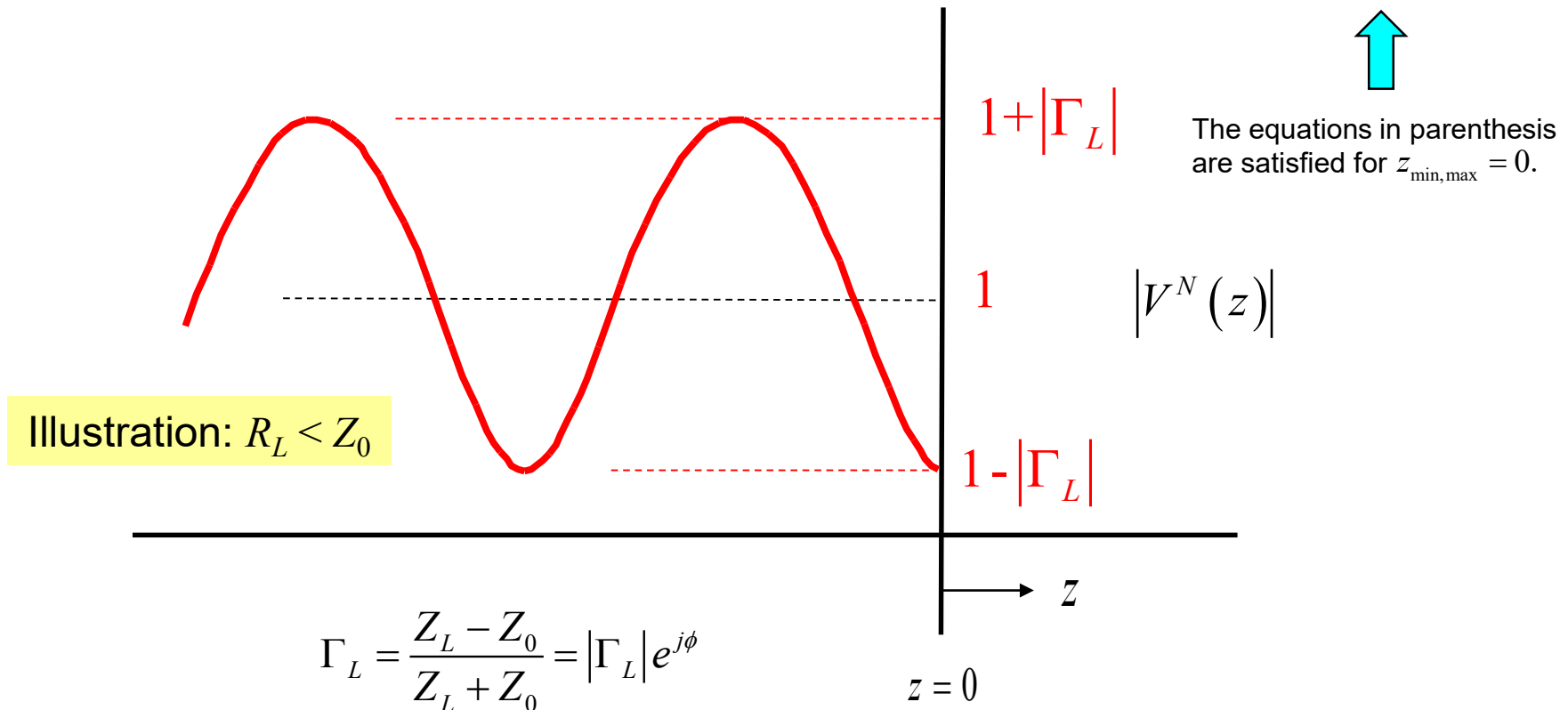
$$R_L > Z_0 \Rightarrow \Gamma_L > 0 \Rightarrow \phi = 0 \Rightarrow \text{voltage maximum at } z = 0 \quad (\phi + 2\beta z_{\max} = 2\pi m)$$





# Standing Wave Ratio: Real Load

Special case of a real load impedance  $Z_L = R_L$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{R_L - Z_0}{R_L + Z_0}$$

$$\text{SWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + \left| \frac{R_L - Z_0}{R_L + Z_0} \right|}{1 - \left| \frac{R_L - Z_0}{R_L + Z_0} \right|}$$

Case a:  $R_L \geq Z_0$

$$\text{SWR} = \frac{1 + \left( \frac{R_L - Z_0}{R_L + Z_0} \right)}{1 - \left( \frac{R_L - Z_0}{R_L + Z_0} \right)} = \frac{(R_L + Z_0) + (R_L - Z_0)}{(R_L + Z_0) - (R_L - Z_0)}$$

# Standing Wave Ratio: Real Load (cont.)

Hence

$$\text{SWR} = \frac{R_L}{Z_0} \quad (R_L \geq Z_0)$$

Case b:  $R_L \leq Z_0$

$$\text{SWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 - \left( \frac{R_L - Z_0}{R_L + Z_0} \right)}{1 + \left( \frac{R_L - Z_0}{R_L + Z_0} \right)} = \frac{\cancel{(R_L + Z_0)} - \cancel{(R_L - Z_0)}}{\cancel{(R_L + Z_0)} + \cancel{(R_L - Z_0)}}$$

Hence

$$\text{SWR} = \frac{Z_0}{R_L} \quad (R_L \leq Z_0)$$

# Standing Wave Ratio: Real Load (cont.)

Hence, for a real load impedance we have:

$$\text{SWR} = \max \left( \frac{R_L}{Z_0}, \frac{Z_0}{R_L} \right)$$

(We choose whichever one is greater than 1.)

# Example (6.6, Shen and Kong)

Given:  $Z_L = 17.4 - j30 \text{ } [\Omega]$  and  $Z_0 = 50 \text{ } [\Omega]$

Find:  $\Gamma_L$ , SWR,  $z_{\min}$ ,  $V_{\max}^N$ ,  $V_{\min}^N$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$




$$\Gamma_L = -0.24 - j0.55$$

$$= 0.6 e^{-j(1.99)}$$

$$|\Gamma_L| = 0.6$$
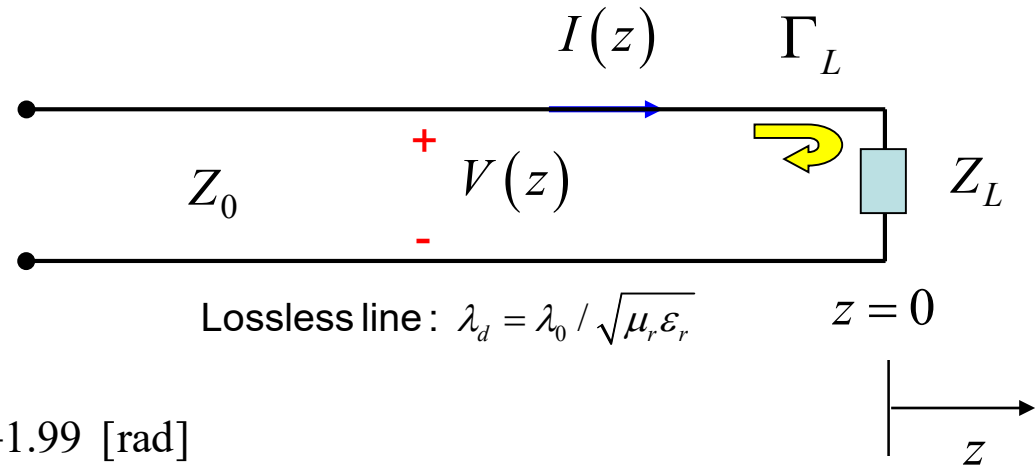
$$\phi = \angle \Gamma_L = -1.99 \text{ [rad]}$$



$$\text{SWR} = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 0.6}{1 - 0.6} = 4.0$$



$$V_{\max}^N = V_{\max} / |V^+| = 1 + |\Gamma_L| = 1.6$$

$$V_{\min}^N = V_{\min} / |V^+| = 1 - |\Gamma_L| = 0.4$$


$$V_{\max} \text{ when } \phi + 2\beta z_{\max} = 0, \pm 2\pi, \dots$$

$$V_{\min} \text{ when } \phi + 2\beta z_{\min} = \pm\pi, \pm 3\pi, \dots$$

$$z_{\min} = \frac{-\pi - \phi}{2\beta} = \frac{(-\pi + 1.99)}{2(2\pi / \lambda_d)} = -0.092\lambda_d$$

(Choose  $-\pi$ : pick the value of  $z_{\min}$  closest to the load.)

# Example (6.6, Shen and Kong) (cont.)

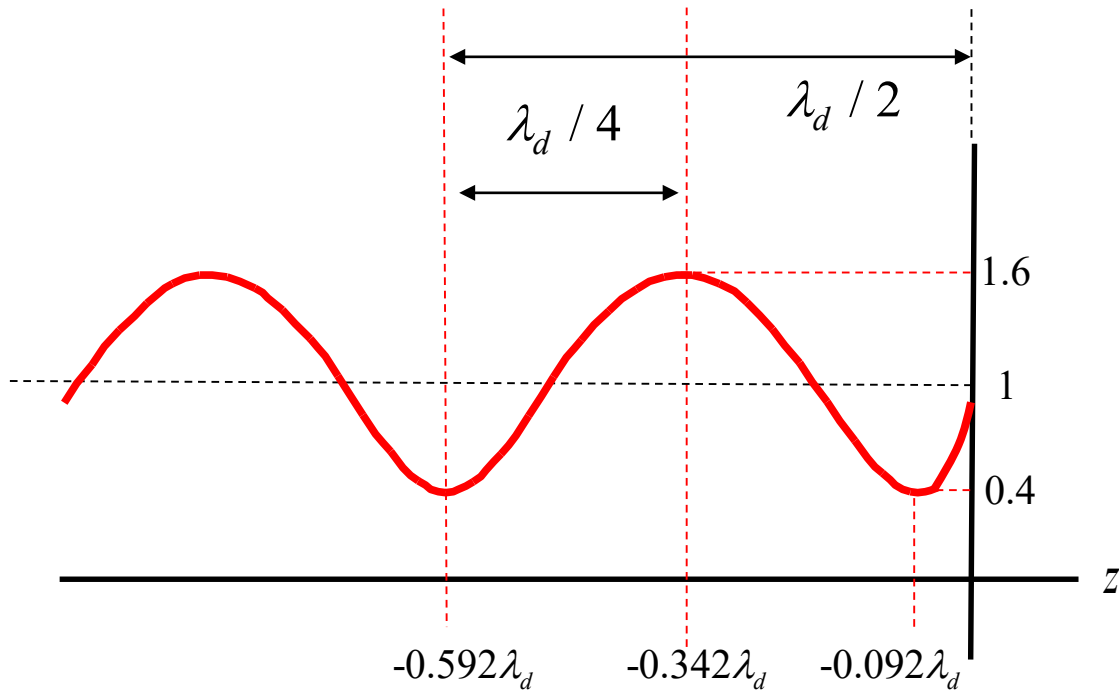

$$|V^N(z)| = \left| 1 + |\Gamma_L| e^{+j(\phi + 2\beta z)} \right|$$



$$|V^N(z)| = \left| 1 + (0.6) e^{+j(-1.99 + 4\pi(z/\lambda_d))} \right|$$

$$|V^N(z)|$$

$$\Gamma_L = -0.24 - j0.55$$

$$= 0.6 e^{-j(1.99)}$$

$$\text{SWR} = 4.0$$

$$z_{\min} = -0.092\lambda_d$$

$$V_{\max} / |V^+| = 1.6$$

$$V_{\min} / |V^+| = 0.4$$

# Example (6.6, Shen and Kong) (cont.)

Reverse problem:

Given:  $\text{SWR} = 4.0$   $z_{\min} = -0.092\lambda_d$

This problem has practical significance: often we are interested in figuring out what an unknown load is.



What is the unknown load impedance?

$$\text{SWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = 4.0 \quad \Rightarrow \quad \text{SWR}(1 - |\Gamma_L|) = 1 + |\Gamma_L| \quad \Rightarrow \quad |\Gamma_L| = \frac{\text{SWR} - 1}{\text{SWR} + 1}$$

$$|\Gamma_L| = 0.6$$

so

$$|\Gamma_L| = \frac{4.0 - 1}{4.0 + 1} = 0.6$$

$$z_{\min} = \frac{-\pi - \phi}{2\beta} = \frac{(-\pi - \phi)}{2(2\pi / \lambda_d)} = -0.092\lambda_d$$

$$\Gamma_L = 0.6 e^{-j(1.99)}$$



$$\phi = \angle \Gamma_L = -1.99 \text{ [rad]}$$

(Note: Any multiple of  $2\pi$  can be added to  $\phi$ .)

Solve for  $\phi$ .

## Example (6.6, Shen and Kong) (cont.)

$$\Gamma_L = 0.6 e^{-j(1.99)}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \Rightarrow \quad (Z_L + Z_0)\Gamma_L = Z_L - Z_0$$

$$\Rightarrow \quad Z_L = Z_0 \left( \frac{1 + \Gamma_L}{1 - \Gamma_L} \right)$$

Hence, we have  $Z_L = 50 \left( \frac{1 + 0.6 e^{-j(1.99)}}{1 - 0.6 e^{-j(1.99)}} \right)$


The calculation yields:

$$Z_L = 17.4 - j30 \text{ } [\Omega]$$

We have solved  
for the unknown  
load impedance!
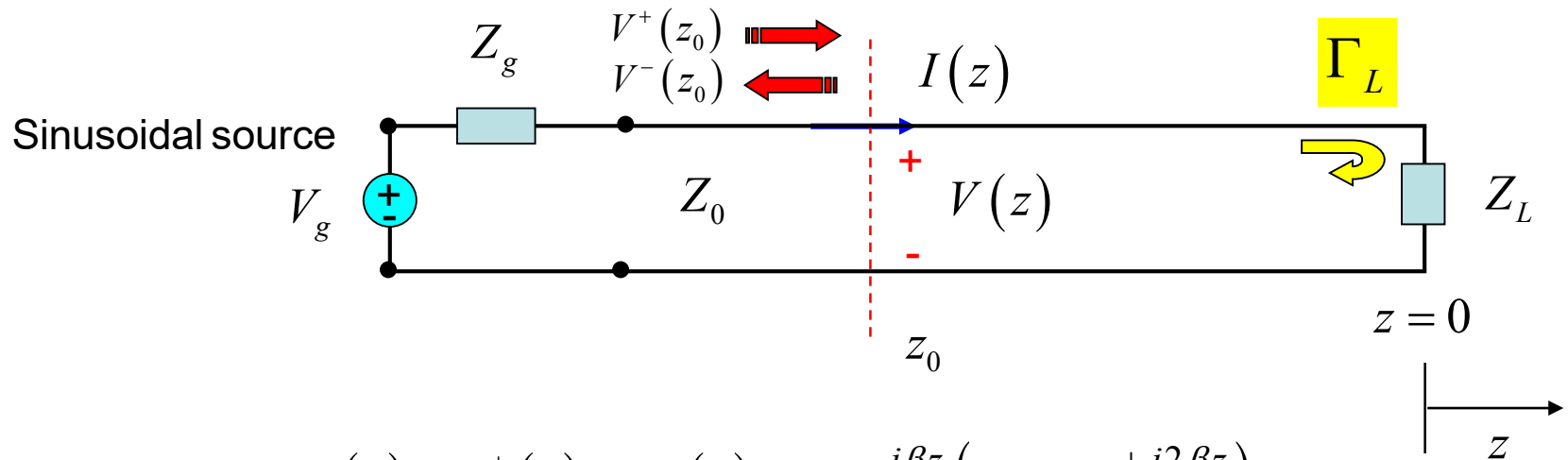
# Generalized Reflection Coefficient


Define the “generalized reflection coefficient” at a point  $z_0$  on the line:



$$V(z) = V^+(z) + V^-(z) = Ae^{-j\beta z} (1 + \Gamma_L e^{+j2\beta z})$$

$$V^+(z) = Ae^{-j\beta z}, \quad V^-(z) = A\Gamma_L e^{+j\beta z}$$
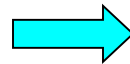
$$\Gamma(z_0) \equiv \frac{V^-(z_0)}{V^+(z_0)}$$




$$\Gamma(z_0) = \Gamma_L e^{+j2\beta z_0}$$


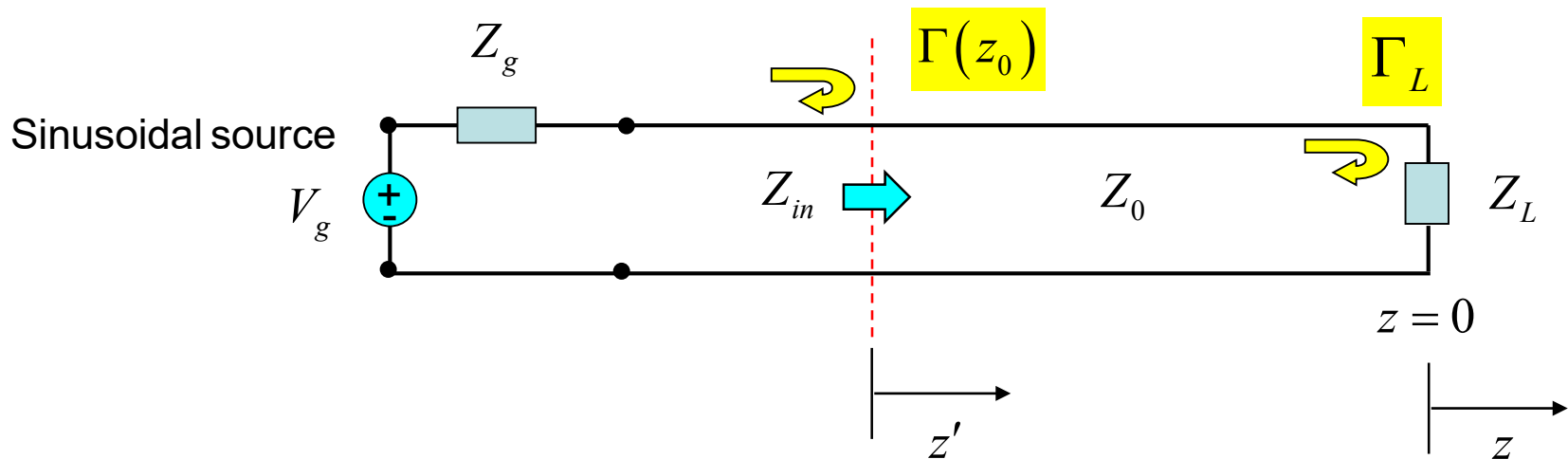
# Generalized Reflection Coefficient (cont.)

We identify  $\Gamma(z_0)$  as the reflection coefficient at the point  $z_0$ , with  $Z_{in}$  acting as the load impedance.



Hence

$$\Gamma(z_0) = \frac{Z_{in}(z_0) - Z_0}{Z_{in}(z_0) + Z_0}$$

# Generalized Reflection Coefficient (cont.)

$$\Gamma(z_0) = \frac{Z_{in}(z_0) - Z_0}{Z_{in}(z_0) + Z_0}$$

Hence

$$(Z_{in}(z_0) + Z_0)\Gamma(z_0) = Z_{in}(z_0) - Z_0$$



$$Z_{in}(z_0)[1 - \Gamma(z_0)] = Z_0[1 + \Gamma(z_0)]$$



$$Z_{in}(z_0) = Z_0 \left( \frac{1 + \Gamma(z_0)}{1 - \Gamma(z_0)} \right)$$

# Generalized Reflection Coefficient (cont.)

Define a normalized input impedance at point  $z_0$ :

$$Z_{in}^N(z_0) \equiv \frac{Z_{in}(z_0)}{Z_0}$$

We then have, from the last slide

$$Z_{in}^N(z_0) = \left( \frac{1 + \Gamma(z_0)}{1 - \Gamma(z_0)} \right)$$

$$\Gamma(z_0) = \Gamma_L e^{+j2\beta z_0}$$

**Note:**

This can be used as an alternative formula to the “tangent formula” for calculating input impedance at  $z_0 = -d$ .

(This is the starting point for the Smith chart discussion.)


# Crank Diagram

$$|V^N(z)| = \left| 1 + |\Gamma_L| e^{+j(\phi + 2\beta z)} \right| = |1 + \Gamma(z)|$$

where  $\Gamma(z) \equiv \Gamma_L e^{+j(2\beta z)}$

$$\Gamma_L = |\Gamma_L| e^{+j\phi}$$

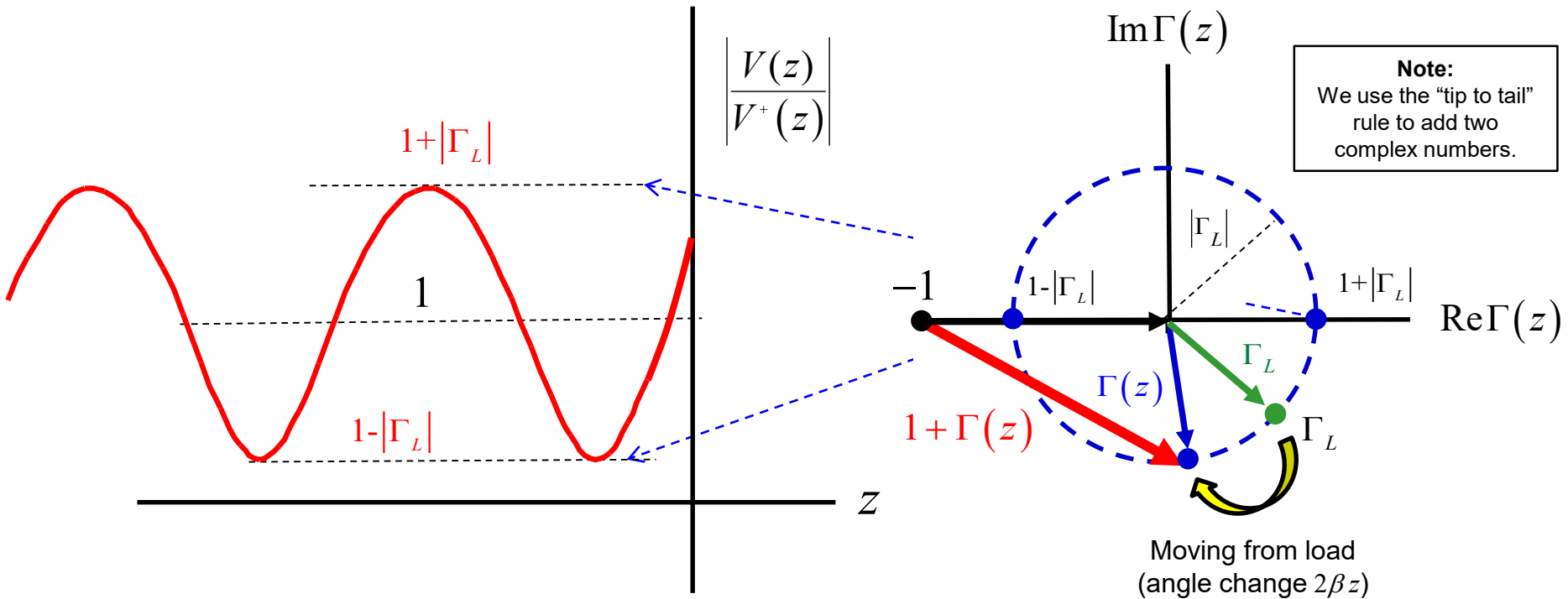Note:  $\Gamma(z) = \frac{V^-(z)}{V^+(z)}$



**Note:** We go all the way around the crank diagram when  $z = -\lambda_d / 2$ :

$$2\beta z = 2 \left( \frac{2\pi}{\lambda_d} \right) \left( -\frac{\lambda_d}{2} \right) = -2\pi$$

# Example

Given:  $Z_L = 100 \text{ } [\Omega]$  and  $Z_0 = 50 \text{ } [\Omega]$

Calculate the reflection coefficient and the input impedance at  $z_0 = -0.125\lambda_d$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1}{3}$$


$$\Gamma(z_0) = \Gamma_L e^{j2\beta z_0}$$

$$= \left(\frac{1}{3}\right) e^{j2\left(\frac{2\pi}{\lambda_d}\right)(-0.125\lambda_d)} = \left(\frac{1}{3}\right) e^{-j\pi/2}$$

so

$$\Gamma(z_0) = -j/3$$
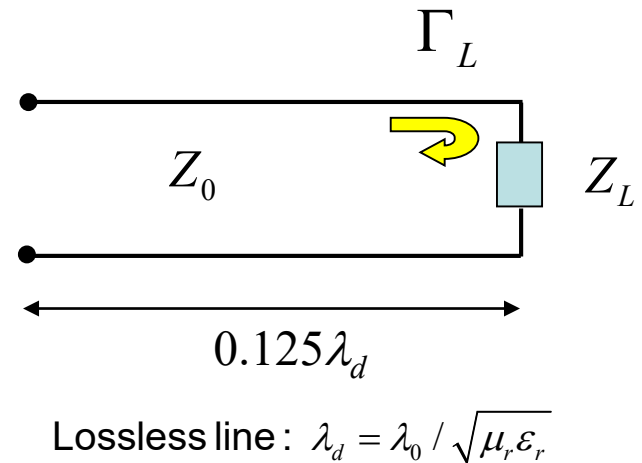
$$Z_{in}^N(z_0) = \left(\frac{1 + \Gamma(z_0)}{1 - \Gamma(z_0)}\right) = \frac{1 - j/3}{1 + j/3} = 0.8 + j(0.6)$$



$$Z_{in}(z_0) = (50) Z_{in}^N(z_0)$$

so

$$Z_{in}(z_0) = 40 + j(30) \text{ } [\Omega]$$

# Appendix: Summary of Formulas

$$\text{SWR} \equiv \frac{V_{\max}}{V_{\min}}$$

$$\text{SWR} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

$$\text{SWR} = \max\left(\frac{R_L}{Z_0}, \frac{Z_0}{R_L}\right)$$

$$|\Gamma_L| = \frac{\text{SWR} - 1}{\text{SWR} + 1}$$

$$Z_{in}(z_0) = Z_0 \left( \frac{1 + \Gamma(z_0)}{1 - \Gamma(z_0)} \right) \quad Z_L = Z_0 \left( \frac{1 + \Gamma_L}{1 - \Gamma_L} \right) \quad Z_{in}^N(z_0) \equiv \frac{Z_{in}(z_0)}{Z_0}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma(z_0) \equiv \frac{V^-(z_0)}{V^+(z_0)}$$

$$\Gamma(z_0) = \Gamma_L e^{+j2\beta z_0}$$

$$\Gamma(z_0) = \frac{Z_{in}(z_0) - Z_0}{Z_{in}(z_0) + Z_0}$$