

ECE 3318

Applied Electricity and Magnetism

Spring 2023

Prof. David R. Jackson
Dept. of ECE



Notes 33
Mutual Inductance

Mutual Inductance



Two coils are in proximity of each other.

Note: Each coil has a set of output terminals, but this is not shown.

Current reference directions and unit normal vectors are defined on both coils.


(The unit normal vectors are each determined from the corresponding current reference directions, by the right-hand rule for inductor flux.)

Reminder:

Right-hand rule for inductor flux: Fingers are in the direction of the current I in the coil, and the thumb gives the direction of the unit normal (the reference direction for the flux).

Mutual Inductance (cont.)

M_{21}

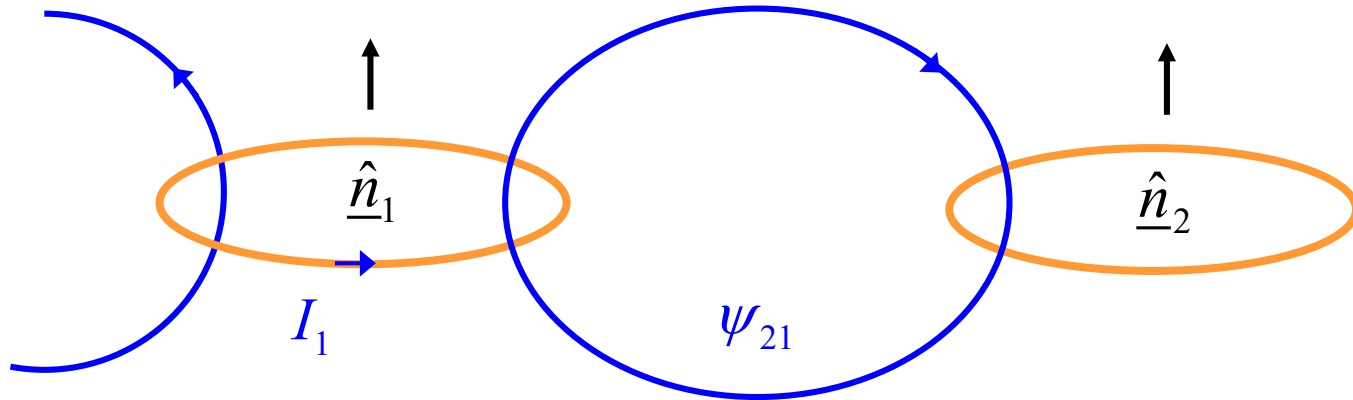

Coil 1 is energized
Coil 2 is left open-circuited

$$\psi_{21} \equiv \int_{S_2} \underline{B}_1 \cdot \underline{\hat{n}}_2 dS$$

Meaning of subscripts:
“the flux through coil 2 due to coil 1”

These two numbers go together.

Define mutual inductance: $M_{21} \equiv \frac{\psi_{21}}{I_1}$


In general, if coil 2 has multiple turns:

$$M_{21} \equiv \frac{\Lambda_{21}}{I_1} = \frac{N_2 \psi_{21}}{I_1}$$

Note:
For the figure shown, $\psi_{21} < 0$ if $I_1 > 0$.
Hence, $M_{21} < 0$.

Mutual Inductance (cont.)

M_{12}

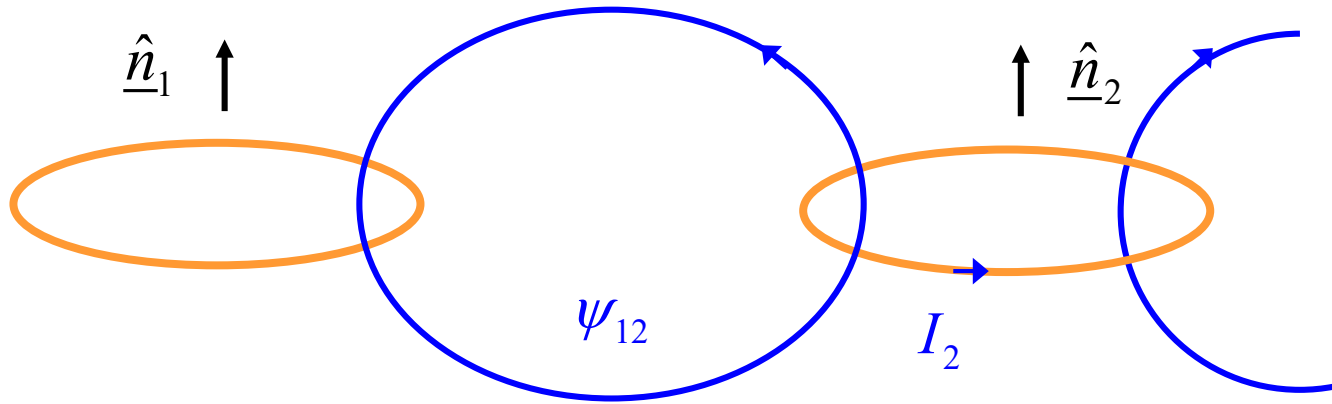

Coil 2 is energized
Coil 1 is left open-circuited

$$\psi_{12} = \int_{S_1} \underline{B}_2 \cdot \underline{\hat{n}}_1 dS$$

Meaning of subscripts:
“the flux through coil 1 due to coil 2”

These two numbers go together.

Define mutual inductance: $M_{12} \equiv \frac{\psi_{12}}{I_2}$

In general, if coil 1 has multiple turns:

$$M_{12} \equiv \frac{\Lambda_{12}}{I_2} = \frac{N_1 \psi_{12}}{I_2}$$

Note:
For the figure shown, $\psi_{12} < 0$ if $I_2 > 0$.
Hence, $M_{12} < 0$.

Mutual Inductance (cont.)

A general property (proof omitted) is that both mutual inductance components are always equal:

$$M_{12} = M_{21} = M$$

Note: The units of M are Henrys.

Circuit Law for Coupled Coils

Total flux through coil 1:

$$\begin{aligned}\Lambda_1 &= \Lambda_{11} + \Lambda_{12} \\ &= L_1 i_1 + M_{12} i_2\end{aligned}$$

Faraday's law:

$$v_1 = \frac{d\Lambda_1}{dt}$$


Total flux through coil 2:

$$\begin{aligned}\Lambda_2 &= \Lambda_{22} + \Lambda_{21} \\ &= L_2 i_2 + M_{21} i_1\end{aligned}$$


Faraday's law:

$$v_2 = \frac{d\Lambda_2}{dt}$$
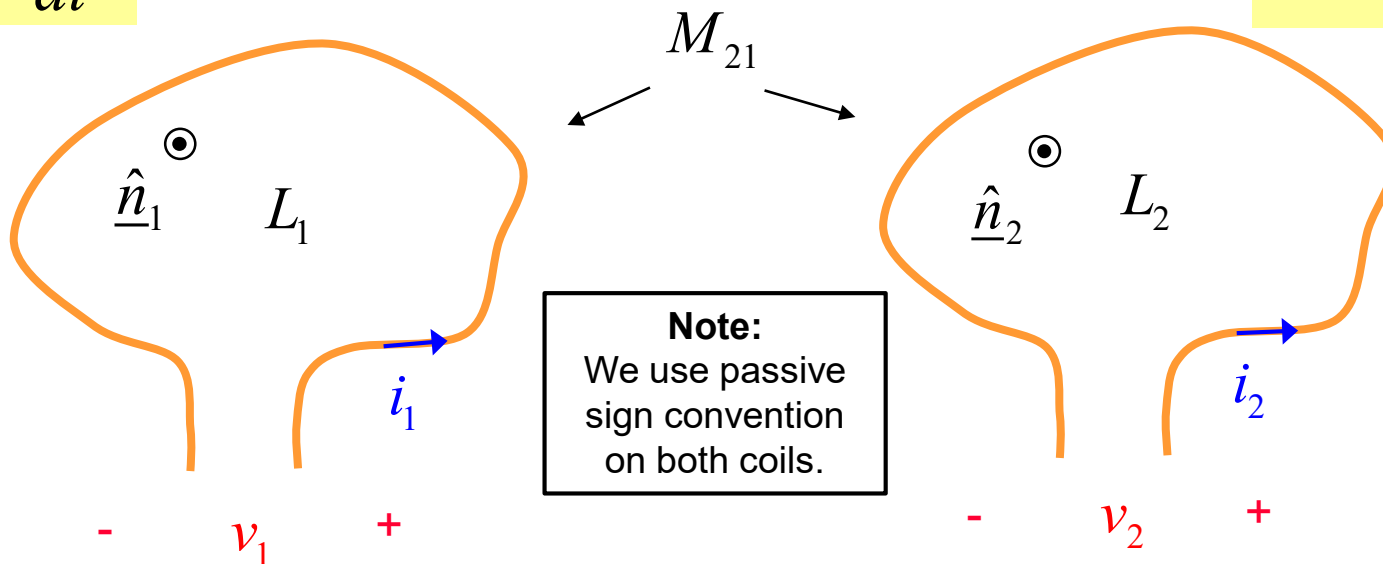
$$\begin{aligned}v_1 &= L_1 \frac{di_1}{dt} + M_{12} \frac{di_2}{dt} \\ v_2 &= L_2 \frac{di_2}{dt} + M_{21} \frac{di_1}{dt}\end{aligned}$$



Example

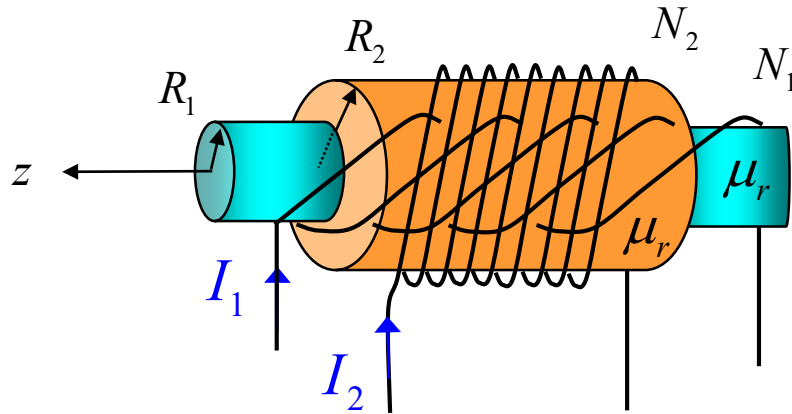

$L_s = \text{length}$

Right-hand rule for inductor flux:

$$\underline{\hat{n}}_1 = \underline{\hat{n}}_2 = \underline{\hat{z}}$$

Find M_{12}, M_{21}

For M_{12} :


$$M_{12} = \frac{\Lambda_{12}}{I_2} = \frac{N_1 \psi_{12}}{I_2}$$

$$\psi_{12} = \int_{S_1} \underline{B}_2 \cdot \underline{\hat{n}}_1 dS = \int_{S_1} B_{z2} dS$$


$$= B_{z2} (\pi R_1^2)$$

$$= \mu_0 \mu_r (n_2 I_2) (\pi R_1^2) = \mu_0 \mu_r \left(\frac{N_2}{L_s} \right) I_2 (\pi R_1^2)$$

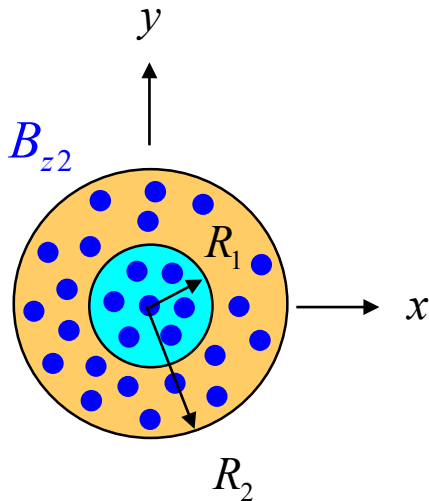
$$M_{12} = N_1 \mu_0 \mu_r \left(\frac{N_2}{L_s} \right) \pi R_1^2 \quad [\text{H}]$$



Example (cont.)

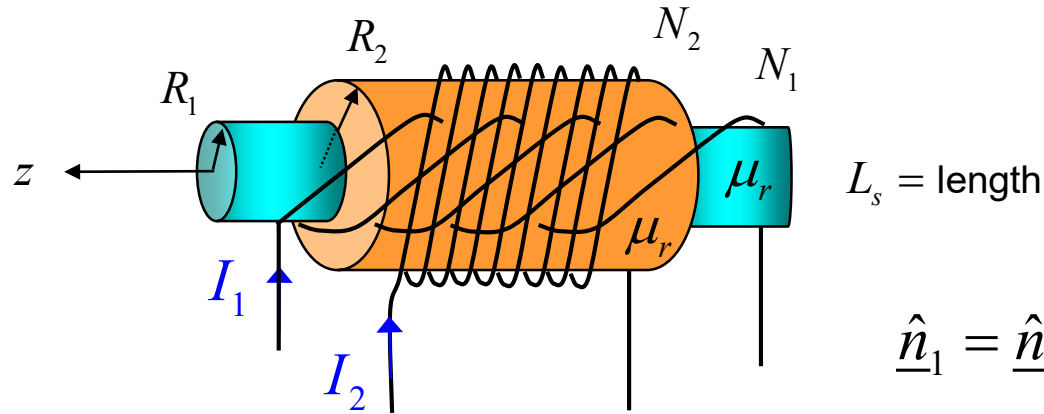

For M_{21} :

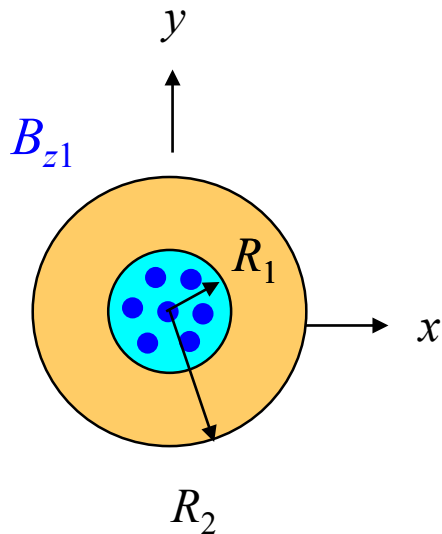

$$M_{21} = \frac{\Lambda_{21}}{I_1} = \frac{N_2 \psi_{21}}{I_1}$$


$$\psi_{21} = \int_{S_2} \underline{B}_1 \cdot \hat{n}_2 dS = \int_{S_2} B_{z1} dS = B_{z1} (\pi R_1^2)$$

$$= \mu_0 \mu_r (n_1 I_1) (\pi R_1^2) = \mu_0 \mu_r \left(\frac{N_1}{L_s} \right) I_1 (\pi R_1^2)$$

$$M_{21} = N_2 \mu_0 \mu_r \left(\frac{N_1}{L_s} \right) \pi R_1^2 \quad [\text{H}]$$

Note:
 $B_{z1} = 0$ for $\rho > R_1$.

Example (cont.)

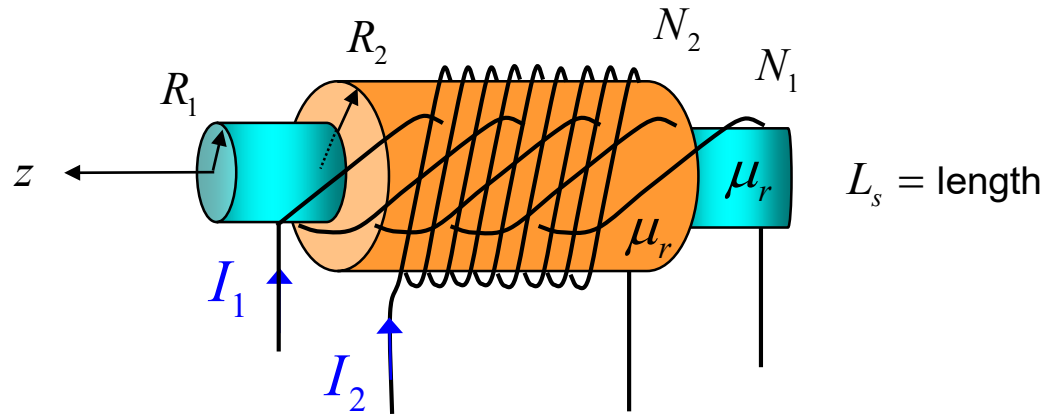

Summary:

$$M_{12} = N_1 \mu_0 \mu_r \left(\frac{N_2}{L_s} \right) \pi R_1^2$$

$$M_{21} = N_2 \mu_0 \mu_r \left(\frac{N_1}{L_s} \right) \pi R_1^2$$

$$M_{12} = M_{21} = M = \mu_0 \mu_r \left(\frac{\pi R_1^2}{L_s} \right) (N_1 N_2) \quad [\text{H}]$$

Dot Convention

The dot convention allows us to use mutual inductance M without having to visually inspect how the coils are wound.

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$


The dots tell us where to put the positive sign for the voltage on one coil, and where the current enters the other coil.

Note:

We also label voltages and currents with the passive sign convention, to be consistent with the self inductance.

Dot Convention (cont.)


Here is one possible dot arrangement:

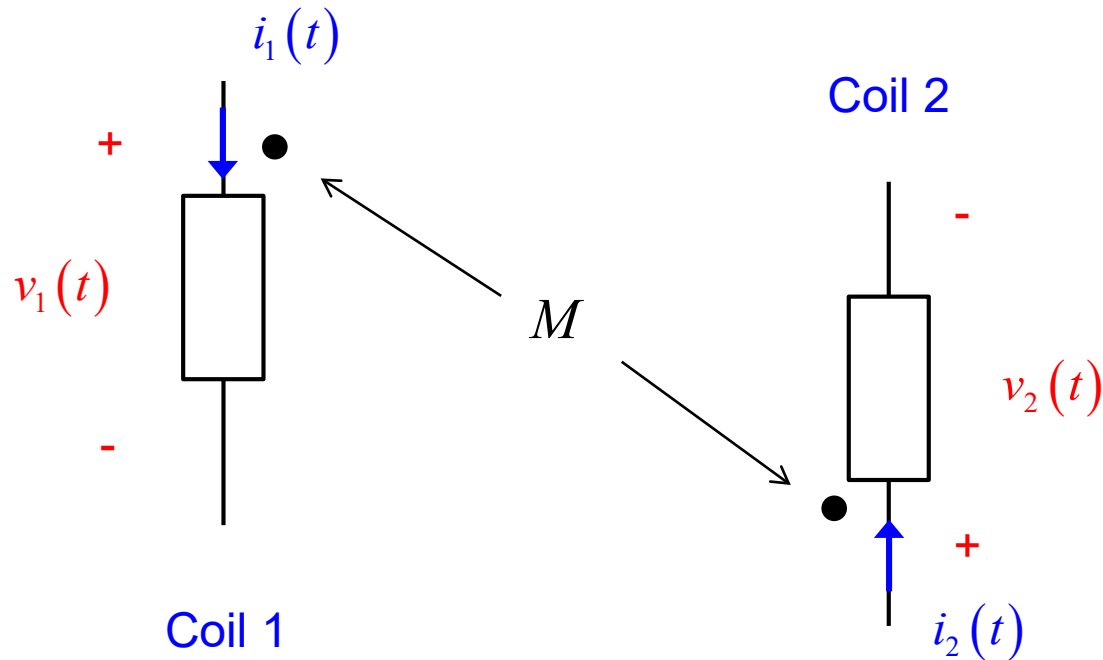

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

Dot Convention (cont.)

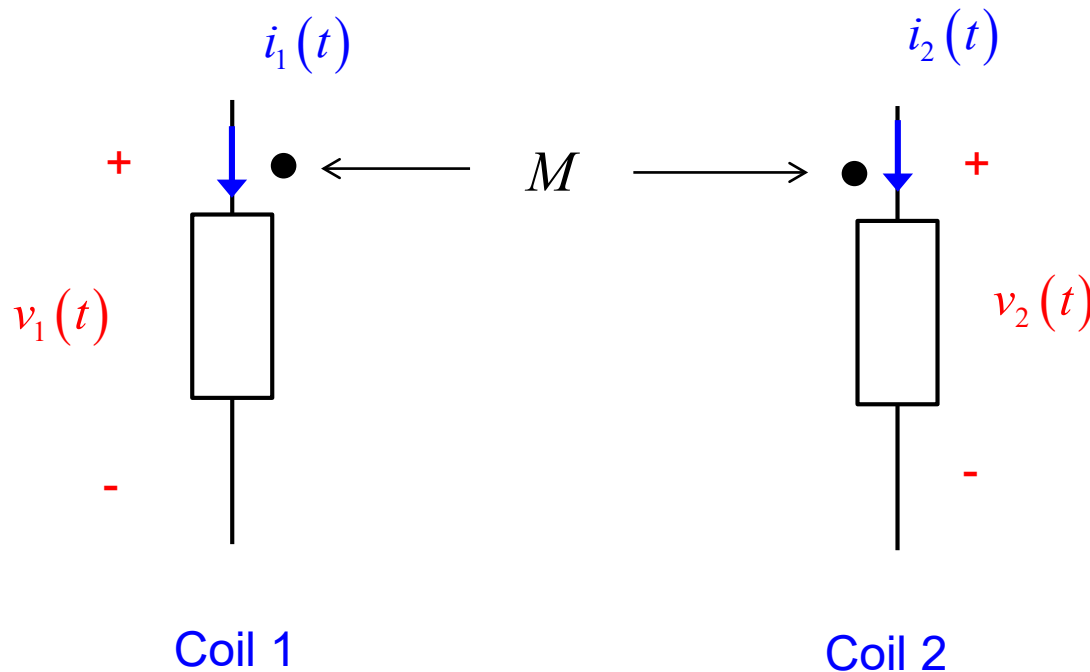Here is another possible dot arrangement:



Note:
The M here is the negative of the M on the last slide (if the coils are the same).


We can always choose the dots to make M positive if we wish.

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

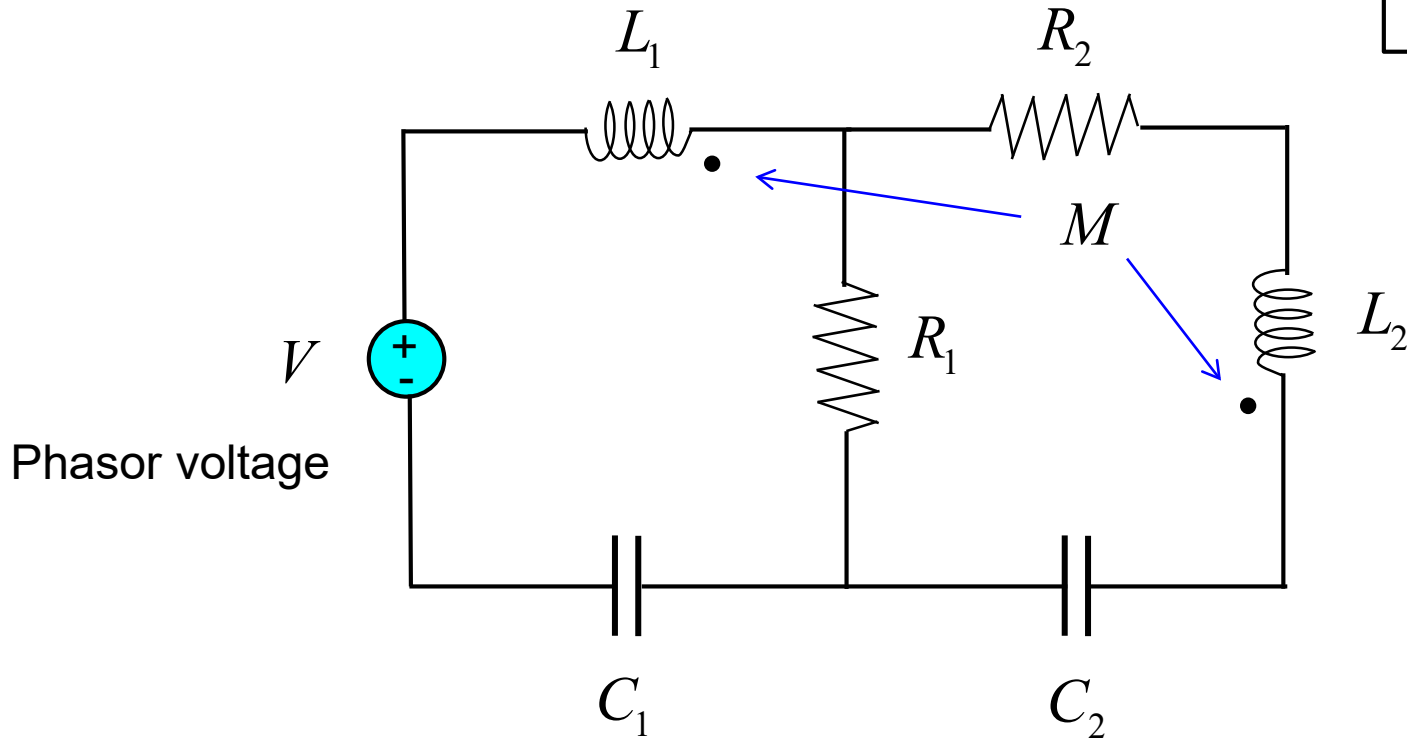Example


Write down KVL phasor-domain mesh-current equations to describe this circuit.

Note:
 M could be either positive or negative.



Example (cont.)

Inductor voltages

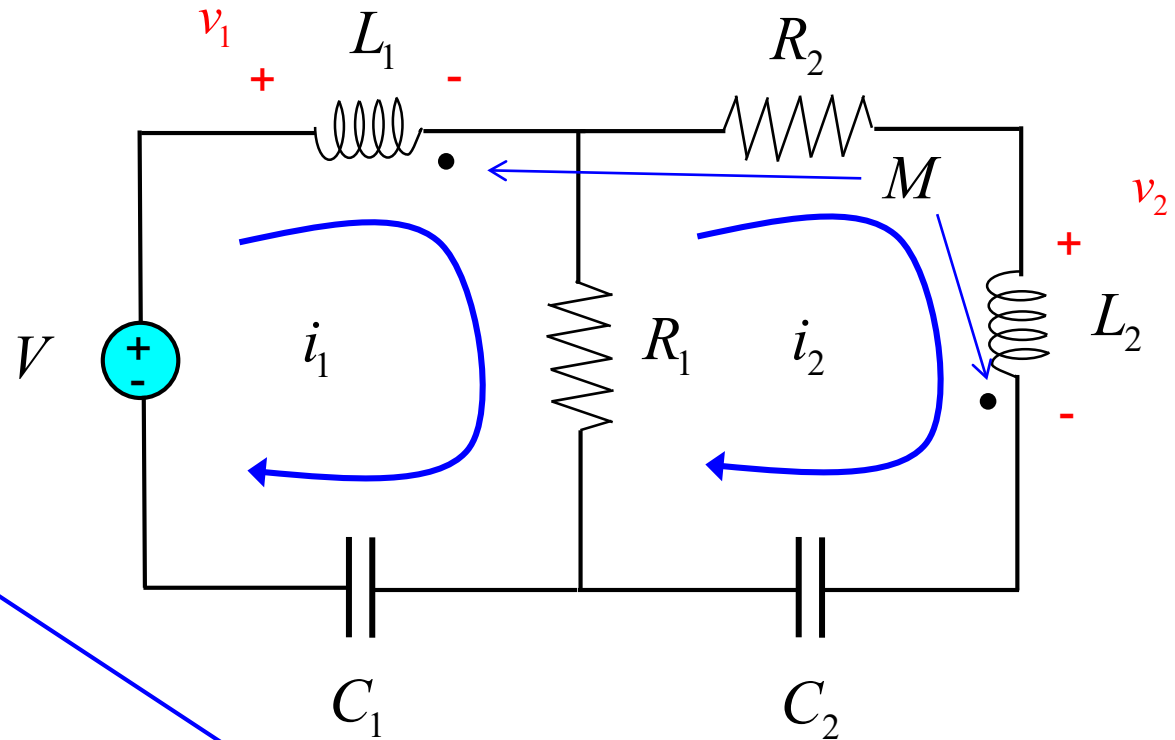

Note:
 In these two equations the first minus sign is from the dot being on the opposite side as the "+" sign of the voltage drop. The second minus sign (the one on the current) is because we want the current going into the dot.

$$v_1 = L_1 \frac{di_1}{dt} - M \frac{d(-i_2)}{dt} \qquad v_2 = L_2 \frac{di_2}{dt} - M \frac{d(-i_1)}{dt}$$




Phasor domain

$$V_1 = j\omega L_1 I_1 + j\omega M I_2 \qquad V_2 = j\omega L_2 I_2 + j\omega M I_1$$

Example (cont.)

KVL

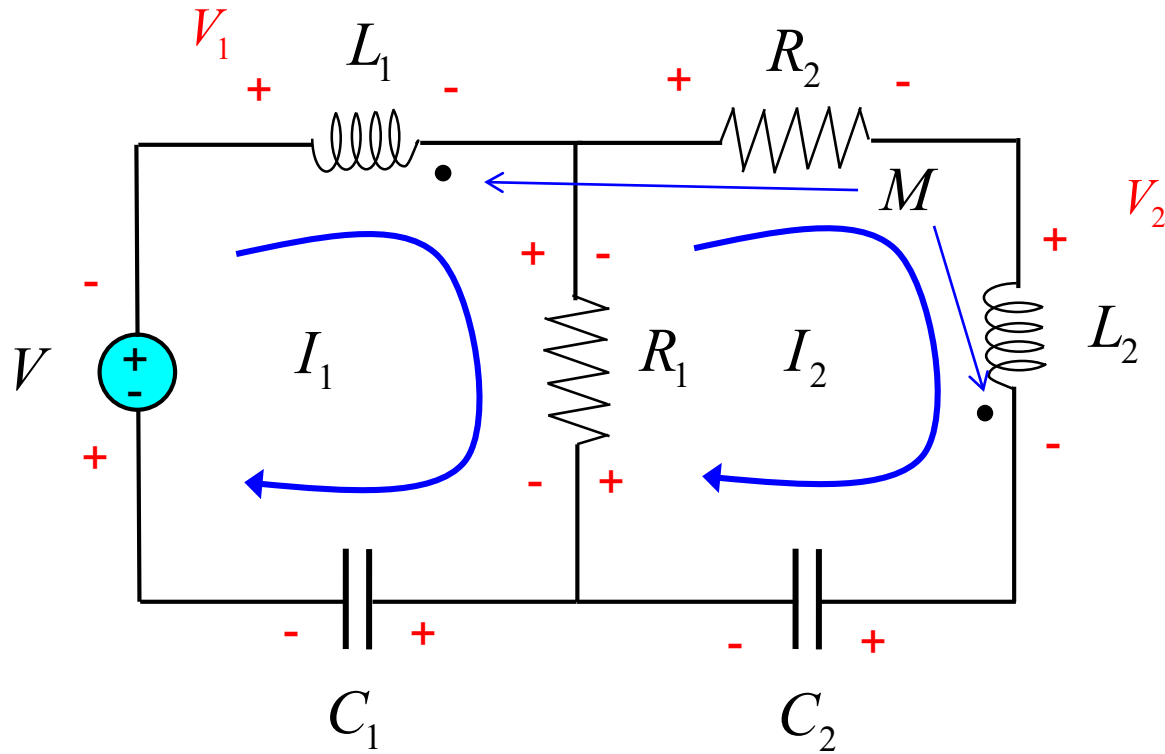

$$-V + [j\omega L_1 I_1 + j\omega M I_2] + R_1 (I_1 - I_2) + \left(\frac{1}{j\omega C_1} \right) I_1 = 0$$

$$R_1 (I_2 - I_1) + R_2 I_2 + [j\omega L_2 I_2 + j\omega M I_1] + \left(\frac{1}{j\omega C_2} \right) I_2 = 0$$