


1-40 points) In the amplifier circuit shown, find

25 a) The transfer function V_o/V_s .

5 b) The Passband gain.

5 c) The input and output resistance in the passband
(do not include the source and the load resistance)

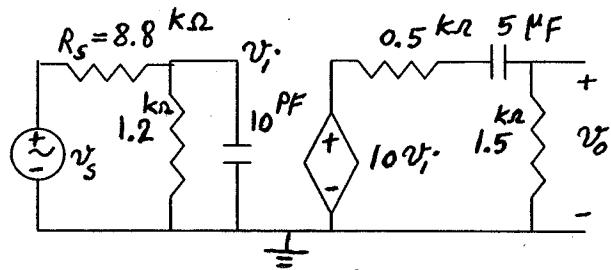5 d) The lower and higher cut-off frequencies and bandwidth.



Solution:

$$a) Z_1 = R_1 \parallel C_1 = \frac{R_1 \times \frac{1}{C_1 s}}{R_1 + \frac{1}{C_1 s}} = \frac{R_1}{1 + R_1 C_1 s}$$

$$\frac{V_i}{V_s} = \frac{Z_1}{Z_1 + R_s} = \frac{\frac{R_1}{1 + R_1 C_1 s}}{\frac{R_1}{1 + R_1 C_1 s} + R_s} = \frac{R_1}{(R_s + R_1) + R_1 R_s C_1 s}$$

$$V_o = \mu V_i \cdot \frac{R_L}{R_L + R_2 + \frac{1}{sC_2}} = \mu V_i \frac{R_L C_2 s}{1 + (R_2 + R_L) C_2 s}$$

$$\frac{V_o}{V_i} = \frac{\mu R_L C_2 s}{1 + (R_2 + R_L) C_2 s}$$


$$\frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s} = \frac{\mu R_1 R_L C_2 s}{[1 + (R_2 + R_L) C_2 s][(R_1 + R_s + R_1 R_s C_1 s)]}$$

Plugging numbers $\frac{V_o}{V_s} = 9 \times 10^{-3} \frac{s}{(1 + 1.056 \times 10^{-8} s)(1 + 10^{-2} s)}$

b) The Passband gain is obtained when C_1 is open and C_2 is short

$$\left| \frac{V_o}{V_s} \right|_{\text{Passband}} = \mu \frac{R_L R_1}{(R_L + R_2)(R_1 + R_s)} = 0.9$$

Passband

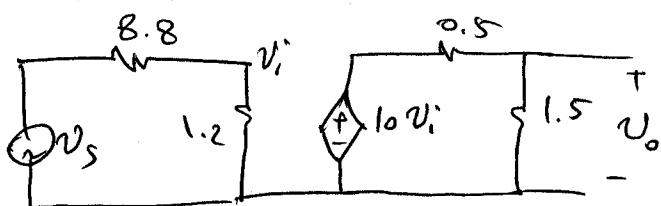

c) $R_i = 1.2 \text{ k}\Omega \quad R_o = 0.5 \text{ k}\Omega$

d) $f_L = \frac{1}{2\pi \times 10^{-2}} = 15.91 \text{ Hz}$

$$f_H = \frac{1}{2\pi (R_1 \parallel R_s) C_1} = 15.9 \text{ MHz}$$

2-20 Points) Draw the bode plot of the magnitude of the transfer function

$$T(s) = -10^8 \frac{s(s+1000)}{(s+100)(s+10000)(s+1000000)}$$

Solution: we can rewrite the above transfer function as


$$T(s) = -10^{-1} \frac{s(1+10^{-3}s)}{(1+10^2s)(1+10^4s)(1+10^6s)}$$


$$\begin{aligned} 20 \log|T(s)| &= 20 \log 0.1 + 20 \log \omega + 20 \log \left| \frac{1+10^{-3}\omega}{1} \right| + 20 \log \frac{1}{1+10^2\omega} \\ &\quad + 20 \log \frac{1}{1+10^4\omega} + 20 \log \frac{1}{1+10^6\omega} \end{aligned}$$

We can draw the magnitude plot
of each part and add them

The sum of shown plots are


in the next page

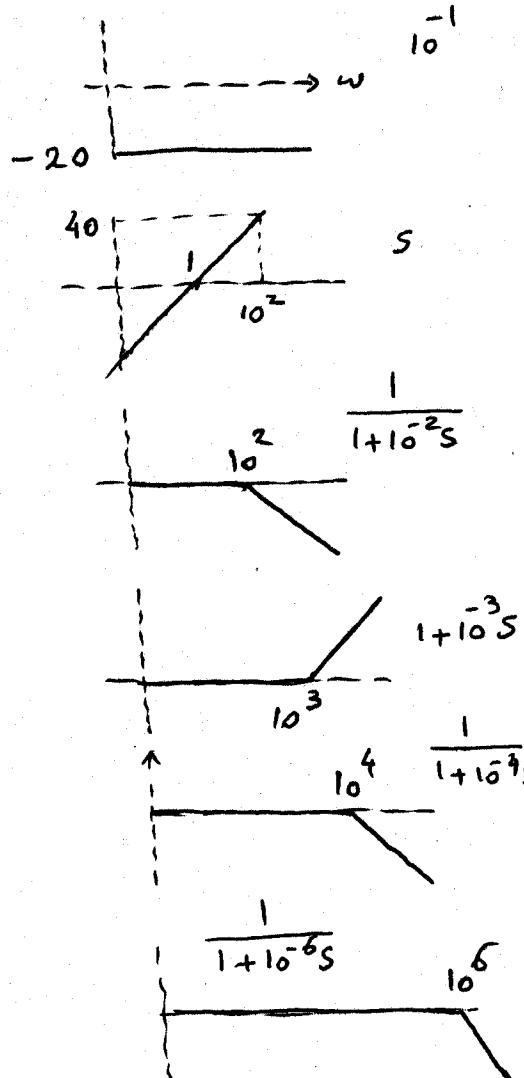

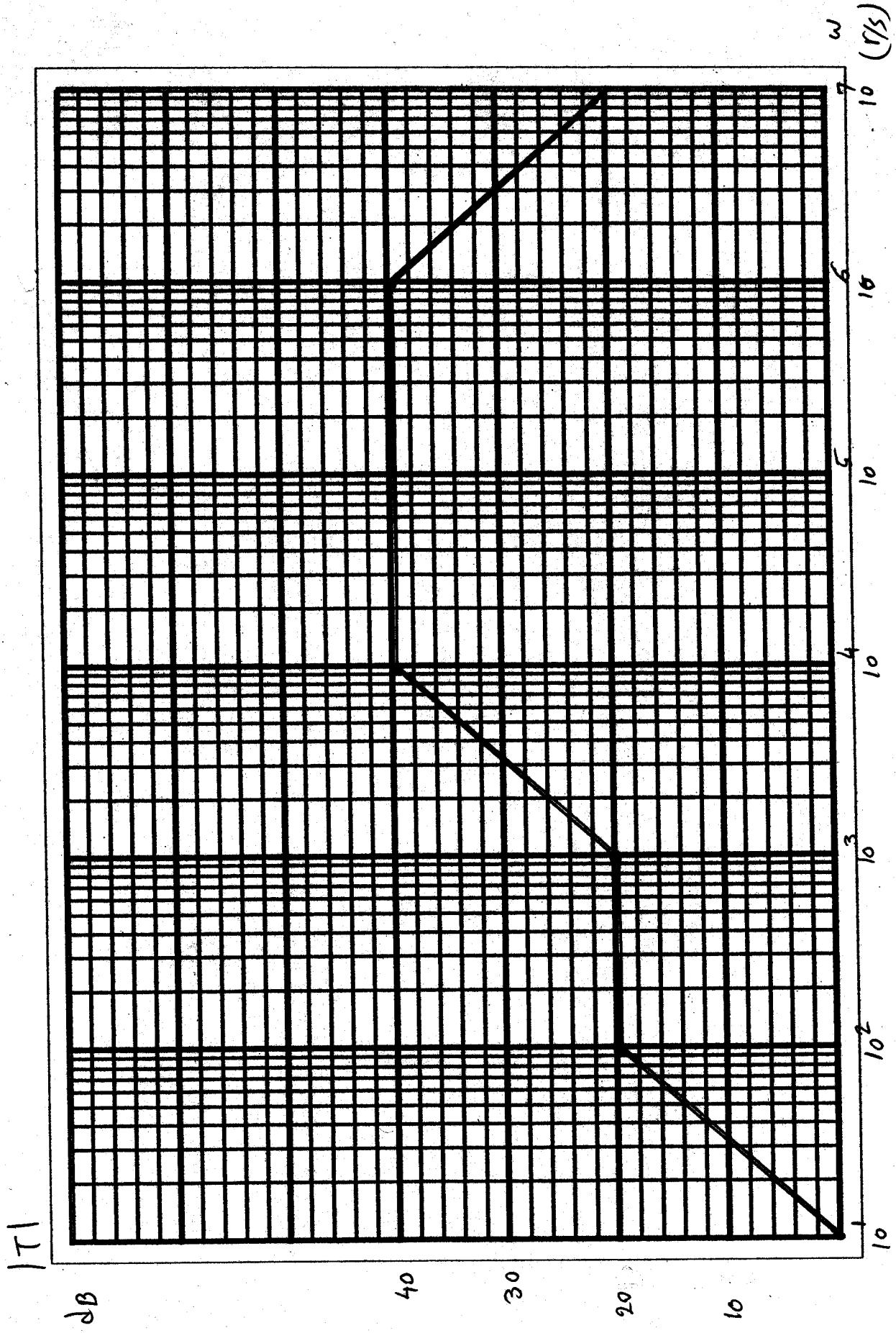

3- 40 Points) In the given circuit, find the transfer function V_o/V_i .

solution:

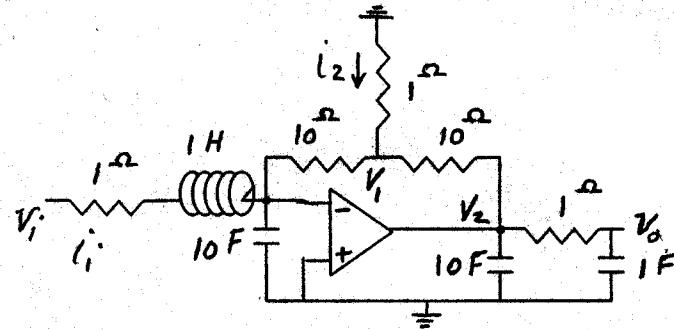

We should note that the two 10 F capacitors one at the V_- input and the other at the OP-Amp output have no effect and can be removed (as explained in class).

$$Z_i = 1 + jL\omega = 1 + j\omega$$

$$I_i = \frac{V_i}{Z_i} \Rightarrow V_1 = -I_i \times 10 = -\frac{V_i}{Z_i} \times 10$$

$$I_2 = -\frac{V_1}{1} = \frac{V_1}{Z_i} \times 10$$

$$V_2 = V_1 - (I_i + I_2)10 = -\frac{V_i}{Z_i} \times 10 - V_i \left(\frac{1}{Z_i} + \frac{10}{Z_i} \right) \times 10$$

$$V_2 = -V_i \left[\frac{10}{Z_i} + \frac{10}{Z_i} + \frac{100}{Z_i} \right] = -V_i \left[\frac{120}{Z_i} \right]$$

$$\frac{V_2}{V_i} = -\frac{120}{Z_i} = -\frac{120}{1 + j\omega}$$

$$\frac{V_o}{V_2} = \frac{\frac{1}{C_2 s}}{R_2 + \frac{1}{C_2 s}} = \frac{1}{1 + R_2 C_2 s} = \frac{1}{1 + j\omega}$$

$$\frac{V_o}{V_i} = \frac{V_2}{V_i} \times \frac{V_o}{V_2} = -\frac{120}{(1 + j\omega)^2}$$

So the transfer function has 2 Poles at $\omega = 1$