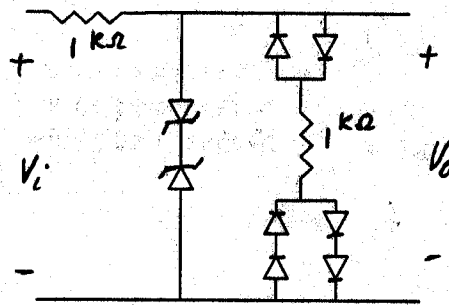


1-30 Points) Draw the transfer characteristic of the circuit shown for $-10 < v_i < 10$ and calculate the break points values.

$V_z = 3$ volts and $V_d(\text{on}) = 0.7$ volts.



solution.

Before the input reaches to $3V_d(\text{on}) = 2.1 \text{ V}$


all diodes are off and $v_o = v_i$ or the slope

of the transfer characteristic is 1 .


when $v_i > 2.1$, diodes conduct and the slope $= 1/2$

when the output reaches $V_z + 0.7 = 3.7 \text{ [V]}$, it will stay

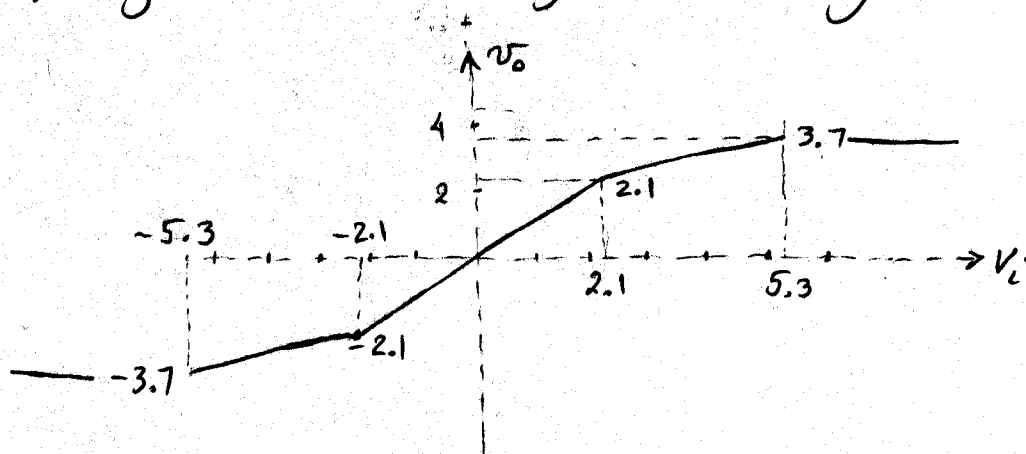at that voltage. The Curve has Symmetric Property.



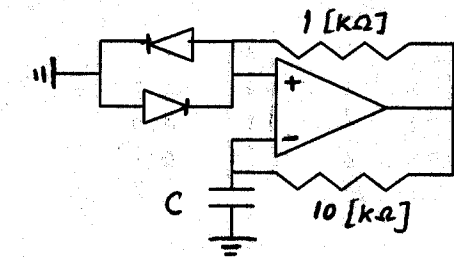2- 35 Points) In the square/triangular waveform generator shown, find the value of C so that the frequency of oscillation is 10 KHZ.
 $V_D(\text{on}) = 0.7 \text{ [V]}$ and $L_+ = -L_- = 10 \text{ [V]}$.



$$L_+ = -L_- = 10 \text{ [V]} \quad V_D(\text{on}) = 0.7 \text{ [V]}$$

Solution :

The Capacitor voltage has the general equation

$$V_C = A + B e^{-t/RC} \quad \text{where } R = 10 \text{ k}\Omega$$

The Capacitor charge and discharge up to V_D and $-V_D$.

$$\begin{cases} V_C(t=0) = -V_D = -0.7 \text{ [V]} \\ A + B = -0.7 \text{ [V]} \end{cases} \quad \begin{cases} V_C(t=\infty) = L_+ = 10 \text{ V} \\ A = 10 \text{ V} \Rightarrow B = -10.7 \text{ [V]} \end{cases}$$

Thus

$$V_C = 10 - 10.7 e^{-t/RC}$$

The Capacitor voltage should reach 0.7 [V] at $\frac{T}{2}$ time

$$\begin{cases} t = \frac{T}{2} \\ V_C = 0.7 \end{cases} \quad 0.7 = 10 - 10.7 e^{-t/RC}$$

$$-10.7 e^{-t/RC} = -9.3$$

$$\frac{t}{RC} = 0.14$$


$$\frac{T/2}{RC} = 0.14$$

$$T = 0.28 RC$$

$$C = \frac{1}{0.28 R f} = \frac{1}{0.28 \times 10^4 \times 10^4}$$

$$C = 35.7 \text{ nF}$$

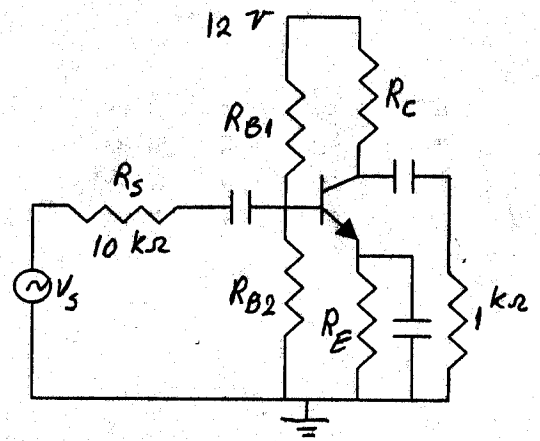3-35 Points) In the circuit shown, Find R_{B1} , R_{B2} , R_E and R_C so that the $I_{CQ} = 2 \text{ mA}$ and $V_{CEQ} = 2 \text{ [V]}$
 Note: Capacitors are open for DC.
 $V_{CC} = 12 \text{ [V]}$ and $\beta = 100$.



Solution :

as a reasonable choice

We choose $V_{BB} = \frac{1}{3} V_{CC} = 4 \text{ [V]}$

and the current in R_{B1}, R_{B2} Branch

$$= \frac{1}{10} I_{CQ} = 0.2 \text{ mA}$$

$$R_{B1} + R_{B2} = \frac{V_{CC}}{I} = \frac{12}{0.2} = 60 \text{ [k}\Omega\text{]}$$

$$R_{B1} + R_{B2} = 60 \text{ k} \quad (1)$$

$$V_{BB} = \frac{R_{B2}}{R_{B1} + R_{B2}} V_{CC} = \frac{1}{3} V_{CC} \quad \frac{R_{B2}}{R_{B1} + R_{B2}} = \frac{1}{3} \quad R_{B1} = 2R_{B2} \quad (2)$$

from (1) and (2) $\Rightarrow \begin{cases} R_{B1} = 40 \text{ [k}\Omega\text{]} \\ R_{B2} = 20 \text{ [k}\Omega\text{]} \end{cases}$

writing a KVL at the input loop

$$4 = 13.33 I_B + 0.7 + R_E I_{CQ} \quad I_{CQ} = 2 \text{ mA} \quad I_B = 0.02 \text{ mA}$$

Then $R_E = 1.5 \text{ k}$

from V_{CEQ} we obtain R_C

$$V_{CEQ} = V_{CC} - I_C (R_C + R_E) \quad 2 = 12 - 2(R_C + 1.5)$$

$R_C = 3.5 \text{ k}$

