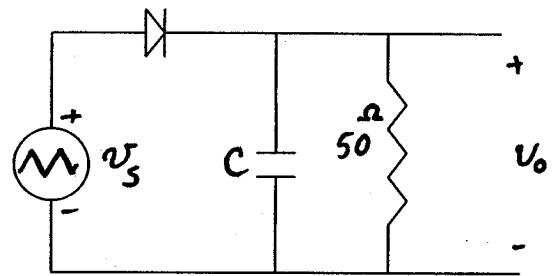
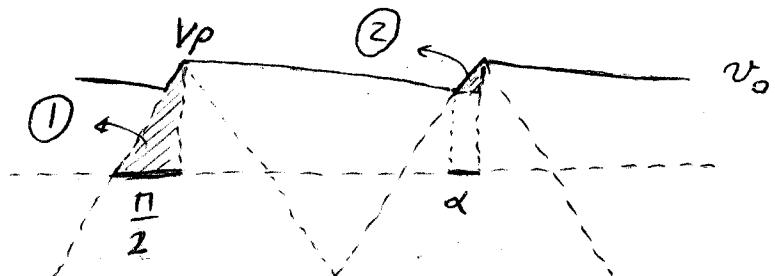


2-20 points) The average output voltage of the power supply shown, is 12 volts with one volt ripple(p-p). If the input voltage is triangular wave with frequency of 100 Hz, calculate,

- The capacitor value.
- The conduction angle of the diode.
- The RMS value of the input voltage V_s .



Solution :



$$V_p = V_o (\text{DC}) + \frac{1}{2} V_r$$

$$V_p = 12 + 0.5 = 12.5 \text{ [v]}$$

(a)

$$C = \frac{V_p}{R \cdot f \cdot V_r} = \frac{12.5}{50 \times 100 \times 1} = \boxed{2500 \text{ MF}}$$

(b)

$$\frac{\alpha}{\frac{\pi}{2}} = \frac{V_r}{V_p} = \frac{1}{12.5} \quad \text{from Similarity between triangle ① and ②}$$

$$\alpha = \frac{\pi}{2 \times 12.5} = \frac{180}{2 \times 12.5} = 7.2^\circ$$

(c)

$$V_s(P) = V_p + 0.7 = 12.5 + 0.7 = 13.2 \text{ [v]}$$

In triangular waveform, the rms value is $\frac{1}{\sqrt{3}}$ of Peak Value

This relation can be obtained by rms definition

$$V_s(\text{rms}) = \frac{V_s(P)}{\sqrt{3}} = \frac{13.2}{\sqrt{3}} = 7.62 \text{ [v]}$$