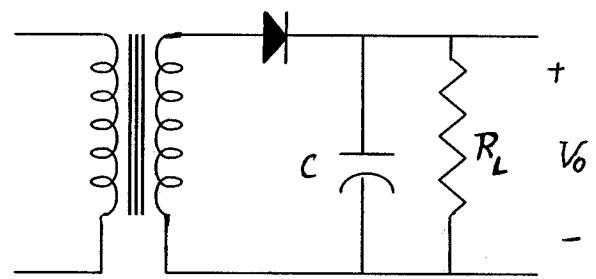


- ECE3455, Q4) In the half-wave power supply shown, the secondary voltage of the transformer is 12 Vrms and the load resistor is 1 Kohm. The diode average current is 414 mA. Find
- The ripple voltage(pp).
 - The DC value of the output voltage.
 - The value of capacitor. $f = 60 \text{ Hz}$



Solution: Since the secondary voltage of the transformer is $V_s = 12 \text{ V(rms)}$

$$V_p = 12\sqrt{2} - 0.7 = 16.97 - 0.7 = 16.27 [\text{V}]$$

The Load Current is about

$$I_L = \frac{V_p}{R_L} = \frac{16.27}{1000} = 16.27 [\text{mA}]$$

We can find the angle of conduction of diode

$$I_D(\text{avr}) \cdot \theta_D = 360 \times I_L = 360 \times 16.27$$

$$\theta_D = \frac{360 \times 16.27}{I_D(\text{avr}) = 414} = 14.15^\circ$$

on the other hand $\cos \theta_D = \frac{V_p - V_r}{V_p} = \cos 14.15 = 0.96966$

or $V_r = 0.03 V_p = 0.493 [\text{V}]$

b) $V_o(\text{DC}) = V_p - \frac{1}{2} V_r = 16.02 [\text{V}]$

c) $C = \frac{V_p}{f \cdot R_L \cdot V_r} = \frac{16.27}{60 \times 10^3 \times 0.493} = 550 \mu\text{F}$