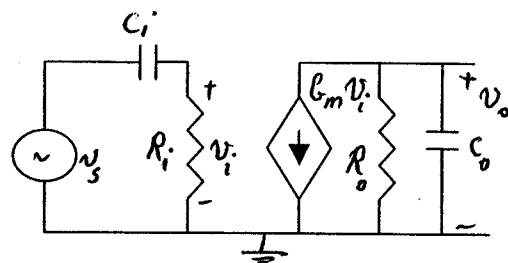


(ECE3455, Q2) In the given model of amplifier

- Find  $R_i$  so that the input resistance is 10K,  $R_o$  so that the output resistance is 1 K, and the  $G_m$  so that the voltage gain  $V_o/V_i$  is -100.
- Find  $C_i$  and  $C_o$  so that the  $f_L = 100$  Hz and  $f_H = 100$  KHz.
- Obtain the transfer function  $T(\omega) = V_o/V_s$
- Draw the magnitude and the phase of the transfer function using bode plot method.



Solution:

$$a) \quad R_i = 10 \text{ k}\Omega, \quad R_o = 1 \text{ k}\Omega$$

$$V_o = -G_m V_i \cdot R_o \Rightarrow \frac{V_o}{V_i} = -G_m R_o$$

$$-G_m R_o = -100 \quad G_m = \frac{100}{R_o} = \frac{100}{1} = 100 \text{ mS}$$

$$b) \quad f_L = \frac{1}{2\pi R_i C_i} \quad f_H = \frac{1}{2\pi R_o C_o}$$

$$C_i = \frac{1}{2\pi R_i f_L} = \frac{1}{2\pi \times 10^4 \times 100} = 0.159 \text{ }\mu\text{F}$$

$$C_o = \frac{1}{2\pi R_o f_H} = \frac{1}{2\pi \times 10^3 \times 10^5} = 1.59 \text{ nF}$$

$$c) \quad T(\omega) = \frac{V_o}{V_s} = \quad Z_o = R_o \parallel C_o = \frac{R_o \times \frac{1}{jC_o\omega}}{R_o + \frac{1}{jC_o\omega}} = \frac{R_o}{1 + jR_o C_o \omega}$$

$$V_o = -G_m V_i Z_o = -G_m V_i \frac{R_o}{1 + jR_o C_o \omega}$$

$$\frac{V_o}{V_i} = -G_m \frac{R_o}{1 + jR_o C_o \omega}$$

$$\frac{V_i}{V_s} = \frac{R_i}{R_i + \frac{1}{jC_i\omega}} = \frac{jR_i C_i \omega}{1 + jR_i C_i \omega} \Rightarrow \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s}$$

$$\frac{V_o}{V_s} = -G_m R_o R_i C_i \frac{j\omega}{(1 + jR_o C_o \omega)(1 + jR_i C_i \omega)}$$