


ECE3455, Q5) In the amplifier shown, beta=100, and $V_A = \infty$

- Find the ICQ and VCEQ of the BJT.
- Find the BJT parameters r_n and g_m .
- Draw the small signal model of the amplifier.
- Find the voltage gain V_o/V_s .
- Find the input and output resistance.

Note: Capacitors are open for DC and short for AC signals.

$$V_{BE(oh)} = 0.7 [V]$$

$$V_T = 25 mV$$

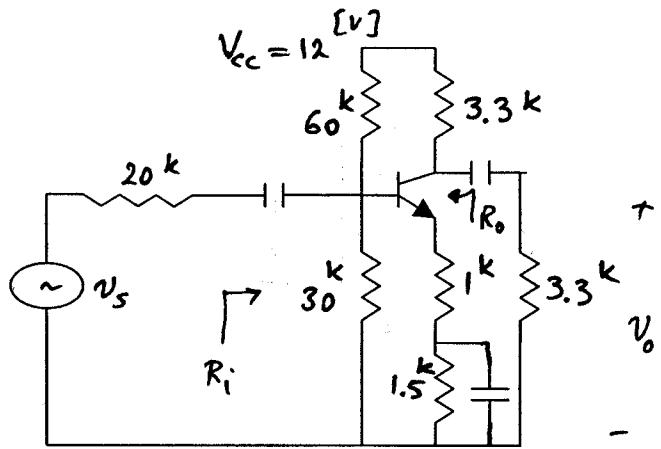


solution :

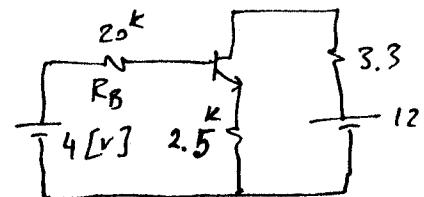- (a) DC values can be found from the DC circuit shown \Rightarrow
writing a kVL in the input loop


$$4 = 20 \frac{I_E}{101} + 0.7 + 2.5 \times I_E \quad I_E = I_C = 1.22 \text{ mA}$$

$$V_{CEQ} = 12 - (2.5 + 3.3) \times 1.22 = 4.92 [V]$$



b) $r_n = \frac{\beta V_T}{I_C} = \frac{100 \times 25}{1.22} = 2.049 [\text{k}\Omega] \quad g_m = \frac{I_C}{V_T} = \frac{1.22}{25} = 48 \text{ mV}$

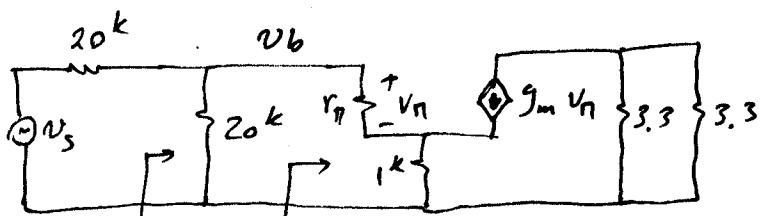- c) The small signal (or Ac) model of amplifier shown \Rightarrow



d) $R_i^! = r_n + 1(101) = 103 \text{ k}\Omega$

$$R_i^! = 20 \text{ k} \parallel R_i^! = 20 \parallel 103 = 16.75 [\text{k}\Omega]$$

$$v_b = \frac{16.75}{20 + 16.75} v_s = 0.455 v_s \Rightarrow v_n = \frac{r_n}{R_i^!} v_b = \frac{2.049}{103} v_b$$

$$v_n = \frac{2.049}{103} \times 0.455 v_s = 9.05 \times 10^{-3} v_s \Rightarrow \frac{v_n}{v_s} = 9.05 \times 10^{-3}$$

$$v_o = -g_m v_n \times 3.3 \parallel 3.3 \Rightarrow \frac{v_o}{v_n} = -48 \times 1.65 = -79.2$$

$$\frac{v_o}{v_s} = \frac{v_n}{v_s} \times \frac{v_o}{v_n} = 9.05 \times 10^{-3} \times (-79.2) = -0.716$$

- e) $R_i^! = 16.75 [\text{k}\Omega]$ as calculated in Part (d)

$$R_o = R_c = 3.3 [\text{k}\Omega]$$