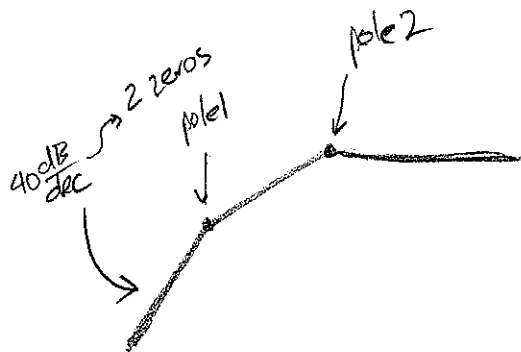


$$V_1 = V_2 = \frac{-V_{in} R_1}{2R_1 + R_i + \frac{1}{j\omega C_1}} = \frac{-V_{in} j\omega R_1 C_1}{1 + j\omega(2R_1 + R_i)C_1}$$


$$V_{out} = \frac{(AV_1 + AV_2) R_4}{R_3 + R_4 + \frac{1}{j\omega C_2}} = \frac{2AV_1 \cdot j\omega R_4 C_2}{1 + j\omega(R_3 + R_4)C_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{-2A(j\omega R_1 C_1)(j\omega R_4 C_2)}{(1 + j\omega(2R_1 + R_i)C_1)(1 + j\omega(R_3 + R_4)C_2)}$$



② $H(j\omega) = 100$

add resistor to make $R_f = 90K\Omega$

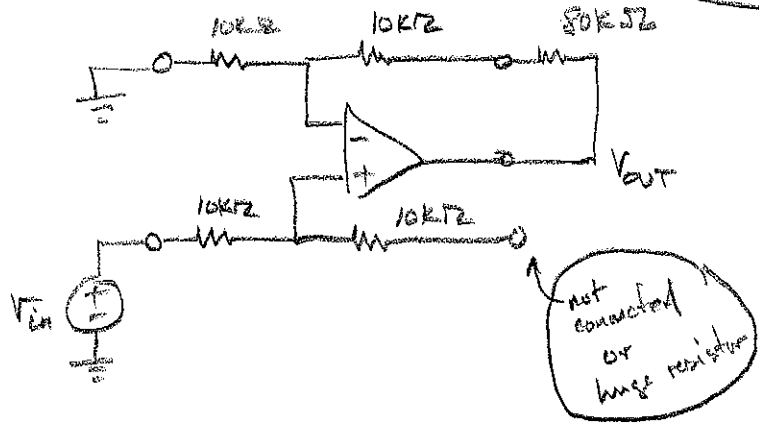

$$\left(1 + \frac{R_f}{R_i}\right) = 10$$

$$\frac{R_f}{R_i} = 9$$


$$R_f = 90K\Omega$$

not connected or huge resistor

$$H(j\omega) = \frac{-100 \left(j \frac{\omega}{10}\right)}{1 + j \frac{\omega}{10}}$$

add cap. to make high-pass filter

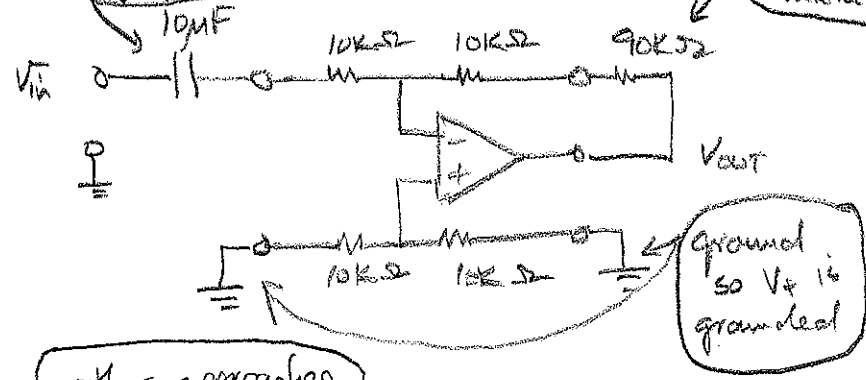add 90KΩ resistor to make pass band gain = -100



$$\frac{1}{RC} = 10 \frac{\text{rad}}{\text{sec}}$$

$$C = \frac{1}{R \cdot 10}$$


$$C = \frac{1}{10,000 \cdot 10} = \frac{1}{100,000}$$

$$C = 10^{-5} = 10\mu\text{F}$$

other approaches are possible

(b) since no current flows through the $5R_1$ resistor $V_+ = V_- = V_{in}$ for both amplifiers.

so we have:

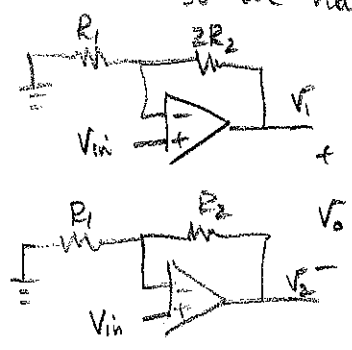

$$V_1 = V_{in} \left(1 + \frac{2R_2}{R_1}\right)$$

$$V_0 = V_1 - V_2$$

$$V_2 = V_{in} \left(1 + \frac{R_2}{R_1}\right)$$

$$\frac{V_0}{V_{in}} = \left(1 + \frac{2R_2}{R_1}\right) - \left(1 + \frac{R_2}{R_1}\right)$$

$$= \frac{R_2}{R_1}$$

③

$$CMRR = \frac{20}{10} \log_{10} \frac{|A_d|}{|A_{cm}|} = 60$$

$$\frac{|A_d|}{|A_{cm}|} = 10^3$$

$$|A_d| = \frac{R_2}{R_1} \rightarrow \frac{10^2}{|A_{cm}|} = 10^3$$

$$= 10^2$$

$$|A_{cm}| = 10^{-1} = 0.1$$

$$\left(\frac{R_4}{R_4 + 1k\Omega} \right) \left(1 - \frac{100k\Omega}{1k\Omega} \cdot \frac{1k\Omega}{R_4} \right) = 0.1$$

$$R_4 - 100k\Omega = 0.1 \cdot R_4 + 0.1 \cdot 1k\Omega$$

$$0.9 \cdot R_4 = 100k\Omega + 100\Omega$$



$$R_4 = \frac{100.1k\Omega}{0.9}$$

$$R_4 = 111.2k\Omega$$

yes, long-division
still works!

$$\begin{array}{r} 111222 \\ 9 \overline{) 1001000} \\ \underline{9} \\ 10 \\ \underline{9} \\ 11 \\ \underline{9} \\ 20 \\ \underline{18} \\ 2 \end{array}$$

4

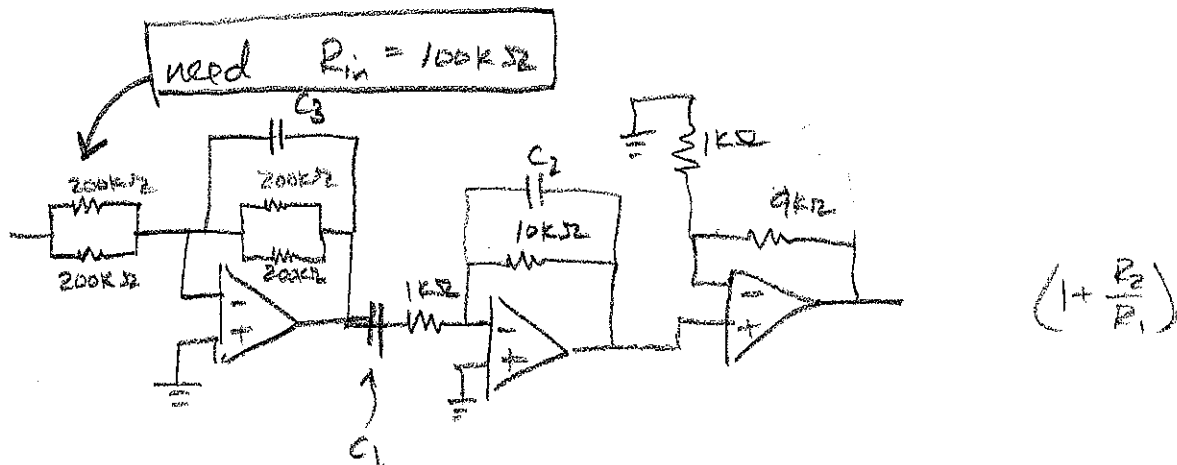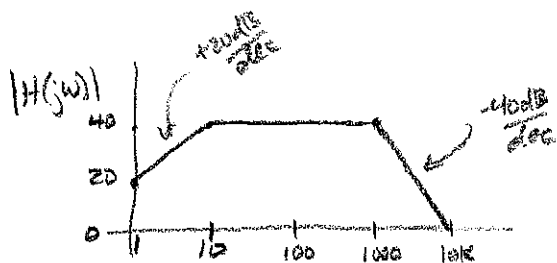

$$\frac{1}{C_2 \cdot 10k\Omega} = 1000 \frac{\text{rad}}{\text{sec}} \rightarrow C_2 = 10^{-7} \text{ F}$$

$$\frac{1}{C_3 \cdot 100k\Omega} = 1000 \frac{\text{rad}}{\text{sec}} \rightarrow C_3 = \frac{1}{10^6} \text{ F} = 10 \text{ nF}$$

$$\frac{1}{C_1 \cdot 1k\Omega} = 10 \frac{\text{rad}}{\text{sec}} \rightarrow C_1 = \frac{1}{10^4} = 10^{-4} \text{ F} = 100 \mu\text{F}$$

$$H(j\omega) = \frac{100 j \frac{\omega}{10}}{\left(1 + j \frac{\omega}{10}\right) \left(1 + j \frac{\omega}{1000}\right)^2}$$

$$\frac{j \frac{\omega}{10}}{1 + j \frac{\omega}{10}}$$


is a low-pass filter,

such as

$$\frac{1}{\left(1 + j \frac{\omega}{1000}\right)^2}$$

is a cascaded low-pass filter, such

as

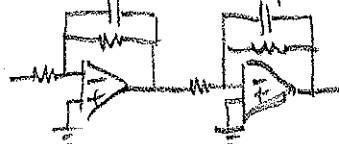

other approaches are possible