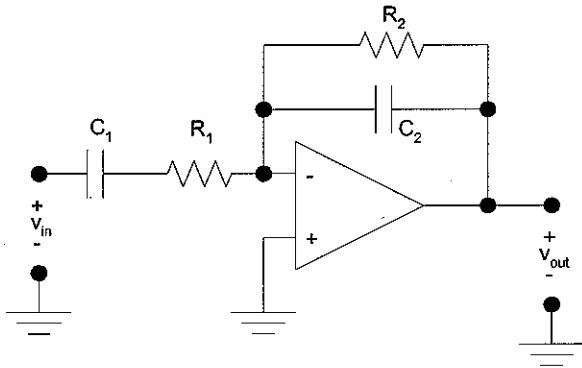


(a) Derive the transfer function, $H_1(j\omega) = v_{out}/v_{in}$, for the circuit below. Assume ideal op amps.

(b) Given that $\frac{1}{R_1 C_1} = 10 \text{ rad/s}$, $\frac{1}{R_2 C_2} = 1,000 \text{ rad/s}$, and $R_1 = R_2$, plot the straight-line approximations to the magnitude and phase Bode plots for this circuit using the semilog graph paper on the next two pages.



(a) This is an inverting Amplifier with

$$H_1(j\omega) = \frac{v_{out}}{v_{in}} = -\frac{Z_2}{Z_1}$$


$$Z_2 = R_2 \parallel \frac{1}{j\omega C_2} = \frac{1}{\frac{1}{R_2} + j\omega C_2} = \frac{R_2}{1 + j\omega R_2 C_2}$$

$$Z_1 = R_1 + \frac{1}{j\omega C_1} = \frac{1 + j\omega R_1 C_1}{j\omega C_1}$$

$$H_1(j\omega) = -\frac{Z_2}{Z_1} = -\frac{\frac{R_2}{1 + j\omega R_2 C_2}}{\frac{1 + j\omega R_1 C_1}{j\omega C_1}} = \frac{-j\omega C_1 R_2}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$

- or -
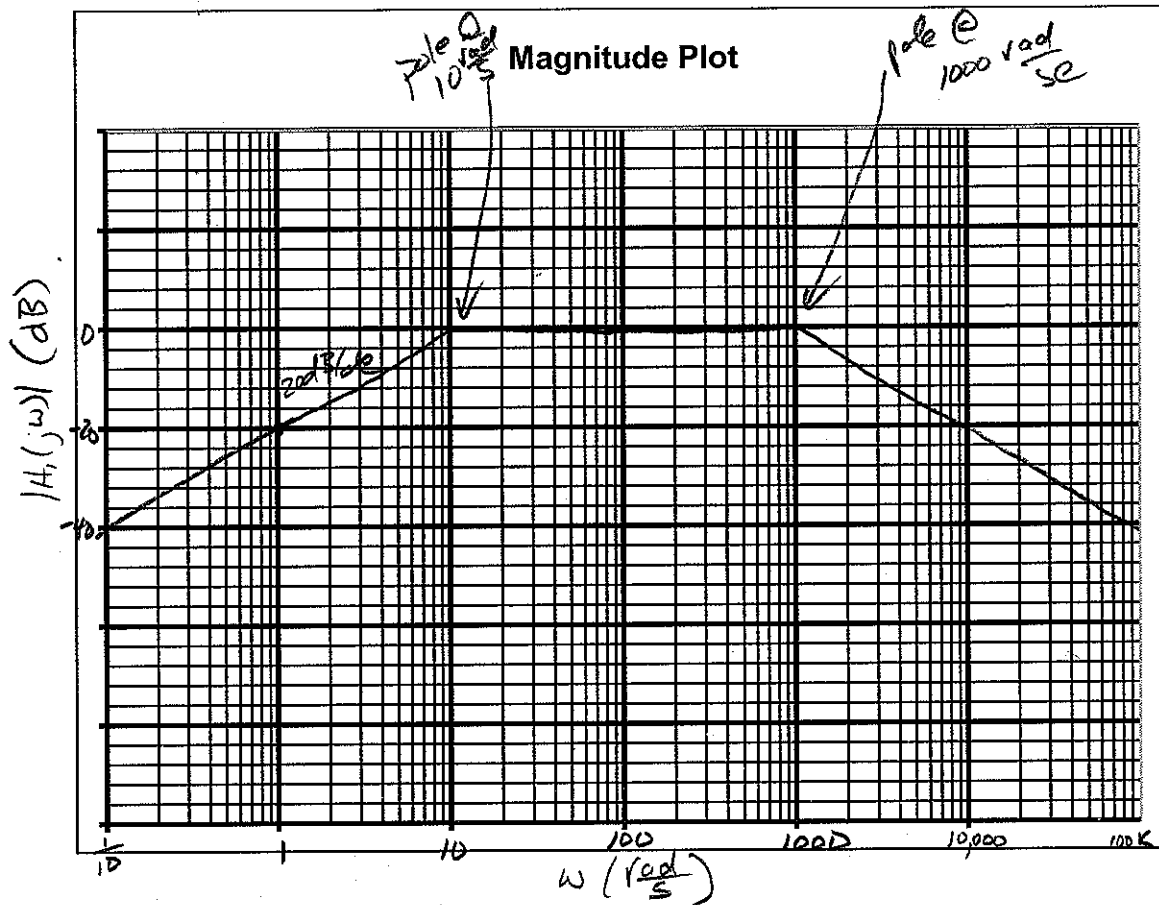
$$H_1(j\omega) = -\frac{R_2}{R_1} \cdot \frac{j\omega C_1 R_1}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$



(b) Rewrite $H_1(j\omega)$ w/ $\frac{1}{RC_1} = 10 \frac{\text{rad}}{\text{s}}$, $\frac{1}{RC_2} = 1 \text{K} \frac{\text{rad}}{\text{s}}$ & $R_1 = R_2$

$$H_1(j\omega) = \frac{-j\frac{\omega}{10}}{(1+j\frac{\omega}{10})(1+j\frac{\omega}{1000})}$$

One zero @ $\omega = 0$, two poles @ $\omega = 10 \text{ \& } 1000 \frac{\text{rad}}{\text{sec}}$

$$H_1(1 \frac{\text{rad}}{\text{sec}}) = \frac{-j\frac{1}{10}}{(1+j(\omega 0))(1+j(\omega 0))} = \frac{-j}{10}$$

$$|H_1(1)| = \frac{1}{10} \rightarrow -20 \text{ dB}$$

$$\angle H_1(1) = \frac{-j}{10} \rightarrow -90^\circ$$

Phase Plot

← pole @ $10 \frac{\text{rad}}{\text{s}}$ → ← pole @ $1000 \frac{\text{rad}}{\text{s}}$ →

