
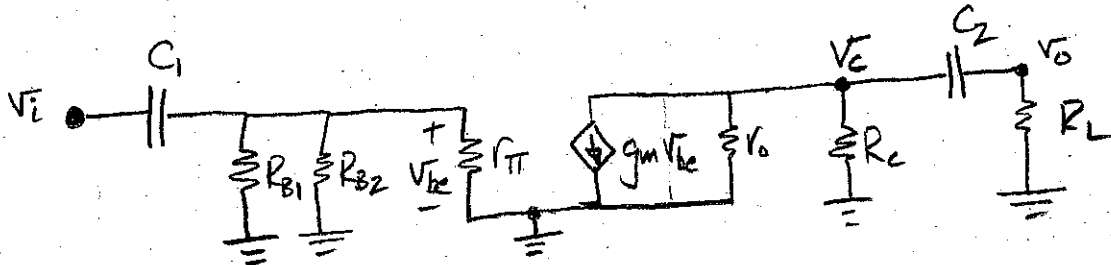


Assume that the transistor in the following circuit is active. Find an expression for the small signal gain ( $v_o/v_i$ ), the input impedance ( $Z_{in}$ ), and the output impedance ( $Z_{out}$ ).

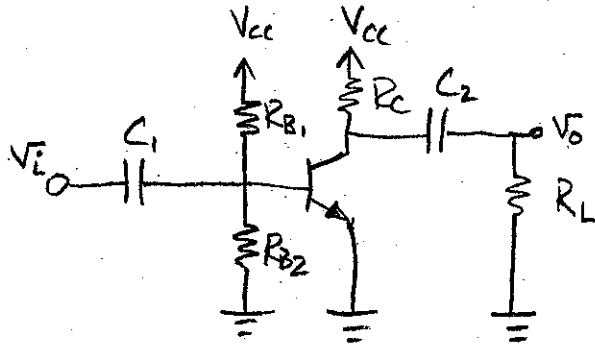Be sure to draw the small signal equivalent circuit and it is recommended that you use the hybrid pi model. Reduce your expressions and express them in terms of the circuit components (resistors and capacitors),  $g_m$  or  $\beta$ ,  $r_o$ , and  $r_{\pi}$ .



$$V_{be} = \frac{v_i \cdot (R_{B1} \parallel R_{B2} \parallel r_{\pi})}{\frac{1}{j\omega C_1} + R_{B1} \parallel R_{B2} \parallel r_{\pi}} = \frac{v_i \cdot j\omega C_1 (R_{B1} \parallel R_{B2} \parallel r_{\pi})}{1 + j\omega C_1 (R_{B1} \parallel R_{B2} \parallel r_{\pi})}$$

$$V_c = -g_m V_{be} \cdot r_o \parallel R_c \parallel \left( \frac{1}{j\omega C_2} + R_L \right)$$

$$v_o = \frac{V_c}{R_L + \frac{1}{j\omega C_2}} \cdot R_L = \frac{V_c j\omega C_2 R_L}{1 + j\omega C_2 R_L}$$

and so:

$$\frac{v_o}{v_i} = - \frac{j\omega C_1 (R_{B1} \parallel R_{B2} \parallel r_{\pi})}{1 + j\omega C_1 (R_{B1} \parallel R_{B2} \parallel r_{\pi})} \cdot \frac{j\omega C_2 R_L}{1 + j\omega C_2 R_L} \cdot g_m [r_o \parallel R_c \parallel \left( \frac{1}{j\omega C_2} + R_L \right)]$$

while this is an acceptable answer, the term  $r_o \parallel R_c \parallel \left( \frac{1}{j\omega C_2} + R_L \right)$  is not particularly useful in understanding the frequency response of the circuit.

For this quiz, the expression is ok. Please note, though, that if we call  $R_c' = R_c \parallel r_o$ , which is useful because typically  $r_o \gg R_c$  and so  $R_c' \approx R_c$ , we can rewrite

$$\begin{aligned} r_o \parallel R_c \parallel \left( \frac{1}{j\omega C_2} + R_L \right) &= R_c' \parallel \left( \frac{1}{j\omega C_2} + R_L \right) = \frac{R_c' \left( \frac{1}{j\omega C_2} + R_L \right)}{R_c' + R_L + \frac{1}{j\omega C_2}} \\ &= \frac{R_c' (1 + j\omega C_2 R_L)}{1 + j\omega C_2 (R_c' + R_L)} \end{aligned}$$

and so:

$$\begin{aligned} \frac{v_o}{v_i} &= -g_m \cdot \frac{j\omega C_1 (R_{B1} \parallel R_{B2} \parallel r_{\pi})}{1 + j\omega C_1 (R_{B1} \parallel R_{B2} \parallel r_{\pi})} \cdot \frac{j\omega C_2 R_L R_c'}{1 + j\omega C_2 (R_c' + R_L)} \\ &= -g_m (R_L \parallel R_c') \cdot \frac{j\omega C_1 (R_{B1} \parallel R_{B2} \parallel r_{\pi})}{1 + j\omega C_1 (R_{B1} \parallel R_{B2} \parallel r_{\pi})} \cdot \frac{j\omega C_2 (R_c' + R_L)}{1 + j\omega C_2 (R_c' + R_L)} \end{aligned}$$

Hence, our bandpass gain is  $-g_m (R_L \parallel R_c')$

and we have two corners in our high-pass response, one at  $\omega_1 = \frac{1}{(R_{B1} \parallel R_{B2} \parallel r_{\pi}) C_1}$  and the other at  $\omega_2 = \frac{1}{(R_c' + R_L) C_2}$

$Z_{in} \& Z_{out}$  can be written as:

$$Z_{in} = \frac{1}{j\omega C_1} + R_{B1} \parallel R_{B2} \parallel r_{\pi} = \frac{1 + j\omega [R_{B1} \parallel R_{B2} \parallel r_{\pi}] C_1}{j\omega C_1}$$

$$Z_{out} = \frac{1}{j\omega C_2} + r_o \parallel R_c = \frac{1 + j\omega [r_o \parallel R_c] C_2}{j\omega C_2}$$

So, as  $\omega \rightarrow 0$   $Z_{in} \& Z_{out} \rightarrow \infty$  (they block DC)

for high frequencies,  $Z_{in} \sim R_{B1} \parallel R_{B2} \parallel r_{\pi}$

and  $Z_{out} \sim r_o \parallel R_c = R_c'$