

Name: _____ (please print)

Signature: _____

ECE 3455
Final Exam
December 11, 2010

Exam duration: 170 minutes

- You may have one 8 ½ x 11 in. "crib" sheet, written on both sides, during the quiz. You may have any calculator you choose, but no computers. No other notes or materials will be allowed.
- Show all work necessary to complete the problem on these pages. A solution without the work shown will receive no credit.
- Show units in intermediate and final results, and in figures.
- If your work is sloppy or difficult to follow, points will be subtracted.

This exam has 12 pages, including the cover sheet. Raise your hand if you are missing a page.

1 _____ /45

2 _____ /35

3 _____ /35

4 _____ /45

5 _____ /40

Total _____ /200


Note: the exam score will be normalized to 100.

1. (45 points) Design a circuit that produces the output shown in the figure below. To do so, assume that you have an unlimited number of the following parts available.


- Ideal dual-power-supply op amps.
- 9 V batteries.
- Ideal BJTs with a β of 100 and a $V_{CE,sat}$ of 0.3 V.
- Diodes that can be modeled using a constant voltage drop model with $V_{th} = 0.7$ V.
- Ideal transformers.
- Capacitors of any value less than or equal to 10 μ F; resistors of any value less than or equal to 500 k Ω ; potentiometers of any number of turns and any resistance.

As an additional specification, the value labeled V_{offset} must be adjustable between -3 to +3 V. (In the figure it is set at -1.5 V.)

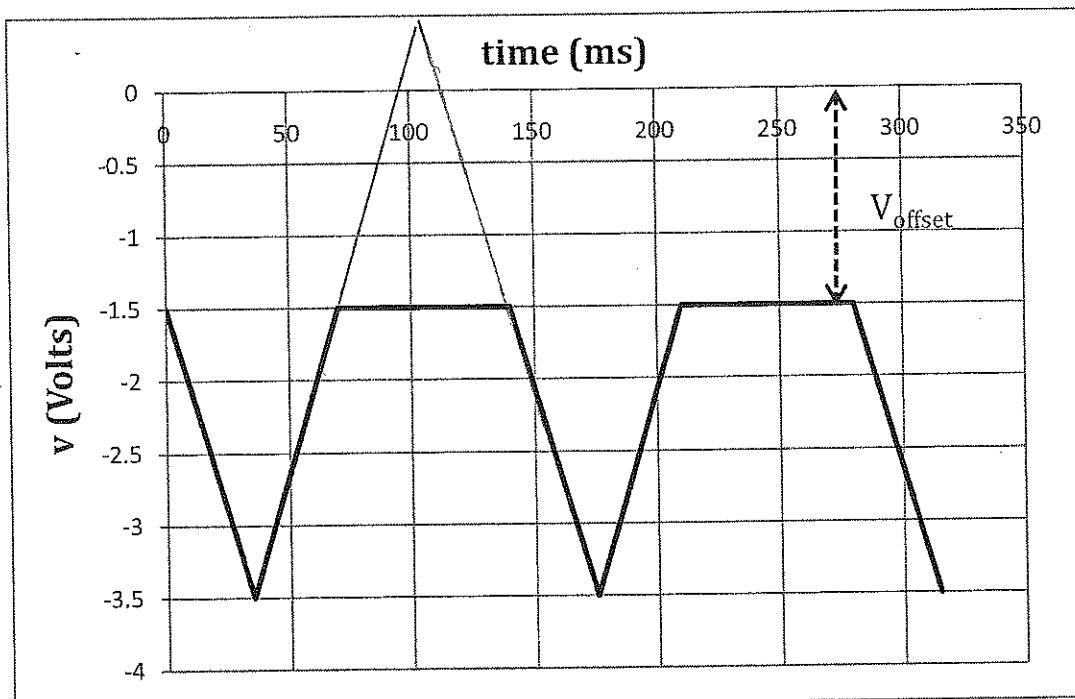To receive full credit, you must provide a brief explanation (a few words or a quick sketch) of what each part of your circuit is intended to do.



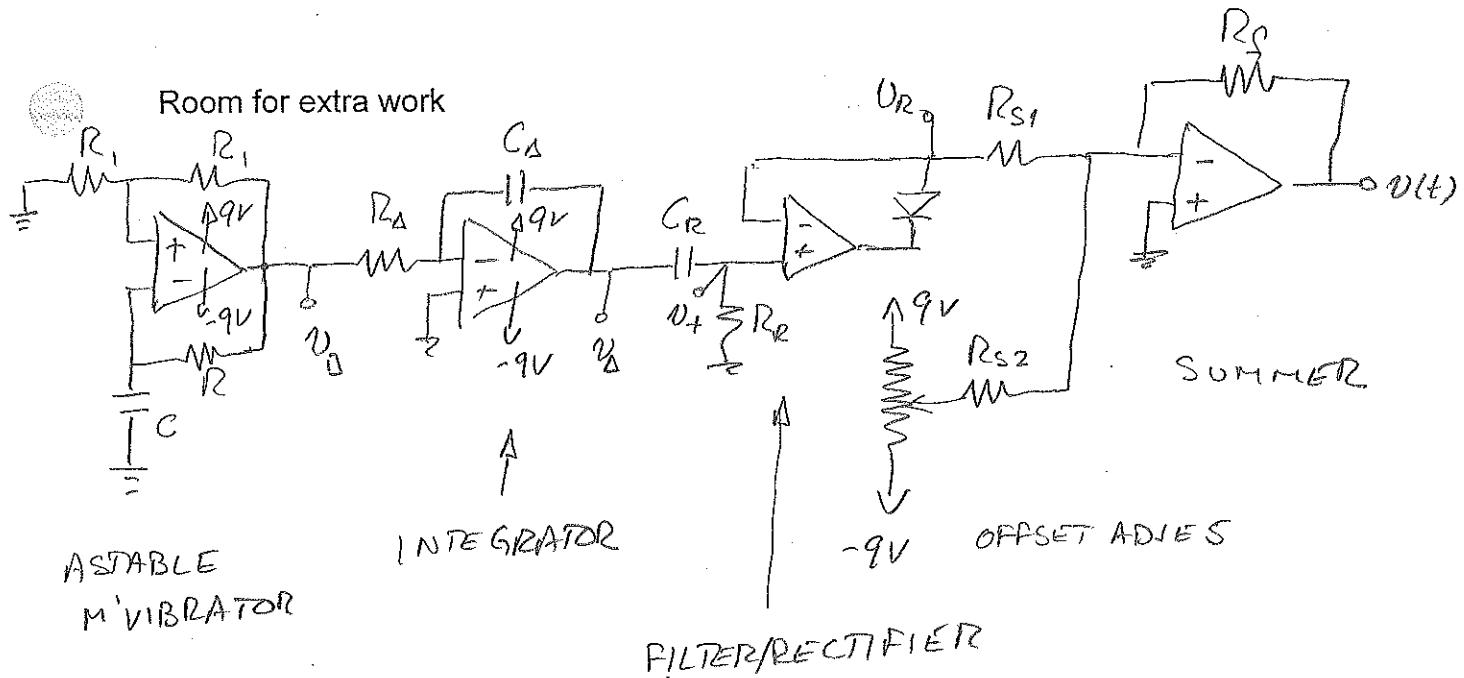
There are several ways this could be done. Here is one...
Evidently this is a half-wave rectified triangle wave with amplitude 4 V and period 140 ms.



Astable mv: $T = 2RC \ln \frac{1+\beta}{1-\beta}$ $R_1 = 10k\Omega \Rightarrow \beta = \frac{R_2}{R_1+R_2} = 0.5$

$T = 0.140 \text{ s} \Rightarrow R_C = \frac{0.140}{2 \ln \frac{3/2}{1/2}} = 0.0637 \text{ s}^{-1}$

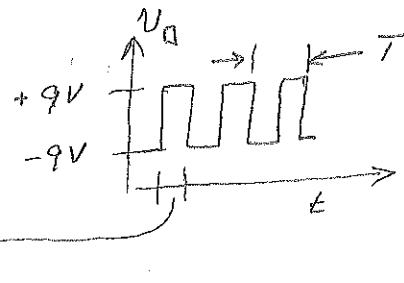$R = 100k \Rightarrow C = 0.64 \mu\text{F}$




Integrator: $V_A = -\frac{1}{R_A C_A} \int_0^{T/2} V_B dt = -\frac{1}{R_A C_A} 9 \cdot \frac{T}{2} = -4 \text{ V}$

The integration gives the peak-to-peak value, which is 4 V.
We have assumed that $V_B(t=0) = +9 \text{ V}$, so our V_A is negative.

$$R_A C_A = 9 \cdot \frac{1}{2} \cdot \frac{1}{4} = 0.1575 \text{ s}^{-1}$$

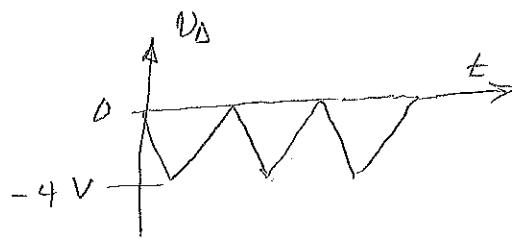
$R_A = 100k\Omega \Rightarrow C_A = 1.58 \mu\text{F}$



Room for Extra Work

Filter: To remove dc, we use a low pass filter. We need the break point to be below the lowest frequency component, which is $f_0 = \frac{1}{T} = 7.14 \text{ Hz}$. We have


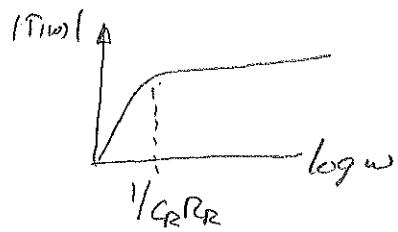
$$T(\omega) = \frac{V_o}{V_s} = \frac{R_o}{R_o + j\omega C_o} = \frac{j\omega C_o R_o}{1 + j\omega C_o R_o}$$



We want $\frac{1}{C_o R_o} \ll 7.14$. So we can

just make $C_o R_o$ large, but if we say $\frac{1}{C_o R_o} = 0.714$ and choose $\boxed{R_o = 100 \text{ k}\Omega \Rightarrow C_o = 7.14 \mu\text{F}}$

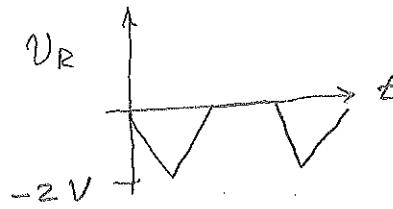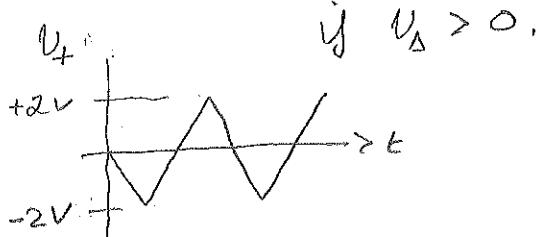Rectifier: This is just a superdiode that outputs 0



Summer: We don't need gain for V_R , so $R_f = R_{S1}$.

Offset: With the pot set for 9V, we want -3V at $V(t)$.

So

$$-\frac{R_f}{R_{S2}} = -3 \Rightarrow R_f = 3R_{S2}$$

Choose $\boxed{R_{S1} = 10 \text{ k}\Omega \quad R_f = 10 \text{ k}\Omega \quad R_{S2} = 3.33 \text{ k}\Omega}$

2. (35 points) The transfer function for a certain filter has the following characteristics.

- i) A double zero at 0 rad/s.
- ii) A pole at 800 rad/s.
- iii) A double pole at 8,000 rad/s.
- iv) A double zero at 40,000 rad/s.
- v) A gain of 54 dB at 4200 rad/s.

- +14
+11
- a) Find the transfer function $T(\omega)$ for this filter. Assume that any constants necessary to adjust the gain are positive and real.
 - b) On the page that follows, draw the straight-line approximation to the phase Bode plot. Include all non-zero poles and zeroes.

$$T(\omega) = K \cdot \frac{(j\omega)^2 (1 + j\omega/40000)^2}{(1 + j\omega/800)(1 + j\omega/8000)^2}$$

$$|T(\omega=4200 \text{ rad/s})| = 54 \text{ dB} \rightarrow 502 \text{ V/V}$$


$$T(\omega=4200 \text{ rad/s}) = \frac{U(4200)^2 (1 + j4200/40000)^2}{(1 + j4200/800)(1 + j4200/8000)^2}$$

$$\approx 2.616 \times 10^6 \angle 57.32^\circ \text{ V/V}$$

+4


$$\text{So } K \cdot 2.616 \times 10^6 = 502 \Rightarrow K = 1.92 \times 10^{-4}$$

A

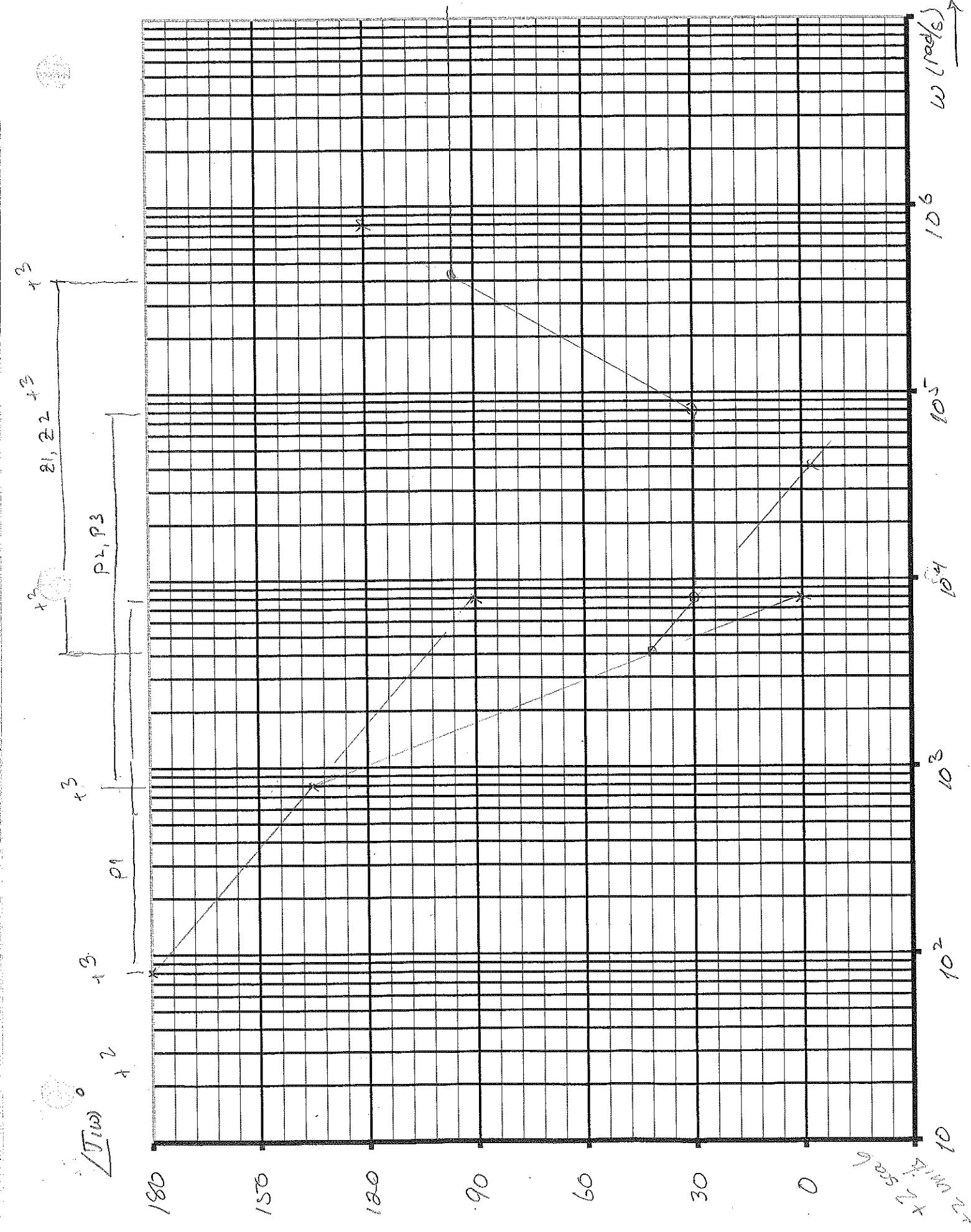

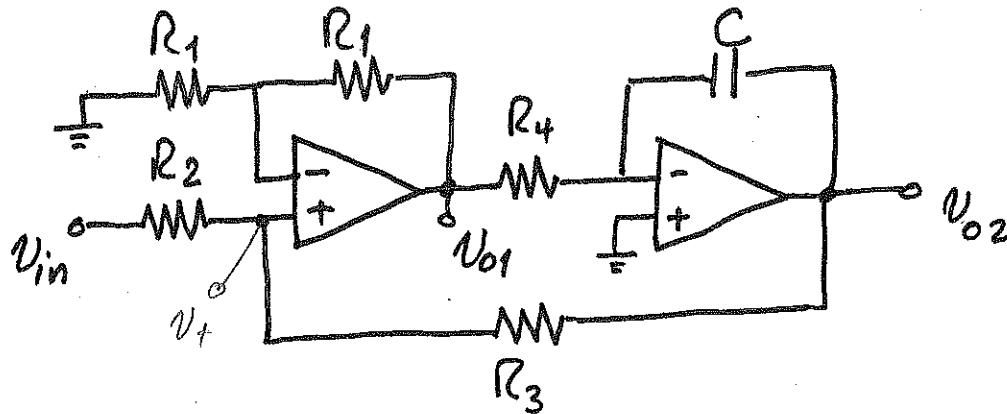3. (35 points) The circuit below is intended to be a dual-purpose filter. Assume ideal op amps in solving it.

- Find the transfer function $T_1(\omega) = V_{o1}/V_{in}$.
- Find the transfer function $T_2(\omega) = V_{o2}/V_{in}$.
- Identify the breakpoint(s) for each of $T_1(\omega)$ and $T_2(\omega)$, and indicate the nature of the filtering action (low pass, high pass, band pass, something else...)



a), b)

$$\frac{\bar{V}_{o2}}{\bar{V}_{o1}} = -\frac{j\omega C}{R_4} = \frac{-1}{j\omega CR_4}$$

HS

$$\bar{V}_{o1} = \alpha \bar{V}_+ \Rightarrow \bar{V}_+ = \frac{1}{2} \bar{V}_{o1}$$

$$\frac{\bar{V}_+ - \bar{V}_{in}}{R_2} + \frac{\bar{V}_+ - \bar{V}_{o2}}{R_3} = 0 \Rightarrow \bar{V}_+ = \frac{R_3}{R_2 + R_3} \bar{V}_{in} + \frac{R_2}{R_2 + R_3} \bar{V}_{o2}$$

simplify ... $\bar{V}_+ = \alpha \bar{V}_{in} + \beta \bar{V}_{o2}$

$$\bar{V}_+ = \frac{1}{2} \bar{V}_{o1} = \alpha \bar{V}_{in} + \beta \frac{\bar{V}_{o1}}{1 + j\omega CR_4}$$

$$\bar{V}_{o1} \left(1 + \frac{2\beta}{j\omega CR_4} \right) = 2\alpha \bar{V}_{in}$$

+S +S

$$T_1(\omega) = \frac{\bar{V}_{o1}}{\bar{V}_{in}} = \frac{2\alpha j\omega CR_4}{2\beta + j\omega CR_4}$$

$$T_2(\omega) = \frac{\bar{V}_{o2}}{\bar{V}_{in}} = \frac{-2\alpha}{2\beta + j\omega CR_4}$$

Room for extra work

c) $T_1(w)$ has a zero at 0 and a pole at

$$w_{p1} = \frac{2\beta}{CR_4} = \frac{2R_2/(R_2+R_3)}{CR_4}$$

+ 5

This is a high-pass filter.

$T_2(w)$ has a pole at


$$w_{p2} = \frac{2\beta}{CR_4} = \frac{2R_3/(R_2+R_3)}{CR_4}$$

+ 5

This is a low-pass filter with the same
breakpoint as the high-pass.

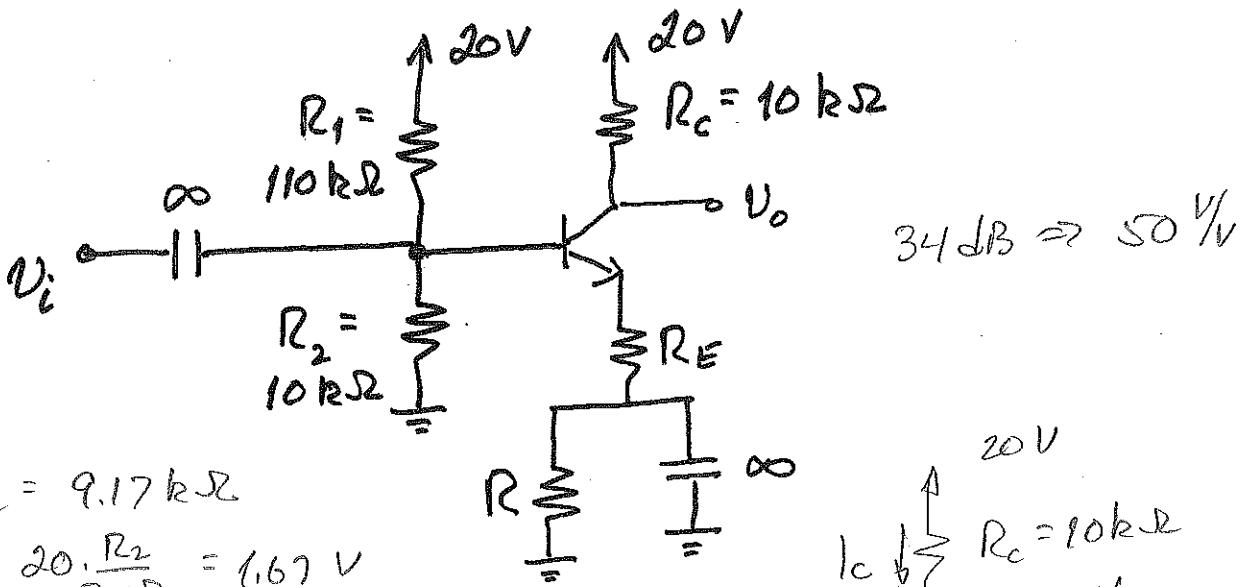4. (45 points) The circuit below is intended to be a high gain voltage amplifier. Find values of R_E and R that will complete the design. The BJT has $\beta = 60$ and $V_{CE,sat} = 0.3$ V. The specifications are as follows.

- The amplifier is to operate over the frequency range 20 Hz to 20 kHz.
- The gain in the pass band v_o/v_i is to be 34 dB.
- The dc value of the collector voltage should be 10 V.




DC Analysis :

We are given $V_C = 10 \text{ V}$

$$\Rightarrow I_C = \beta I_B = 1 \text{ mA.}$$

$$\text{Then } I_B = \frac{I_C}{\beta} = 16.67 \mu\text{A}$$
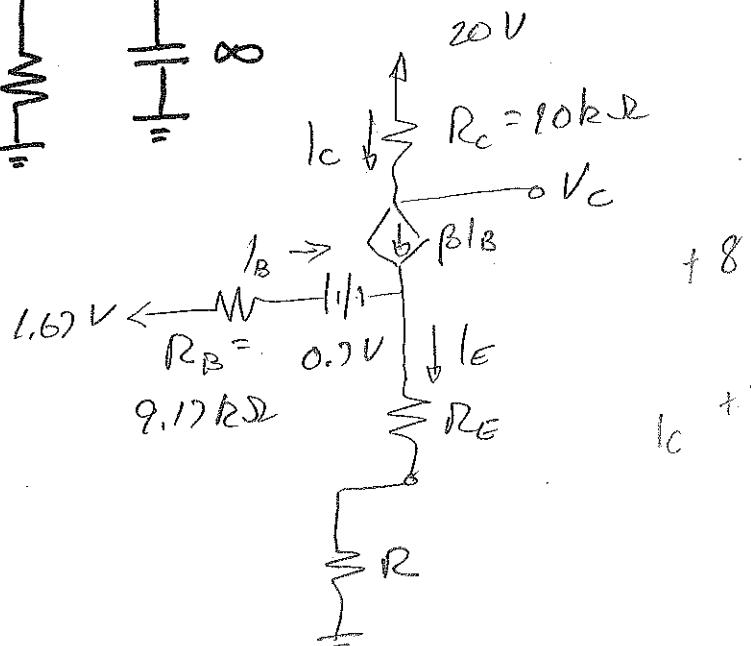
$$I_E = (\beta + 1)I_B = 1.017 \text{ mA}$$



This allows us to determine only the sum $R_E + R$:


$$-1.67 + I_B R_B + 0.7 + (\beta + 1) I_B (R_E + R) = 0$$

$$(V_E = 1.67 - 0.7 - I_B R_B = 0.817 \text{ V})$$

Room for extra work

$$R_E + R = \frac{1,67 - 0,7 - I_B R_B}{(\beta + 1) I_B} = 804 \Omega \quad +10$$

To go farther we need the ac model.

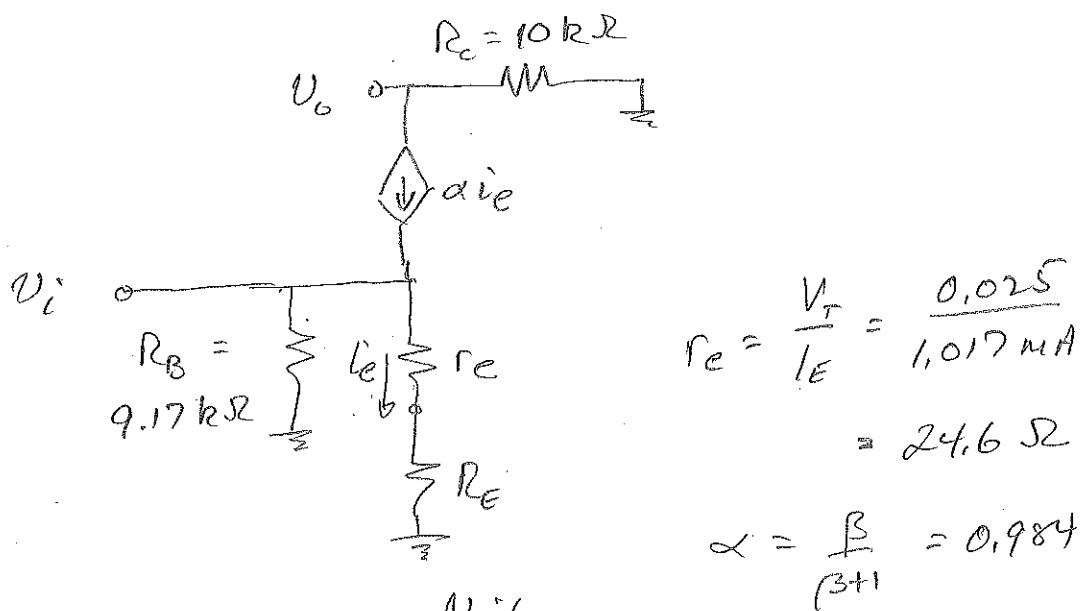

$$V_o = -\alpha i_e R_C \quad i_e = \frac{V_i}{(r_e + R_E)}$$

$$\left\{ \frac{V_o}{V_i} = \frac{-\alpha R_C}{r_e + R_E} \Rightarrow \frac{\alpha R_C}{r_e + R_E} = 50 \right.$$

$$\therefore R_E + R_E = \frac{\alpha R_C}{50} = 197 \Omega$$


$$\therefore \boxed{R_E = 172 \Omega \Rightarrow R = 632 \Omega}$$

+5%


So the operating frequency range is irrelevant!

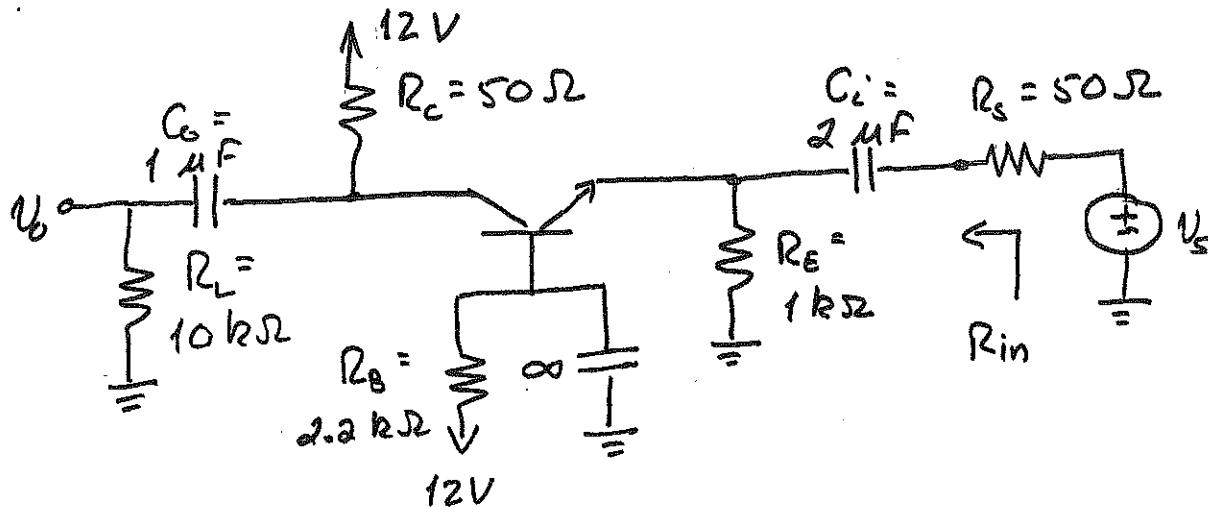5. (40 points) The circuit below is a common base amplifier. You may assume that it is operating in the linear region. It is characterized by $\beta = 100$ and $V_{CE,sat} = 0.3$ V.

- Find the gain v_o/v_s in the pass band.
- Find the input resistance R_{in} in the pass band.




DC Analysis

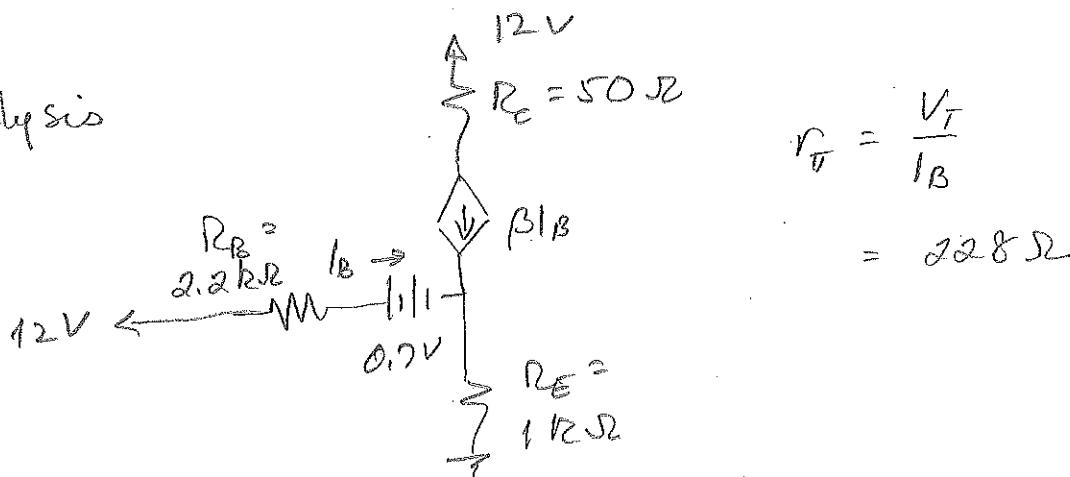

$$r_T = \frac{V_T}{I_B} \\ = 228 \Omega$$

$$I_B = \frac{12 - 0.7}{2.2 k\Omega + (\beta+1)(1000)} = 0.1095 \text{ mA}$$

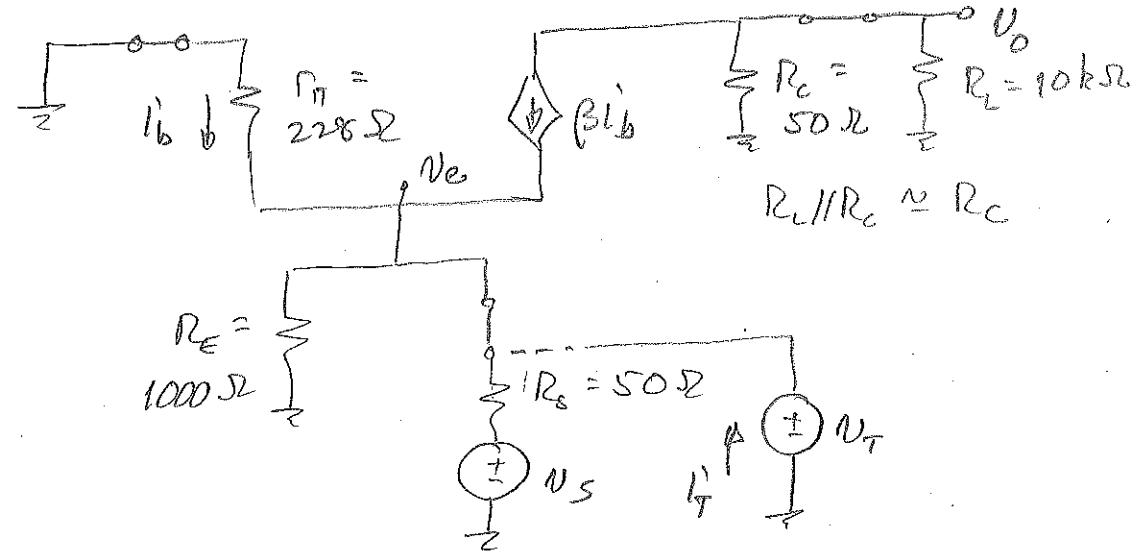In the pass band, $C_i \rightarrow \text{short}$, $C_o \rightarrow \text{short}$. Also, the base capacitor is infinite, so it is also a short at ac.



a) Replace V_s , R_s with a test voltage. Then

$$+ 8 \quad I_T' = \frac{V_T}{R_E} - (\beta + 1) I_b' \quad I_b' = -\frac{V_T}{R_\pi}$$

$$\therefore I_T' = V_T \left(\frac{1}{R_E} + \frac{\beta + 1}{R_\pi} \right)$$

$$\boxed{R_{in} = \frac{1}{(\beta + 1)R_E + R_\pi} = 2.25 \Omega}$$

b) $V_o = \beta I_b \cdot R_C // R_L$

$$+ 10 \quad (\beta + 1) \frac{V_e}{R_\pi} + \frac{V_e}{R_E} + \frac{V_e - V_s}{R_s} = 0$$

$$I_b' = -\frac{V_e}{R_\pi} \quad V_e \left(\frac{\beta + 1}{R_\pi} + \frac{1}{R_E} + \frac{1}{R_s} \right) = \frac{V_s}{R_s}$$

$$\frac{V_e}{V_s} = \frac{1}{50} \cdot \left(\frac{101}{228} + \frac{1}{1000} + \frac{1}{50} \right)^{-1}$$

$$= 4.31 \times 10^{-2}$$

$$\frac{V_o}{V_s} = \frac{\beta}{R_\pi} \cdot \frac{V_e}{V_s} R_C // R_L$$

$$= \frac{100}{228} \cdot 4.31 \times 10^{-2} (50)$$

$$\boxed{\frac{V_o}{V_s} = 0.945 V}$$