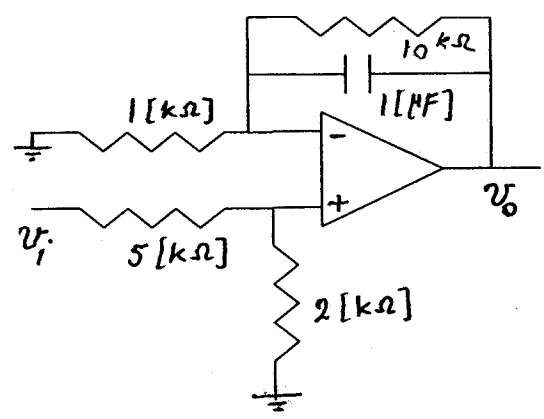


(ECE3455, Q3) In the circuit shown,

- Find the transfer function.
- Find the frequency at which the input and output amplitudes are equal.
- Find the phase difference between input and output at this frequency.

Hint: You can use either Bode plot or analytic method for Part(b) and (c) or both or the sake of comparison.



Solution:

$$Z_2 = 10[k] \parallel 1[\mu F] = \left(10^4 \times \frac{1}{10^{-6} s} \right) \frac{1}{10^4 + \frac{1}{10^{-6} s}}$$

$$Z_2 = \frac{10^4}{1 + 10^{-2} s}$$

$$\frac{V_o}{V_i} = \left[1 + \frac{Z_2}{1k} \right] \left[\frac{2}{2+5} \right] = \left[1 + \frac{10}{1 + 10^{-2} s} \right] \left[\frac{2}{7} \right]$$

$$T(s) = \frac{V_o}{V_i} = \frac{11 + 10^{-2} s}{1 + 10^{-2} s} \times 0.285 = 3.13 \frac{(1 + s/1100)}{1 + s/100}$$

ω is around 300 rad/sec from bode plot (magnitude) where the gain is ①


and the phase difference is around -50° at this freq.

Exact values are 313 rad/s and -57°

$$\text{Since } |T| = 3.13 \sqrt{\frac{1 + \omega^2/1100^2}{1 + \omega^2/100^2}} = 1 \Rightarrow \omega = 313$$

$$\angle T = \tan^{-1} \frac{313}{1100} - \tan^{-1} \frac{313}{100} = -57^\circ$$

171

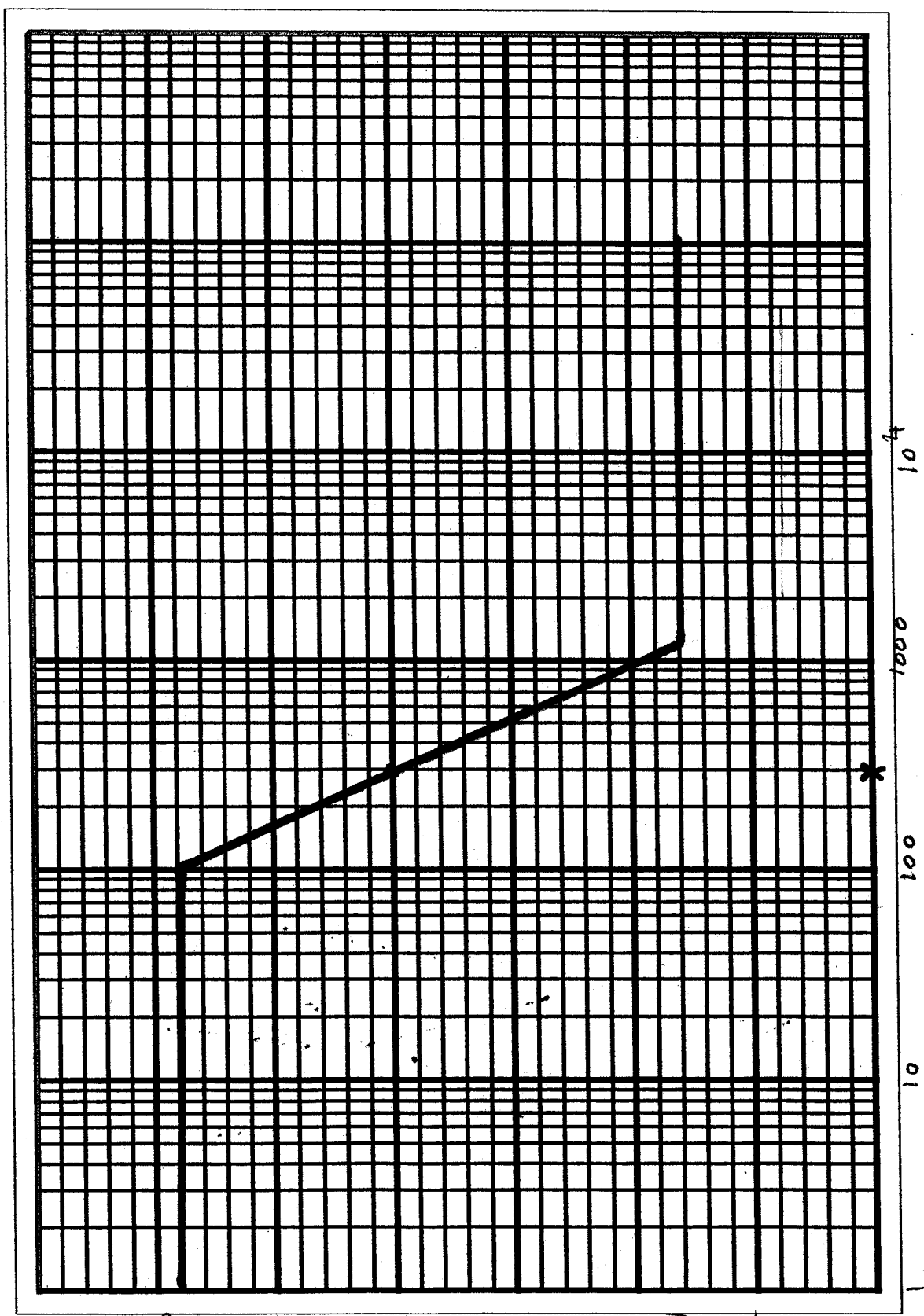

10 ←

5

0

-5

-10

-15

-20

10⁴


1000

100 *

10

1

17

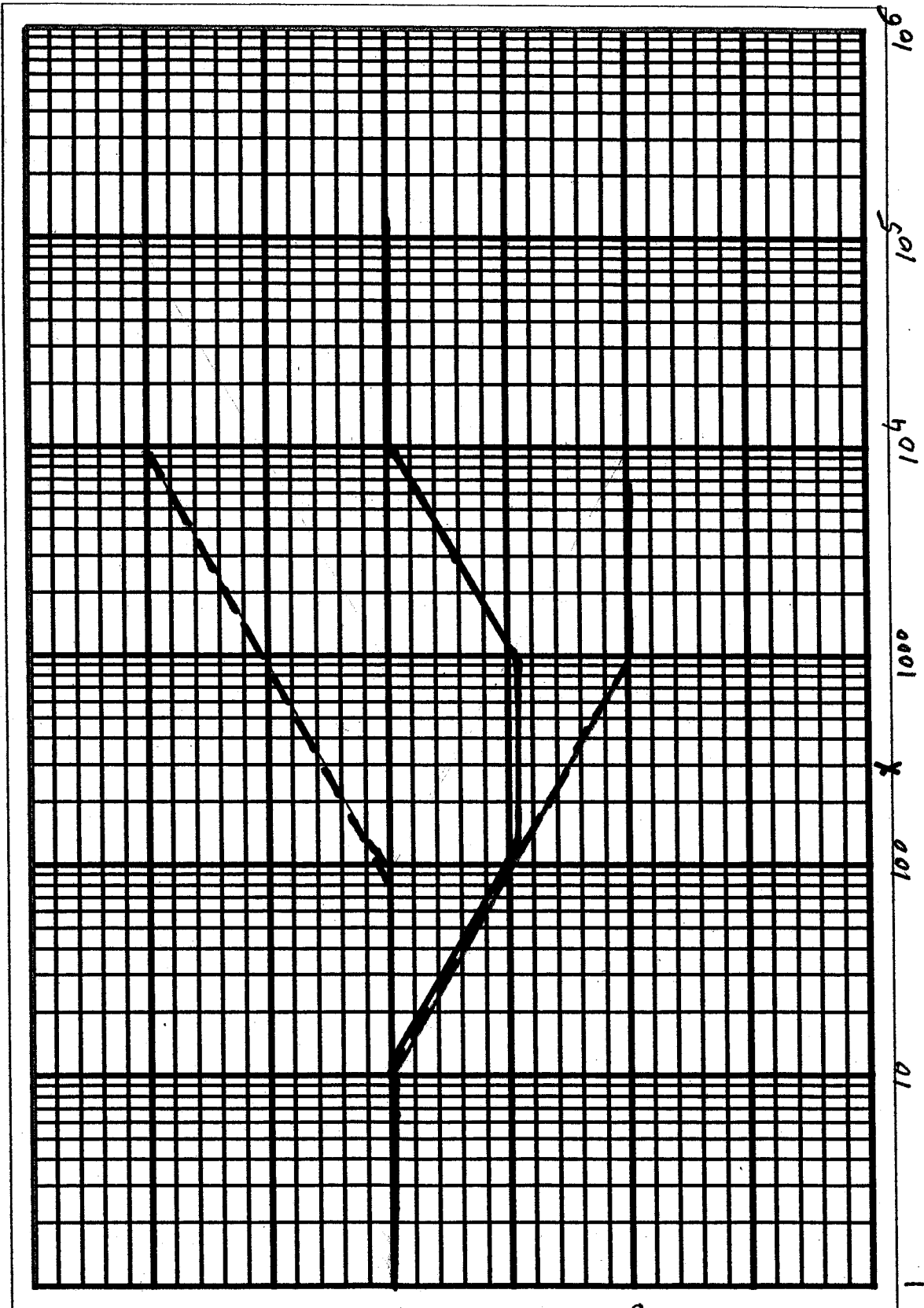

-45
-90

10⁶
10⁵
10⁴
1000
100
10
x