

Name: _____ (please print)

Signature: _____

ECE 3455
Exam 1
March 1, 2008

Exam duration: 90 minutes

- You may have one 8 ½ x 11 in. “crib” sheet, written on both sides, during the quiz. You may have any calculator you choose, but no computers. No other notes or materials will be allowed.
- Show all work necessary to complete the problem on these pages. A solution without the work shown will receive no credit.
- Show units in intermediate and final results, and in figures.
- If your work is sloppy or difficult to follow, points will be subtracted.

This exam has 10 pages, including the cover sheet. Raise your hand if you are missing a page.

1 _____ /25


2 _____ /25

3 _____ /25


4 _____ /25

Total _____ /100

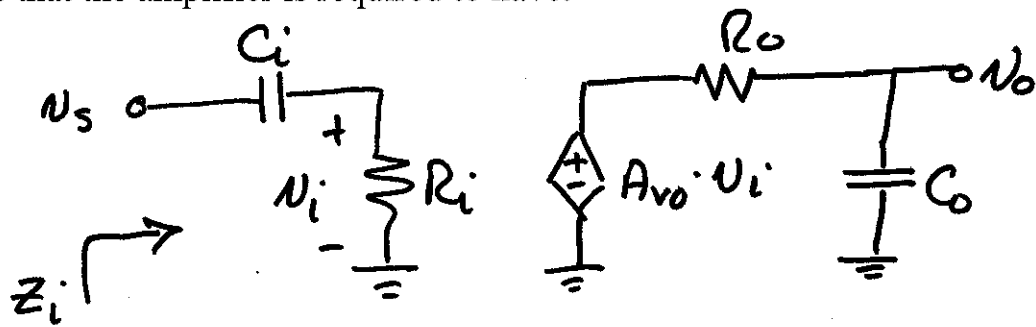1. (25 points) We want to design a band-pass filter based on the circuit shown below. The Bode plot indicates schematically the specifications for frequency response that the amplifier is required to have.



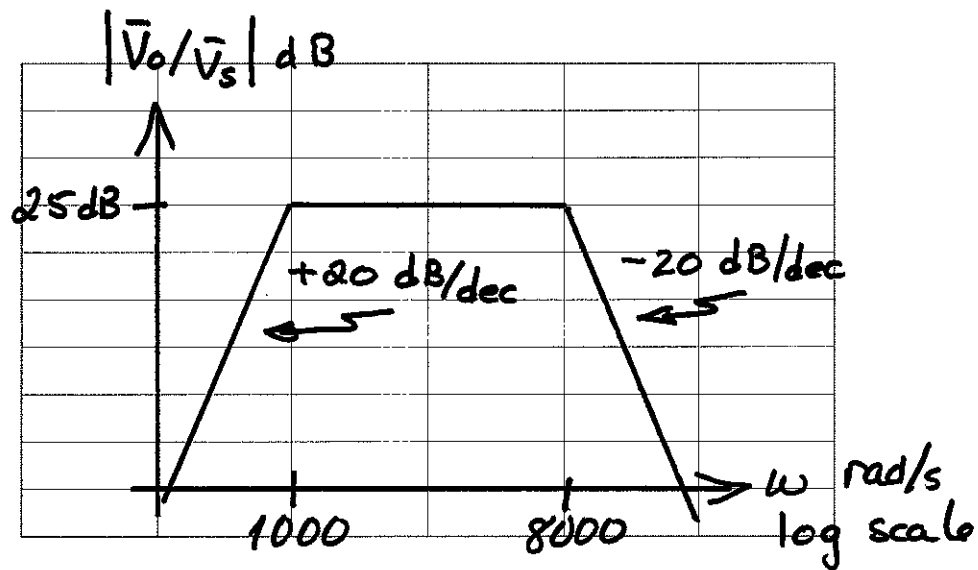- Find the transfer function, V_o/V_s for the circuit.
- Choose values for the resistors and capacitors, and for A_{vo} , such that (i) the input impedance Z_i approaches $22\text{ k}\Omega$ at very high frequencies and (ii) the frequency response shown in the Bode plot is obtained.



$$a) \quad \bar{V}_o = A_{vo} \cdot \bar{V}_i \cdot \frac{j\omega C_o}{j\omega C_o + R_o} = A_{vo} \bar{V}_i \cdot \frac{1}{1 + j\omega C_o R_o}$$

$$\bar{V}_i = \bar{V}_s \cdot \frac{R_i}{R_i + j\omega C_i} = \bar{V}_s \cdot \frac{j\omega C_i R_i}{1 + j\omega C_i R_i}$$

$$\therefore \frac{\bar{V}_o}{\bar{V}_s} = A_{vo} \frac{j\omega C_i R_i}{(1 + j\omega C_i R_i)(1 + j\omega C_o R_o)}$$

Room for extra work

So we have a zero at 0 rad/s ; one pole each at $1/CR_i$ and $1/CR_o \text{ rad/s}$.

b) For $\omega \rightarrow \infty$, $Z_i \rightarrow R_i = 22 \text{ k}\Omega$.

$$\text{So } 1/CR_i = 1000 \text{ rad/s} \Rightarrow C_i = \frac{1}{22000 \cdot 1000}$$

$$\boxed{\begin{array}{l} R_i = 22 \text{ k}\Omega \\ C_i = 45.45 \text{ nF} \end{array}}$$

$$= 45.45 \text{ nF.}$$

$$1/CR_o = 8000 \text{ rad/s}$$

We have no constraint on C_o or R_o so we'll choose $R_o = 100 \Omega$

$$\therefore 1/CR_o = 8000 \text{ rad/s} \Rightarrow C_o = \frac{1}{8000 \cdot 100}$$

$$= 1.25 \mu\text{F}$$

$$\boxed{\begin{array}{l} R_o = 100 \Omega \\ C_o = 1.25 \mu\text{F} \end{array}}$$

Let's evaluate V_o/\bar{V}_s at $\omega = 3000 \text{ rad/s} \Rightarrow \frac{V_o}{V_c} = 25 \text{ dB}$

$$\left. \frac{V_o}{V_c} \right|_{\omega=3000 \text{ rad/s}} = A_{vo} \cdot \frac{j(3000)(1/1000)}{(1+j3000 \cdot 1/1000)(1+j \frac{3000}{8000})}$$

$$\left. \frac{\bar{V}_o}{\bar{V}_s} \right|_{\omega = 3000 \text{ rad/s}} = A_{vo} \cdot (0.8877 - j0.0329)$$


$$= A_{vo} \cdot 0.8883 \angle -2.12^\circ$$

So $20 \log \left| \frac{\bar{V}_o}{\bar{V}_s} \right| = 20 \log A_{vo} \cdot 0.8883 = 25$

$$\log A_{vo} \cdot 0.8883 = \frac{25}{20} = \log A_{vo} + \log 0.8883$$

$$\Rightarrow \underline{A_{vo} = 20.02}$$

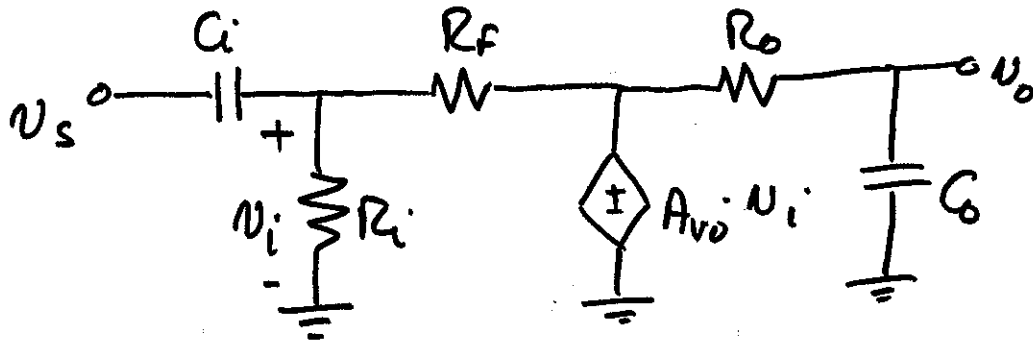2. (25 points) A feedback resistor, R_F , is added to the circuit of Problem 1, as shown below. Find the transfer function V_o/V_s with R_F in place. (Just find the transfer function; you do not need to re-calculate R , C , and A_{vo} to get the proper Bode plot behavior.)



$$\bar{V}_o = A_{vo} \bar{V}_i \frac{1}{1 + j\omega C_o R_o}$$

$$\frac{\bar{V}_i}{R_i} + \frac{\bar{V}_i - \bar{V}_s}{j\omega C_i} + \frac{\bar{V}_i(1 - A_{vo})}{R_F} = 0$$

$$\bar{V}_i = \bar{V}_s \frac{j\omega C_i \bar{V}_s}{\frac{1}{R_i} + j\omega C_i + \frac{1 - A_{vo}}{R_F}}$$

$$= \bar{V}_s \frac{j\omega C_i R_i R_F}{R_F + R_i(1 - A_{vo}) + j\omega C_i R_i R_F}$$

$$\therefore \frac{\bar{V}_o}{\bar{V}_s} = A_{vo} \frac{j\omega C_i R_i R_F}{(R_F + R_i(1 - A_{vo}) + j\omega C_i R_i R_F)(1 + j\omega C_o R_o)}$$

3. (25 points) The transfer function for a particular amplifier is shown below.

a) State clearly the poles and zeros of the transfer function.

b) On the paper provided on the next page, plot the **phase** Bode plot for this transfer function.

$$T(\omega) = \frac{6.7 \times 10^{-2} * (1 + j\omega/500)^2 (2 + j\omega/4000)}{(1 + j\omega/800)(10000 + j\omega)^2 (j\omega)}$$

ZERO'S: $\omega = 500$ rad/s DOUBLE ZERO

$$2 = \omega/4000 \Rightarrow \omega = 8000 \text{ rad/s}$$

POLES: $\omega = 800$ rad/s $\omega = 10000$ rad/s DOUBLE POLE

$$\omega = 0$$


$$\text{For } \omega \rightarrow 0, T(\omega) \rightarrow \frac{-6.7 \times 10^{-2} (1)^2 (2)}{(1)(10000)^2 (j\omega)}$$

$$\Rightarrow \angle T(\omega) \rightarrow \angle \frac{1}{-j} = 90^\circ$$

$$\omega \rightarrow \infty T(\omega) \rightarrow \frac{-6.7 \times 10^{-2} (j\omega/500)^2 (j\omega/4000)}{(j\omega/800)(j\omega)^2 (j\omega)}$$

$$\angle T(\omega) \rightarrow \angle \frac{1}{-j} = -90^\circ$$

$\angle T_{100}^{\circ}$

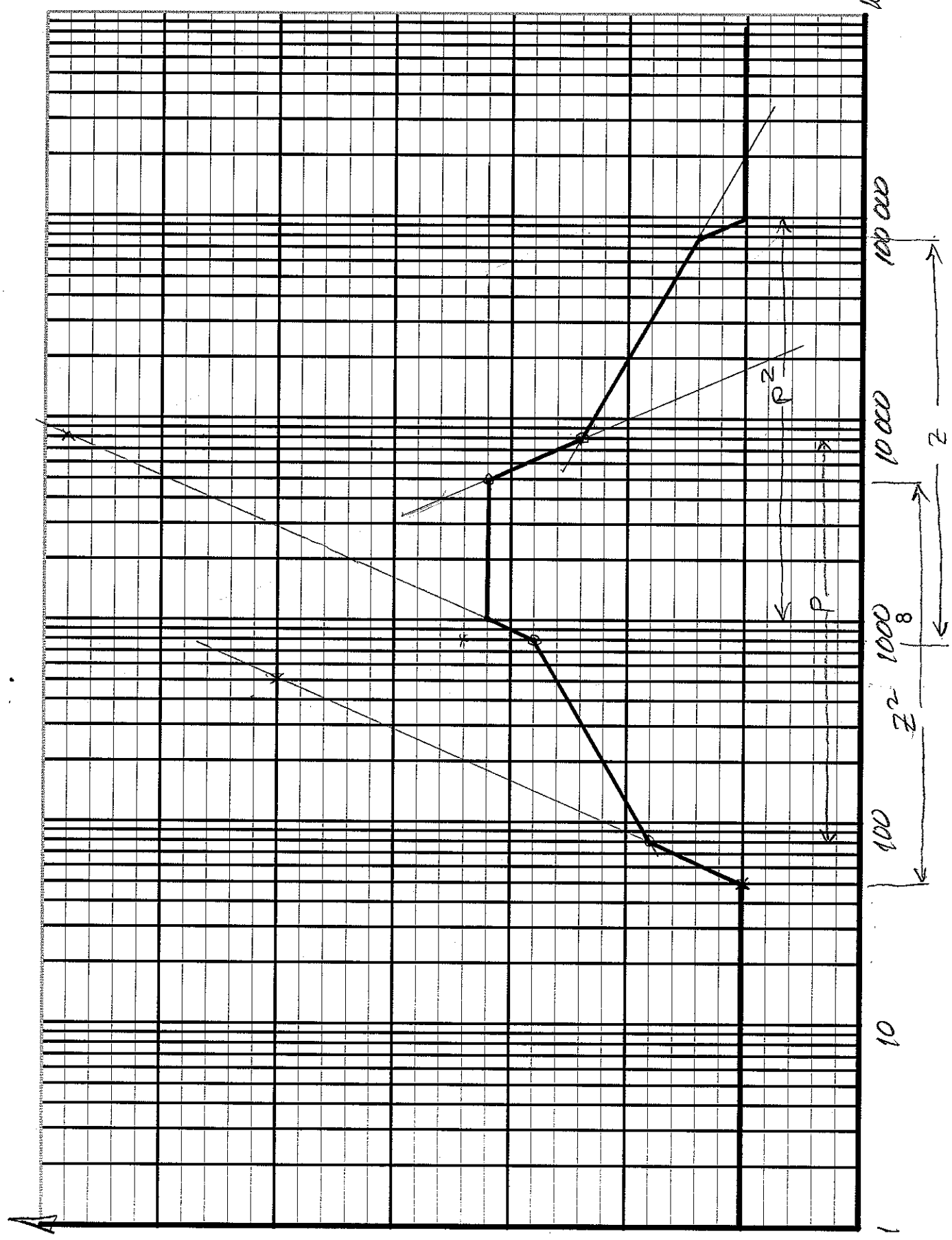

57
100000

1081

1000

1000

90

101

100


1000

10000

100000

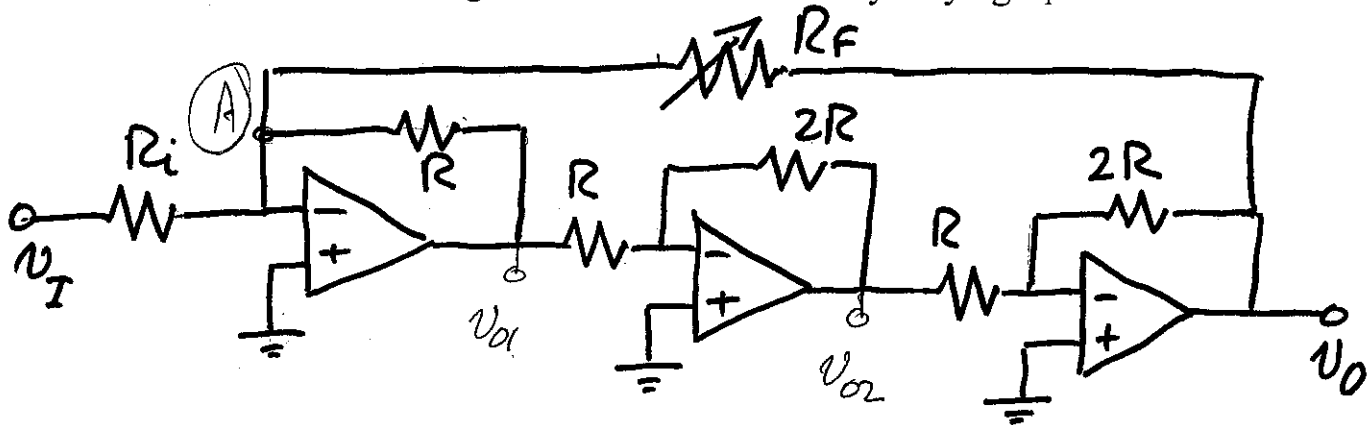4. (25 points) The op amps in the circuit below are "ideal". By varying R_F , a range of voltage gain (v_O/v_I) can be obtained.

- Find the gain v_O/v_I in terms of the various resistances.
- Considering values of R_F that are positive or 0, what are the maximum and minimum values of gain that can be obtained by varying R_F ?



$$v_{O2} = -\frac{2R}{R} v_{O1} \quad v_O = -\frac{2R}{R} v_{O2} = \underline{\underline{4 v_{O1}}}$$

$$\Rightarrow v_{O1} = \frac{1}{4} v_O$$

KCL at (A)

$$\frac{v_{O1}}{R} + \frac{v_I}{R_i} + \frac{v_O}{R_F} = 0$$

$$\frac{v_O}{4R} + \frac{v_I}{R_i} + \frac{v_O}{R_F} = 0$$

$$v_O \frac{R_F}{4R} + v_I \frac{R_F}{R_i} + v_O = 0$$

$$v_O \left(1 + \frac{R_F}{4R}\right) = -\frac{R_F}{R_i} v_I$$

$$\boxed{\frac{v_O}{v_I} = \frac{-R_F/R_i}{1 + R_F/4R}}$$

Room for extra work

b) Consider extremes in R_F :

$$R_F = 0 \Rightarrow \boxed{\frac{V_o}{V_I} = 0} \quad (\text{output is shorted to ground via } R_F)$$

$$R_F = \infty \Rightarrow \begin{aligned} V_{o1} &= -V_I \frac{R}{R_i} \\ V_{o2} &= -2V_{o1} = 2V_I \frac{R}{R_i} \\ V_o &= -2V_{o2} = -4V_I \frac{R}{R_i} \end{aligned}$$

(no connection through R_F)

$$\boxed{\frac{V_o}{V_I} = -\frac{4R}{R_i}}$$

We can look at this mathematically as well:

$$\frac{V_o}{V_I} = \frac{-1/R_i}{1/R_F + 1/4R}$$
$$R_F \rightarrow \infty \Rightarrow \frac{V_o}{V_I} = \frac{-1/R_i}{1/4R} = -\frac{4R}{R_i} \quad \checkmark$$