

Name: _____ (please print)

Signature: _____

ECE 3455
Final Exam
April 30, 2008

Exam duration: 170 minutes

- You may have *two* 8 ½ x 11 in. “crib” sheets, written on both sides, during the exam. You may have any calculator you choose, but no computers. No other notes or materials will be allowed.
- Show all work necessary to complete the problem on these pages. A solution without the work shown will receive no credit.
- Show units in intermediate and final results, and in figures.
- If your work is sloppy or difficult to follow, points will be subtracted.

This exam has 11 pages, including the cover sheet. Raise your hand if you are missing a page.

1 _____ /20

2 _____ /20

3 _____ /25


4 _____ /25

5 _____ /10

Total _____ /100

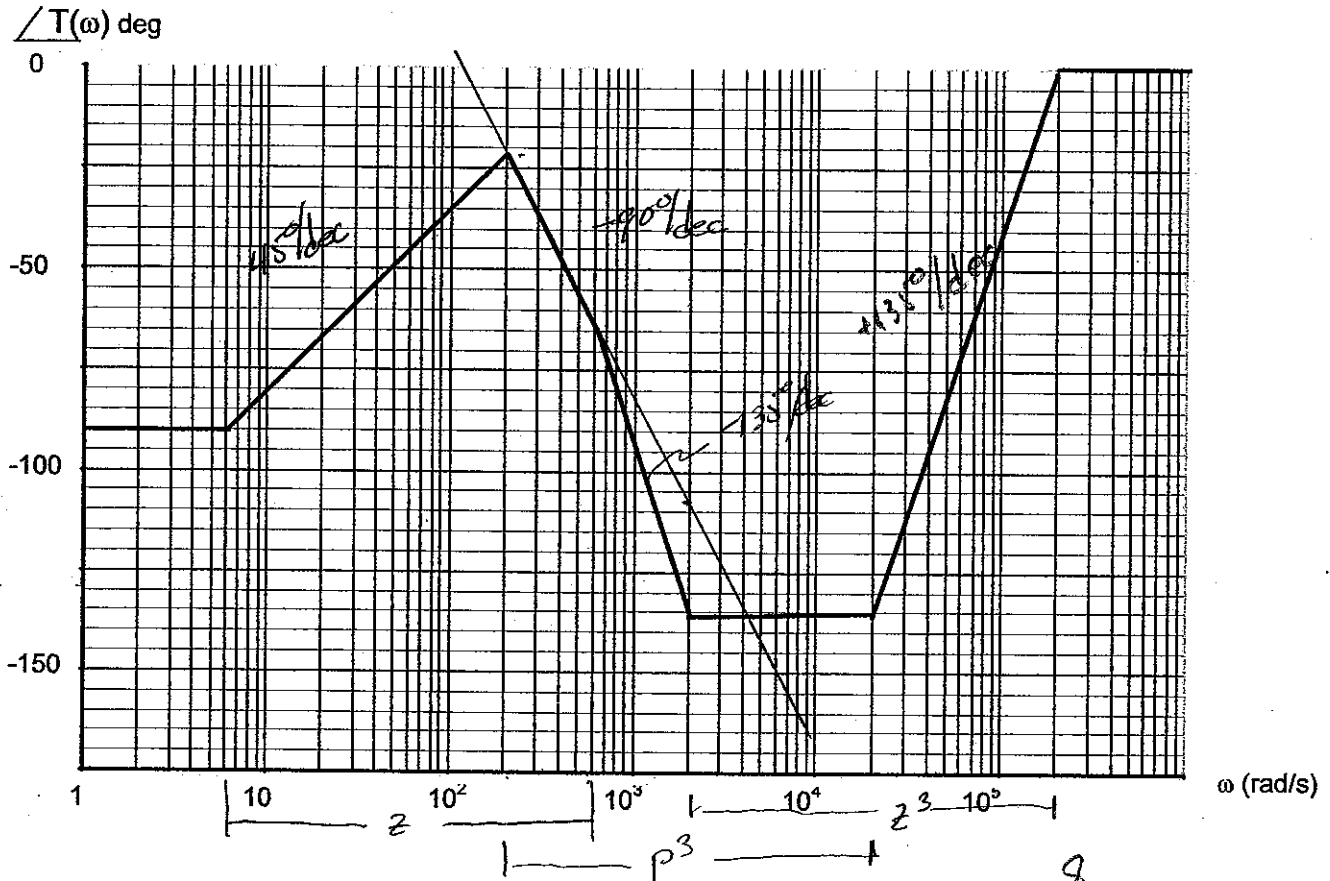1. (20 points) A phase Bode plot corresponding to a certain transfer function is sketched below. The magnitude of the transfer function at very large ω is 15 dB, and as ω approaches 0, the transfer function magnitude approaches ∞ .

- Find the transfer function $T(\omega)$, including any constants necessary to specify the magnitude.
- Plot the magnitude Bode plot on the paper provided on the next page.



Analysis of slopes shows:

zeros: 60, 3 at 20000 rad/s

poles: 3 at 2000 rad/s

$$\Rightarrow T(j\omega) = K \cdot \frac{(j\omega + 60)(j\omega + 20000)^3}{(j\omega + 2000)^3(j\omega)}$$

$$\omega \rightarrow 0 \Rightarrow \angle T(j\omega) \rightarrow -90^\circ \Rightarrow \text{Pole at } 0$$

$$\omega \rightarrow \infty \Rightarrow T(j\omega) \rightarrow K \Rightarrow 20 \log K = 15 \text{ dB}$$


$$\therefore K = 10^{15/20} = 5.62$$

Magnitude plot next page \rightarrow

check: $|T(j\omega)|_{300 \text{ rad/s}} \approx 75.3$ so plot is OK at this ω .

Labels, Units: +1
 Magnitude: +2
 BP's: +2 ea.
 Pole at 0: +1


$|T(\omega)| / \text{dB}$

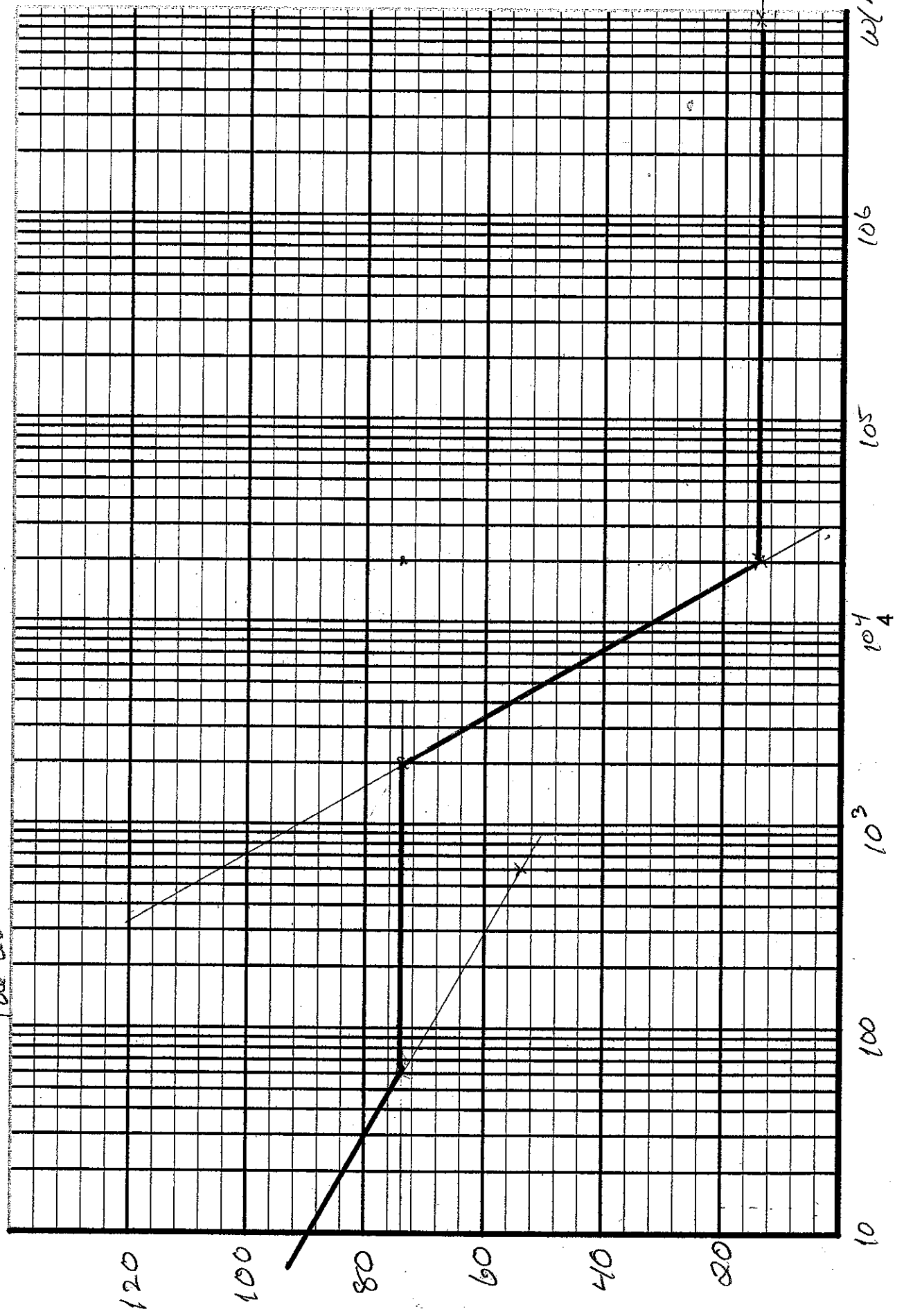

(Speed ω)

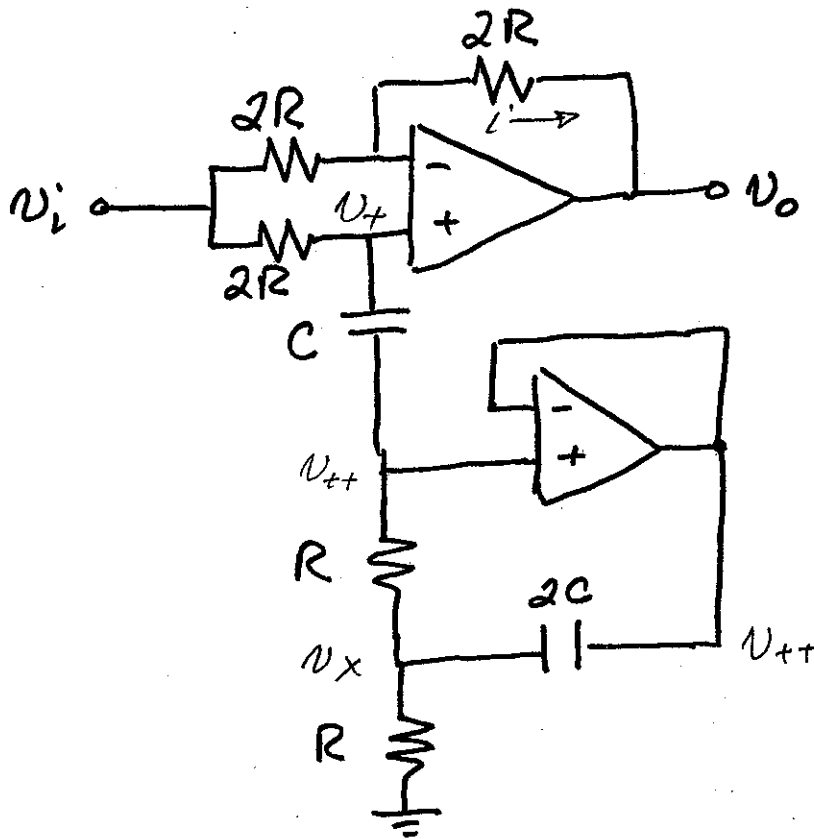2. (20 points) The op amps in the circuit below may be considered ideal.

Write a set of equations that could be used to find the transfer function $T(\omega) = V_o/V_i$ for the circuit. Do not attempt to solve the equations. Draw a box around the equations that are part of your solution; equations not in a box will not be counted. Points will be deducted if you do not have a sufficient number of independent equations to find the transfer function, or if your equations are redundant or otherwise unnecessary.



$$\left. \begin{aligned} \bar{V}_o - \bar{V}_+ + 2R \cdot \bar{I} &= 0 \\ \bar{I} &= \frac{\bar{V}_i - \bar{V}_+}{2R} \end{aligned} \right\} \Rightarrow \boxed{\bar{V}_o = 2\bar{V}_+ - \bar{V}_i} \quad (1)$$

We need \bar{V}_+ in terms of \bar{V}_i :

$$\boxed{\frac{\bar{V}_+ - \bar{V}_i}{2R} + \frac{\bar{V}_+ - \bar{V}_{++}}{1/s\omega C} = 0} \quad (2)$$

Now we need an equation for \bar{V}_{++} and another for \bar{V}_x

Room for Extra work

$$\left\| \frac{\bar{V}_{++} - \bar{V}_+}{1/j\omega C} + \frac{\bar{V}_{++} - \bar{V}_x}{R} = 0 \right. \quad (3)$$

$$\left\| \frac{\bar{V}_x - \bar{V}_{++}}{R} + \frac{\bar{V}_x - \bar{V}_{++}}{1/2j\omega C} + \frac{\bar{V}_x}{R} = 0 \right. \quad (4)$$

Now (3) and (4) together will give us \bar{V}_{++} in terms of \bar{V}_+ (by eliminating \bar{V}_x); this gets plugged into (2) to eliminate \bar{V}_{++} and the result goes into (1).

The 4 equations above are all we were asked to do, but let's solve anyway...

$$\text{From (4): } \bar{V}_x = \bar{V}_{++} \frac{1 + j\omega 2CR}{2 + j\omega 2CR}$$

$$\text{From (3): } \bar{V}_{++} \left(j\omega C + \frac{1}{R} \right) - \bar{V}_x \left(\frac{1}{R} \right) = \bar{V}_+ j\omega C$$

Substituting \bar{V}_x and multiplying by R gives

$$\bar{V}_{++} \left(j\omega CR + 1 - \frac{1 + j\omega 2CR}{2 + j\omega 2CR} \right) = \bar{V}_+ j\omega C$$

Solving for \bar{V}_{++} and clearing fractions... ($\rightarrow 2$)

Room for Extra Work

$$\bar{V}_{++} = \bar{V}_+ \frac{j\omega CR(2+j\omega 2CR)}{(1+j\omega CR)(2+j\omega 2CR) - (1+j\omega 2CR)}$$

From (2)

$$\bar{V}_+ \left(\frac{1}{2R} + j\omega C \right) - \bar{V}_{++} j\omega C = \bar{V}_i \left(\frac{1}{2R} \right)$$


Multiplying by $2R$ and substituting V_{++} from above gives

$$\bar{V}_+ \left[(1+j\omega 2CR) - \frac{j\omega CR(2+j\omega 2CR)(j\omega 2CR)}{(1+j\omega CR)(2+j\omega 2CR) - (1+j\omega 2CR)} \right] = \bar{V}_i$$

This now goes into (1) but we will leave that for the student ...

Although not obvious from the equations, this is a notch filter. For $CR = 10^{-3}$ s, the notch frequency is ~ 700 rad/s and the 3dB bandwidth is 1 decade.

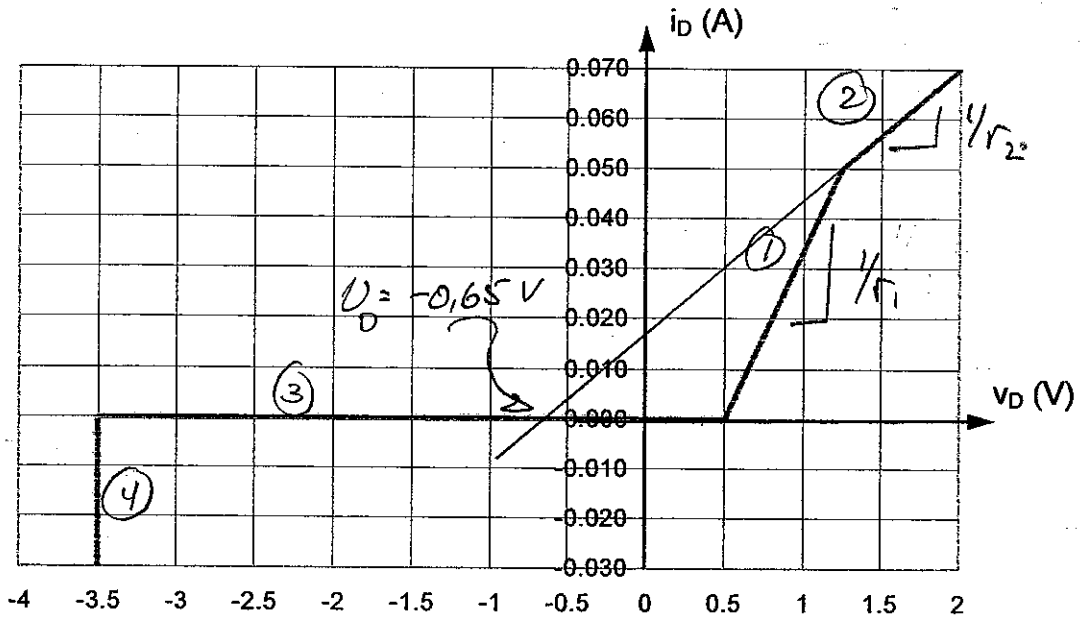3. (25 points) The current-voltage characteristics for a particular diode are shown below. Use the graph provided to plot the transfer characteristics (i.e., v_O/v_I) for the circuit shown. Be sure to account for an input voltage large enough to bias the diodes in all possible regions.





$$r_1 = \frac{1.25 - 0.5}{0.05 - 0}$$

$$r_1 = 15 \Omega$$

$$r_2 = \frac{2 - 1.25}{0.02}$$


$$r_2 = 37.5 \Omega$$

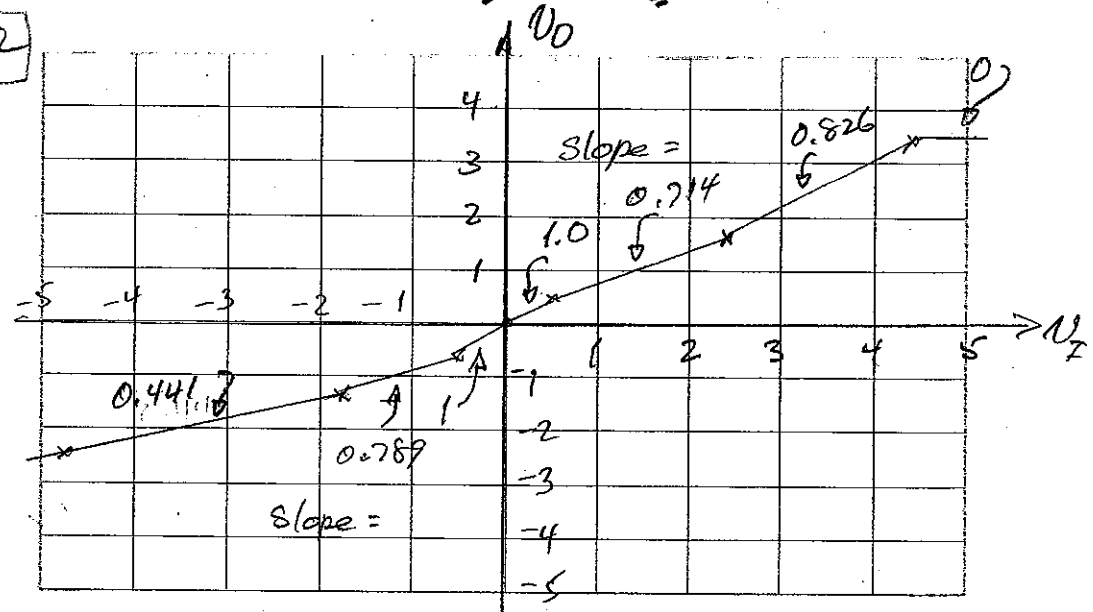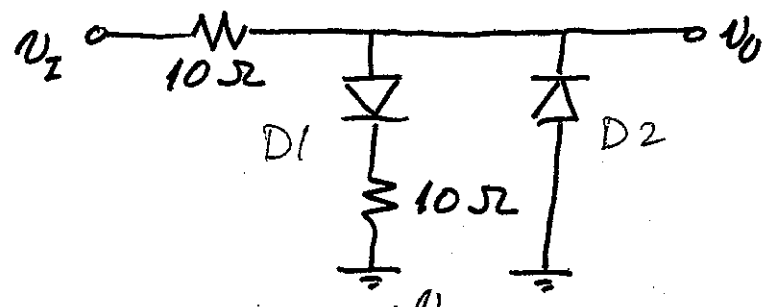

Room for extra work

$$V_I > 0: \quad 0 \leq V_i \leq 0.5 \text{ V} \Rightarrow \begin{matrix} D_1 \text{ OFF} \\ D_2 \text{ OFF} \end{matrix} \Rightarrow V_O = V_I$$
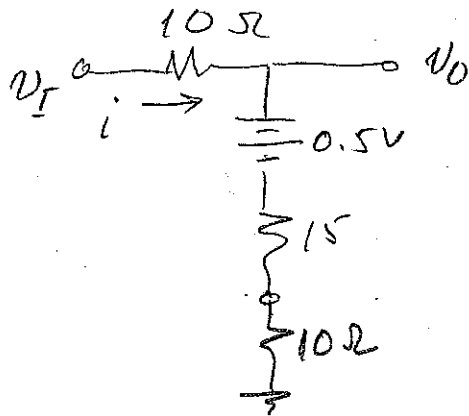
$$0.5 \text{ V} \leq V_i \leq ? \Rightarrow \begin{matrix} D_1 \text{ ON} \\ D_2 \text{ OFF} \end{matrix}$$




$$I = \frac{V_I - 0.5}{35}$$

$$V_O = 0.5 + \frac{25}{35} V_I - \frac{25}{35} (0.5)$$

$$V_O = 0.143 + 0.714 V_I \text{ [V]}$$

Where does D_1 go to region 2?

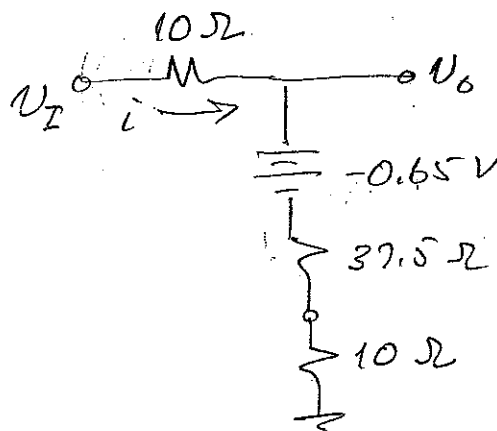

$$I = \frac{V_I + 0.65}{57.5}$$

$$V_O = -0.65 + \frac{47.5}{57.5} (V_I + 0.65)$$

$$= -0.113 + 0.826 V_I$$

Set this result equal to that from previous region:

$$-0.113 + 0.826 V_I = 0.143 + 0.714 V_I \Rightarrow V_I = 2.29 \text{ V}$$

$$\approx 2.3 \text{ V.}$$


At this point, $V_O = 1.79 \text{ V}$

Finally, for $V_D = 3.5 \text{ V}$, D_2 goes ON (reverse-bias)
 This happens at V_I such that

$$3.5 = -0.113 + 0.826 V_I \Rightarrow V_I = 4.37 \text{ V}$$

After that, V_D is constant at 3.5 V
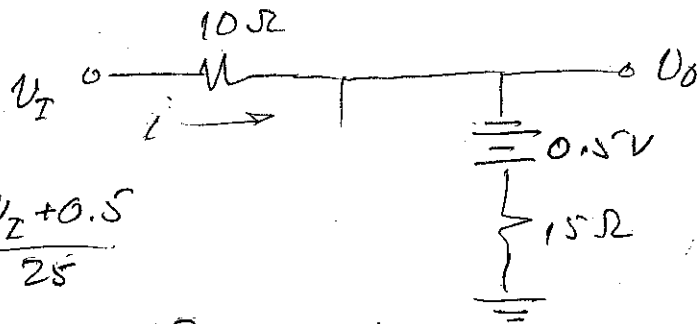
$$V_I < 0: \quad V_I > -0.5 \text{ V} \Rightarrow D_1 \text{ OFF} \quad D_2 \text{ OFF} \Rightarrow V_D = V_I$$




$$i = \frac{V_I + 0.5}{25}$$

$$V_D = -0.5 + \frac{15}{25} (V_I + 0.5)$$

$$V_D = -0.2 + 0.6 V_I$$

To get D_2 to region 2 we need:

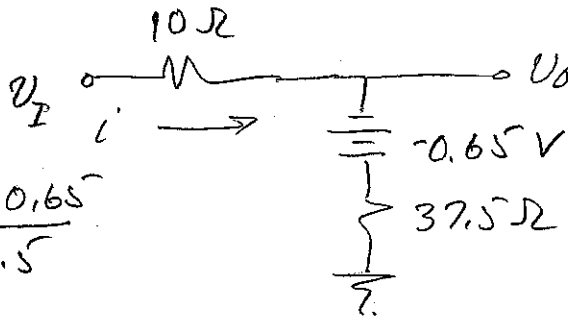

$$i = \frac{V_I + 0.65}{47.5}$$

$$V_D = +0.65 + \frac{37.5}{47.5} (V_I + 0.65)$$


$$V_D = 10.137 + 0.789 V_I$$

Again setting this equal to the previous result gives

$$+0.137 + 0.789 V_2 = -0.2 + 0.6 V_2 \Rightarrow V_2 = -1.78 \text{ V.}$$

At this point, $V_0 \approx -1.27 \text{ V.}$

For DI in reverse-breakdown we have

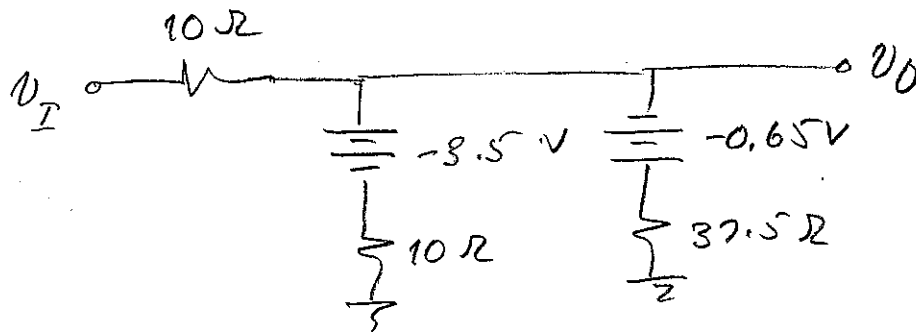

$$\frac{V_0 + 3.5}{10} + \frac{V_0 - 0.65}{37.5} + \frac{V_0 - V_I}{10} = 0$$

$$V_0 \left(\frac{1}{10} + \frac{1}{37.5} + \frac{1}{10} \right) = V_I \left(\frac{1}{10} \right) - \frac{3.5}{10} + \frac{0.65}{37.5}$$

$$V_0 (0.2267) = 0.1 V_I - 0.333$$

$$V_0 = 0.441 V_I - 1.47 \text{ V.}$$

To find where this happens, set

$$0.441 V_2 - 1.47 = 0.137 + 0.789 V_2 \Rightarrow V_2 = -4.62 \text{ V}$$


$$\Rightarrow V_0 = -2.37 \text{ V.}$$

THE END


NOTE: This problem is a nice exercise but is TOO LONG !!!
(Sorry to SP 2008 class)

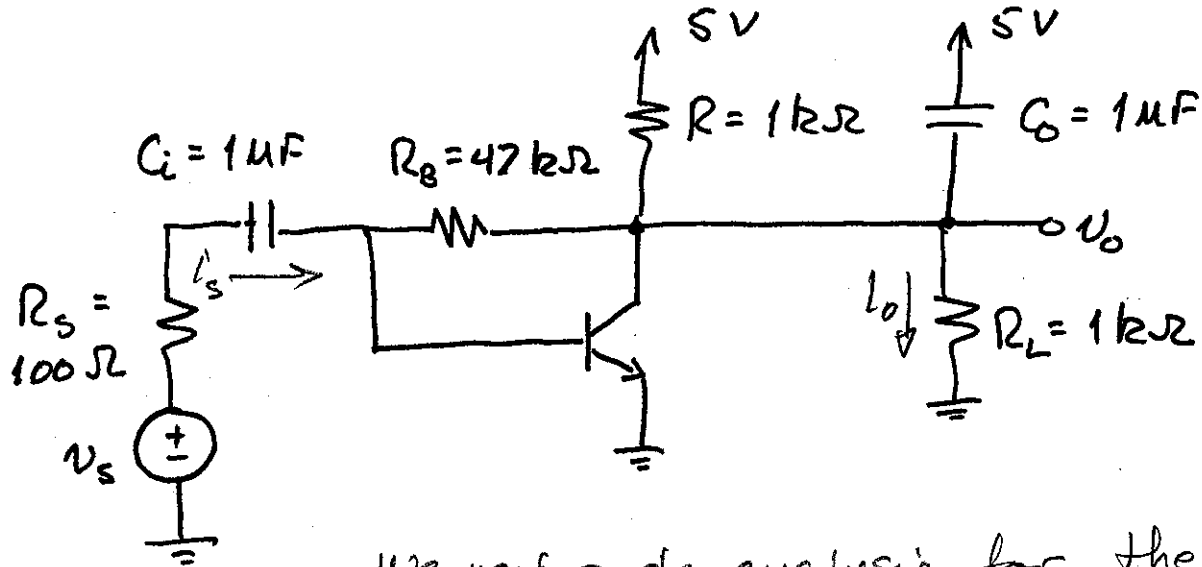4. (25 points) The BJT in the circuit below has $\beta = 100$ and $V_{CE,SAT} = 0.2$ V. It is biased in the linear region; there is no need to prove this is the case.

- Find the current gain i_o/i_s in the pass band.
- Find the voltage gain v_o/v_s in the pass band.



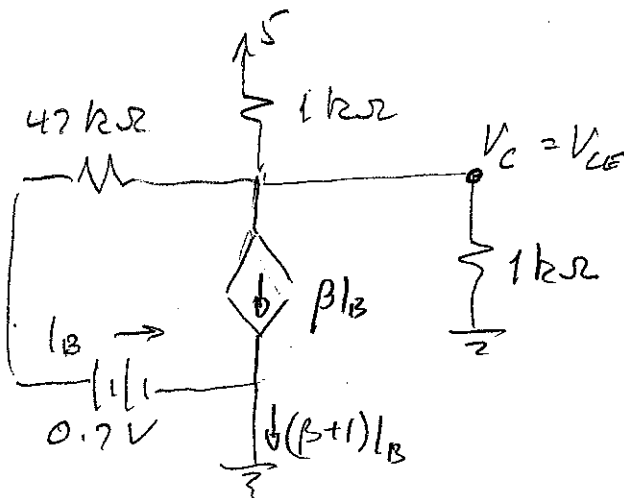We need a dc analysis for the ac model parameters:



$$0 = \frac{V_C - 5}{1000} + \frac{V_C}{1000} + (\beta + 1) \frac{V_C - 0.7}{47000}$$

$$V_C \left(\frac{1}{1000} + \frac{1}{1000} + \frac{101}{47000} \right) = \frac{5}{1000} + (\beta + 1) \frac{0.7}{47000}$$

$$\Rightarrow V_C = 1.568 \text{ V}$$


$$I_B = \frac{V_C - 0.7}{47000} = 18.47 \mu\text{A}$$

$$\Rightarrow r_{\pi} = \frac{V_T}{I_B} = 1354 \Omega$$

$$g_m = \frac{I_C}{V_T} = 73.87 \text{ mS}$$

x3

Room for extra work

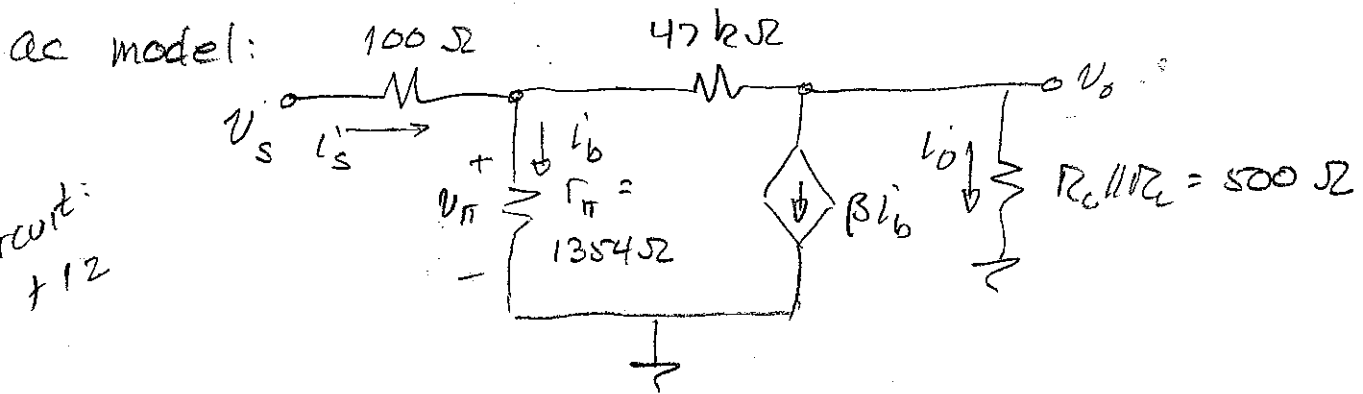

current: +12

Capacitors have been shorted since we are in the pass band. Analysis:

$$\textcircled{1} \quad \frac{V_{\pi} - V_s}{100} + \frac{V_{\pi} - V_o}{47000} + \frac{V_{\pi}}{1354} = 0 \quad \textcircled{2} \quad \frac{V_o - V_{\pi}}{47000} + 100 \frac{V_{\pi}}{1354} + \frac{V_o}{500} = 0$$

$$\textcircled{2} \Rightarrow V_{\pi} \left(\frac{100}{1354} - \frac{1}{47000} \right) = -V_o \left(\frac{1}{47000} + \frac{1}{500} \right)$$

$$V_{\pi} \approx -0.0271 V_o$$

$$\textcircled{1} \quad V_{\pi} \left(\frac{1}{100} + \frac{1}{47000} + \frac{1}{1354} \right) - V_o \left(\frac{1}{47000} \right) = \frac{V_s}{100}$$

$$V_{\pi} (0.0107) = -2.908 \times 10^{-4} V_o - \left(\frac{1}{47000} \right) V_o = \frac{V_s}{100}$$

x 5

$$V_o = -32.04 V_s \checkmark$$

$$\frac{V_o}{V_s} = -32.0$$

x 5

$$\frac{i_o}{i_s} = -48.2$$

over \rightarrow

$$l'_D = \frac{V_0}{500} = \frac{-32V_S}{500}$$

$$l'_S = \frac{V_S - V_{II}}{100} = \frac{V_S - (-0.0271)V_0}{100}$$

$$= V_S \left(\frac{1}{100} + \frac{0.0271(-32)}{100} \right)$$

$$= 1.328 \times 10^{-3} V_S$$

$$\therefore \frac{l'_D}{l'_S} = \frac{-32/500}{1.328 \times 10^{-3}} = -48.2$$

$$\frac{l'_D}{l'_S} = -48.2$$

$$\frac{l'_D}{l'_S} = \frac{V_{II}/V_{II}}{(V_S - V_{II})/100} = \frac{100}{V_{II}} \frac{V_{II}}{V_S - V_{II}}$$

$$V_S - V_{II} = V_S + (0.0271)V_0$$

$$= V_S + (0.0271)(-32)V_S$$

$$= V_S (1 - 32 \times 0.0271)$$

$$= 0.1328 V_S$$

$$V_{II} = -0.0271 V_0$$

$$= 0.8672 V_S$$

$$\therefore \frac{l'_D}{l'_S} = \frac{100}{V_{II}} \frac{0.8672}{0.1328}$$


$$= 0.482$$

5. (10 points) The transfer function for the op amp in Problem 2 is greatly simplified in the case that the frequency is either very high or very low. For that op amp problem, do the following.

- Find the transfer function for very low frequencies. Explain in a sentence or two how you arrived at your answer.
- Find the transfer function for very high frequencies. Explain in a sentence or two how you arrived at your answer.

For $\omega \rightarrow \infty$, capacitors short. That means the voltage across R' is 0 so i_+ is 0.

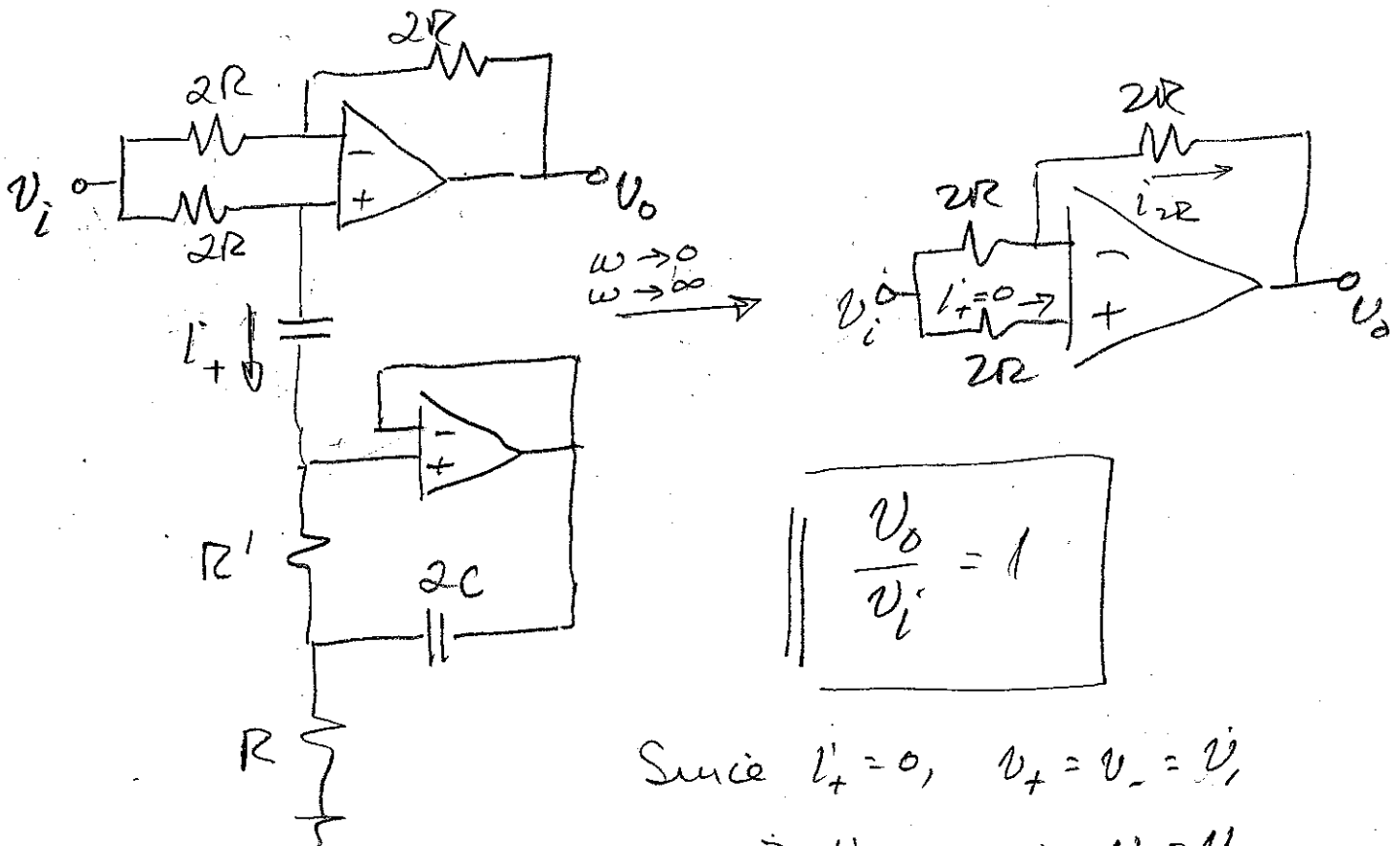For $\omega \rightarrow 0$, capacitors open. In either case we are left with just the upper circuit:



Since $i_+ = 0$, $v_+ = v_- = v_i$
 $\Rightarrow i_{2R} = 0 \Rightarrow v_o = v_i$

correct circuit

+4 ea.