

Name: \_\_\_\_\_ (please print)

Signature: \_\_\_\_\_


ECE 3455  
Quiz #6  
April 28, 2008

Quiz duration: 30 minutes

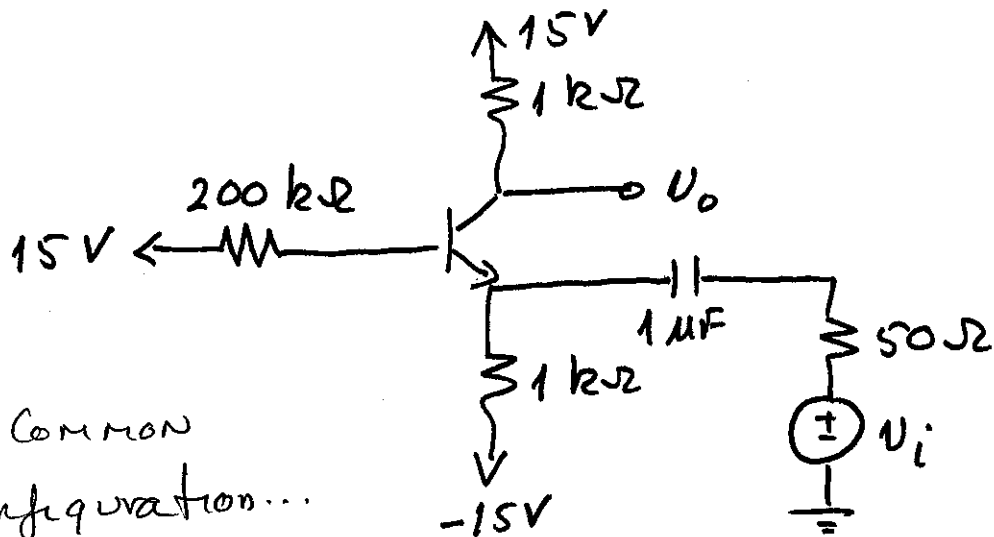1. You may have one 8 ½ x 11 in. “crib” sheet, written on both sides, during the quiz. You may have any calculator you choose, but no computers. No other notes or materials will be allowed.
2. Show all work necessary to complete the problem on these pages. A solution without the work shown will receive no credit.
3. Show units in intermediate and final results, and in figures.
4. If your work is sloppy or difficult to follow, points will be subtracted.

\_\_\_\_\_/20

The BJT in the circuit below has  $\beta = 100$  and  $V_{CE,SAT} = 0.3 \text{ V}$ . It is biased in the linear region; you may assume this without proof. Find the gain  $v_o/v_i$  in the pass band.




This is a common base configuration...

We were not asked for proof that the BJT is in the linear region but let's do it anyway. We need  $I_B$  or  $I_C$  for our ac model anyway...

### DC ANALYSIS

$C \rightarrow$  open circuit

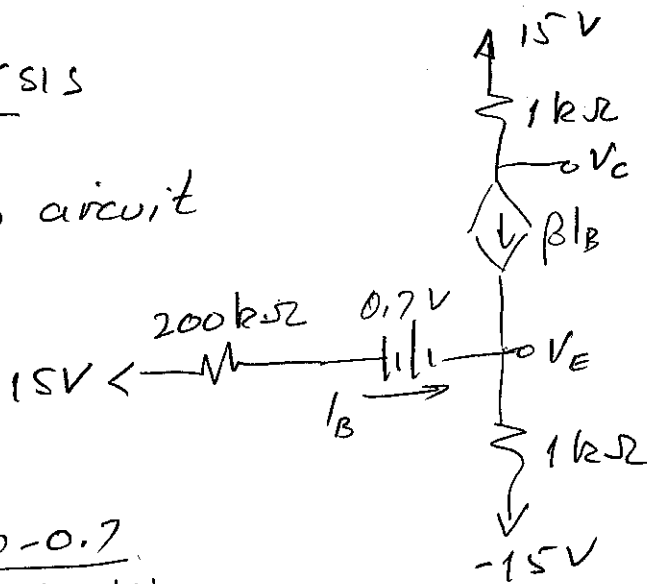


$$I_B = \frac{30 - 0.7}{200k + (\beta + 1)1k}$$

$$= 98.7 \mu\text{A}$$

$$\begin{aligned} V_{CE} &= (15 - 1000\beta I_B) - (1000(\beta + 1)I_B - 15) \\ &= 5.13 - (-5.03) \\ &= 10.33 \text{ V} \end{aligned}$$

Room for Extra Work

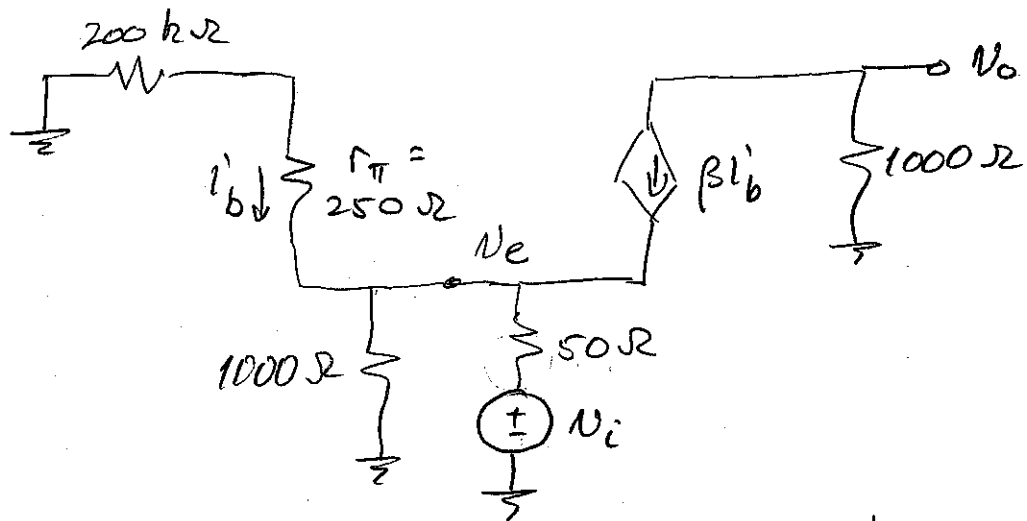So  $r_{\pi} = \frac{V_T}{I_B} \approx 250 \Omega$  so the small signal model is ...



We were asked for  $V_o/V_i$  in the pass band so we have shorted the capacitor (otherwise the gain is 0 - actually, there is no output).

$r_{\pi}$  is negligible in comparison with  $200 \text{ k}\Omega$ , so ...

$$\frac{V_e}{200 \text{ k}} + \frac{V_e}{1 \text{ k}} + \frac{V_e - V_i}{50} - \beta \left( \frac{-V_e}{200 \text{ k}} \right) = 0$$

$$V_e \left( \frac{1}{200 \text{ k}} + \frac{1}{1 \text{ k}} + \frac{1}{50} + \frac{100}{200 \text{ k}} \right) = \frac{V_i}{50} \Rightarrow \underline{V_e = 0.93 V_i}$$

$$V_o = \beta I_b' \cdot 1 \text{ k} = \frac{\beta V_e}{200 \text{ k}} \cdot 1 \text{ k} = \frac{\beta (0.93 V_i)}{200 \text{ k}} \cdot 1 \text{ k}$$

$$\frac{V_o}{V_i} = \frac{\beta (0.93)}{200 \text{ k}} \cdot 1000 \approx 0.46$$