

Name: _____ (please print)

Signature: _____

ECE 3455
Final Exam
May 6, 2009

Exam duration: 170 minutes

- You may have **two** 8 ½ x 11 in. "crib" sheets, written on both sides. You may have any calculator you choose, but no computers. No other notes or materials will be allowed.
- Show all work necessary to complete the problem on these pages. A solution without the work shown will receive no credit.
- Show units in intermediate and final results, and in figures.
- If your work is sloppy or difficult to follow, points will be subtracted.

This exam has 11 pages, including the cover sheet. Raise your hand if you are missing a page.

1 _____ /35

2 _____ /40

3 _____ /40

4 _____ /45

5 _____ /40

Total _____ /200

1. (35 points) A certain amplifier has a magnitude Bode plot with the following characteristics.

- A double zero at 0;
- a single pole at $\omega = 2,000 \text{ rad/sec}$;
- a single pole at $\omega = 8,000 \text{ rad/sec}$;
- a double pole at $\omega = 30,000 \text{ rad/sec}$;
- a gain of 20 dB at $\omega = 10,000 \text{ rad/sec}$.

- i) Find the transfer function $T(\omega)$.
- ii) On the graph provided on the next page, plot the PHASE Bode plot for this amplifier.

2)

$$T(\omega) = K \cdot \frac{(j\omega)^2}{(2000+j\omega)(8000+j\omega)(30,000+j\omega)^2} + 4$$

We need K : $|T(\omega=10\text{krad/s})| = K \cdot 2,66 \times 10^{-10}$

$$20 \text{ dB} \Rightarrow \left| \frac{V_o}{V_i} \right| = 10 \Rightarrow K = 1,3 \times 10^{10} + 2$$

ii) Plot next page.

$$\omega \rightarrow 0 \Rightarrow \angle T(\omega) \rightarrow 180^\circ$$

$$\omega \rightarrow \infty \Rightarrow \angle T(\omega) \rightarrow -180^\circ$$

Alternative:

$$T(\omega) = K \cdot \frac{(j\omega)^2}{(1+j\omega/2000)(1+j\omega/8000)(1+j\omega/30000)^2}$$

$$K \cdot |T(\omega=10\text{krad/s})| = K \cdot 1,103 \times 10^7 = 10$$


$$\Rightarrow K = 9,07 \times 10^{-7}$$

SCALE: +3 BP +2 ea (6)

SLOPES +2 ea (6)


$\angle T_w$)

UNITS +1
LABELS +1

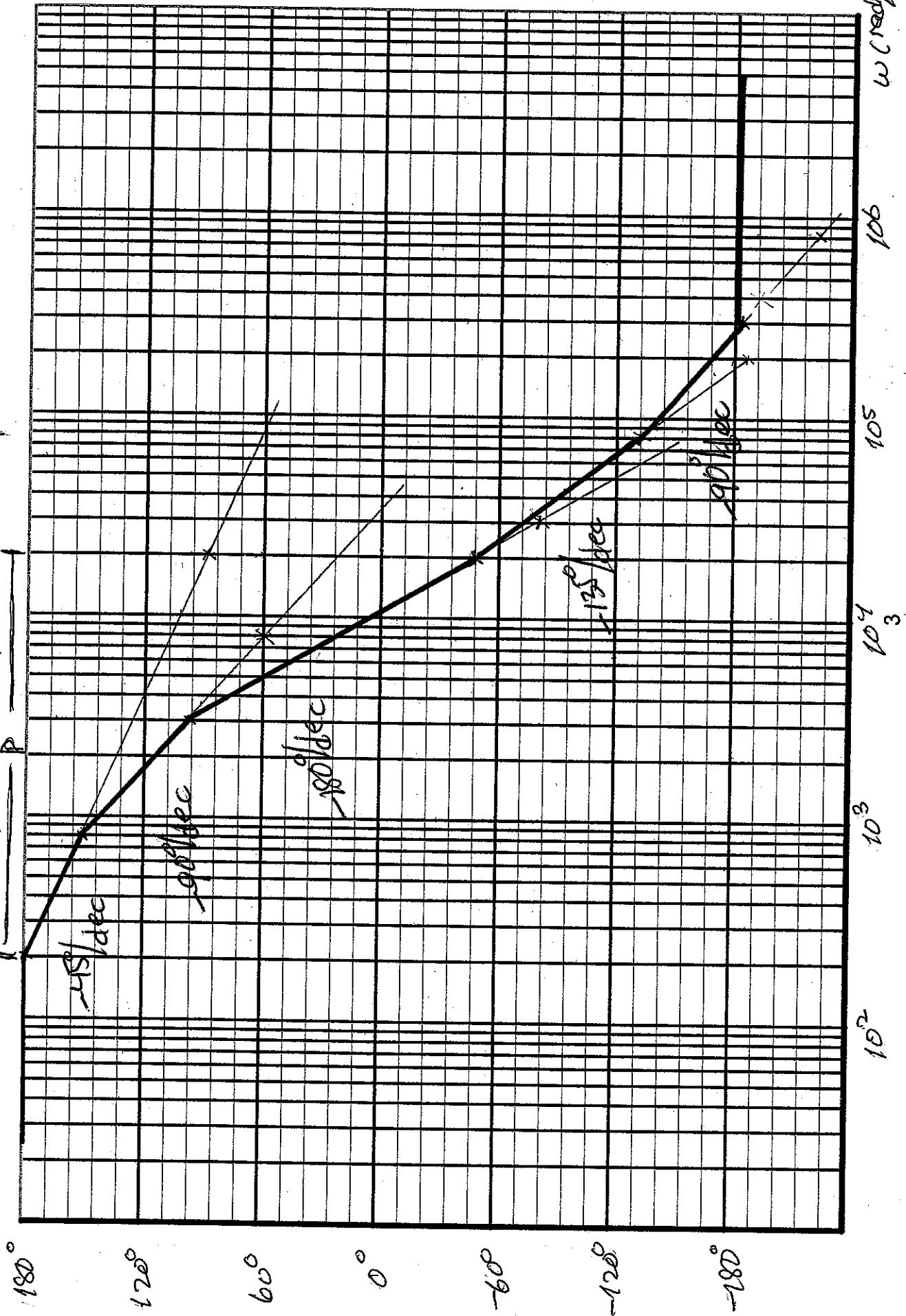

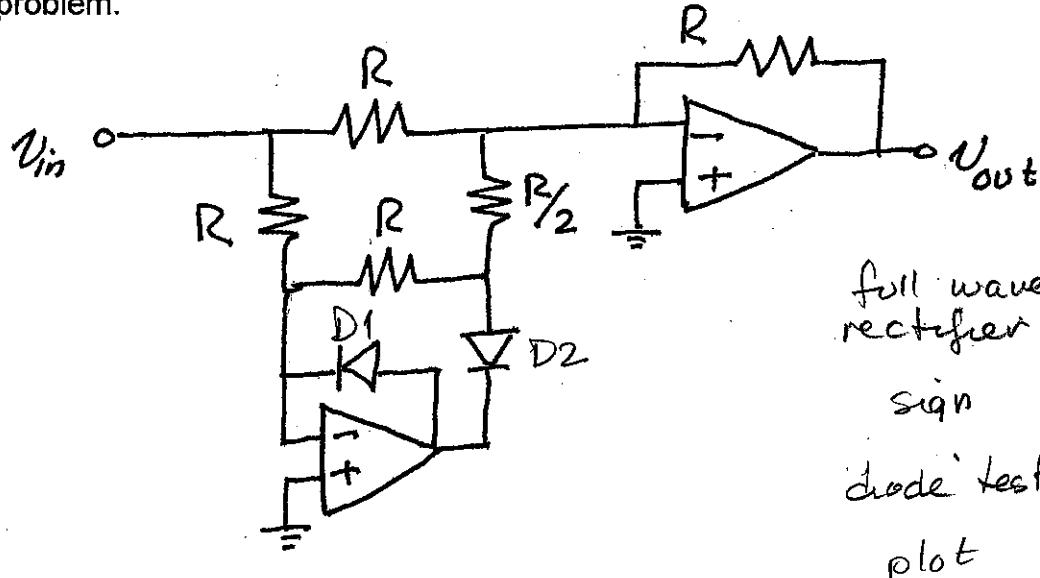
2. (40 points) The op amp in the circuit below may be considered ideal. The diodes are approximated by a constant voltage model with a threshold of 0.7 V. The resistance R is 2.2 k Ω .

~~and period 1 ms~~
 Assuming the input to this circuit is a triangle wave with 0 mean (no dc offset) and an amplitude of 2 V, make a neat sketch of the output V_{out} as a function of time. Show at least two cycles. If your sketch is sloppy or difficult to read, you will not get credit for the problem.



full wave rectifier	+ 24
sign	+ 2
diode tests	+ 8
plot	+ 6

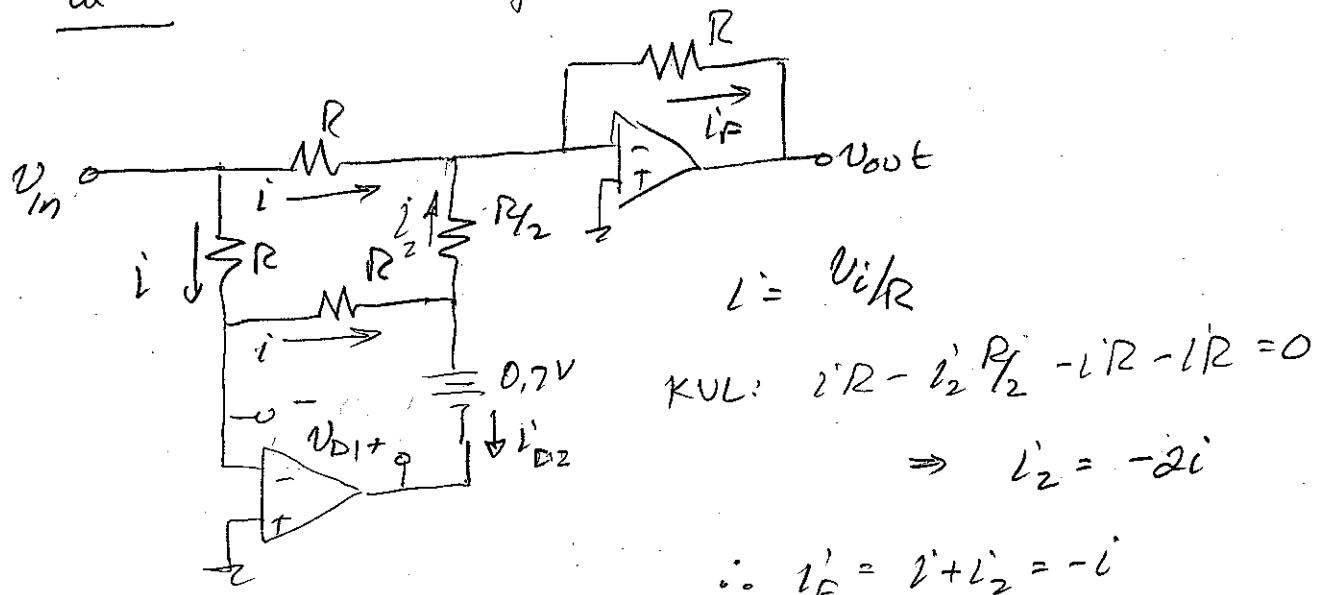For $V_{in} > 0$ we will guess D_2 ON, D_1 OFF, so ...



$$\therefore i'_F = i + i_{D2} = -i$$

TEST:


- $i'_{D2} = i - i_{D2} = 3i > 0 \checkmark$
- $V_{D1} = -2iR - 0.7 \leq -0.7V$
 for $i > 0$, so OK \checkmark

$$V_{out} = -i'_F R = 2iR = V_{in}$$

27

Room for extra work

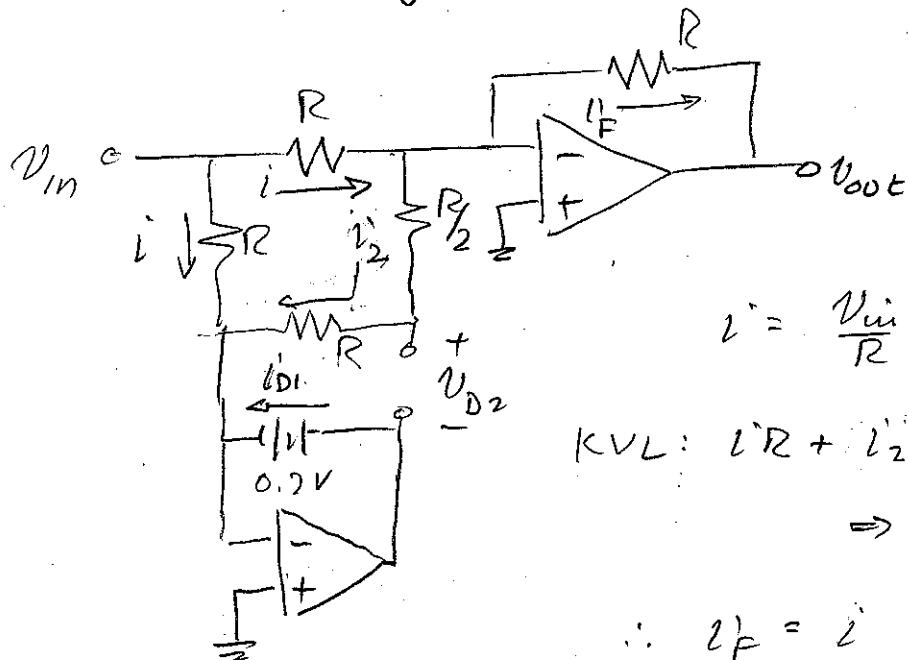$V_{in} < 0$ we will guess D_2 OFF, D_1 ON ..



$$i = \frac{V_{in}}{R} \text{ (negative)}$$

$$\text{KVL: } i'R + i_2 \frac{3R}{2} - i'R = 0$$

$$\Rightarrow i_2 = 0$$

$$\therefore i_F = i$$


$$\Rightarrow \underline{V_{out}} = -iR = -\underline{V_{in}}$$

But V_m is negative, so V_{out} is the absolute value of V_m - it is a full-wave rectified version of V_i !

TEST: $i_{D1} = i^+ + i^- = i$ (negative) ✓

$$V_{D2} = i_2'R - 0.7 = -0.7 \quad \checkmark$$

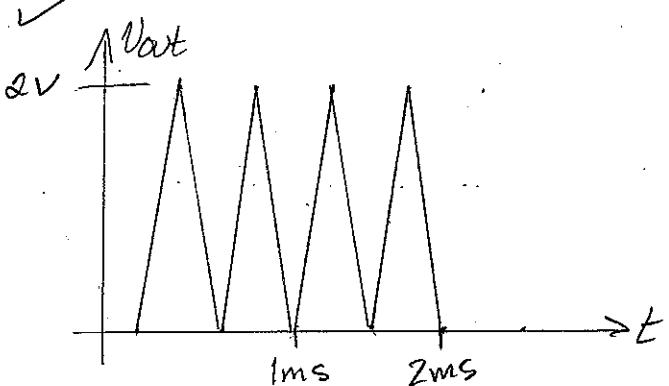There is no diode voltage drop (V_D never enters in to the calculation of V_{out}).




t20
3. (40 points) The op amp in the circuit below is ideal. The circuit is a filter whose type (bandpass, notch, low pass...) we will try to determine.

i) Write a set of equations that could be used to find the transfer function $T(\omega) = V_{out}/V_{in}$ for the circuit. In this step, do not try to solve or simplify the equations. Draw a box around the equations that are part of your solution; equations not in a box will not be counted.

t10
ii) Find an expression for $T(\omega)$; any valid algebraic expression involving only V_{out} and V_{in} (as well as the capacitances and resistances) will do. There is no need to simplify; do not spend time multiplying terms or reducing complex fractions to get your expression into a standard form.

t5
t4
iii) We can guess what is going on with this filter by letting $\omega \rightarrow 0$ and $\omega \rightarrow \infty$. Let ω approach these limits, and for each case (0 and ∞), find $T(\omega)$. At these values of ω , your expression for $T(\omega)$ will simplify dramatically.

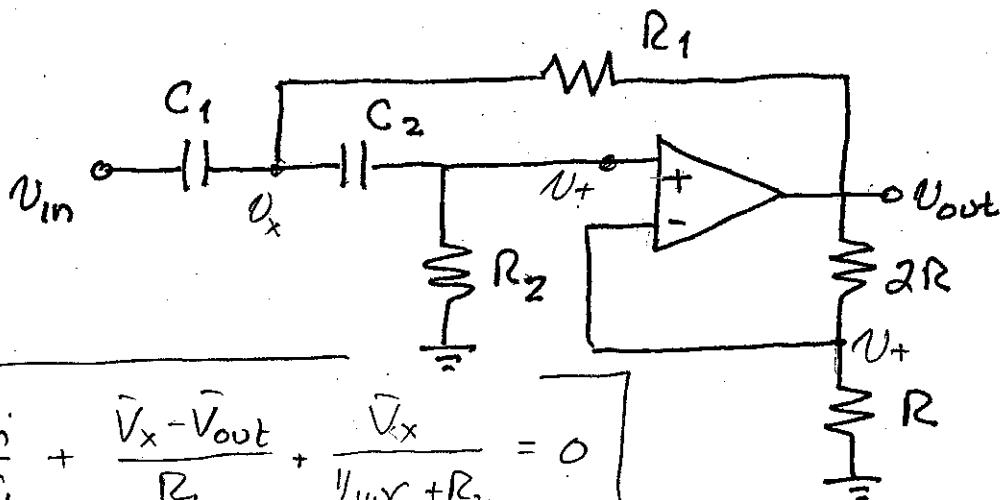x2
iv) Based on iii), what type of filter do you think this is?



$$\frac{\bar{V}_x - \bar{V}_{in}}{1/j\omega G} + \frac{\bar{V}_x - \bar{V}_{out}}{R_1} + \frac{\bar{V}_x}{1/j\omega C_2 + R_2} = 0$$

$$|\bar{V}_+ = \bar{V}_x \cdot \frac{R_2}{R_2 + 1/j\omega C_2}|$$

$$|\bar{V}_+ = \bar{V}_{out} \cdot \frac{R}{R + 2R} = \frac{\bar{V}_{out}}{3}|$$

This is all we need. The second two equations give us \bar{V}_+ in terms of \bar{V}_{out} and hence \bar{V}_x in terms of \bar{V}_{in} using the first equation... *etd*

Room for extra work.

$$ii) \quad \tilde{V}_x = \tilde{V}_+ \cdot \frac{R_2 + 1/j\omega C_2}{R_2} = \tilde{V}_+ \cdot \frac{1 + j\omega C_2 R_2}{j\omega C_2 R_2} = \frac{\tilde{V}_{\text{out}}}{3} \cdot \frac{1 + j\omega C_2 R_2}{j\omega C_2 R_2}$$

From the first equation:

$$\tilde{V}_x (j\omega G + \frac{1}{R_1} + \frac{j\omega C_2}{1 + j\omega C_2 R_2}) - \frac{\tilde{V}_{\text{out}}}{R_1} = j\omega C_1 \tilde{V}_{\text{in}}$$

$$\tilde{V}_{\text{out}} \left[\frac{1}{3} \frac{1 + j\omega C_2 R_2}{j\omega C_2 R_2} \left(\frac{1 + j\omega C_2 R_2}{R_1} + \frac{j\omega C_2}{1 + j\omega C_2 R_2} \right) - \frac{1}{R_1} \right] = j\omega C_1 \tilde{V}_{\text{in}}$$

$$* \quad \frac{\tilde{V}_{\text{out}}}{\tilde{V}_{\text{in}}} = \left[\frac{1}{3} \frac{1 + j\omega C_2 R_2}{j\omega C_2 R_2} \left(\frac{1 + j\omega C_2 R_2}{R_1} + \frac{j\omega C_2}{1 + j\omega C_2 R_2} \right) - \frac{1}{R_1} \right]^{-1} \cdot j\omega C_1$$

This satisfies the requirements of ii).

iii) For $\omega \rightarrow \infty$, we have

$$\begin{aligned} \frac{\tilde{V}_{\text{out}}}{\tilde{V}_{\text{in}}} &\approx \left[\frac{1}{3} \cdot 1 \cdot (j\omega G + 1) - \frac{1}{R_1} \right]^{-1} \cdot j\omega G \\ &\approx \left[\frac{1}{3} \cdot j\omega C_1 \right]^{-1} \cdot j\omega G = 3. \end{aligned}$$

$(\frac{1}{R_1} \text{ and } 1 \text{ are small compared to } j\omega G \text{ at } \omega \rightarrow \infty)$


For $\omega \rightarrow 0$, we have

$$\frac{\tilde{V}_{\text{out}}}{\tilde{V}_{\text{in}}} \approx \left[\frac{1}{3} \cdot \frac{1}{j\omega C_2 R_2} \cdot \left(\frac{1}{R_1} + 0 \right) - \frac{1}{R_1} \right]^{-1} \cdot j\omega G \rightarrow 0$$

iv) HIGH PASS FILTER!

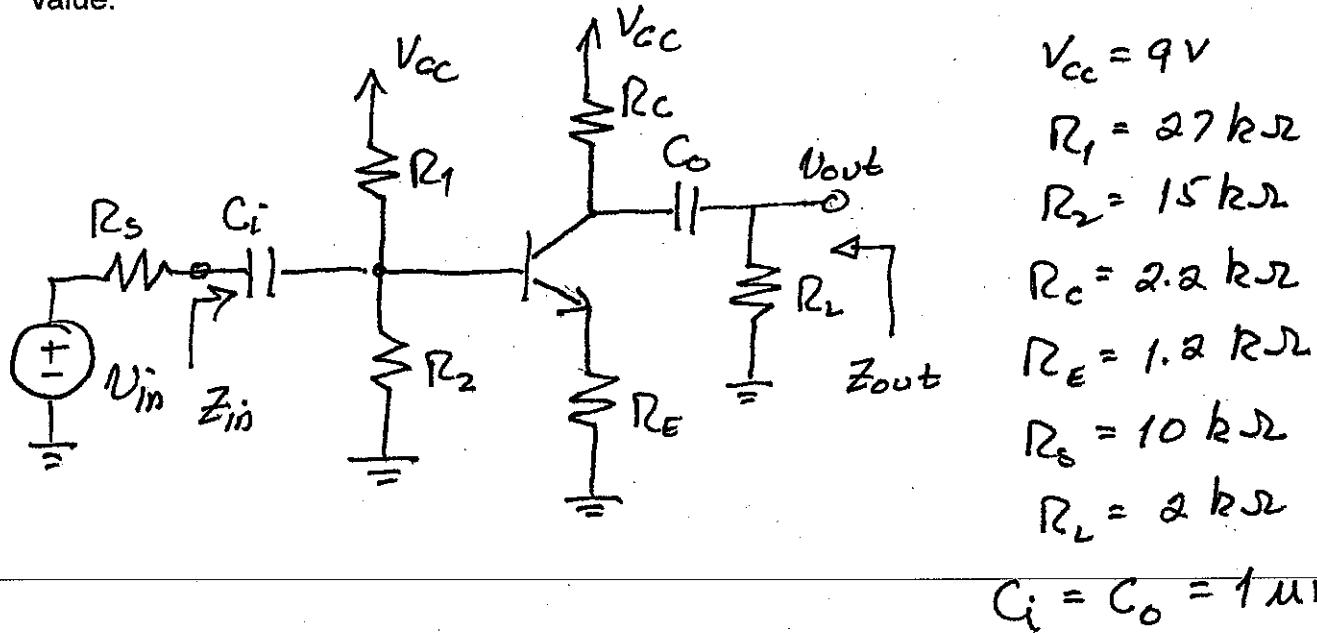
4. (45 points) The BJT in the circuit below has $\beta = 100$ and $V_{CE,SAT} = 0.2$ V. It is biased in the linear region; there is no need to prove this is the case.

- Find the input impedance Z_{in} . Express the result symbolically; do not substitute component values.
- Find the output impedance Z_{out} . Express the result symbolically; do not substitute component values.
- Find the voltage gain v_{out}/v_{in} in the pass band. For the gain, provide a numerical value.




We will look at the dc case because we need r_T or r_E :

$$V_{BB} = V_{cc} \cdot \frac{R_2}{R_1 + R_2} = 3.21 \text{ V} \quad R_{BB} = R_1 \| R_2 = 9.64 \text{ k}\Omega$$

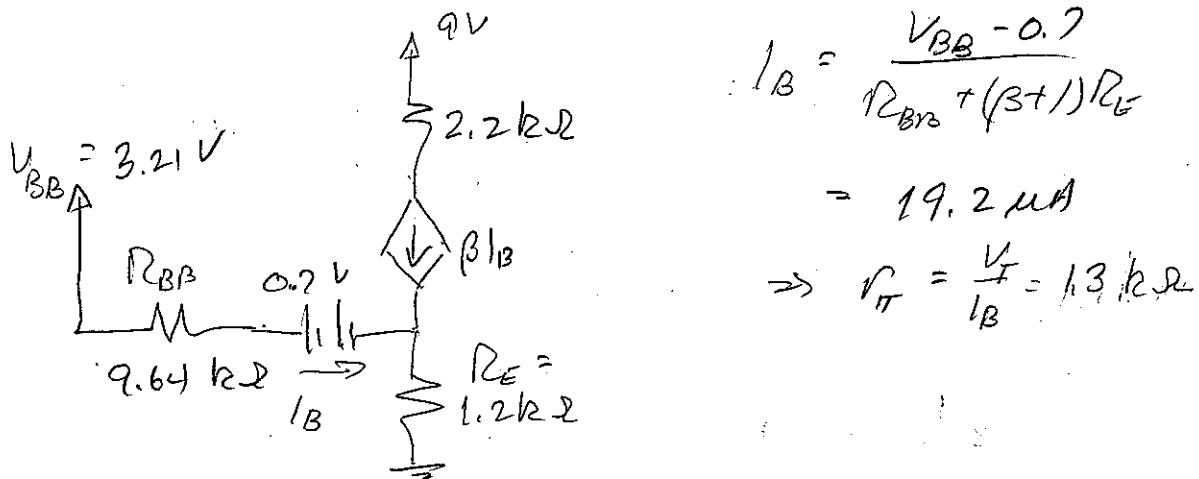

Room for extra work.

ac model:

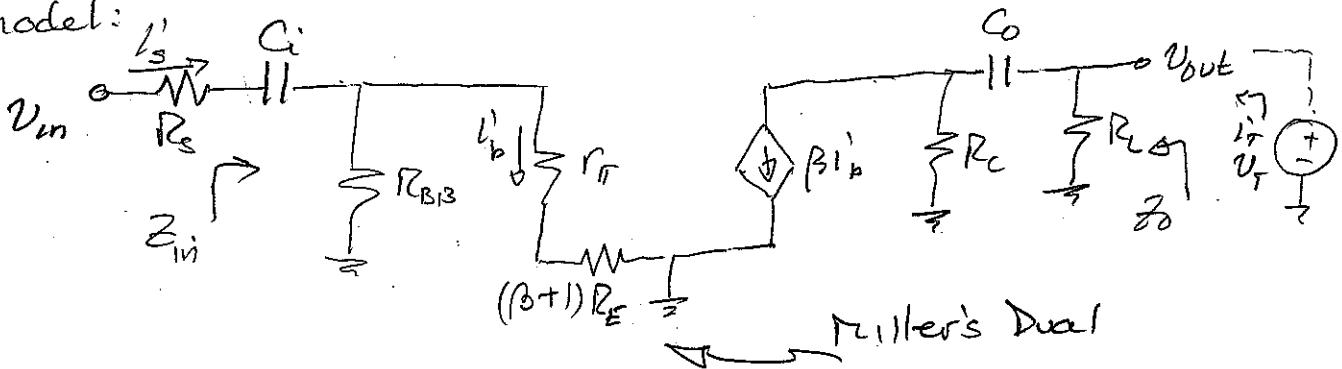

+15

Z_0 : with source attached and de-activated (after applying a test source at the output), we have

$$+6 \quad Z_0 = \frac{V_T}{I_T} = R_L \parallel (\frac{1}{j\omega C_0} + R_c) = \frac{j\omega C_0 R_L R_c + R_L}{1 + j\omega C_0 (R_L + R_c)}$$

$$Z_i^-: Z_{i^-} = \frac{1}{j\omega C_i} + R_{BB} \parallel (r_\pi + (\beta + 1)R_E)$$

$$x6 \quad (r_\pi = 1.3 \text{ k}\Omega; (\beta + 1)R_E = 121 \text{ k}\Omega \Rightarrow r_\pi + (\beta + 1)R_E \approx (\beta + 1)R_E)$$

In the passband, both C_i and $C_o \rightarrow$ short, so...

$$1.058 \text{ k}\Omega \quad V_{out} = -\beta I_b \cdot (R_L \parallel R_c) \quad I_s^1 = \frac{V_{in}}{R_s + R_{BB} \parallel (r_\pi + (\beta + 1)R_E)}$$

+16

$$I_b^1 = I_s^1 \cdot \frac{R_{BB}}{R_{BB} + (r_\pi + (\beta + 1)R_E)}$$


Taking $r_\pi \ll (\beta + 1)R_E$ we get

$$\frac{V_{out}}{V_{in}} = - \frac{\beta R_L \parallel R_c}{R_{BB} + (\beta + 1)R_E} \cdot \frac{R_{BB}}{R_s + R_{BB} \parallel (\beta + 1)R_E} = - \frac{1.058 \times 10^5}{1.308 \times 10^5} \cdot \frac{9.64 \times 10^3}{1.89 \times 10^4}$$

$$R_{BB} \parallel (\beta + 1)R_E = 8.93 \text{ k}\Omega$$

$$9 \quad \boxed{\frac{V_{out}}{V_{in}} = -0.414}$$

#4 w/ T-model

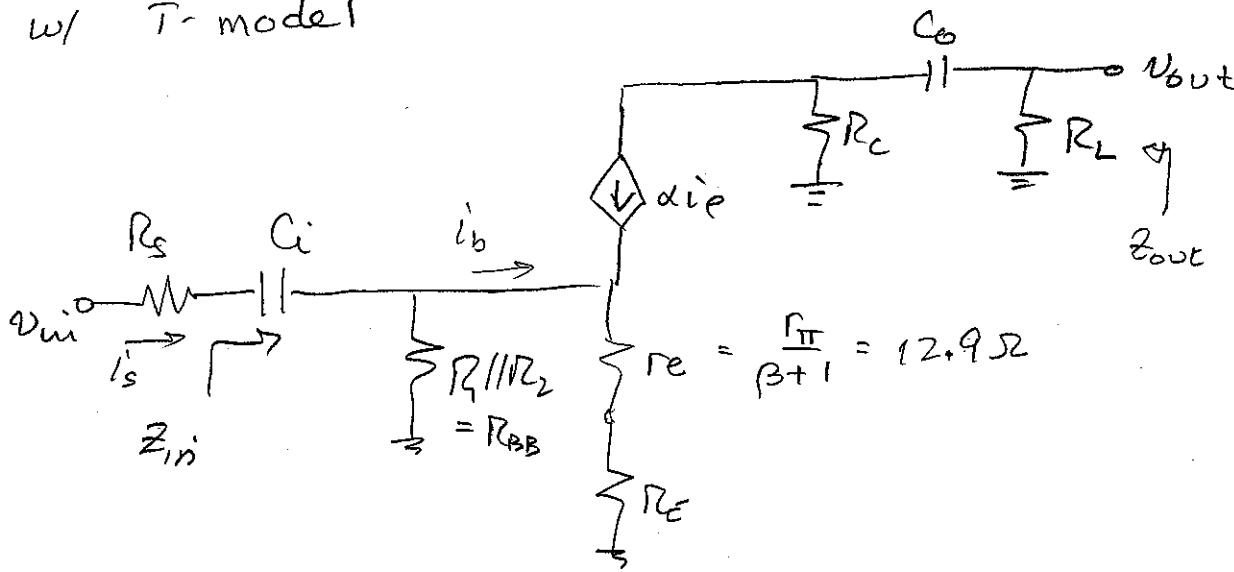

$$Z_{in} = \frac{1}{j\omega C_i} + (R_{BB} + (\beta+1)(r_e + R_E))$$


$$Z_{out} = R_c // (R_E + \frac{1}{j\omega C_o})$$

$$V_{out} = -\alpha i_e \cdot R_c // R_L = -(\beta+1) i_b (R_c // R_L)$$

$$i_s = \frac{v_{in}}{R_s + R_{BB} // (\beta+1)(r_e + R_E)} \quad i_b = i_s \cdot \frac{R_{BB}}{R_{BB} + (\beta+1)(r_e + R_E)}$$

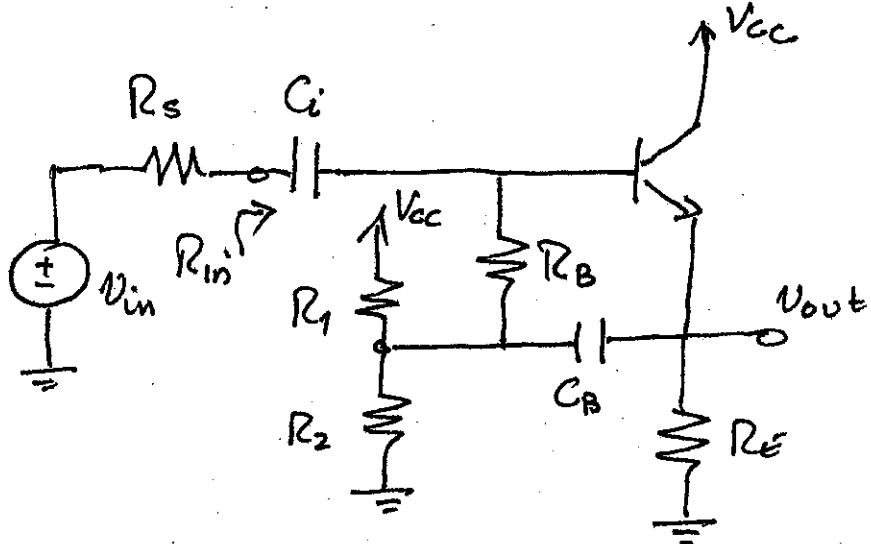
5. (40 points) The BJT in the circuit below has $\beta = 100$ and $V_{CE,SAT} = 0.2$ V. It is biased in the linear region; there is no need to prove this is the case. The configuration shown is called a bootstrap follower: the addition of the capacitor allows for a trade-off between input resistance and voltage gain, which we will explore.

- With the capacitor C_B in place, find the input resistance R_{in} and the voltage gain V_{out}/V_{in} .
- With the capacitor removed, again find R_{in} and V_{out}/V_{in} .
- Explain what is gained or lost by adding the capacitor C_B .



$$\begin{aligned}
 V_{CC} &= 9 \text{ V} \\
 R_1 &= R_2 = 20 \text{ k}\Omega \\
 R_B &= 10 \text{ k}\Omega \\
 C_i &= \infty \\
 C_B &= \infty \\
 R_s &= 10 \text{ k}\Omega \\
 R_E &= 2 \text{ k}\Omega
 \end{aligned}$$

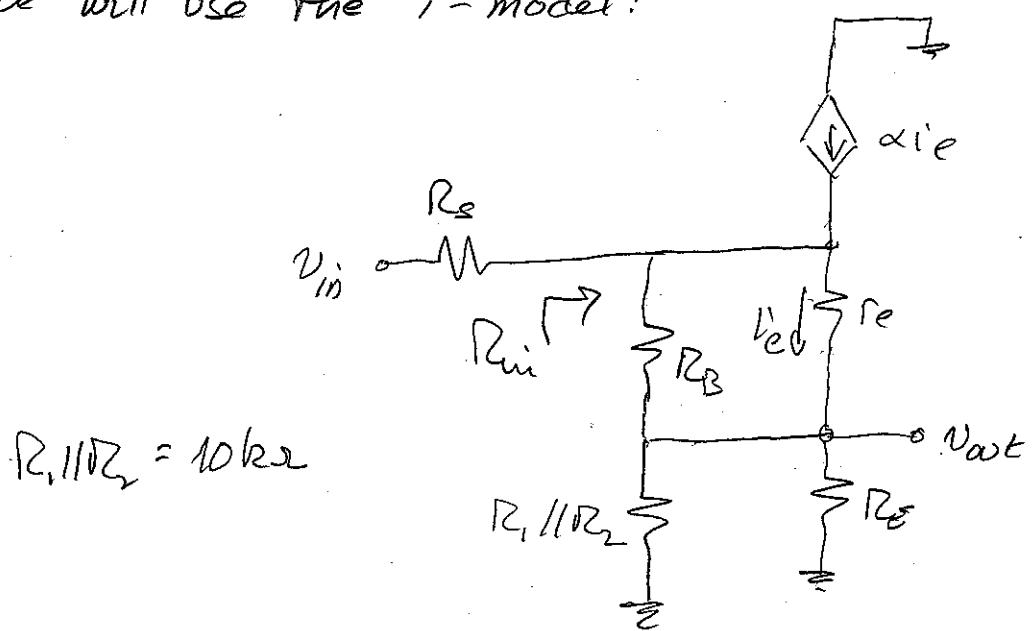Since the capacitors are large (∞ !) they are short:
we will use the T-model:



$$R_1/R_2 = 10 \text{ k}\Omega$$

We need r_E :

Room for extra work.

$$V_{BB} = 9, \frac{R_2}{R_1 + R_2} = 4.5 \text{ V}$$

$$R_{BB} = R_1 // R_2 = 10 \text{ k}\Omega$$

With both capacitors open, we have:


$$I_B = \frac{9 - 0,7}{10k + 10k + (\beta+1)R_E} = 12,1 \mu\text{A}$$

$$R_1/R_2 = 10 \text{ k}\Omega \quad R_B = 10 \text{ k}\Omega$$

$$I_B = 12,1 \mu\text{A}$$


$$I_E = (\beta+1)I_B = 1,23 \text{ mA}$$
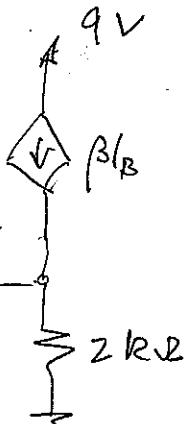
$$x^2 \Rightarrow r_e = \frac{V_T}{I_E} = 14,5 \text{ }\Omega$$



Now we can simplify the ac circuit:
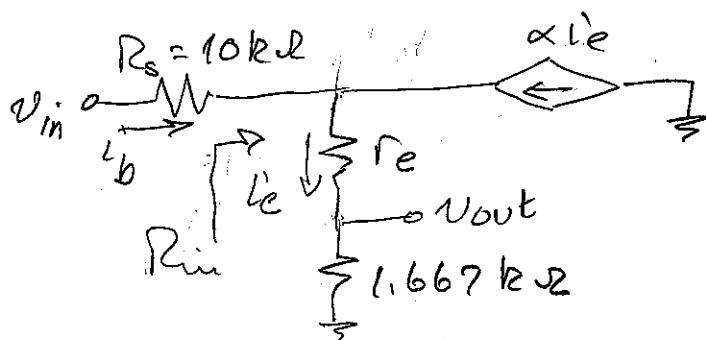
$$R_B // r_e \approx r_e \quad (R_1 // R_2) // R_E = 1,667 \text{ k}\Omega$$




$$R_{in} = \frac{i_e(r_e + 1,667 \text{ k}\Omega)}{i_b} = (\beta+1)(r_e + 1,667 \text{ k}\Omega) \approx 169,8 \text{ k}\Omega$$

$$V_{out} = i_e(1,667 \text{ k}\Omega) \quad V_{in} = i_b(R_s + (\beta+1)(r_e + 1,667 \text{ k}\Omega))$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{(\beta+1)i_b \cdot (1,667 \text{ k}\Omega)}{i_b \cdot (R_s + (\beta+1) \cdot (r_e + 1,667 \text{ k}\Omega))} = 0,936$$

If we remove the capacitor:

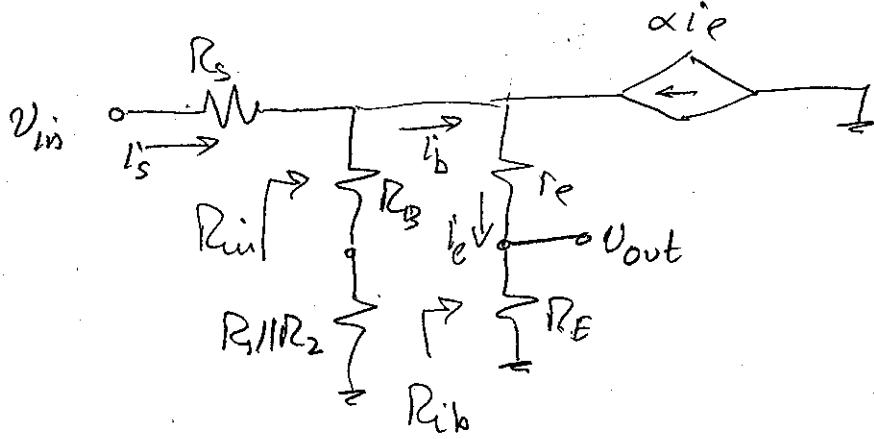

$$\left. \begin{array}{l} R_{ib} = (\beta + 1)(r_e + R_E) \\ = 203.5 \text{ k}\Omega \end{array} \right| \quad \left. \begin{array}{l} R_{in} = (R_B + R_1 || R_2) || R_{ib} \\ = 20 \text{ k}\Omega || 203.5 \text{ k}\Omega = 18.2 \text{ k}\Omega \end{array} \right.$$

$$i_s = \frac{V_{in}}{R_s + R_{in}} = \frac{V_{in}}{28.2 \text{ k}\Omega} \quad i_b = \frac{V_{in}}{28.2 \text{ k}\Omega} \cdot \frac{10k + 10k}{10k + 10k + R_{ib}}$$

$$= V_{in} \cdot 3.173 \times 10^{-6}$$

$$V_{out} = (\beta + 1) i_b \cdot R_E = 2 \cdot 0.3 \times 10^5 i_b = 0.644 V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = 0.644$$

iii) The input resistance has increased from 18 kΩ to 170 kΩ when the capacitor is in place, but the voltage gain has dropped from 0.94 to 0.64.