

Name: \_\_\_\_\_ (please print)

Signature: \_\_\_\_\_

**ECE 3355 – Exam #2 ONLINE**  
**April 18, 2020**

1. This exam is open book, open notes. Please turn on your video feed during the exam.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit.
3. Show all units in solutions, intermediate results, and figures.
4. If the grader has difficulty following your work because it is messy or disorganized, you will lose credit.
5. Do not use red ink. Do not use red pencil.
6. You will have 90 minutes to work on this exam, and an additional 15 minutes to scan and upload to Blackboard. You must STOP work when time is called. You MAY NOT use the 15 minutes scan time to continue work.

Choose three of these problems to work on, and indicate by circling the problem numbers which ones you want me to grade. No additional credit will be given for working on a fourth problem.

1. \_\_\_\_\_ /33 1/3

2. \_\_\_\_\_ /33 1/3

3. \_\_\_\_\_ /33 1/3


4. \_\_\_\_\_ /33 1/3

\_\_\_\_\_ /100

Room for extra work

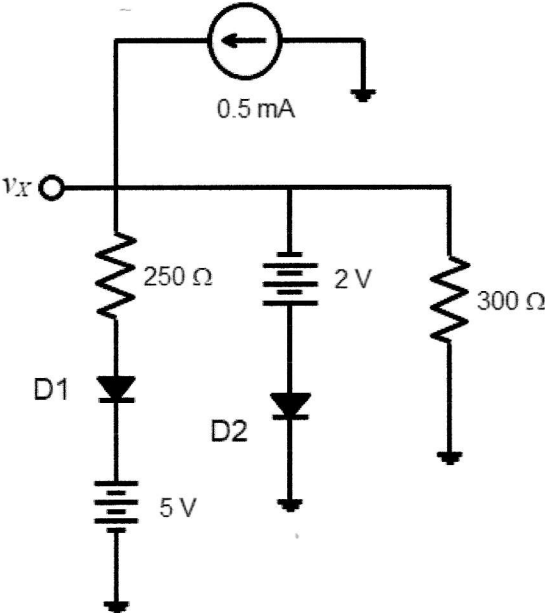1. (33 1/3 points) In the circuit below, the diodes are modeled using a piece-wise continuous model with  $V_{th} = 1.5 \text{ V}$ ,  $r_D = 100 \ \Omega$ , and  $I_S = 2 \text{ mA}$ .


Find  $v_x$ . Be sure that any guesses you make as to the state of the diodes are tested. Even if your guess is wrong, you will get credit for proving it is wrong.



Room for extra work

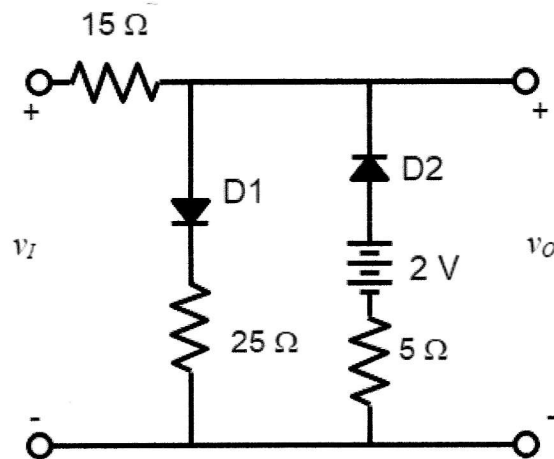2. (33 1/3 points) For the circuit below, the diodes are modeled using a piece-wise linear model with  $V_{th} = 1.0\text{ V}$ ,  $r_D = 5\ \Omega$ , and  $I_S = 0$ .


Find  $v_O$  for  $v_I = 0\text{ V}$ ,  $2\text{ V}$ , and  $4\text{ V}$ . Be sure to prove that your diodes are in the state you assume them to be in.



Room for extra work

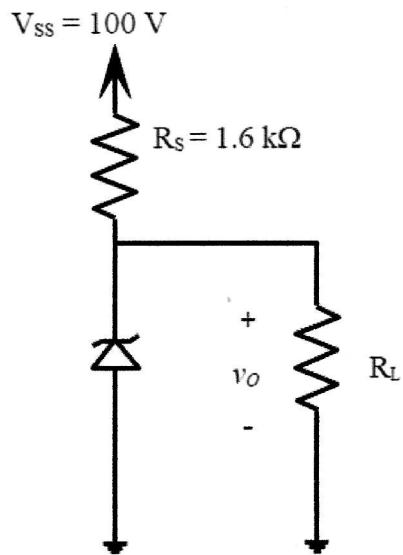3. (33 1/3 points) A 20 V Zener diode is connected into the circuit below. In the breakdown region, the diode is rated at a resistance  $r_Z = 30 \Omega$  at a current of 50 mA. The Zener is intended to provide a constant output voltage  $v_O$  of approximately 20 V to the load  $R_L$ .

- Find the model voltage  $V_{Z0}$  for this Zener diode.
- Using the value of  $V_{Z0}$  you just calculated, and  $r_Z$  as given, find the output voltage  $v_O$  for a load resistance  $R_L = 500 \Omega$ .
- If the power supply  $V_{SS}$  can vary to as high as 110 V and as low as 95 V, *use the small signal diode model* to find the corresponding variation in the load voltage.
- Repeat part c) for a load resistance  $R_L = 10 \text{ k}\Omega$ .




Room for extra work



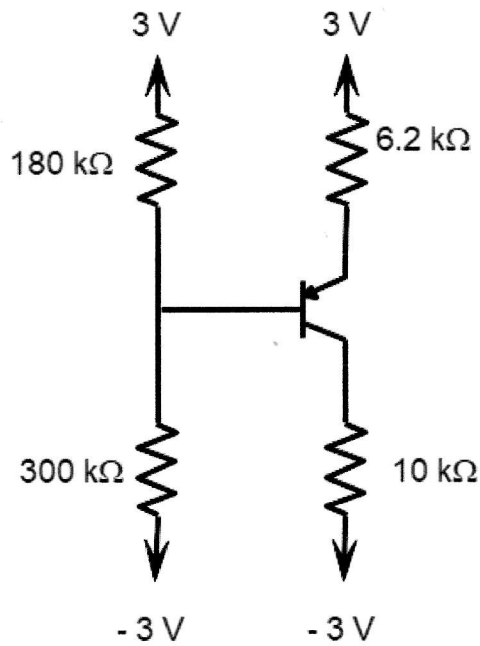4. (33 1/3 points) For the BJT below, the rated value of  $\beta$  is  $\beta = 100$ , and  $V_{CESAT} = 0.4 \text{ V}$ . The BJT is biased in the linear region.

- Find the BJT terminal voltages  $V_B$ ,  $V_E$ ,  $V_C$ . These are not labeled on the diagram since you should know what they are! Be sure to conduct the tests necessary to prove that the BJT is in the linear region.
- Suppose that in actual transistors,  $\beta$  can be larger than the rated value. Is it possible that in this circuit, a higher value of  $\beta$  will cause the BJT to be biased into a different region than you found in part a)? If so, what is the smallest value of  $\beta$  that will cause this to happen?



Name: \_\_\_\_\_ (please print)  
Signature: SOLUTIONS 6

**ECE 3355 – Exam #2 ONLINE**  
**April 18, 2020**

1. This exam is open book, open notes. Please turn on your video feed during the exam.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit.
3. Show all units in solutions, intermediate results, and figures.
4. If the grader has difficulty following your work because it is messy or disorganized, you will lose credit.
5. Do not use red ink. Do not use red pencil.
6. You will have 90 minutes to work on this exam, and an additional 15 minutes to scan and upload to Blackboard. You must STOP work when time is called. You MAY NOT use the 15 minutes scan time to continue work.

Choose three of these problems to work on, and indicate by circling the problem numbers which ones you want me to grade. No additional credit will be given for working on a fourth problem.

1. \_\_\_\_\_ /33 1/3

2. \_\_\_\_\_ /33 1/3


3. \_\_\_\_\_ /33 1/3

4. \_\_\_\_\_ /33 1/3


\_\_\_\_\_ /100

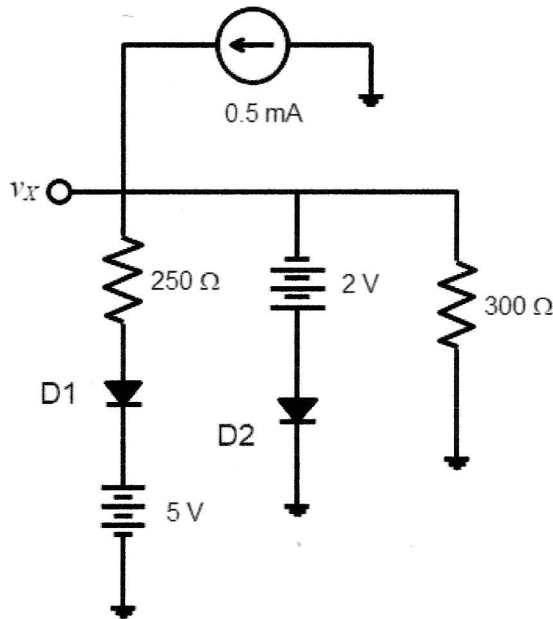1. (33 1/3 points) In the circuit below, the diodes are modeled using a piece-wise continuous model with  $V_{th} = 1.5 \text{ V}$ ,  $r_D = 100 \Omega$ , and  $I_S = 2 \text{ mA}$ .

Find  $v_x$ . Be sure that any guesses you make as to the state of the diodes are tested. Even if your guess is wrong, you will get credit for proving it is wrong.



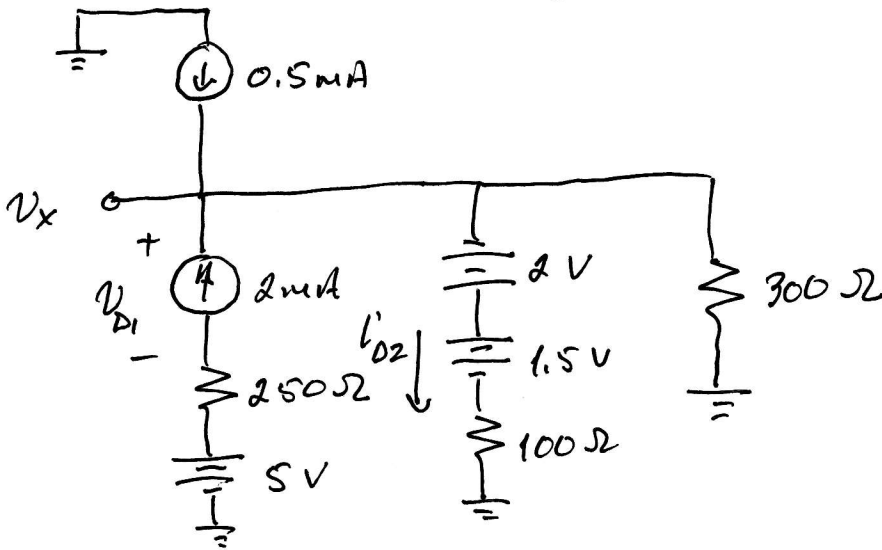The 2 V source will act to turn D2 ON. The 5 V source will act to turn D1 OFF. Assume D2 region 4 (full bias), D1 OFF (reverse bias).



Prove:

$$v_{D1} < 0$$

$$i'_{D2} > 0$$



Room for extra work

$$\frac{V_x + 2 - 1.5}{100} + \frac{V_x}{300} - 0.0025 = 0 \Rightarrow V_x = -0.1875 \text{ V}$$


$$D1: -5 + 0.002(250) - V_{D1} + V_x = 0 \Rightarrow V_{D1} = -4.6875 \text{ V} \checkmark$$

$$D2: i_{D2}' = \frac{V_x + 2 - 1.5}{100} = 3.125 \text{ mA} \checkmark$$

So the guesses were correct, and  $V_x = -0.1875 \text{ V}$

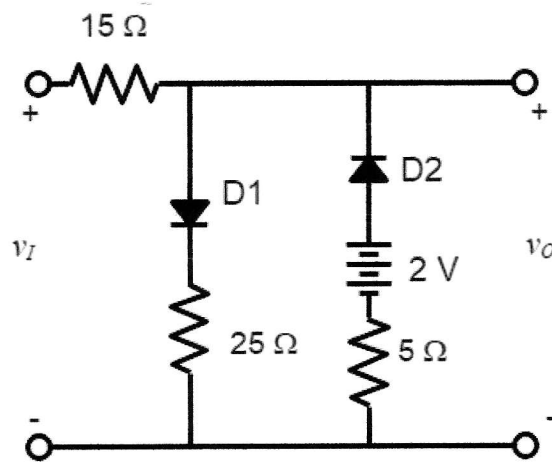2. (33 1/3 points) For the circuit below, the diodes are modeled using a piece-wise linear model with  $V_{th} = 1.0\text{ V}$ ,  $r_D = 5\ \Omega$ , and  $I_S = 0$ .


Find  $v_O$  for  $v_I = 0\text{ V}$ ,  $2\text{ V}$ , and  $4\text{ V}$ . Be sure to prove that your diodes are in the state you assume them to be in.



This problem is essentially a transfer characteristics problem, but a plot of  $v_O$  vs.  $v_I$  is not asked for.

The 2V source will act to turn D2 ON. But if  $v_I$  gets large enough, it will turn off.

$v_I = 0$  Assume D1 OFF, D2 ON

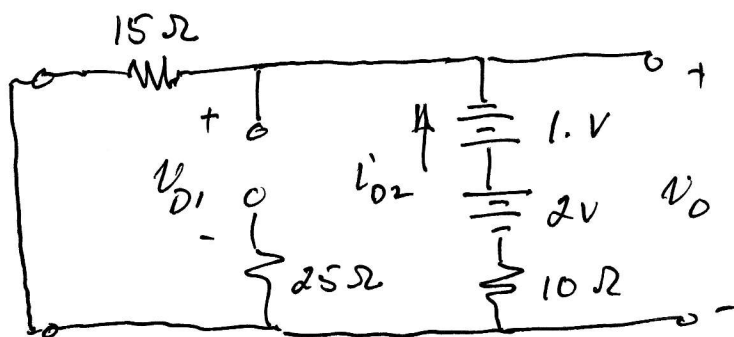

$$\frac{v_O}{15} + \frac{v_O - 2 + 1}{10} = 0$$

$$\Rightarrow v_O = 0.6\text{ V}$$

$$v_{D1} = v_O = 0.6\text{ V} \checkmark$$


$$i_{D2} = - \frac{v_O - 2 + 1}{10} = 40\text{ mA} \checkmark$$

Prove:  $i_{D2} > 0$

$$v_{D1} < 1.0\text{ V}$$

Room for extra work

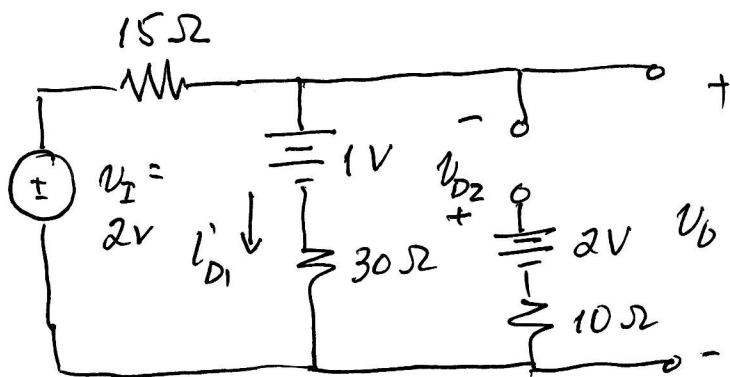$V_I = 2V$  We will guess that 2V is enough to turn D1 ON, and that it's enough to turn D2 OFF.



Prove:

$$i_{D1} > 0$$

$$V_{D2} < 1V$$

$$-2 + i_{D1} \cdot 45 + 1 = 0 \Rightarrow i_{D1} = \frac{1}{45} A \quad \checkmark$$

$$V_o = 1.667 V$$

$$V_o = 1 + 30i_{D1} = 1 \frac{2}{3} V$$

$$V_o - 2 + V_{D2} = 0 \Rightarrow V_{D2} = 2 - V_o = \frac{1}{3} V \quad \checkmark$$

$V_I = 4V$  This will leave both diodes in the same region, but  $V_o$  will change.

$$-4 + 2i_{D1} \cdot 45 + 1 = 0 \Rightarrow i_{D1} = \frac{3}{45} A \quad \checkmark$$



$$V_o = 3V$$

$$V_o = 1 + 30i_{D1} = 3V$$

$$V_o - 2 + V_{D2} = 0 \Rightarrow V_{D2} = 2 - V_o = -1V \quad \checkmark$$

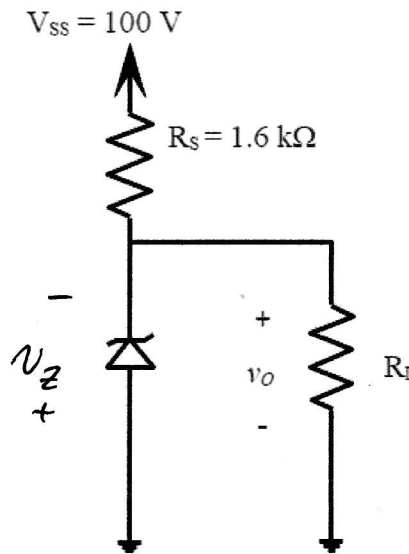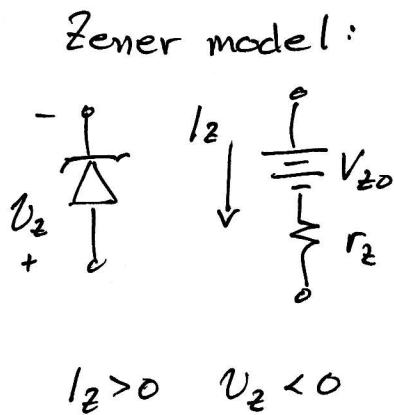3. (33 1/3 points) A 20 V Zener diode is connected into the circuit below. In the breakdown region, the diode is rated at a resistance  $r_Z = 30 \Omega$  at a current of 50 mA. The Zener is intended to provide a constant output voltage  $v_O$  of approximately 20 V to the load  $R_L$ .

- Find the model voltage  $V_{Z0}$  for this Zener diode.
- Using the value of  $V_{Z0}$  you just calculated, and  $r_Z$  as given, find the output voltage  $v_O$  for a load voltage  $R_L = 500 \Omega$ .
- If the power supply  $V_{SS}$  can vary to as high as 110 V and as low as 95 V, *use the small signal diode model* to find the corresponding variation in the load voltage.
- Repeat part c) for a load resistance  $R_L = 10 \text{ k}\Omega$ .




$$V_Z = 20 \text{ V}$$

$$V_{Z0} + I_Z r_Z = 20 \text{ V}$$

$$\Rightarrow V_{Z0} = 18.5 \text{ V}$$

at  $I_Z = 50 \text{ mA}$

a)  $V_{Z0} = 18.5 \text{ V}$

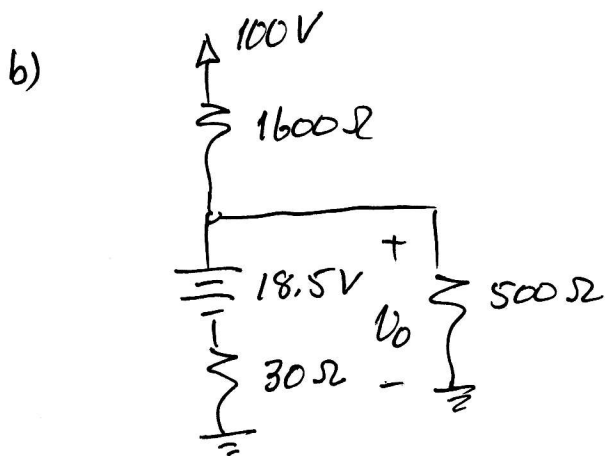


$$\frac{v_O}{500} + \frac{v_O - 100}{1600} + \frac{v_O - 18.5}{30} = 0$$

$$v_O = 18.89 \text{ V}$$



Room for extra work

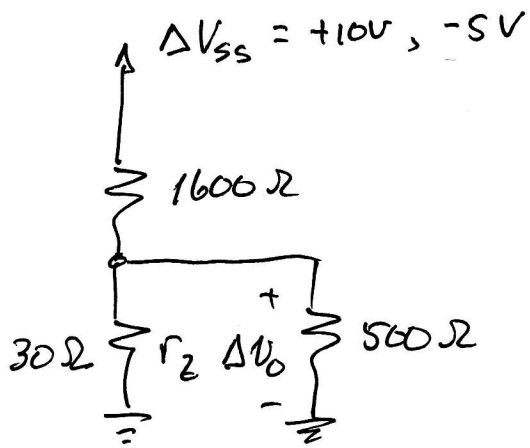c) Small signal model  $\Rightarrow$  deactivate DC components.



$$\Delta V_D = \Delta V_{SS} \frac{500 \parallel 30}{500 \parallel 30 + 1600}$$

$$\Delta V_D^+ = 10V \cdot \frac{28.3}{28.3 + 1600} = 0.1738V$$

$$\Delta V_D^- = 5V \cdot \frac{28.3}{28.3 + 1600} = 0.0869V$$

d) For  $R_L = 10k\Omega$ ,  $10k\Omega \parallel 30 = 29.91 \Omega$

$$\Delta V_D^+ = 10 \frac{29.91}{29.91 + 10000} = 29.82 \text{ mV}$$

$$\Delta V_D^- = 5 \frac{29.91}{29.91 + 10000} = 14.91 \text{ mV}$$




4. (33 1/3 points) For the BJT below, the rated value of  $\beta$  is  $\beta = 100$ , and  $V_{CESAT} = 0.4$  V. The BJT is biased in the linear region.

- Find the BJT terminal voltages  $V_B$ ,  $V_E$ ,  $V_C$ . These are not labeled on the diagram since you should know what they are! Be sure to conduct the tests necessary to prove that the BJT is in the linear region.
- Suppose that in actual transistors,  $\beta$  can be larger than the rated value. Is it possible that in this circuit, a higher value of  $\beta$  will cause the BJT to be biased into a different region than you found in part a)? If so, what is the smallest value of  $\beta$  that will cause this to happen?

The pnp linear region model is shown below. We need to prove:

$$I_B > 0$$


$$V_{CE} < -0.4 \text{ V}$$

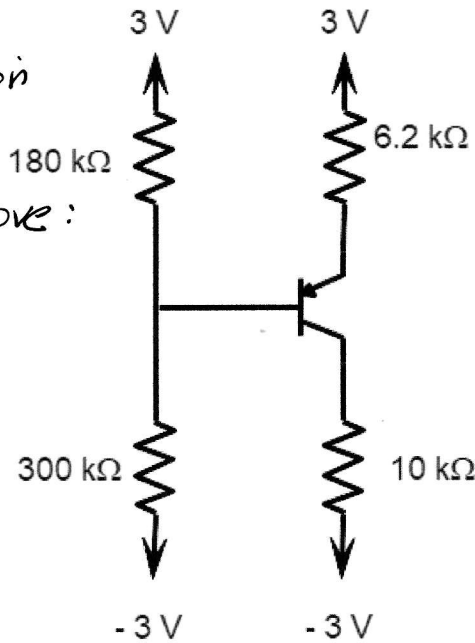

Thevenize the base:

$$V_{BB} = 3 \cdot \frac{300}{300 + 180} - 3 = 0.75 \text{ V}$$
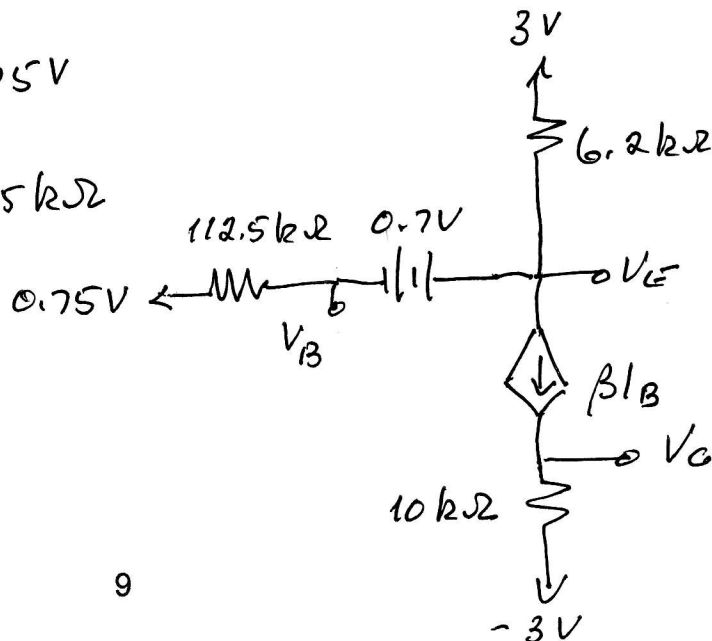
$$R_B = 300 \text{ k}\Omega // 180 \text{ k}\Omega = 112.5 \text{ k}\Omega$$



Room for extra work

$$I_E = (\beta + 1) I_B$$

KVL

$$-3 + 6200(101)I_B + 0.7 + 112.5 \times 10^3 I_B = 0$$

$$\Rightarrow I_B = 2.0983 \mu\text{A} \checkmark$$

$$V_C = 100 I_B (10000) - 3 = -0.9017 \text{ V}$$

$$V_E = 3 - 101 I_B (6200) = 1.689 \text{ V}$$

$$V_{CE} = -0.9017 - 1.689 = -2.591 \text{ V} \checkmark$$

$$V_B = 112.5 \times 10^3 I_B + 0.75 = 0.9861 \text{ V}$$

b) If  $\beta$  increases, we expect a larger  $V_C$  and smaller  $V_E$ , and at some point,  $V_{CE}$  will no longer be less than  $-0.4 \text{ V}$ . Let's see where that point is: set  $V_{CE} = -0.4 \text{ V}$

$$V_{CE} = (\beta I_B (10000) - 3) - (3 - 6200(\beta + 1)I_B) = -0.4$$

Since  $\beta + 1 \approx \beta$ , we can make that approximation and solve for  $\beta$ :

$$\beta I_B (10000 + 6200) = 6 - 0.4 \Rightarrow \beta = 158.9$$

This would be a very large deviation ( $\approx 60\%$ )! But if it happened, the BJT would be in saturation.