

Name: _____ (please print)

Signature: _____

ECE 3355 – Exam #1
February 22, 2020

**Keep this exam closed and face up
until you are told to begin.**

1. This exam is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution which is not given in a reasonable order will lose credit.
3. Show all units in solutions, intermediate results, and figures.
4. If the grader has difficulty following your work because it is messy or disorganized, you will lose credit.
5. Do not use red ink. Do not use red pencil.
6. You will have 90 minutes to work on this exam.

_____ /35

_____ /30



_____ /35

_____ /100

Room for extra work

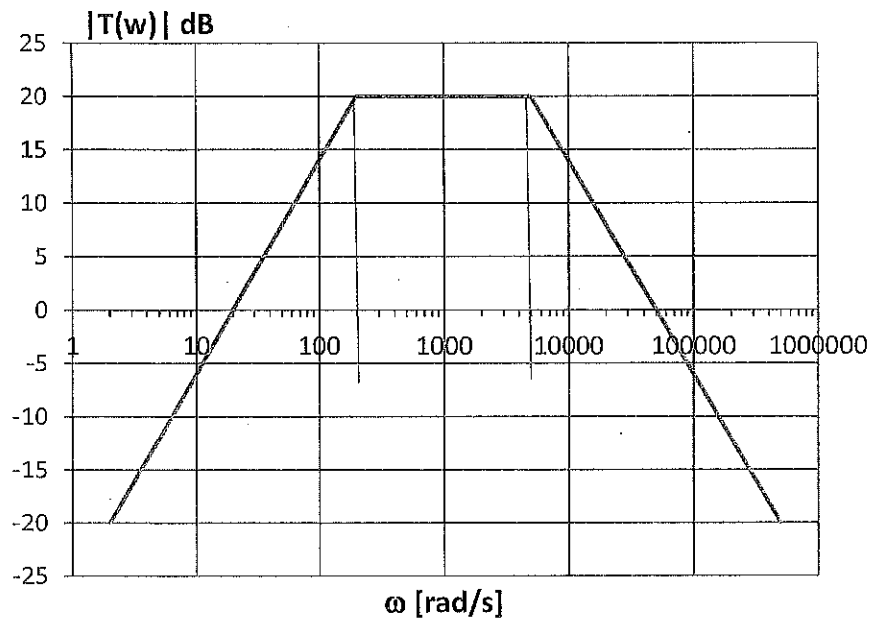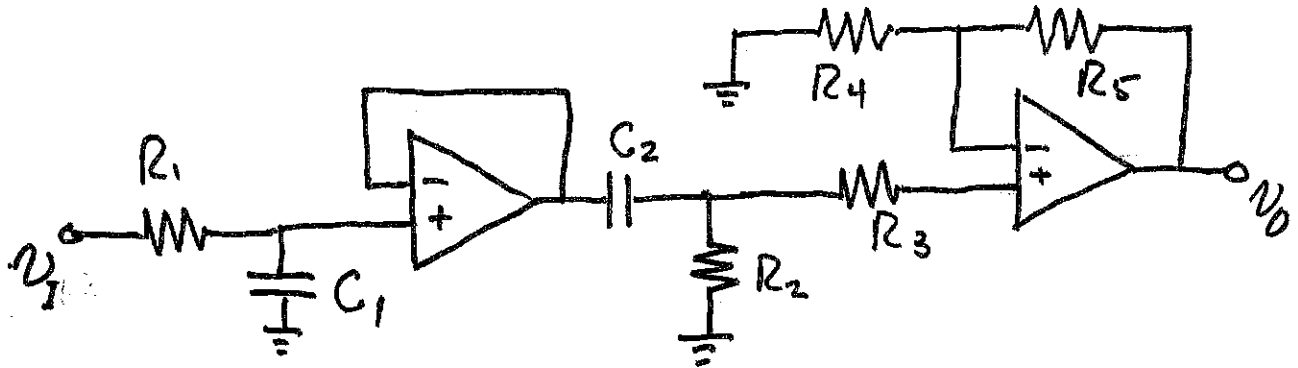1. (35 points) For the circuit below, do the following.

Find the transfer function $T(\omega) = V_o/V_i$. Then choose resistor and capacitor values such that the magnitude Bode plot for this transfer function has the form shown in the graph. Be sure your results account for the breakpoints in the transfer function as well as the magnitude. Assume the op amps are ideal.



Room for extra work

2. (30 points)


a) Using the graph paper on the next page, sketch the straight-line approximation to the phase Bode plot for the following transfer function. Note that the values of C and R are unknown.

$$T(\omega) = -\frac{j\omega CR(j\omega + 2000)(j\omega + 200,000)}{(j\omega + 400)^2}$$

The image displays a large grid table with 10 columns and 10 rows. The grid is divided into four quadrants by a central vertical line and a central horizontal line. Each quadrant contains a 5x5 grid of smaller cells. The grid is empty, with no data or text present within the cells.

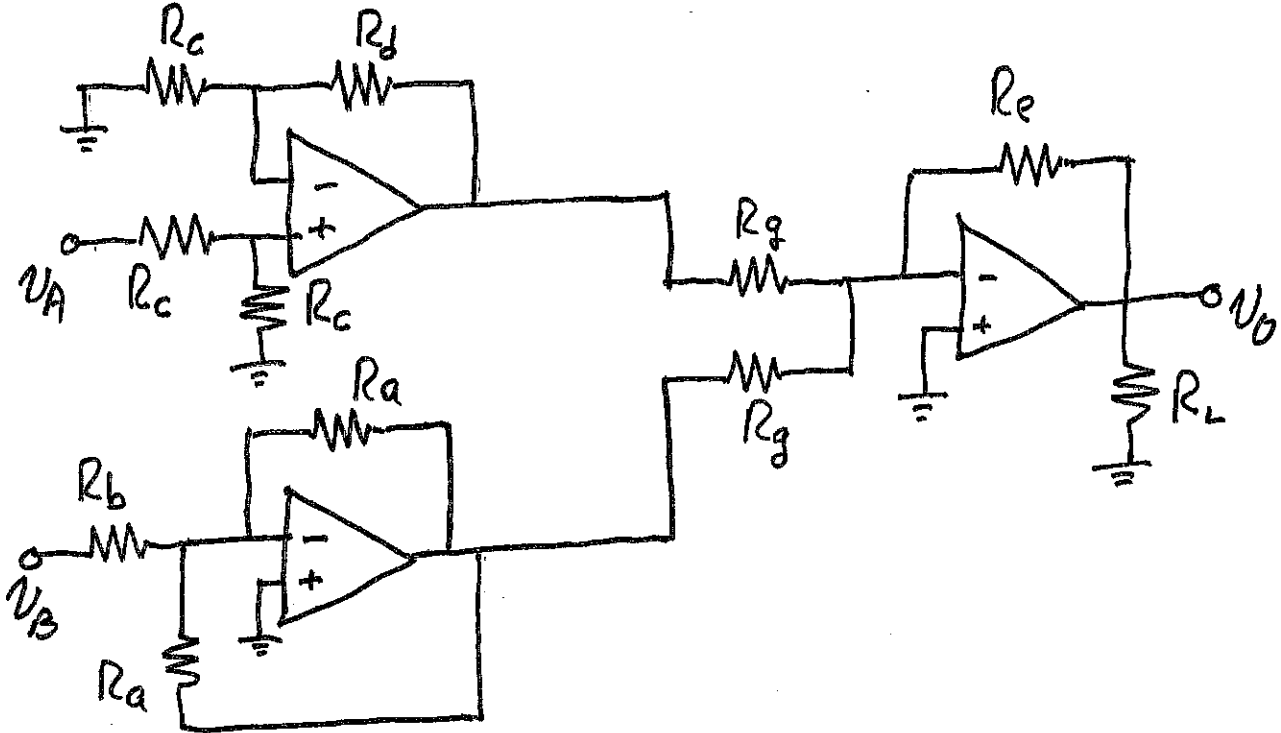3. (35 points) For the circuit below, do the following. Assume the op amps are ideal.

- Find v_O in terms of v_A and v_B , and the resistances.
- Find the input resistance seen by v_A .
- Find the input resistance seen by v_B .



Room for extra work

Name: SOLUTIONS (please print)

Signature: _____

ECE 3355 – Exam #1
February 22, 2020

**Keep this exam closed and face up
until you are told to begin.**

1. This exam is closed book, closed notes. You may use one 8.5" x 11" crib sheet, or its equivalent.
2. Show all work on these pages. Show all work necessary to complete the problem. A solution without the appropriate work shown will receive no credit. A solution which is not given in a reasonable order will lose credit.
3. Show all units in solutions, intermediate results, and figures.
4. If the grader has difficulty following your work because it is messy or disorganized, you will lose credit.
5. Do not use red ink. Do not use red pencil.
6. You will have 90 minutes to work on this exam.

_____ /35



_____ /30

_____ /35

_____ /100

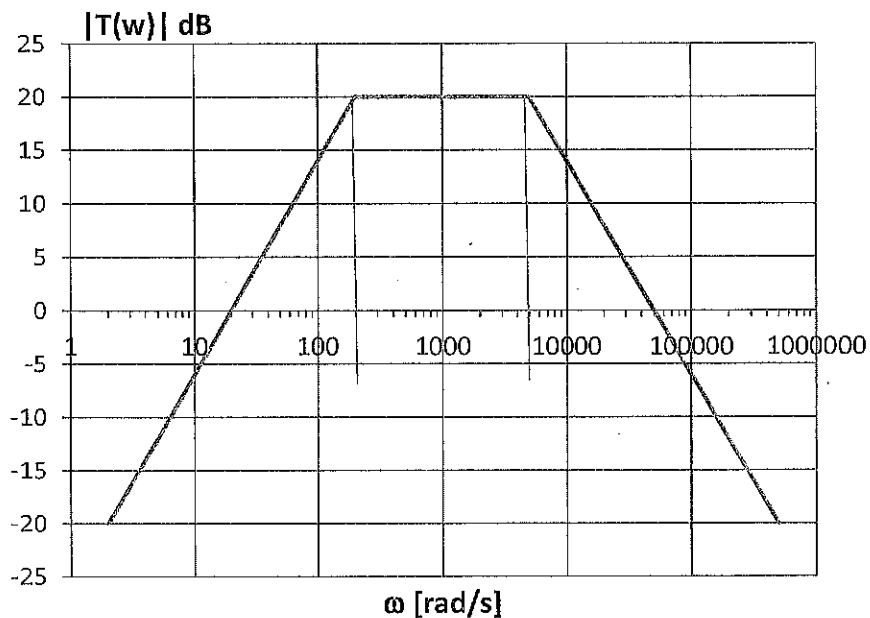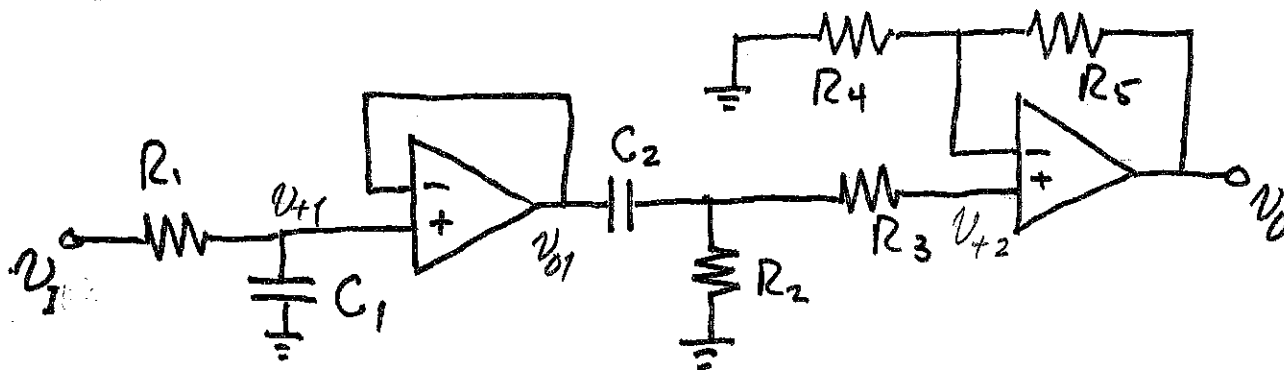1. (35 points) For the circuit below, do the following.

Find the transfer function $T(\omega) = V_o/V_i$. Then choose resistor and capacitor values such that the magnitude Bode plot for this transfer function has the form shown in the graph. Be sure your results account for the breakpoints in the transfer function as well as the magnitude. Assume the op amps are ideal.



$$\vec{V}_{+1} = \vec{V}_i \frac{1/j\omega C_1}{1/j\omega C_1 + R_1} = \vec{V}_i \frac{1}{1 + j\omega C_1 R_1} \quad \vec{V}_{o1} = \vec{V}_{+1}$$

$$\vec{V}_{+2} = \vec{V}_{o1} \frac{R_2}{R_2 + 1/j\omega C_2} = \vec{V}_{o1} \frac{j\omega C_2 R_2}{1 + j\omega C_2 R_2}$$

$$\vec{V}_o = \vec{V}_{+2} \left(1 + \frac{R_5}{R_4} \right)$$

Room for extra work

$$\overset{+15}{\underline{V}_0} = \frac{(1 + R_5/R_4) \cdot j\omega C_2 R_2}{1 + j\omega C_1 R_1} \cdot \frac{j\omega C_2 R_2}{1 + j\omega C_2 R_2}$$

So we have

$$\text{zero: } 0 \text{ rad/s} \quad +2$$

$$\text{poles: } 1/C_1 R_1 \quad +2$$

$$1/C_2 R_2 \quad +2$$

From the Bode plot, we have poles at 200 rad/s and at 5000 rad/s. There is no way to tell which pole is which, so we'll choose something.

$$\textcircled{1} \quad 1/C_1 R_1 = 200 \text{ rad/s} \quad \textcircled{2} \quad 1/C_2 R_2 = 5000 \text{ rad/s} \quad +2 \quad +2$$

At 1000 rad/s, where $|T(\omega)|$ does not depend on ω , we have

$$\omega_0 = 1000 \text{ rad/s} \quad \omega_0 \gg 1/C_1 R_1 \Rightarrow \omega_0 C_1 R_1 \gg 1$$

$$\omega_0 \ll 1/C_2 R_2 \Rightarrow \omega_0 C_2 R_2 \ll 1$$

$$\text{So ... } \frac{\underline{V}_0}{\underline{V}_i} \approx \frac{(1 + R_5/R_4) \cdot j\omega_0 C_2 R_2}{j\omega_0 C_1 R_1} = (1 + R_5/R_4) \cdot \frac{C_2 R_2}{C_1 R_1} \quad +4$$

$$|T(\omega_0)| = (1 + R_5/R_4) \frac{C_2 R_2}{C_1 R_1} = (1 + R_5/R_4) \frac{200}{5000} = 10 \quad (= 20 \text{ dB}) \quad \textcircled{3}$$

So 1, 2, & 3 are the constraints that must be satisfied.

$$\text{We'll choose } R_1 = 10 \text{ k}\Omega \Rightarrow C_1 = 0.5 \mu\text{F} \quad +1 \quad +1$$

$$R_2 = 1 \text{ k}\Omega \Rightarrow C_2 = 200 \text{ nF} \quad +1 \quad +1$$

$$R_4 = 500 \Omega \Rightarrow R_5 = 0.125 \text{ M}\Omega \quad +1 \quad +1$$

↗
Pg. 2.

We have neglected 1 in comparison with R_5/R_4

Room for extra work

+1

+1

If we had chosen $\frac{1}{C_1 R_1} = 50000 \text{ rad/s}$, $\frac{1}{C_2 R_2} = 200 \text{ rad/s}$,
we would have ($\omega_0 = 1000 \text{ rad/s}$)

$$\omega_0 \gg \frac{1}{C_2 R_2} \Rightarrow \omega_0 C_2 R_2 \gg 1$$

$$\omega_0 \ll \frac{1}{C_1 R_1} \Rightarrow \omega_0 C_1 R_1 \ll 1$$

+5

$$|T(\omega_0)| \approx (1 + R_5/R_4) \frac{1 + \omega_0 C_2 R_2}{1 + \omega_0 C_1 R_1} = 1 + R_5/R_4 = 10$$

$$R_1 = 1 \text{ k}\Omega \Rightarrow C_1 = 20 \text{ nF} \quad +1 \quad +1$$

$$R_2 = 10 \text{ k}\Omega \Rightarrow C_2 = 0.5 \mu\text{F} \quad +1 \quad +1$$

$$R_4 = 10 \text{ k}\Omega \quad R_5 = 90 \text{ k}\Omega \quad +1 \quad +1$$

2. (30 points)

a) Using the graph paper on the next page, sketch the straight-line approximation to the phase Bode plot for the following transfer function. Note that the values of C and R are unknown.

$$T(\omega) = -\frac{j\omega CR(j\omega + 2000)(j\omega + 200,000)}{(j\omega + 400)^2}$$

zeros: 0, 2000, 200000 rad/s

poles: 400, 400 rad/s (double pole)


$$T(\omega \rightarrow 0) \rightarrow -j\omega CR \quad \angle T(\omega \rightarrow 0) = -90^\circ$$

The plot on the next page shows the result.

$$\text{Check: } T(\omega \rightarrow \infty) \rightarrow -j\omega CR \quad \angle T(\omega \rightarrow \infty) = -90^\circ$$

So we come back to where we started, as the plot shows.


ω (rad/s) z z z z z

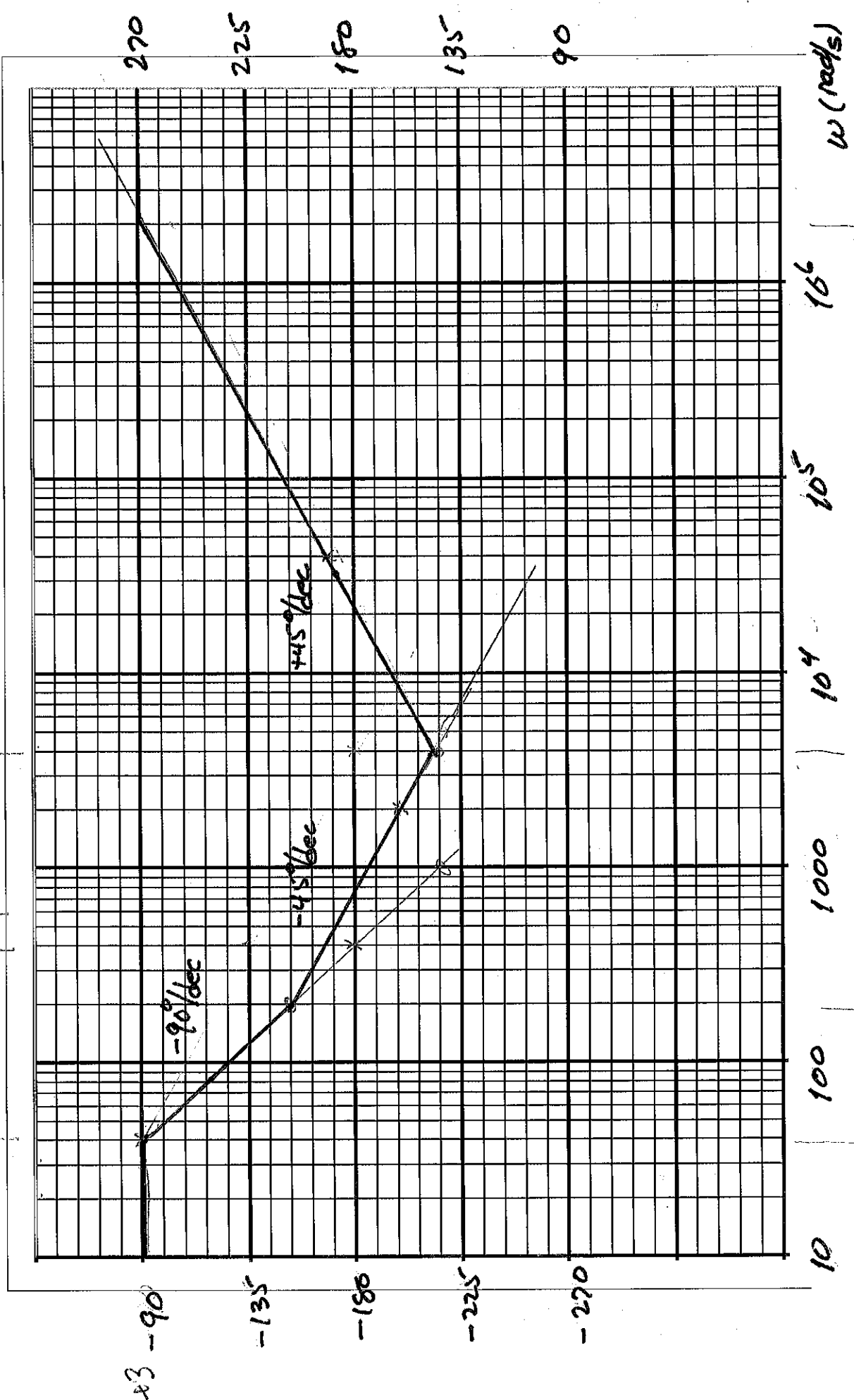

bkpt $+2$ $+2$ $+2$ $+2$ $+2$ $+2$
 slope $+3$ $+3$ $+3$ $+3$ $+3$ $+3$

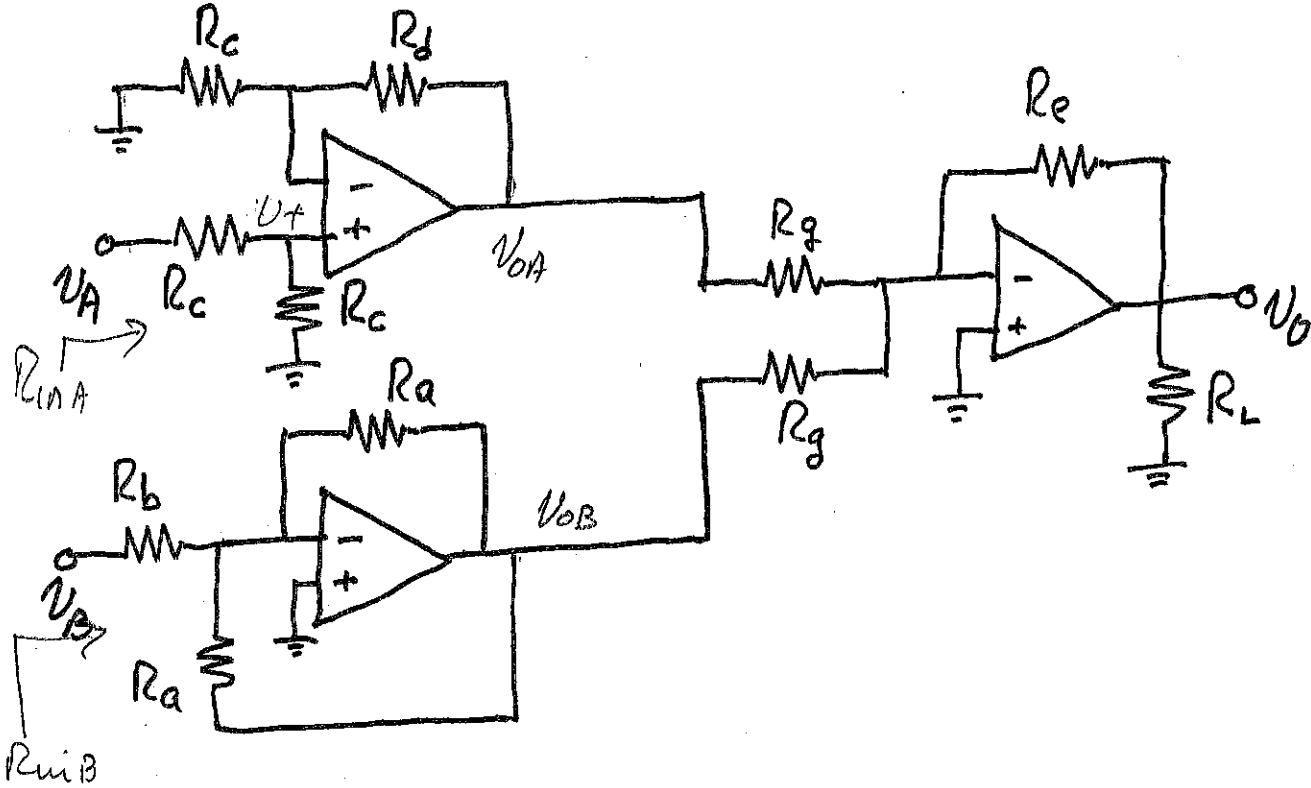3. (35 points) For the circuit below, do the following. Assume the op amps are ideal.

- Find v_O in terms of v_A and v_B , and the resistances.
- Find the input resistance seen by v_A .
- Find the input resistance seen by v_B .



$$v_+ = \frac{1}{2} v_A \quad v_{OA} = \frac{1}{2} \left(1 + \frac{R_d}{R_c}\right) v_A \quad + 10$$

Note that R_a and R_a are in parallel $\rightarrow \frac{1}{2} R_a$

$$v_{OB} = -v_B \frac{\frac{1}{2} R_a}{R_b} = -v_B \frac{R_a}{2R_b} \quad + 10$$

So

$$v_O = -v_{OB} \left(\frac{R_e}{R_g}\right) - v_{OA} \left(\frac{R_e}{R_g}\right)$$

$$v_O = v_B \frac{R_a}{2R_b} \frac{R_e}{R_g} - \frac{1}{2} v_A \left(1 + \frac{R_d}{R_c}\right) \frac{R_e}{R_g}$$

+ 10

Room for extra work

$$R_{inA} = 2R_c \quad +3$$

$$R_{inB} = R_b. \quad +2$$