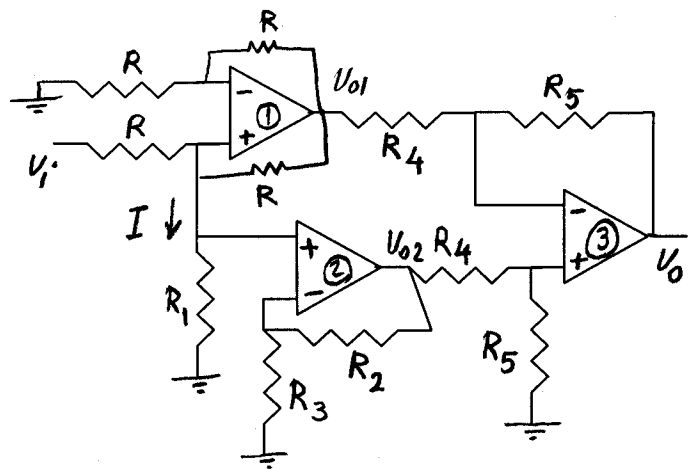


- (25 Points)(1) (a) Find V_o/V_i in term of R, R_1, R_2, R_3, R_4 and R_5 .
 b) If $R=10\text{ K}$, $R_1=3.3\text{ K}$, $R_2=4.7\text{ K}$,
 $R_3=5.6\text{ K}$, $R_4=18\text{ K}$ and $R_5=33\text{ K}$,
 Calculate V_o/V_i using relation obtained
 From part (a).



solution :

The current I shown is equal to V_i/R . (refer to Positive Integrator)

The voltage of V_+ at op-Amp #2 is

$$V_+(2) = I \cdot R_1 = \frac{V_i}{R} \cdot R_1 \quad \text{also } V_{01} = 2 V_i \frac{R_1}{R}$$

op-Amp #2 is a non-inverting Amp.

$$V_{02} = V_+ \left(1 + \frac{R_2}{R_3}\right) = V_i \frac{R_1}{R} \left(1 + \frac{R_2}{R_3}\right)$$

The third op-amp is a differential amplifier

$$V_o = \frac{R_5}{R_4} (V_{02} - V_{01})$$

substituting for V_{01} and V_{02} from previous results


$$V_o = \frac{R_5}{R_4} \left(V_i \frac{R_1}{R} \left(1 + \frac{R_2}{R_3}\right) - 2 V_i \frac{R_1}{R} \right)$$

or

$$\frac{V_o}{V_i} = \frac{R_1}{R} \cdot \frac{R_5}{R_4} \left(\frac{R_2}{R_3} - 1 \right)$$

$$b) \quad \frac{V_o}{V_i} = \frac{3.3}{10} \cdot \frac{33}{18} \left(\frac{4.7}{5.6} - 1 \right) = -0.097$$

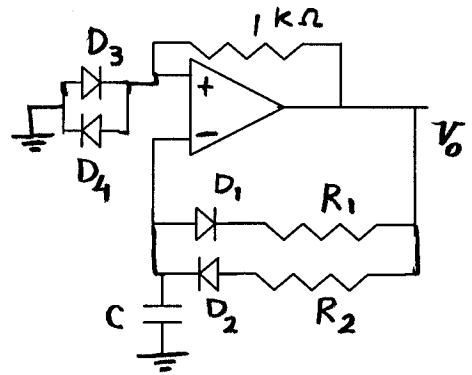(20 Points) (2) In the square wave generator shown, assume diodes D1 and D2 are ideal but assume constant voltage drop model of 0.7 [V] for D3 and D4. $L^+ = -L^- = 10[V]$. Find the frequency of the waveform if $R_1 = 10\text{ K}$, $R_2 = 1.2\text{ K}$ and $C = 1\text{ microF}$.



Solution :

The voltage of V_+ is ± 0.7 Volts.

The β is $\beta = \frac{0.7}{10} = 0.07$

$$T_1 = 2\beta R_1 C$$

$$T_2 = 2\beta R_2 C$$

$$T = T_1 + T_2 = 2\beta C (R_1 + R_2)$$


$$T = 2 \times 0.07 \times 1 \times 10^{-6} (10 + 1.2) \times 10^3$$

$$T = 1.57 \text{ ms}$$

$$f = \frac{1}{T} = 638 \text{ Hz}$$

$$T_1 = 2\beta C R_2$$


$$T_2 = 2\beta C R_1$$

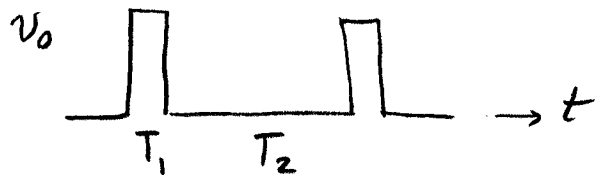

$$T_1 = 2 \times 0.07 \times 1 \times 10^{-6} \times 1.2 \times 10^3 = 0.168 \text{ ms}$$

$$T_2 = 2 \times 0.07 \times 1 \times 10^{-6} \times 10 \times 10^3 = 1.4 \text{ ms}$$

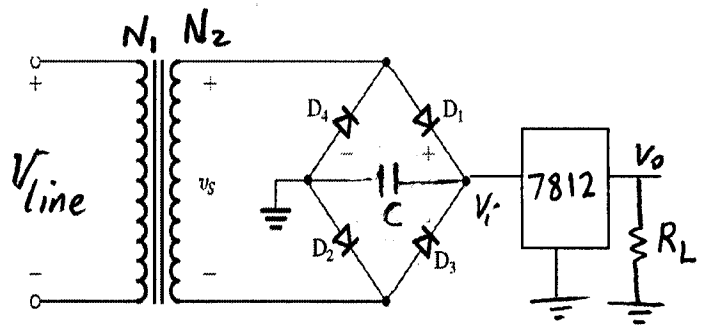(20Points) (3) In the regulated power supply shown, $V(\text{line})=170\cos(377t)$ and V_o is 9 volt(DC). If $R_L=60$ ohms, find appropriate value for C and transformer turn ratio N_2/N_1 .



solution :

$$V_o(\text{DC}) = 9 [\text{V}]$$

$$V_i(\text{DC}) = 4 + 9 = 13 [\text{V}]$$

$$V_r = 1.3 [\text{V}]$$

$$V_p = 13 + \frac{1}{2} \times 1.3 = 13.65 [\text{V}]$$

$$R'_L = \frac{13}{I_L} = \frac{13}{9/60} = 86.6 \Omega$$

$$C = \frac{V_p}{2 \times f \times R'_L \times V_r}$$

$$C = \frac{13.65}{2 \times 60 \times 86.6 \times 1.3} = 1010 \text{ MF}$$

$$V_s = V_p + 1.4 = 13.65 + 1.4 = 15.05 [\text{V}]$$

$$\frac{N_2}{N_1} = \frac{V_s}{170} = \frac{15.05}{170} = 0.088$$

(25 Points) (4) In the circuit shown, find the DC current of collector of Q1 and Q2. $V_{(BE)}=0.7$ V and $\beta=100$.

Solution:

By Putting the thevenin eq. of R_{B1} and R_{B2} , as in Fig 2

Now we can write 2 Mesh Current equations,

$$\begin{cases} 4 = 200 I_1 + 0.7 + (101 I_1 - I_2) \times 1 \\ (101 I_1 - I_2) \times 1 = 0.7 + (101 I_2) \times 0.1 \end{cases}$$

$$\begin{cases} 301 I_1 - I_2 = 3.3 \\ 101 I_1 - 11.1 I_2 = 0.7 \end{cases}$$

From the first eq. $\Rightarrow I_2 = 301 I_1 - 3.3$

$$101 I_1 - 11.1 (301 I_1 - 3.3) = 0.7$$

$$-3240.1 I_1 + 36.63 = 0.7$$

$$I_1 = I_{B1} = 0.011$$

$$I_2 = 301 I_1 - 3.3$$

$$I_2 = 0.037$$

$$I_{C1} = 1.1 \text{ mA}$$

$$I_{C2} = 3.78 \text{ mA}$$


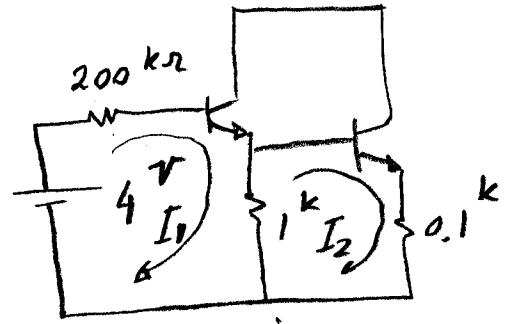
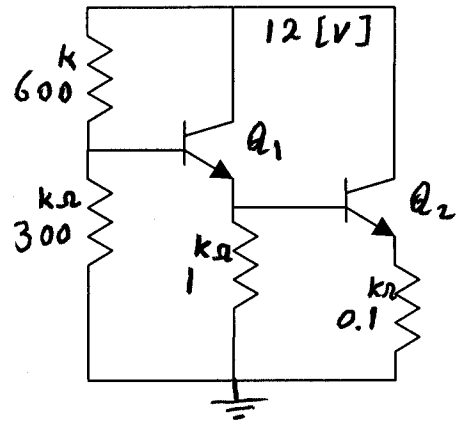


Fig 2

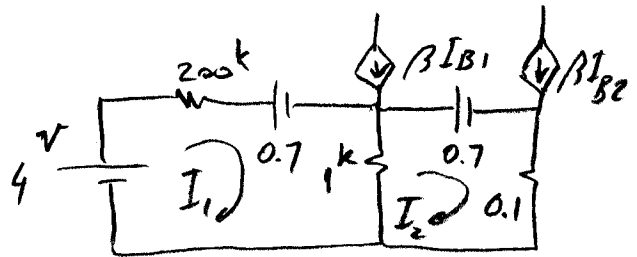

(25 Points) (5) Find R_c , C_1 , C_2 and C_3 so that the amplifier has a passband gain of -20 and lower cut-off frequency of 100 Hz. Assume that all 3 capacitors has equal time constants.

Solution:

First we do DC analysis to find I_c . From Fig. 2

$$4 = 30 I_B + 0.7 + 3(101 I_B)$$

$$I_B = 0.01 \text{ mA} \quad \boxed{I_c = 1 \text{ mA}}$$

$$r_\pi = \frac{\beta V_T}{I_c} = \frac{100 \times 25}{1} = 2.5 \text{ k}\Omega$$

$$g_m = I_c / V_T = \frac{1}{25} = 40 \text{ mS}$$

From Fig. 3, we can find the passband gain as a function of R_c .

$$v_i / v_s = \frac{2.5 \parallel 30}{2.5 \parallel 30 + 10} = \frac{2.3}{2.3 + 10} = 0.187$$

$$v_o / v_i = -g_m (R_c \parallel 4.7)$$

$$v_o / v_s = -40 (R_c \parallel 4.7) \times 0.187 = -20$$

$$R_c \parallel 4.7 = 2.67 \quad \frac{1}{R_c} + \frac{1}{4.7} = \frac{1}{2.67}$$

$$\boxed{R_c = 6.18 \text{ k}\Omega}$$


$$\tau_1 = \tau_2 = \tau_3 = \tau \quad \omega_L = \frac{1}{\tau_1} + \frac{1}{\tau_2} + \frac{1}{\tau_3} = \frac{3}{\tau} \quad \tau = \frac{3}{\omega_L} = \frac{3}{2\pi \times 100}$$

$$\tau = 4.77 \text{ ms}$$

$$C_1 [10 + 30 \parallel 2.5] = 4.77 \text{ ms}$$

$$C_2 [3 \parallel \frac{2.5 + 30 \parallel 10}{101}] = 4.77$$

$$C_3 [6.18 + 4.7] = 4.77$$

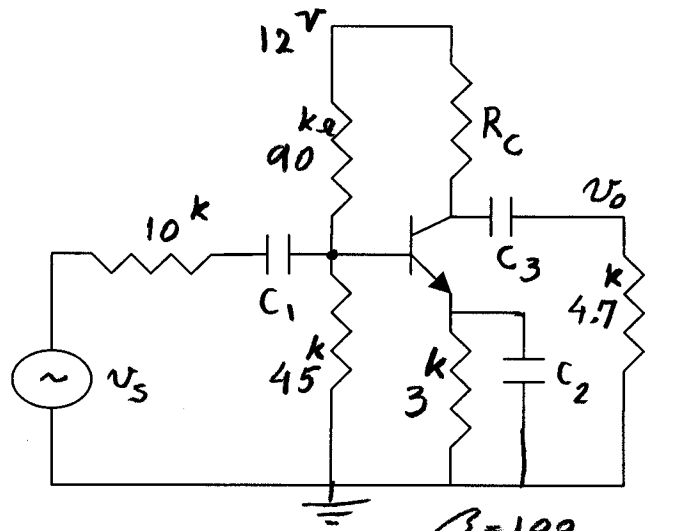

$\beta = 100$
 $V_T = 25 \text{ mV}$
 $V_{BE} = 0.7 \text{ V}$
 $v_o / v_s = -20$

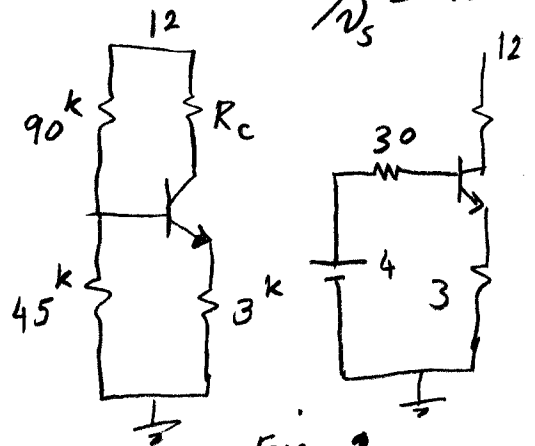


Fig. 2

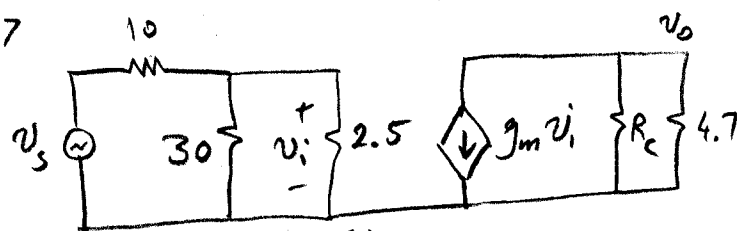


Fig. 3

$C_1 = 0.38 \text{ }\mu\text{F}$
$C_2 = 64.2 \text{ }\mu\text{F}$
$C_3 = 0.43 \text{ }\mu\text{F}$