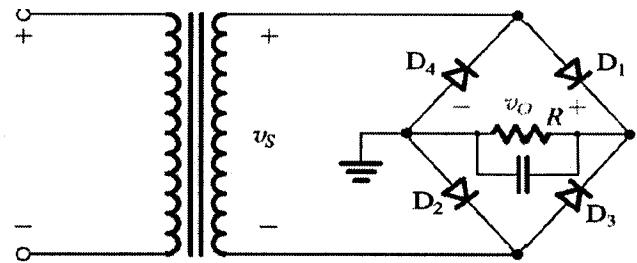


ECE3455, Q4) In the circuit shown, the input of the transformer is a **triangular** wave with amplitude of 100[V] and frequency of 100 [Hz]. If  $V_D(\text{on})=0.7$  [V] and  $R=100$  [ohms]. If the average output voltage is 12 volts and the ripple is 2 V(pp).

- Find the value of the capacitor.
- Find the turn ratio of the transformer ( $N_2/N_1$ ).
- Find the conduction angle and the average current of each diode.



Solution :

(B)

$$V_o(\text{av}) = V_p - \frac{1}{2} V_r \Rightarrow 12 = V_p - \frac{1}{2} \times 2 \quad V_p = 13 \text{ V}$$

$$V_s = V_p + 1.4 = 13 + 1.4 = 14.4 \text{ V}$$

$$\text{a)} \quad C = \frac{V_p}{2 \cdot f \cdot R \cdot V_r} = \frac{13}{2 \times 100 \times 100 \times 2} = 325 \mu\text{F}$$

$$\text{b)} \quad n = \frac{N_2}{N_1} = \frac{V_s}{V_{\text{line}}} = \frac{14.4}{100} = 0.144$$

$$\text{c)} \quad \theta = \frac{V_r}{V_p} \times 90 = \frac{2}{13} \times 90 = 13.84^\circ$$

$$I_D(\text{av}) = \frac{180}{\theta} \times \frac{V_p}{R} = \frac{180}{13.84} \times \frac{13}{100} =$$

$$I_D(\text{av}) = 1.69 \text{ A}$$