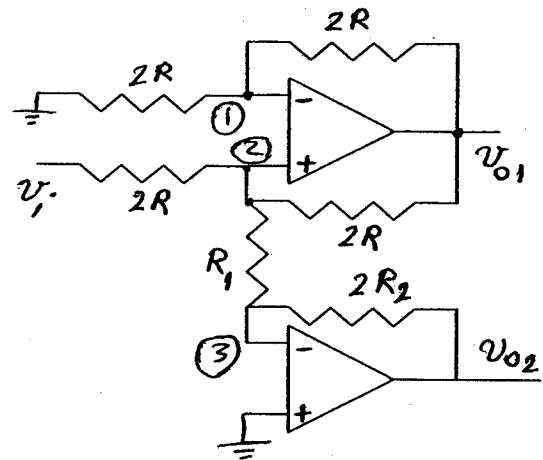


- (ECE3455, Q3, Sum03) In the circuit shown,  
 a) Find the gain  $V_{o1}/V_i$  as a function of resistors.  
 b) Find the gain  $V_{o2}/V_i$  as a function of resistors.

(A)



solution :

a) The voltage of node ① is

half of the  $V_{o1}$  or  $V_{o1}/2$

so the voltage of node ② is also  $V_{o1}/2$ , the voltage of node ③ is zero (0),

if we write a KCL at node ② we'll have

$$\frac{V_i - V_{o1}/2}{2R} = \frac{V_{o1}/2 - V_{o1}}{2R} + \frac{V_{o1}/2}{R_1}$$

$$\frac{V_i}{2R} - \frac{V_{o1}}{4R} = -\frac{V_{o1}}{4R} + \frac{V_{o1}}{2R_1}$$

$$① \boxed{\frac{V_{o1}}{V_i} = \frac{R_1}{R}}$$

So it is a non-invert amp. with a gain similar to inverting form

b) writing a node voltage eq. at node ③

$$\frac{V_{o1}/2}{R_1} = \frac{0 - V_{o2}}{2R_2} \quad \text{or} \quad V_{o2} = -\frac{R_2}{R_1} V_{o1}$$

using eqn ①  $V_{o2} = -\frac{R_2}{R_1} \times \frac{R_1}{R} V_i = -\frac{R_2}{R} V_i$

$$\boxed{\frac{V_{o2}}{V_i} = -\frac{R_2}{R}}$$